

# Lab Report 2

## *Team Members :*

**Name:** Chanda Akshay Kumar

**Roll No. :** 2024102014


**Name:** Samadhi Venkata Santhosh Kumar yadav

**Roll No.:** 2024102054

**Team I'D :** 42

## *Aim/Objective:*

Implementing RC Circuit on PCB

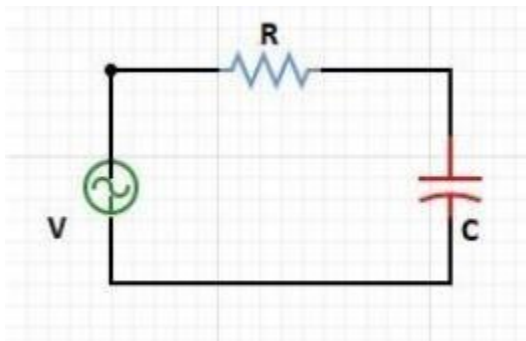

## *Materials Used:*

1. Capacitor
2. Power Supply
3. PCB(new)
4. Resistors
5. Digital Multimeter
6. Soldering kit(Including flux,lead,etc...)
7. Connecting wires
8. DSO (Digital Storage Oscillator) & Wave Generator

### Procedure:



1. Identify all the components of your RC circuit: resistor(s), capacitor(s), and any input/output connections.

Sr No	R (in ohms)	C (in farad/microfarad)	Time Constant (Theoretical)	Time Constant (Practical)	Cutoff Frequency (Theoretical)	Cutoff Frequency (Practical)
1	2190 ohm	$457 \times 10^{-12}$ farad	$10^{-6}$ s	$0.78 \times 10^{-6}$ s	$0.16 \times 10^6$ hz	$0.2 \times 10^6$ hz
2	11600 ohm	$10^{-9}$ farad	$11.6 \times 10^{-6}$	$14.7 \times 10^{-6}$	$13.7 \times 10^3$ hz	$10 \times 10^3$ hz
3						

2. Place the components on the PCB according to the circuit diagram, ensuring that polarized components (like electrolytic capacitors) are oriented correctly.
3. Solder each component to the PCB, starting with the lowest profile components (usually resistors) and working your way up to taller components.
4. After soldering, visually inspect each joint for good, shiny connections, and check for any solder bridges between adjacent pads.
5. Once all components are soldered, use a multimeter to check for continuity and correct resistance values. Connect the circuit to your function generator and oscilloscope to verify its operation.
6. If the circuit doesn't work as expected, recheck your connections and component values. Use the oscilloscope to trace the signal through the circuit and identify any issues.
7. Then follow the same experiment 1 had done in 1<sup>st</sup> lab with the circuit constructed before,
8. Note the values by obtained signal in DSO.



### Observation Result and Table


#### PCB & DSO IMAGE

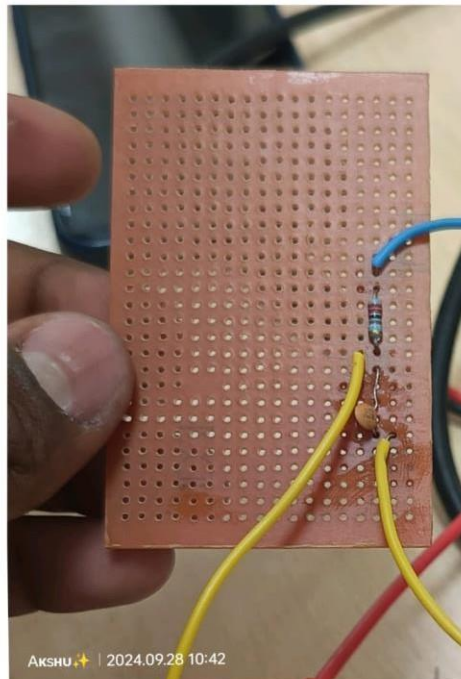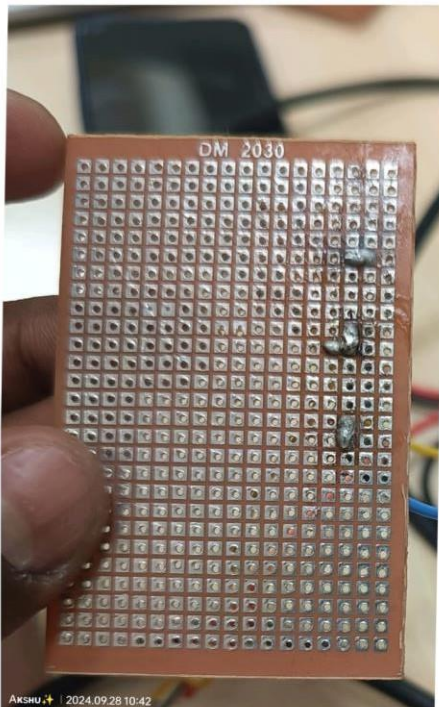





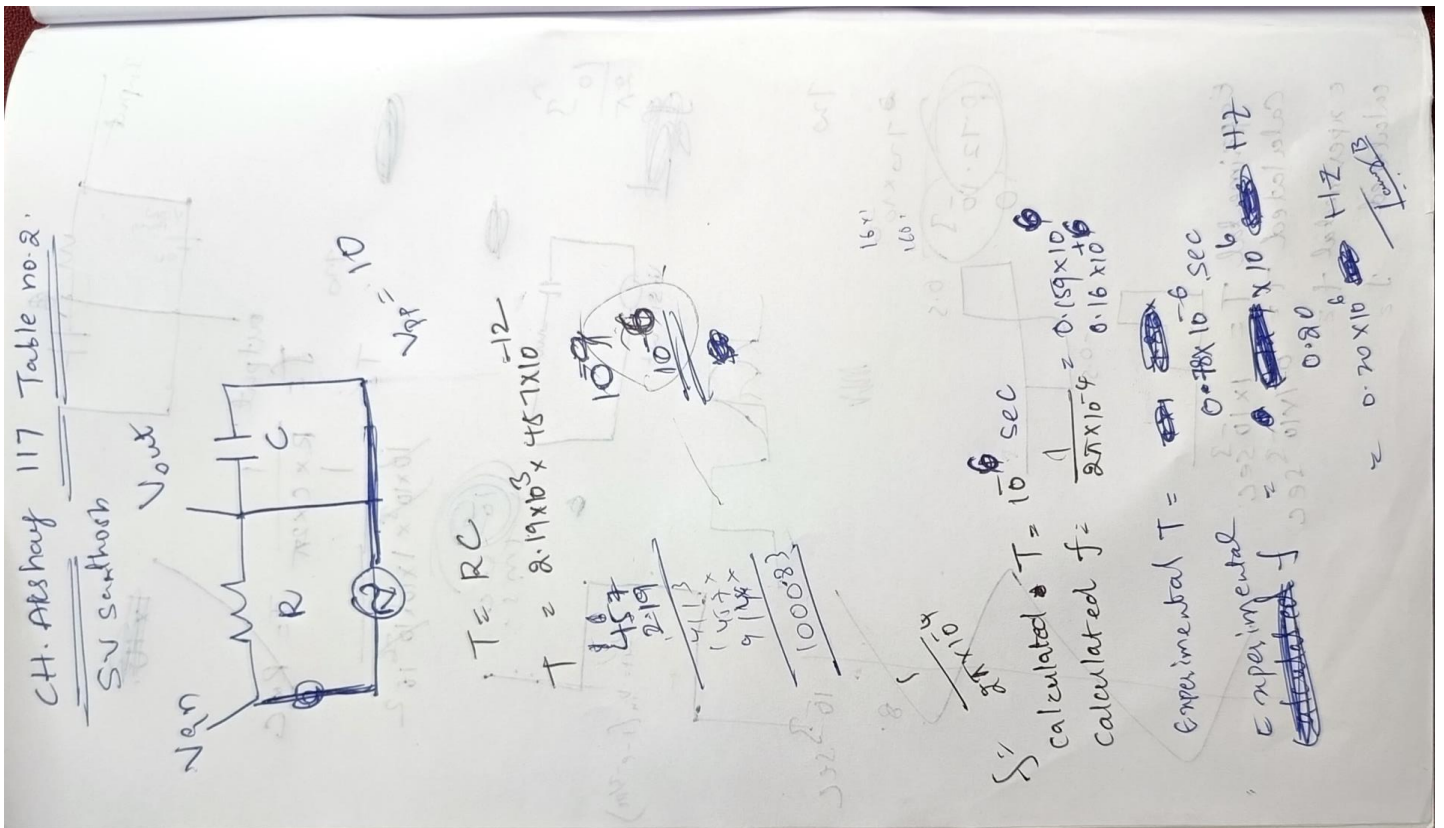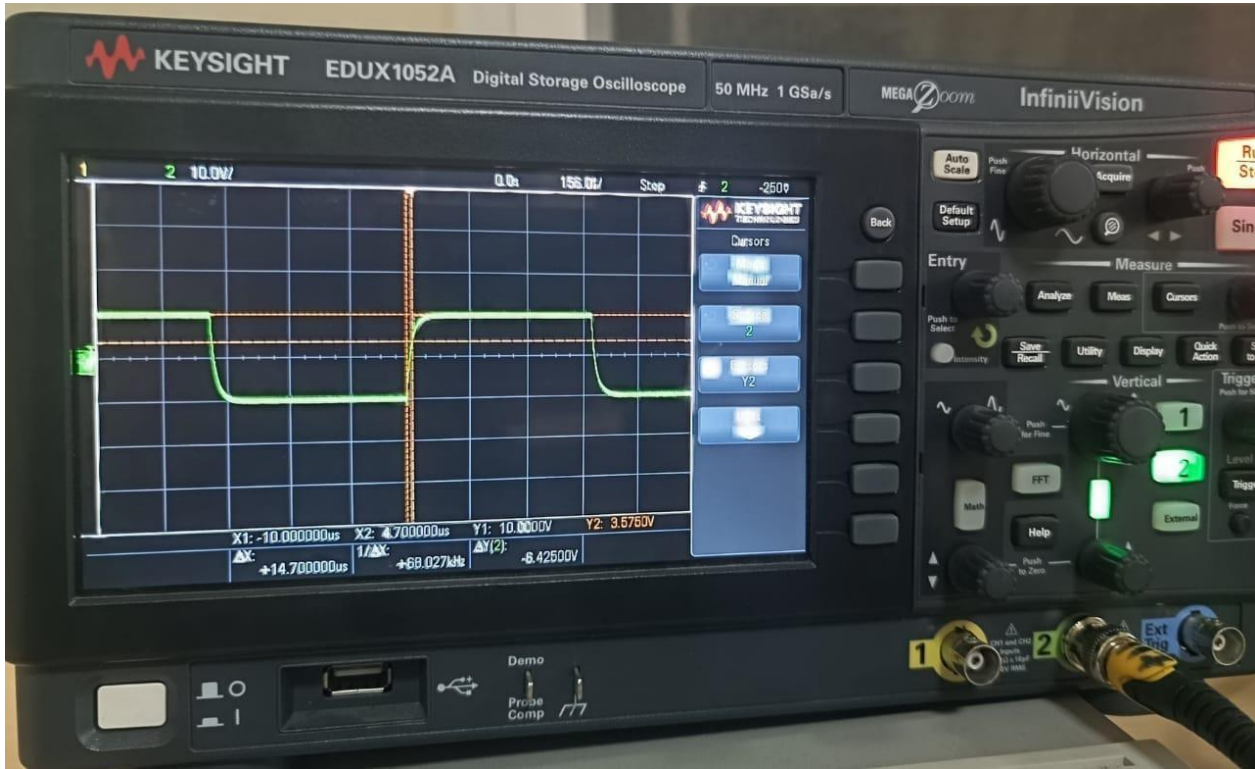

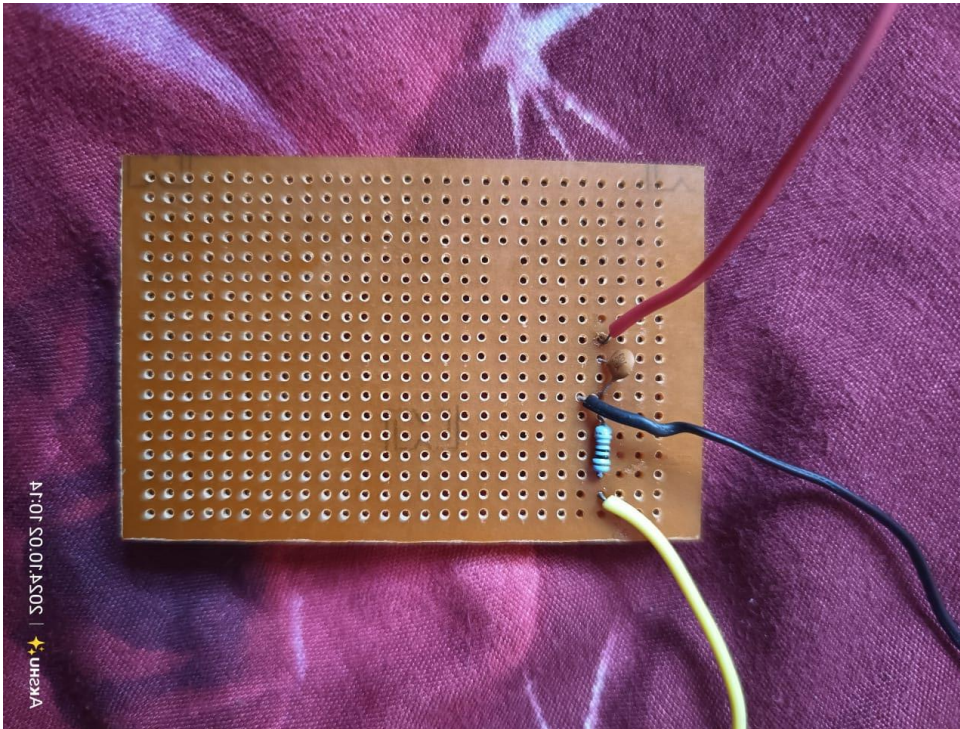

### **Conclusion:**

*constructing the RC circuit on a PCB involved properly placing and soldering components to test the circuit for time constant and cutoff frequency. We replicated the charging and discharging behavior of the capacitor using a square wave, as observed in the breadboard experiment. The overall goal was to determine the time constant and cutoff frequency in the PCB version of the circuit.*