

About LTspice, Download and Install

- SPICE : Simulation Program with Integrated Circuit Emphasis
- LTspice is a high performance SPICE simulation software, schematic capture and waveform viewer with enhancements and models for easing the simulation of analog circuits
- For SPICE, any circuit is described as an interconnection of various active, passive elements. This interconnection of elements is also called **Net-List**
- DC, transient, AC, pole-zero, noise - analysis can be performed using LTspice
- Result plots can be viewed and saved
- Download LTspice from following path and install:
<https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>
- LTspice documentation can be also downloaded from the same site

Getting Started

- Circuit schematic
- Models used to describe circuit elements is included
- Type of analysis to be done on the circuit to be mentioned in SPICE directive
- Results can be plotted with the help of probes and expressions

Getting Started-Creating New Schematic


Start with a New Schematic

New Schematic



Getting Started-Toolbar

Summary of Schematic Editor Toolbar

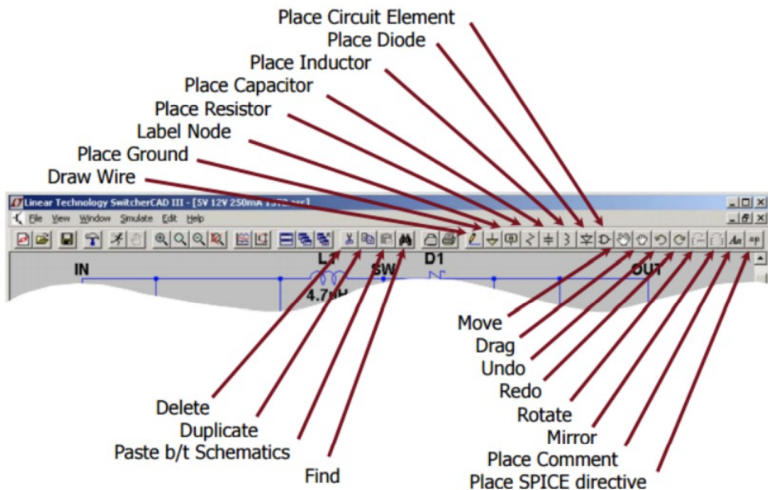

Use the following labels to specify units for circuit element attributes

◆ **K** = k = kilo = 10^3

◆ **MEG** = meg = 10^6

◆ **G** = g = giga = 10^9

◆ **T** = t = terra = 10^{12}

◆ **m** = M = milli = 10^{-3}

◆ **u** = U = micro = 10^{-6}

◆ **n** = N = nano = 10^{-9}

◆ **p** = P = pico = 10^{-12}

◆ **f** = F = femto = 10^{-15}

Simulation Setup

- Left click on simulation menu
- Left click on Edit Simulation Cmd
- Left click on requires simulation type tab
- Enter necessary parameters
- Click OK

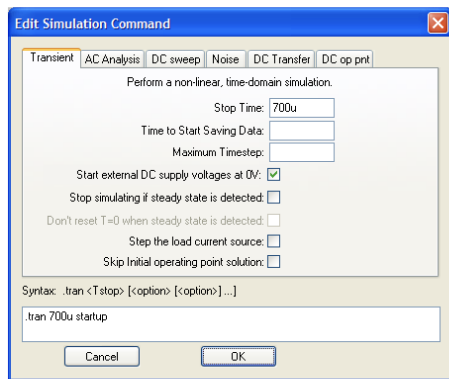


Figure: Edit simulation command window

Probing Circuit

- Left click on any wire to plot the voltage on the waveform viewer



Voltage probe cursor

- Left click on the body of the component to plot the current on the waveform viewer



Current probe cursor

- For voltage difference across 2 nodes, left click and hold on a node and drag the mouse to the other node

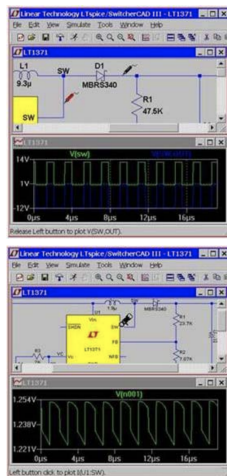


Figure: Edit simulation command window


Instantaneous and average power dissipation

- Instantaneous power dissipation

- Hold down ALT key and left click on the component
- Pointer will change to a thermometer

- Average power dissipation

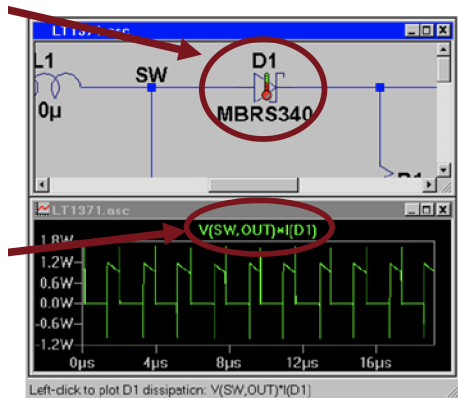- Hold down Ctrl key and left click on the trace label of the power dissipation waveform



RC circuit

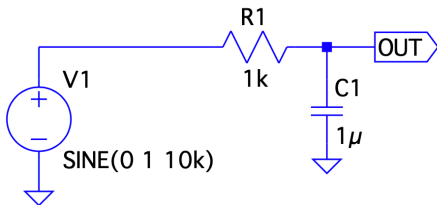


Figure: Schematic

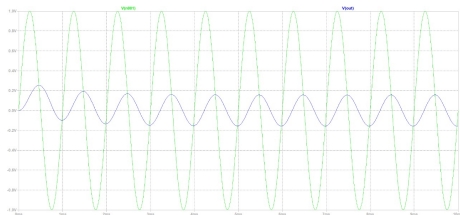


Figure: Transient Simulation Results

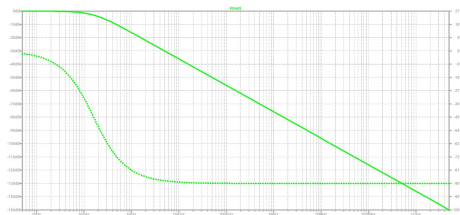


Figure: AC Simulation Results

Diode Rectifier

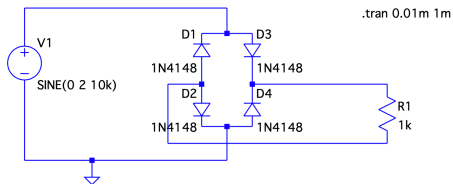


Figure: Schematic

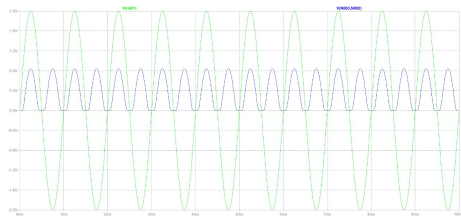


Figure: Transient analysis results

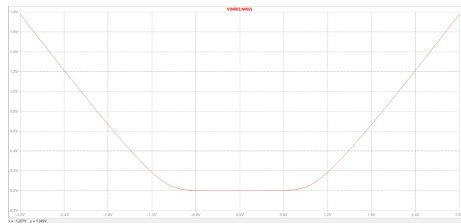


Figure: DC analysis results

OPamp inverting amplifier

Include library file lm741.lib when using this circuit.

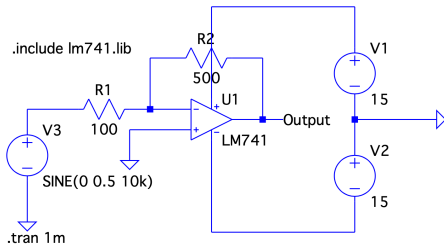


Figure: Schematic

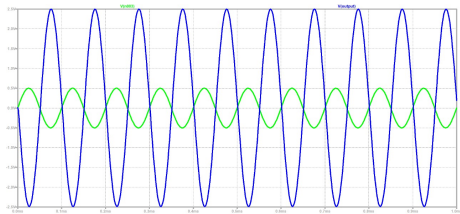


Figure: Transient analysis results

LTspice shortcuts on OS X

■ G	GROUND
■ S	ADD SPICE DIRECTIVE
■ CMD+N	NEW SCHEMATIC
■ CMD+O	OPEN
■ CMD+S	SAVE
■ CMD+Z	UNDO
■ CMD+SHIFT+Z	REDO
■ F2	COMPONENT
■ F3	WIRE
■ F4	NET NAME
■ F5	DELETE
■ F6	DUPLICATE
■ F7	MOVE
■ F8	DRAG
■ SPACE BAR	ZOOM TO FIT