

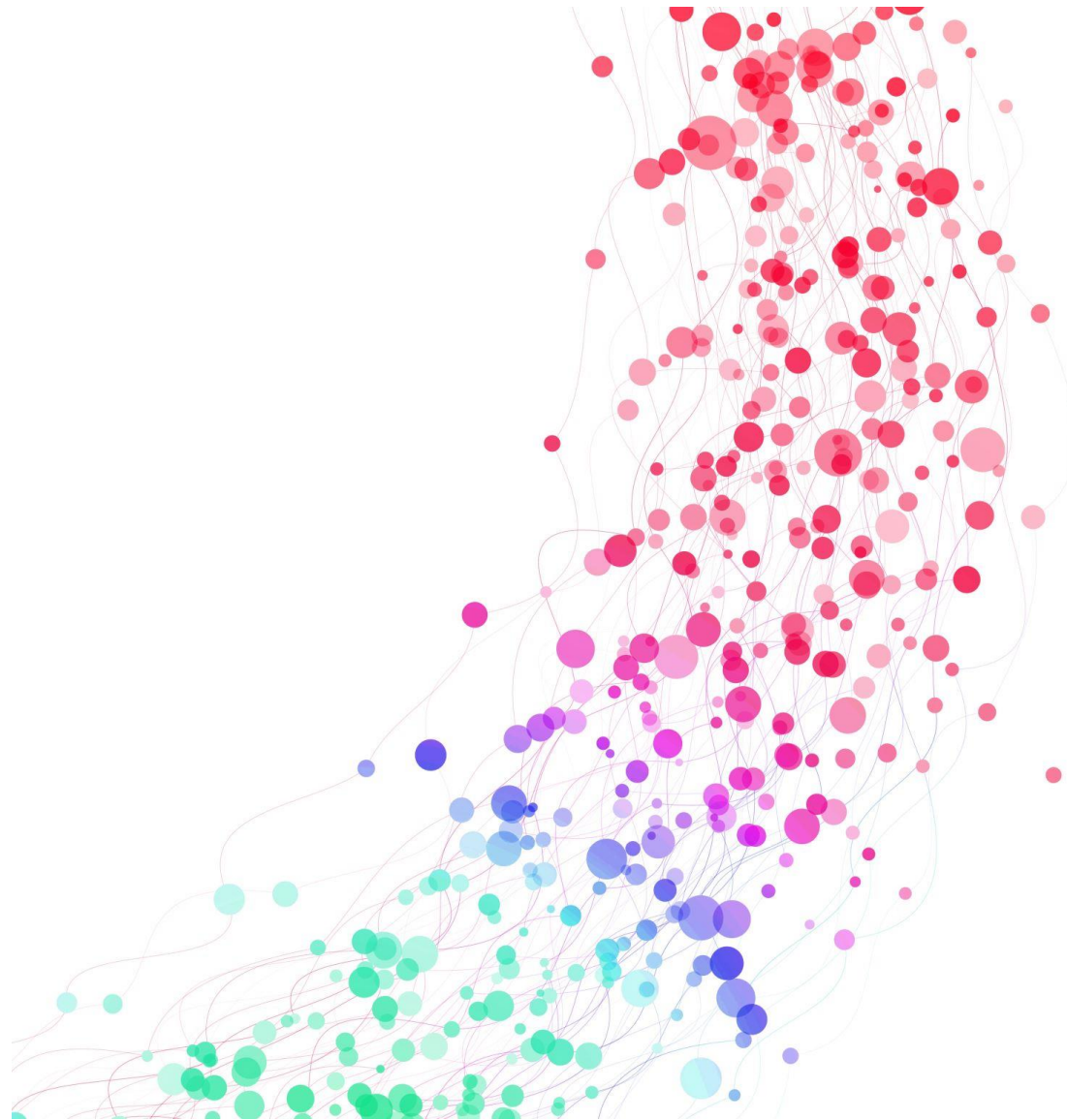
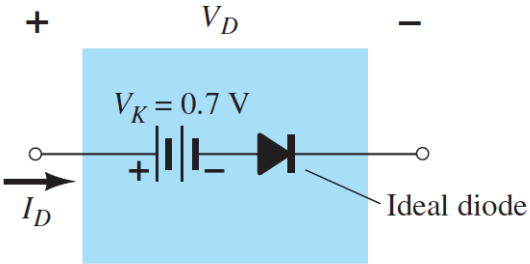
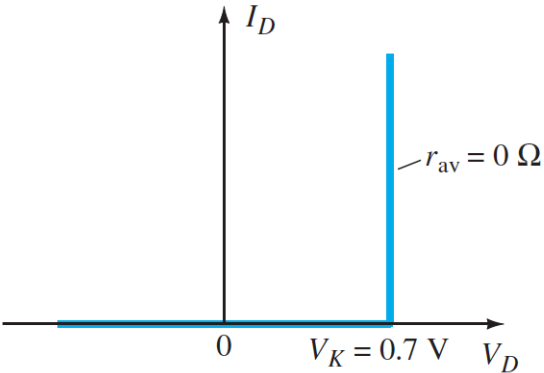


Fundamentals of Electronics









# ECE 101

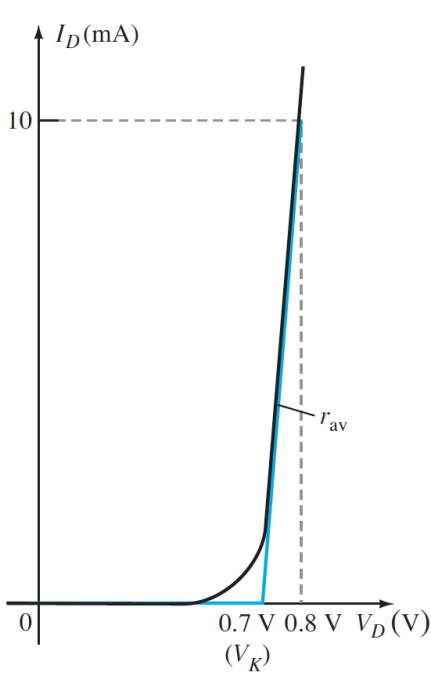

# Summary




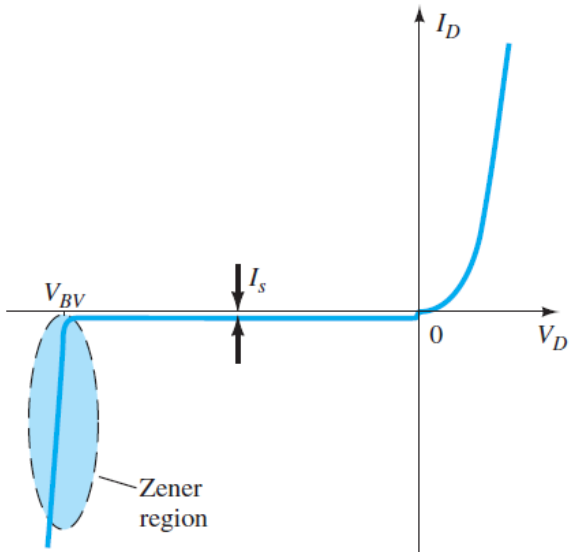


Si

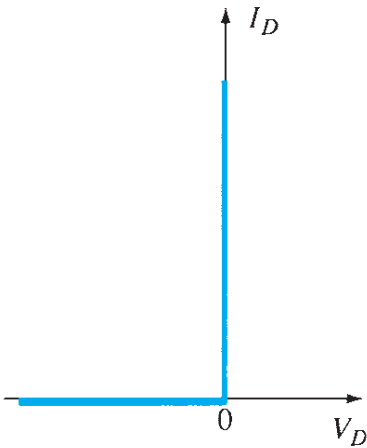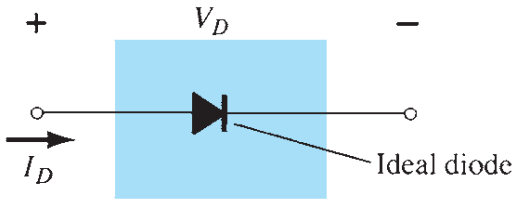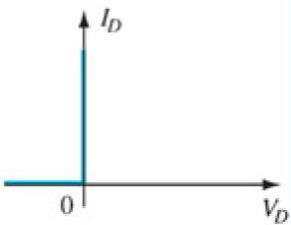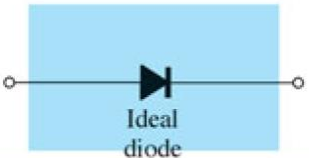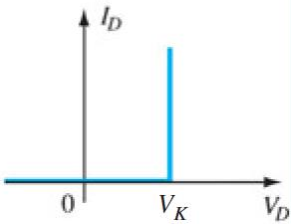
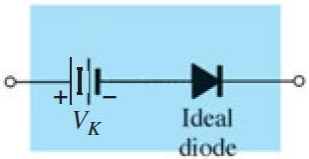
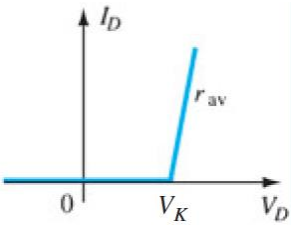
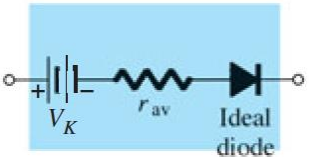


# Diode as clipper

## In series


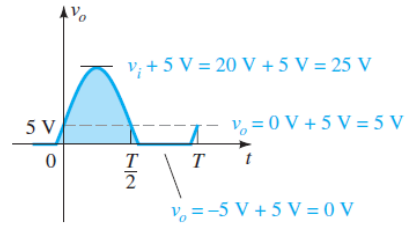
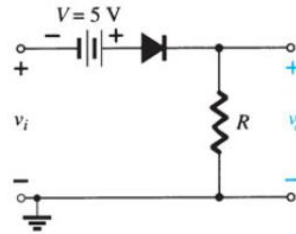
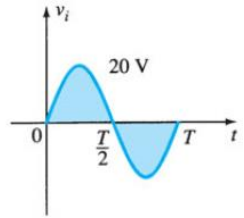
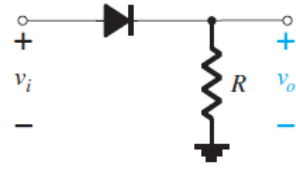


## In parallel

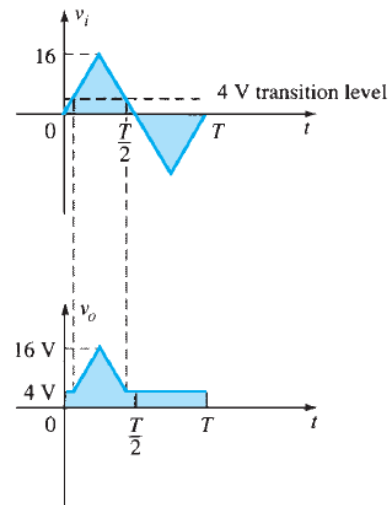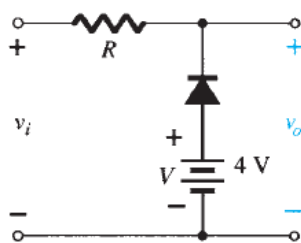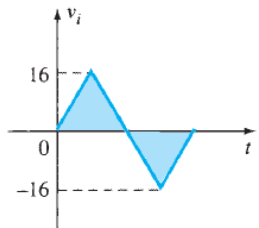
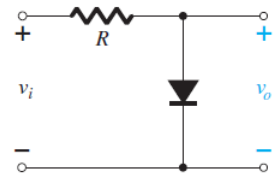

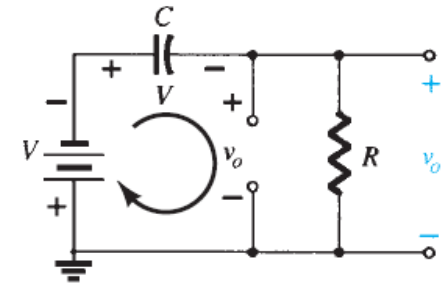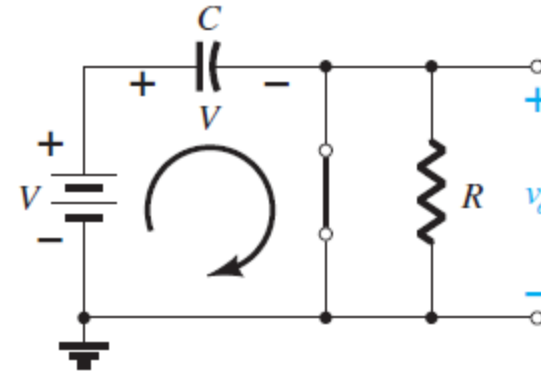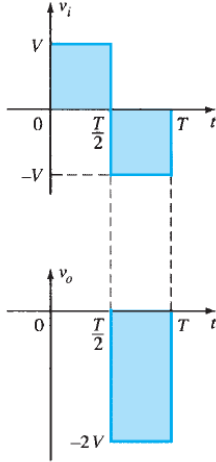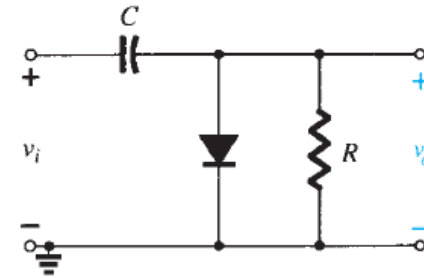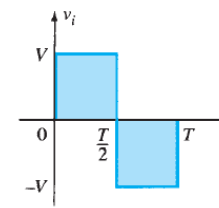
# Diode as clamper





Clamper is a circuit that changes the dc level of a waveform without changing its appearance.



Determine the output voltage


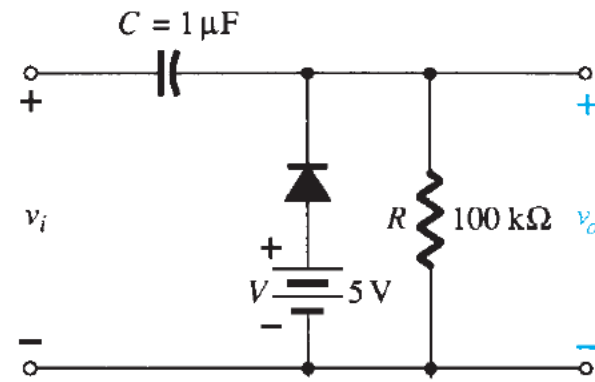
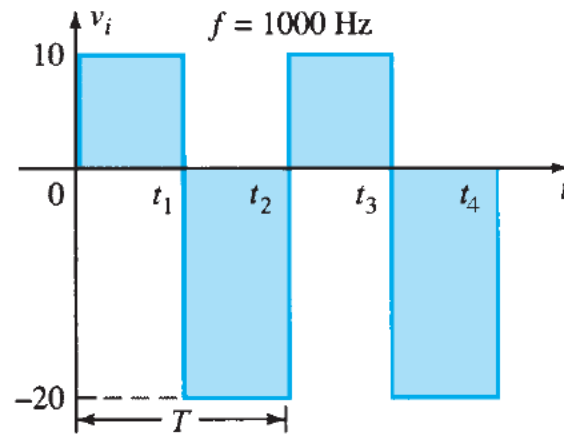


# Zener Voltage Regulation

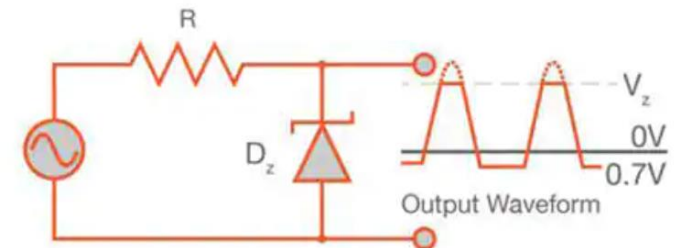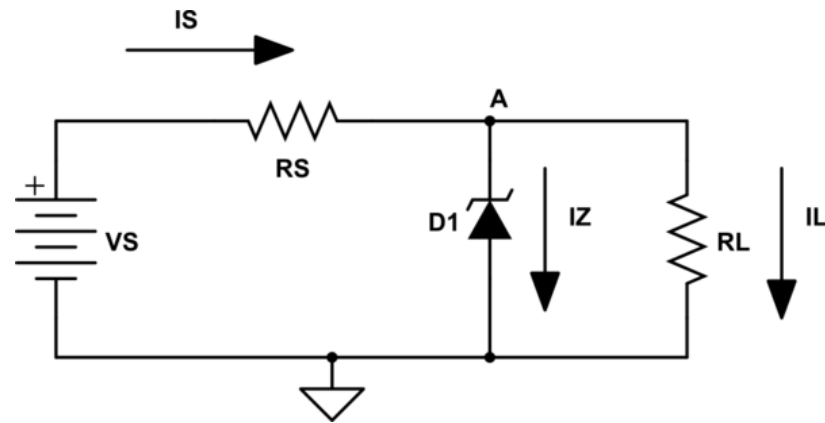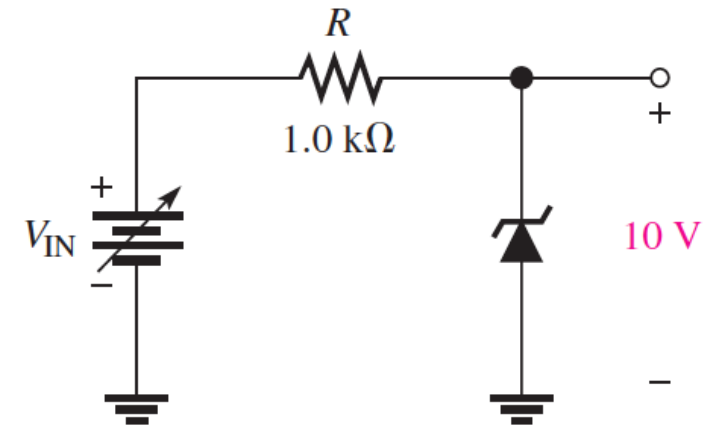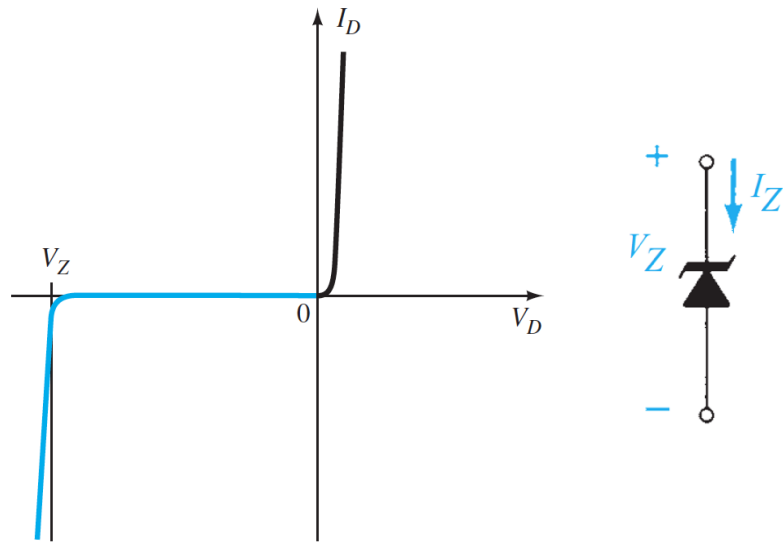

**Zener regulation**

# Voltage regulator

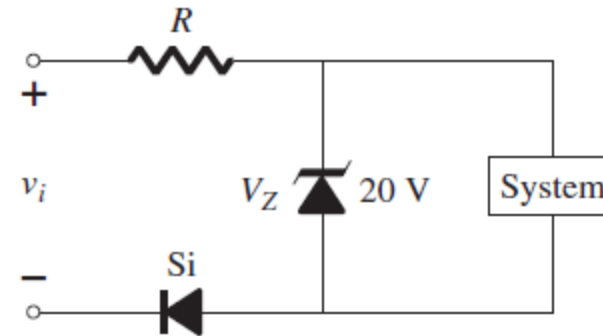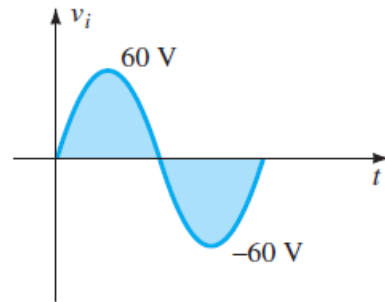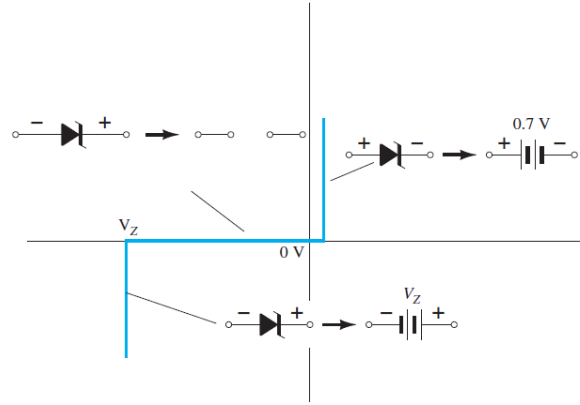


# The Transistor

Amplification and switching

## Transistor

- Key characteristic:
  - The transistor is a three-terminal device with the feature that the current through two terminals can be controlled by small changes we make in the current or voltage at the third terminal.
  - This control feature allows us to amplify small ac signals or to switch the device from an *on* state to an *off* state and back.
  - These two operations, *amplification* and *switching*, are the basis of a host of electronic functions.
  - This forms the basis for both bipolar junction transistors (BJT) and field effect transistors (FET).

# The transistor action - 1

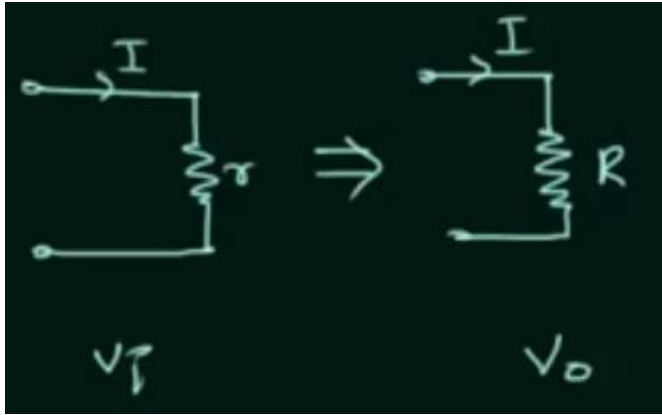


$$V_i = I \times \underline{r} \quad V_o = I \times \underline{R}$$
$$V_i < \underline{V_o} \quad (\text{amplification})$$

Active mode  
 $J_1 \rightarrow f-b. \quad R_{es} = 0$   
 $J_2 \rightarrow r-b. \quad R_{es} = \infty$






# The transistor action - 2

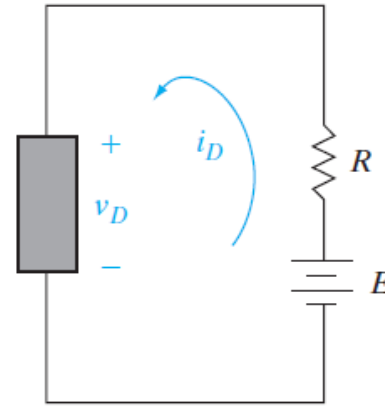

Load line

$$E = i_D R + v_D$$

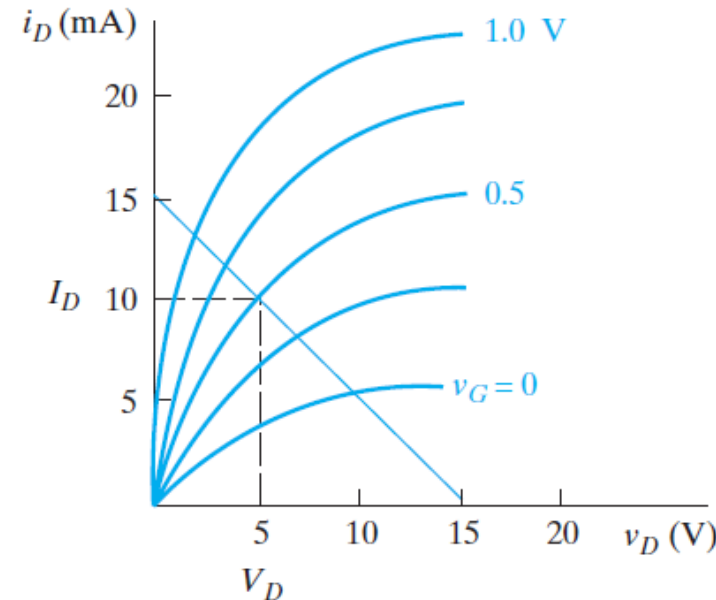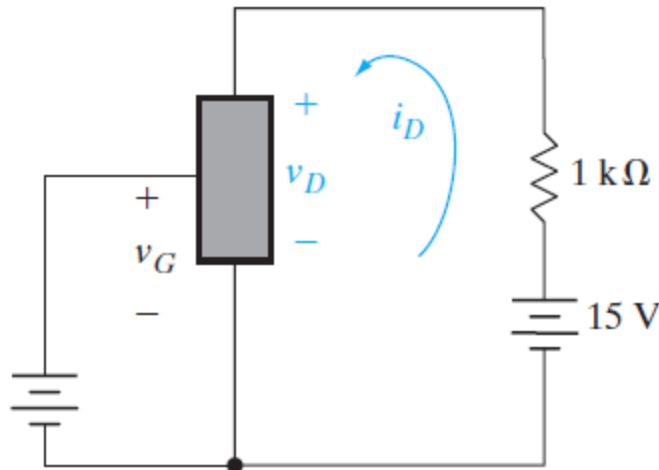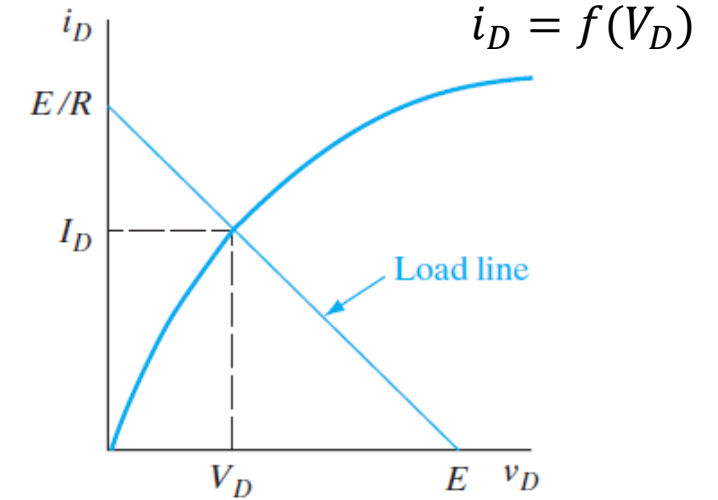







- If an ac source is added to the control voltage
  - We can achieve large variations in  $i_D$  by making small changes in  $V_G$
  - For example if  $V_G$  changes by value of 0.25V,  $V_d$  varies about its dc 2V.
  - Thus the amplification of the ac signal is  $2/0.25 = 8$ .
  - we can switch from the bottom of the load line to almost the top by appropriate changes in  $V_G$ .

For BJTs, this kind of control is achieved by current control.



# Field Effect Transistors

The idea
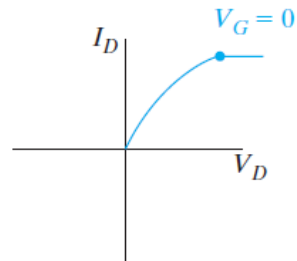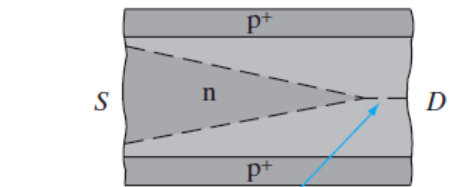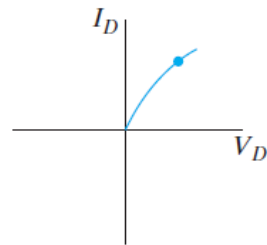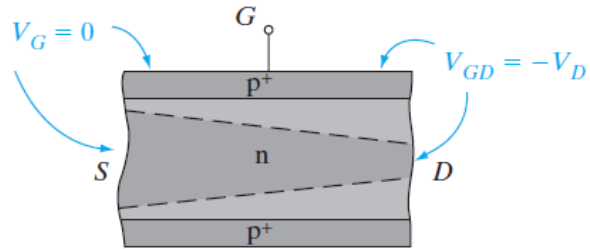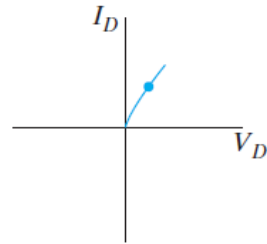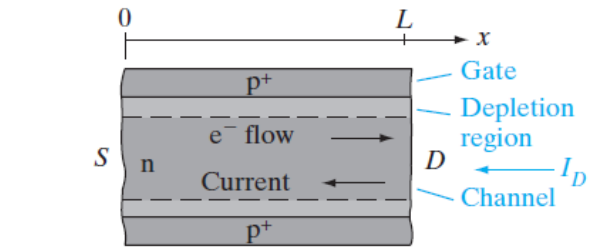
## Junction Field Effect Transistor: JFETs



Field-Effect Transistors

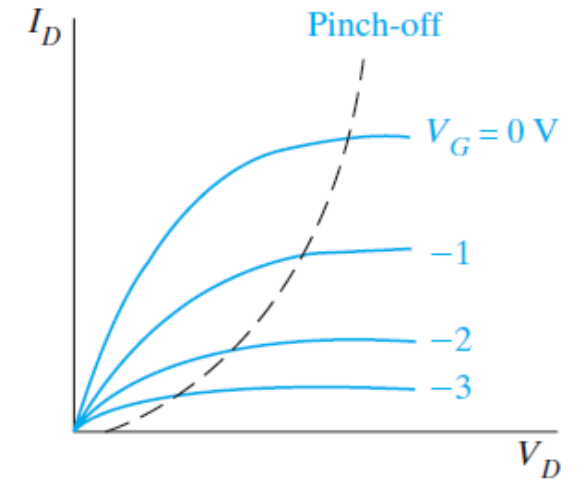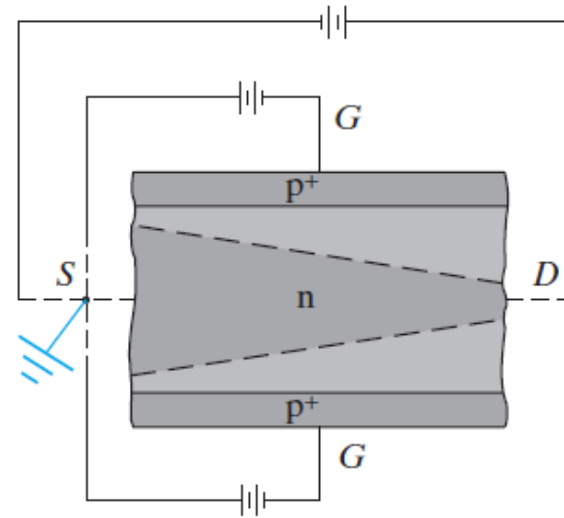

Gate control

**Thank you**