

$$\frac{12 - V_D}{R_1} = \frac{V_S}{R_2} = \frac{1}{2} K (3 - V_S - V_{TH})^2$$

$$\Rightarrow V_D$$

$$\Rightarrow V_S$$

$$\Rightarrow I_D$$

$$V_D > V_G - V_{TH}$$

Project (40 marks)

30 viva

5
simu

5
report

Sine wave generator
and
cosine wave generator

mixer



LPF

Op-amps:

High gain amplifiers

input impedance $\Rightarrow \infty$



output impedance $\rightarrow 0$

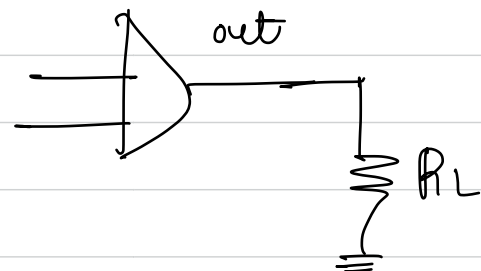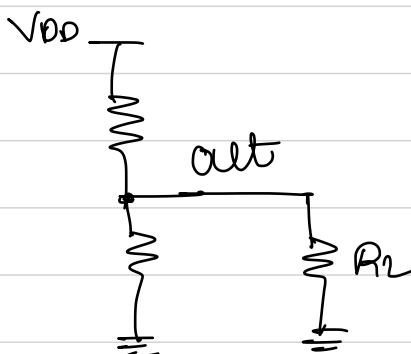


VCVS

V_p $\overset{+}{\rule{1cm}{0.4pt}}$

V_n $\overset{-}{\rule{1cm}{0.4pt}}$

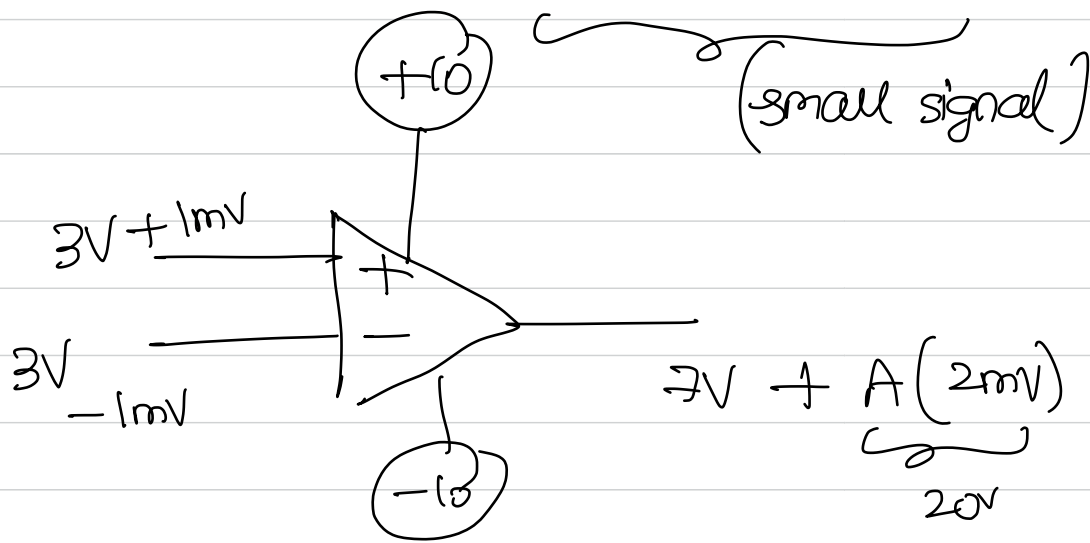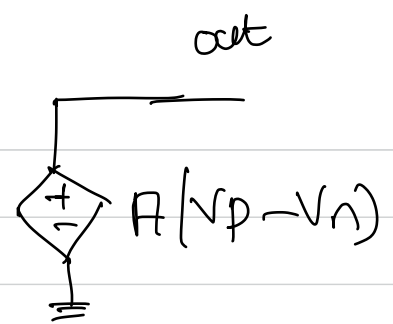

saturated to $10V$

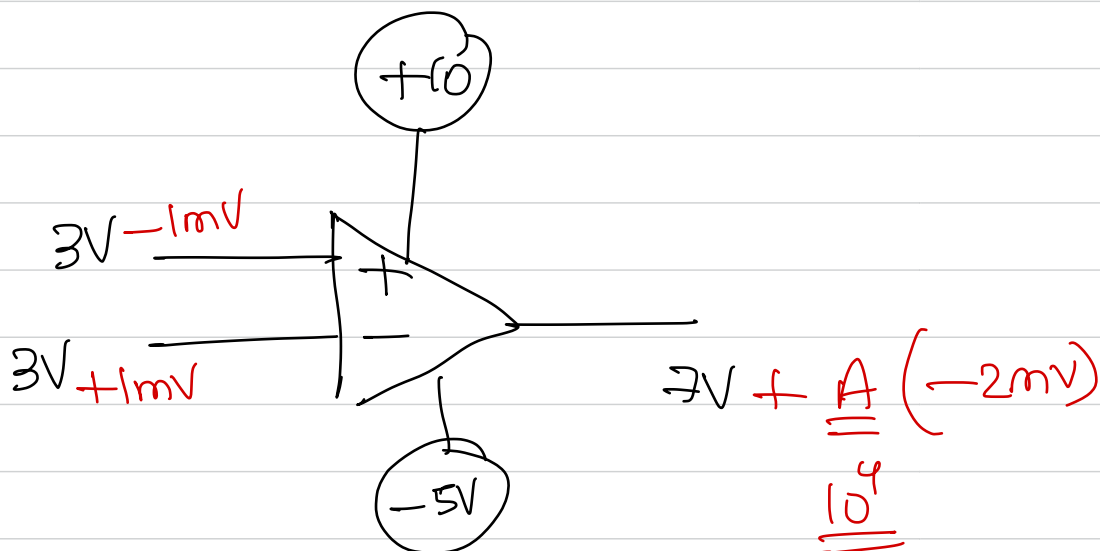

$7 + -20$



-13

output saturated to



$-5V$

Feedback:

Positive feedback:

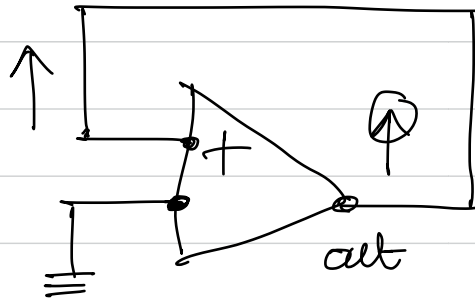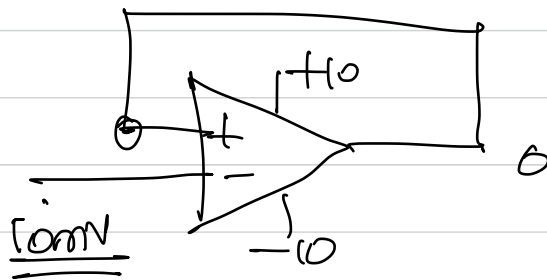


Negative feedback:

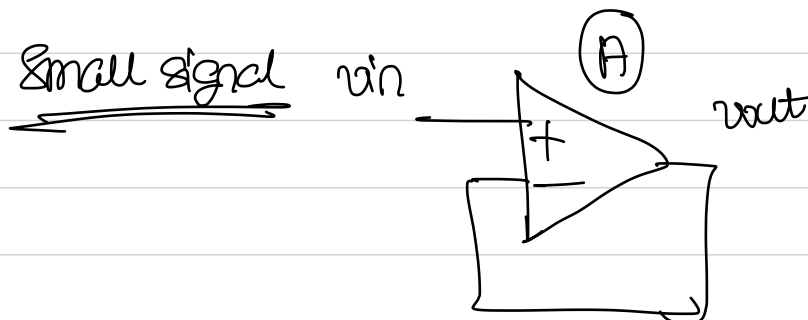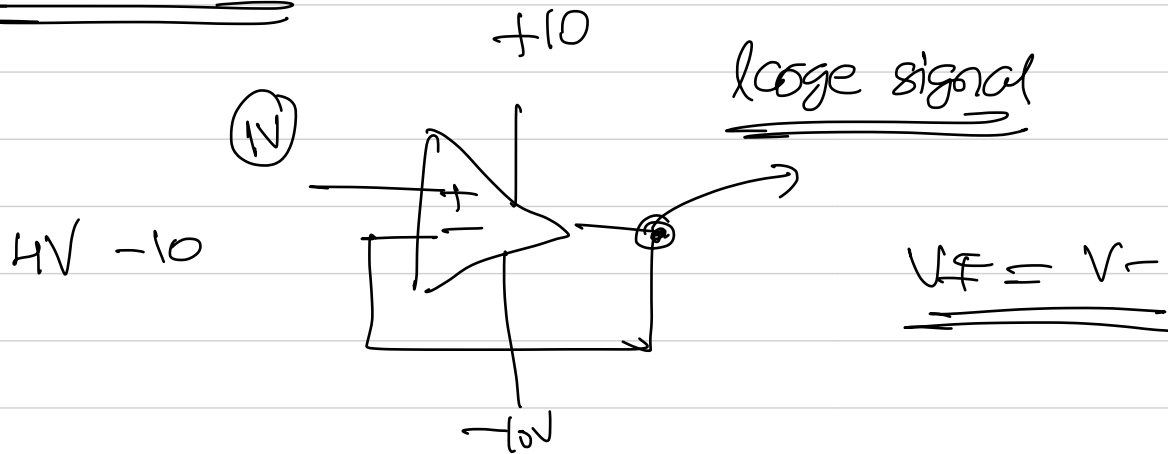

$$A(v_{in} - v_{out}) = v_{out}$$


$$\frac{v_{out}}{v_{in}} = \frac{A}{1+A} \approx 1$$
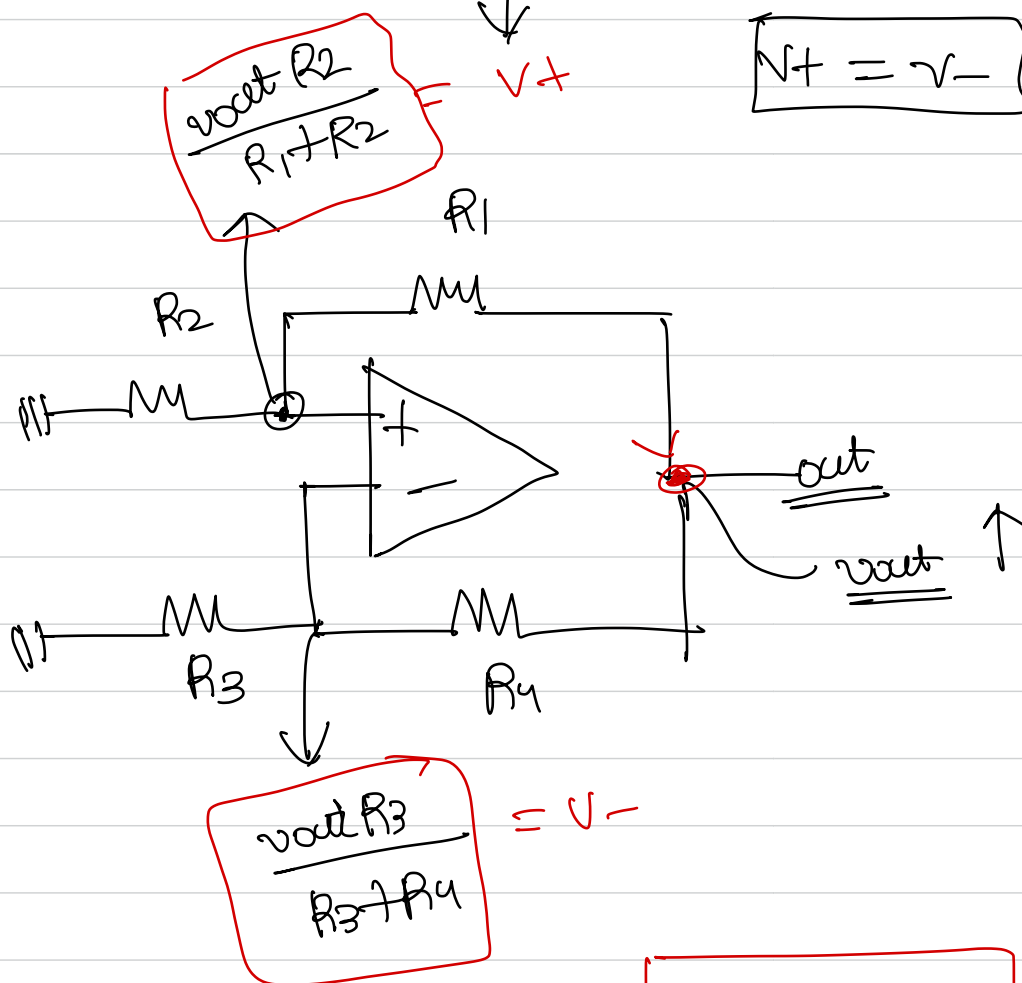
$$\underline{v_{out} = v_{in}} \quad \checkmark$$




$$V_+ > V_- \quad \text{+ve feedback}$$

$$V_+ < V_- \quad \text{-ve feedback}$$

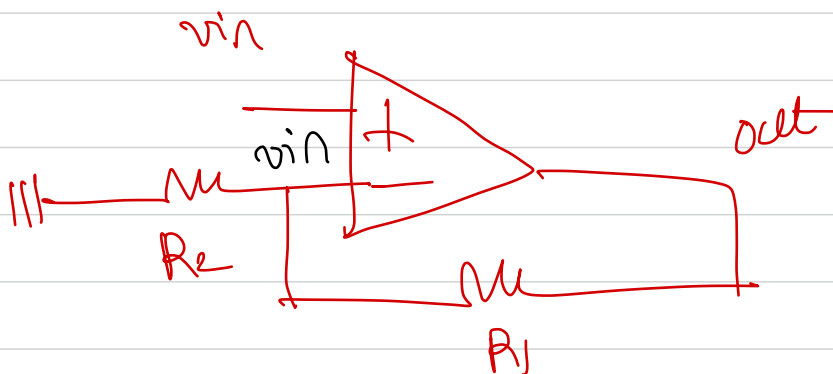

$$\frac{v_{out}}{v_{in}} = 1 + \frac{R_1}{R_2}$$

(NIA)

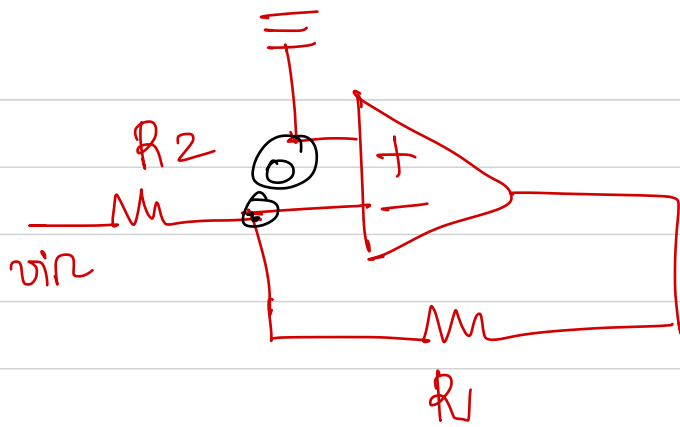


$$\frac{V_{out}}{v_{in}} = -\frac{R_1}{R_2}$$

(IA)

Positive feedback:

Oscillators:

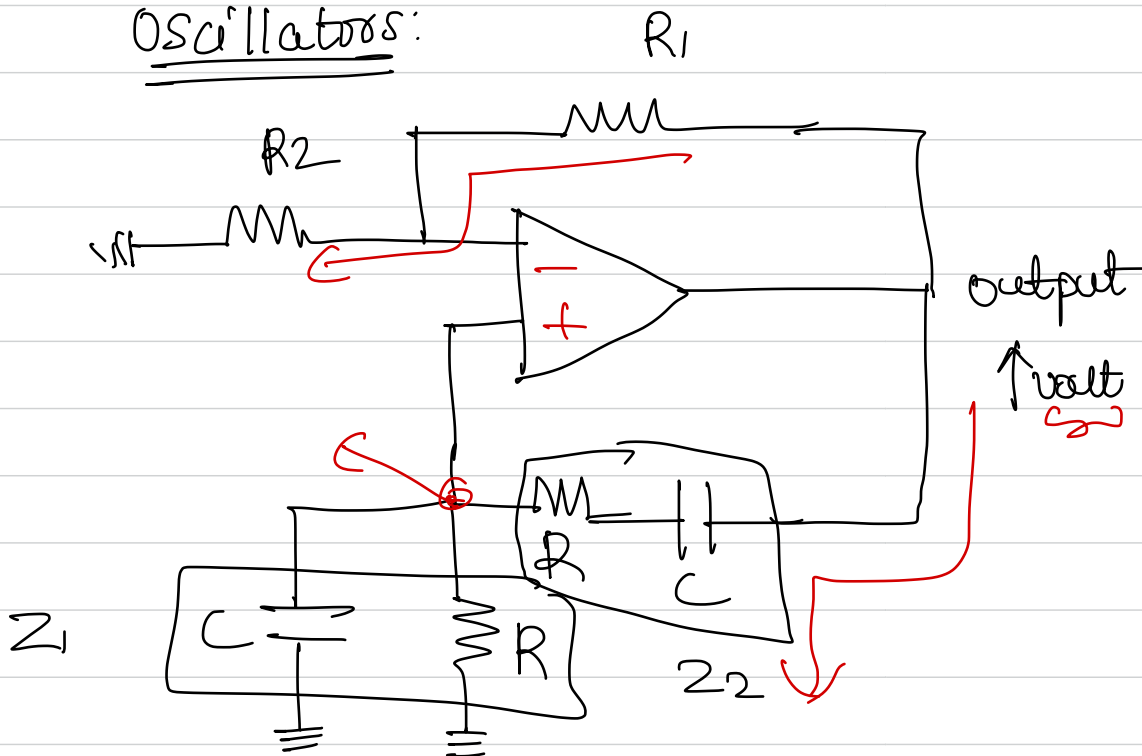

$$V_- = \frac{V_{out} R_2}{R_1 + R_2}$$

$$Z_1 = R \parallel \frac{1}{sC}$$

$$Z_2 = R + \frac{1}{sC}$$

$$V_+ = \frac{V_{out} Z_1}{Z_1 + Z_2}$$

$$\frac{V_{out} Z_1}{Z_1 + Z_2} > \frac{V_{out} R_2}{R_1 + R_2}$$

$$\left| \frac{Z_1}{(Z_1 + Z_2)} \frac{R_1 + R_2}{R_1} \right| > 1$$

$$\frac{\frac{R}{1+SRC}}{\frac{R}{1+SRC} + \frac{SRC+1}{SC}} \times \left(1 + \frac{R_2}{R_1}\right) > 1$$

$$\Rightarrow \frac{SRC}{SRC + (SRC+1)^2} \times \left(1 + \frac{R_2}{R_1}\right) > 1$$

$$\frac{SRC}{SRC + 3SRC + 1}$$

$$\left[\frac{1}{3 + \left(SRC + \frac{1}{SRC}\right)} \right] \times \left(1 + \frac{R_2}{R_1}\right)$$

$$\frac{1}{3 + j\omega RC + \frac{1}{j\omega RC}}$$

$$3 + j\omega RC - \frac{j}{\omega RC}$$

$$\left[3 + j\left(\omega RC - \frac{1}{\omega RC}\right) \right] \times \left(1 + \frac{R_2}{R_1}\right)$$

$$\frac{1}{3 + j\left(\omega RC - \frac{1}{\omega RC}\right)} \times \left(1 + \frac{R_2}{R_1}\right)$$

$$\tan^{-1}(\omega RC)$$

$$V_t = \frac{V_{out} Z_1}{Z_1 + Z_2}$$

$$\frac{V_{out}}{Z_1 + Z_2} \cdot \frac{Z_1}{3 + j\left(\omega RC - \frac{1}{\omega RC}\right)}$$

$$j\left(\omega RC - \frac{1}{\omega RC}\right) = 0$$

$$\omega RC = \frac{1}{\omega RC}$$

$$\frac{1}{1 + j\omega RC}$$

$$\omega = \frac{1}{RC}$$

But \rightarrow single frequency signal

$$\left(\omega = \frac{1}{RC}\right)$$

Req \Rightarrow (2)

$$\left(\frac{Z_1}{Z_1 + Z_2} \right) \left(1 + \frac{R_2}{R_1} \right) > 1$$

$$\left(\frac{1}{3} \right) \left(1 + \frac{R_2}{R_1} \right) > 1$$

$$\boxed{\frac{R_2}{R_1} > 2} \quad \checkmark$$

$\sin($

