

# Bipolar Junction Transistor


→ Structure of BJT

→ BJT Operations

→ Amplifier :

◦ A Basic Amplifier :-

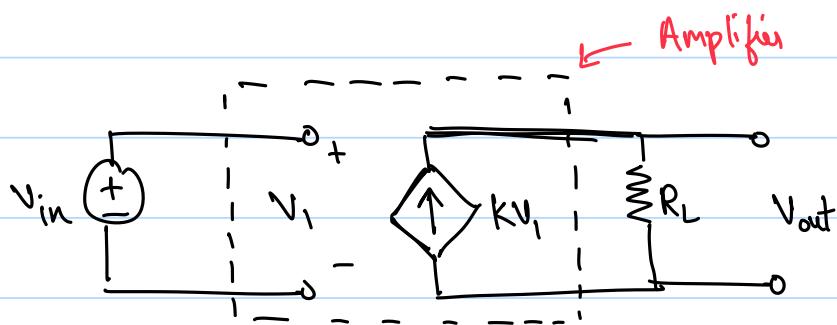We can easily construct a amplifier using dependent sources . ex:



$$V_{out} = (KV_1) R_L$$

$$V_1 = V_{in} \text{ (obv)}$$

$$\Rightarrow V_{out} = KR_L V_{in}$$

$$\Rightarrow V_{out}/V_{in} = KR_L$$

• If  $KR_L > 1$ , then this circuit can act like an amplifier


• Problem: We do not have dependent sources easily available.

• Therefore we use transistors to build amplifiers.

→ Four Observations : (From PN)

◦ Carrier Injection :

In a reverse biased PN junction,

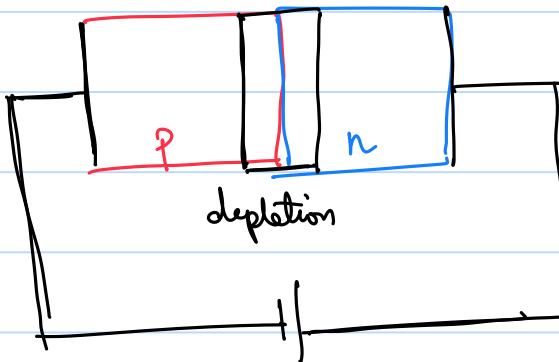


- Suppose some electrons are injected into the depletion region, The electric field in the depletion region is directed from n to p.

Therefore electron will go to the n side and towards the +ve terminal of the battery

- As such we can maintain a constant current from the depletion to the n section and to the battery

◦ Effect Of Asymmetric Doping :

In a forward biased pn junction

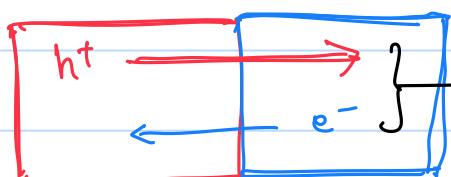


2 components of the fwd bias


- If  $N_D \gg N_A$ , the diffusion current is heavily dominated by electrons.

→ Structure and Symbol of BJT:-

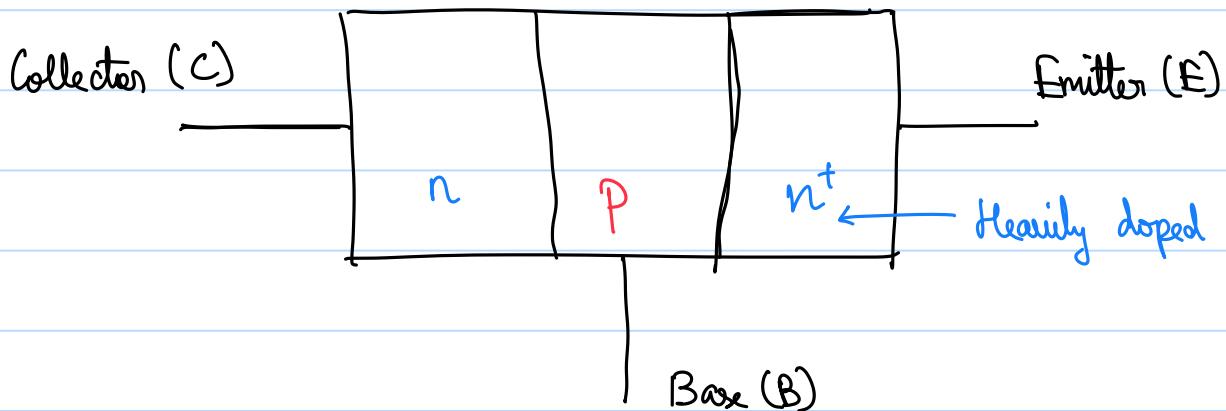- 3 terminal device w/ 3 semiconductor region.





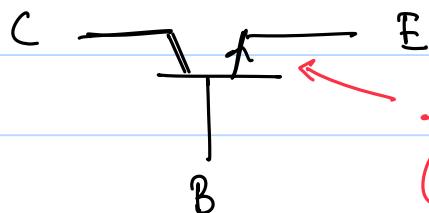- Since n<sup>+</sup> is heavily doped, the device is asymmetric.
- It can be seen that C is the input terminal and E is the output, from the names given.
- Symbol




*Since the device must be asymmetric  
(Specific for npn transistor).*

- For amplification,

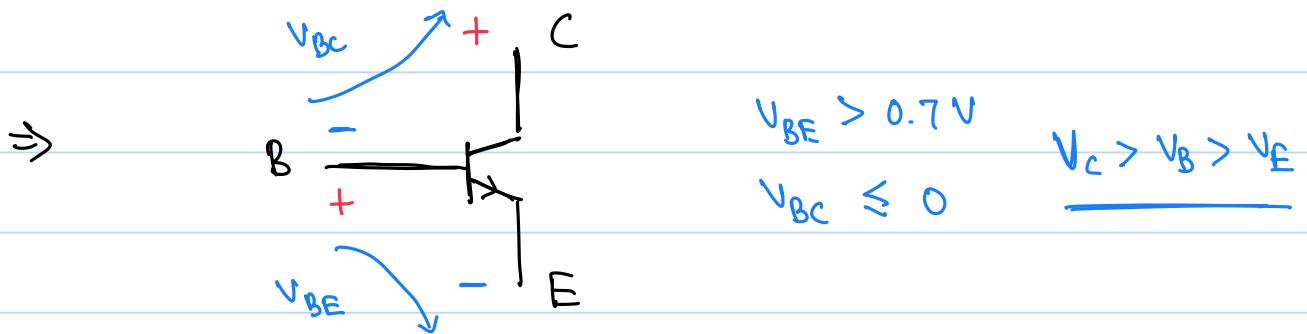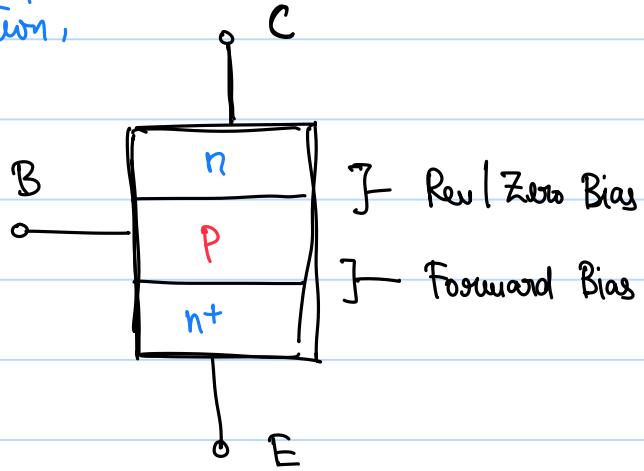


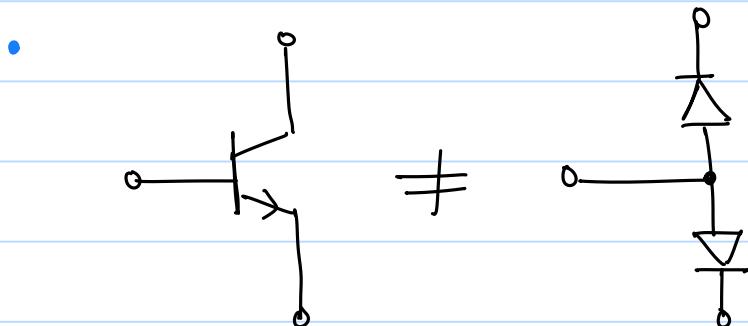This is known as forward active biasing / region.




- The base region is very thin in a good BJT.

## → Operation of BJT:-

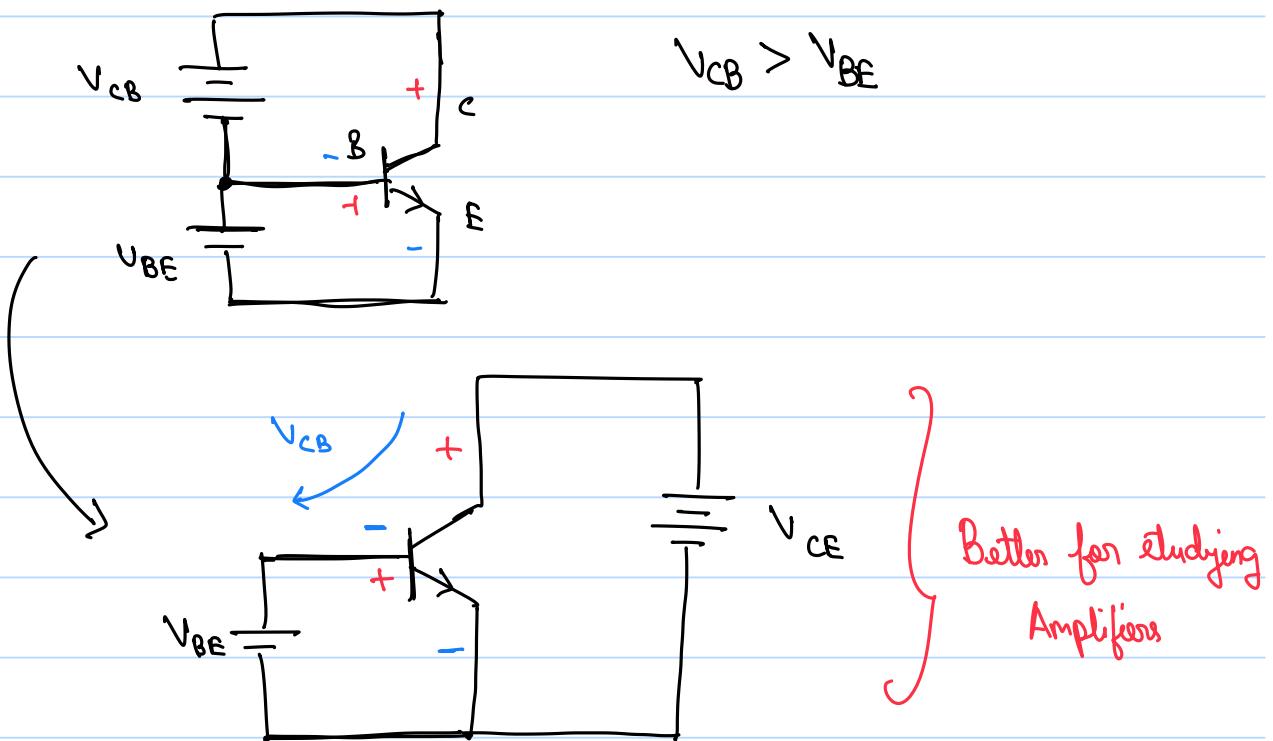


$$V_{CE} = V_{CB} - V_{BE} \geq 0$$
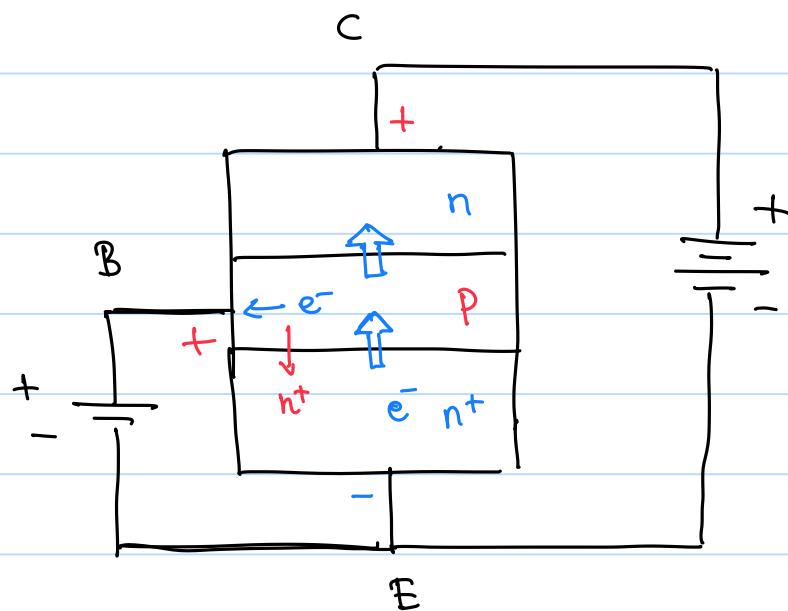
$$\Rightarrow V_{CB} \geq V_{BE} > 0.7V$$




- Since Base-Emitter Junction (BEJ) is forward biased, current will flow in the BE loop.

- This BE current will be dominated by electrons (due to highly doped n+).
- Since CBJ is in reverse bias, it will have a depletion region.
- The electrons coming from the emitter has 2 options:
  - 1) Exit through the base terminal and get absorbed by the battery.
  - 2) Go to the CBJ depletion region.
- If the electron enters the CBJ depletion region, it will be swept across into the Collector region (Carrier injection), ie, the Collector region "collects" the electrons, after which they go to the battery.
- Most electrons from the EBJ will go to the CBJ. This is why base is very thin.

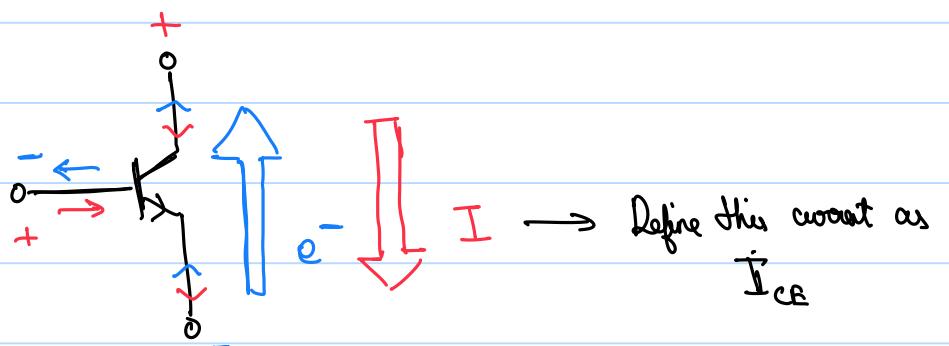


- The base region is thin and sustain little voltage across it  
⇒ Negligible drift current.

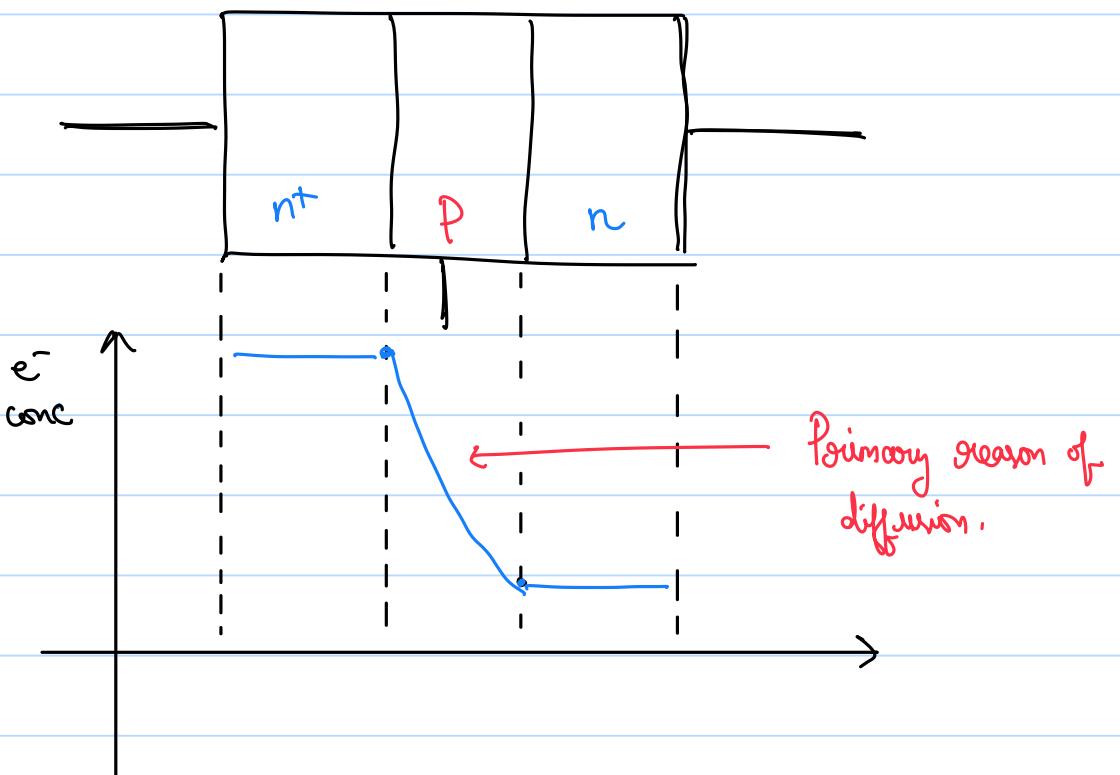- Is the current flow  $I_{CB}$  is majorly governed by diffusion



- If  $V_{BE}$  increases, the current across EBJ increases (forward bias).

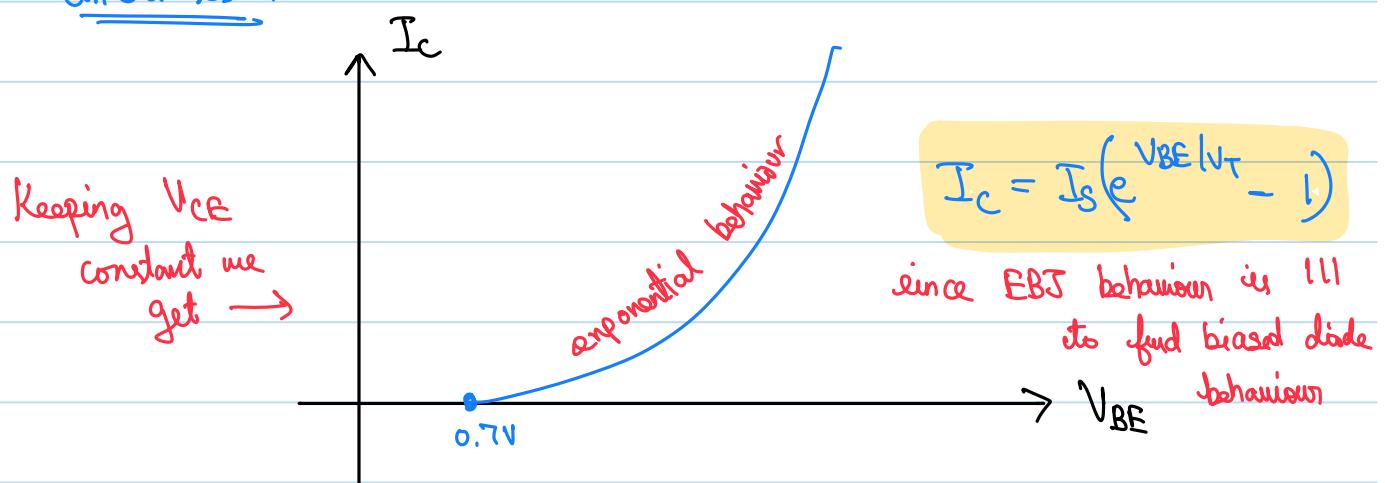— If  $i$  in EBJ,  $i$  in CBJ also increases  $\Rightarrow$  Collector current increases.



- $I_S = A_E \frac{q n_i^2 D_n}{w_B N_B} \leftarrow \text{Diffusivity of } e^- \Rightarrow I_S \propto T \text{ (By } n_i^2\text{)}$

$\uparrow \quad \downarrow$   
Emitter Area      Base Width  
 $\leftarrow \text{Doping of Base}$

- $I_c = I_s (e^{\frac{V_{BE}}{V_T}} - 1) \Rightarrow I_c$  is dependent of  $V_{BE}$   
Voltage Dependent Current

- If  $\Delta V_{BE} = +60\text{ mV}$ , the current increases by a factor of 10. (Same as forward biased diode)

$$I_c = I_s (e^{\frac{V_{BE}}{V_T}} - 1) \approx I_s e^{\frac{V_{BE}}{V_T}} \quad (\text{same approximation as diode})$$

$$\Rightarrow V_{BE} = V_T \ln(I_c/I_s)$$

Example:

The cross sectional area of a transistor is doubled and  $V_{BE}$  is decreased by 60mV. What is the change in the collector current?

We know,  $I_s \propto A \therefore I_s \rightarrow 2I_s$



$$\Rightarrow I_c = 2I_s (e^{\frac{V_{BE}}{V_T}} - 1) \Rightarrow I_{c2} = 2I_{c1}$$

Since 60mV decrease in  $V_{BE}$  creates a 10 times decrease in  $I_c$ .


$$I_{c3} = \frac{2I_{c1}}{10} \Rightarrow 0.2I_{c1}$$

$\therefore$  The new collector current is 0.2 times the initial one.

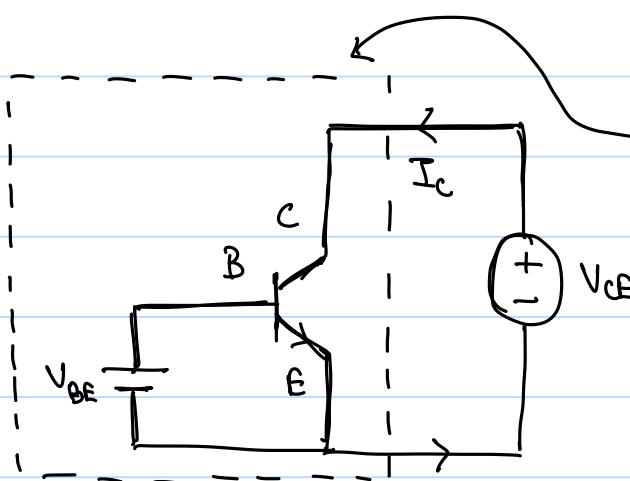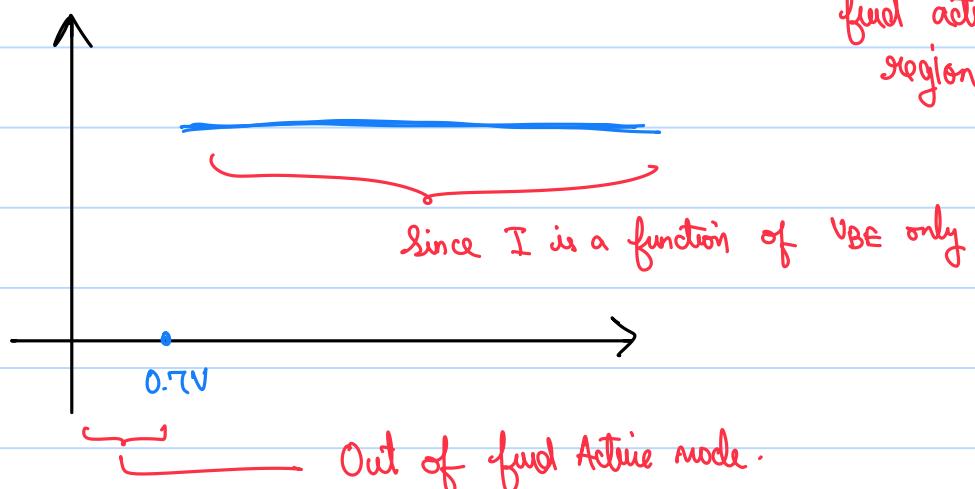
- Now if we kept  $V_{BE}$  constant and vary  $V_{CE}$  (within the *forward active region*)



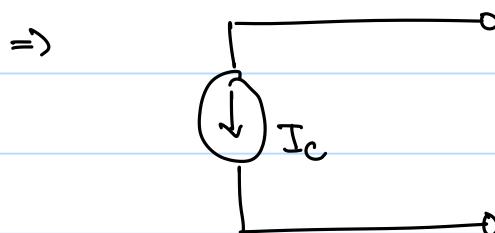
This is a device such that a variation in  $V_{CE}$  will NOT create a change in current, ie, An ideal current source.



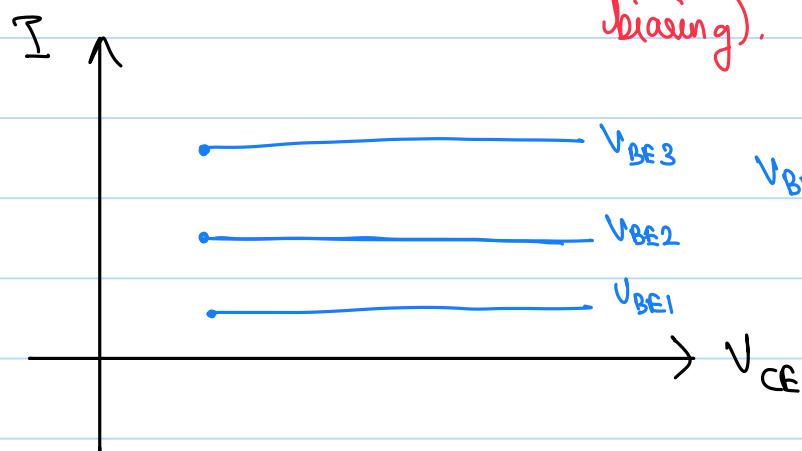If  $V_{BE}$  is kept constant, the transistor can act as a current source (provided *forward active biasing*).



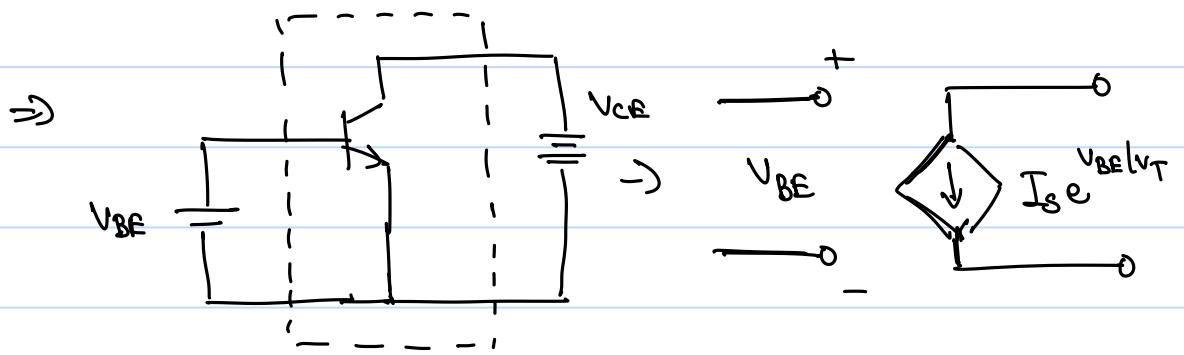Therefore, the device is also a **Moltage dependent courrent source**.



- Terminal Currents:

- 1) Collector Current:

$$I_C = I_S e^{V_{BE}/V_T}$$

- 2) Base Current:

From the electrons that come from the emitter, it was seen that a majority of them will go into the collector region.

- However a small amount of the electrons may exit the device through the base terminal and get absorbed by the battery, or recombine with the holes of the base region

- The above 2 components form the base current.

- Base current  $\propto$  Collector Current


$$\Rightarrow I_B \propto I_C$$

$$\Rightarrow I_C = \beta I_B \quad \text{In practice } \beta : 50 - 200 .$$

- $\beta$  is termed as the current gain of the transistor (common emitter current gain - Sedra Smith).

$$- I_B = \frac{I_S}{\beta} (e^{\frac{V_{BE}}{V_T}} - 1)$$

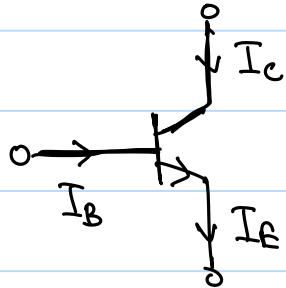- $I_B$  is directed into the base region



By KCL we get,


$$\begin{aligned} I_E &= I_C + I_B \\ &= \left( \frac{\beta + 1}{\beta} \right) I_S e^{\frac{V_{BE}}{V_T}} \end{aligned}$$

Since usually  $\beta \gg 1$ ,

$$I_E \approx I_S e^{\frac{V_{BE}}{V_T}} = I_C$$

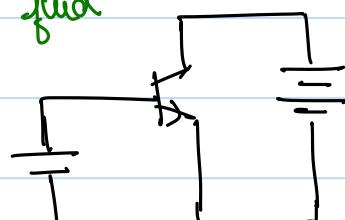Example:

A BJT has a collector current of 1 mA and  $I_S = 10^{-16}$  A. How much is  $V_{BE}$ , given  $\beta = 100$ ?



Ans:

Given,  $I_C = 1 \text{ mA}$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow V_{BE} = V_T \ln \frac{I_C}{I_S}$$

$$V_{BE} = (26) \ln \frac{10^{-3}}{10^{-16}} \text{ mV}$$

$$\begin{aligned}
 V_{BE} &= 26 \ln 10^3 \text{ mV} \\
 &= 338 \ln 10 \text{ mV} \\
 &= 338 \times 2.303 \text{ mV} \\
 &= 778.273 \text{ mV} \\
 &\approx \underline{\underline{0.78 \text{ V}}}
 \end{aligned}$$

Example: In the given scenario, if  $\beta$  is known to be 50, find base current.

Ans:


Given  $I_C = 1 \text{ mA}$  &  $\beta = 50$ .

$$\beta = \frac{I_C}{I_B}$$

$$\begin{aligned}
 I_B &= \frac{I_C}{\beta} = \frac{1}{50} \text{ mA} \\
 &= \underline{\underline{0.02 \text{ mA}}}
 \end{aligned}$$

→ BJT as an Amplifier :-


- We know that,

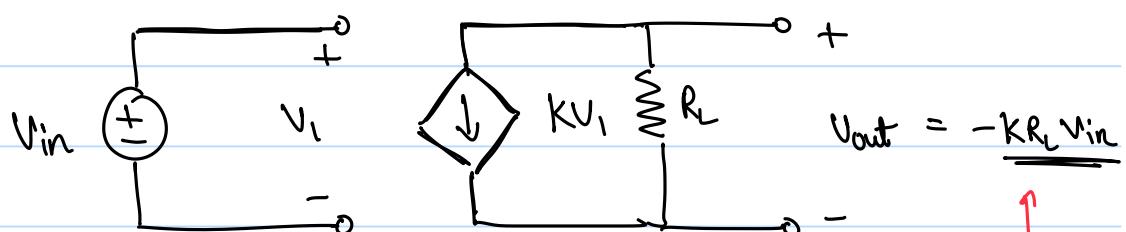

is a simple amplifier

inverted output  
due to direction  
of  $KV_1$ .

- Using a BJT,

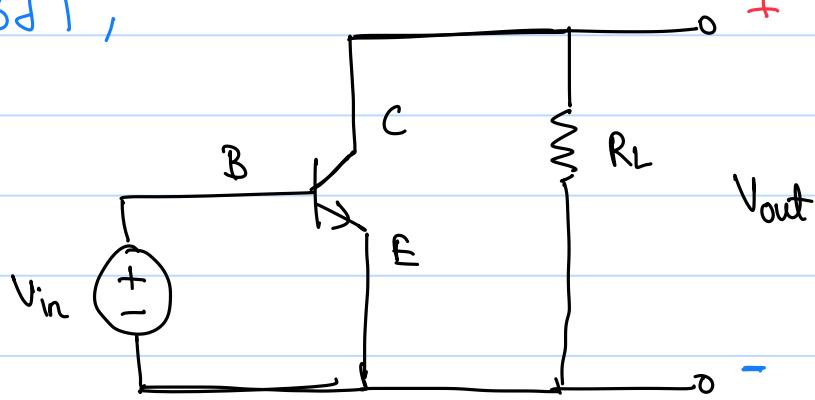

starting place  
for making  
a BJT  
Amplifier

Clearly, the design is flawed and will not work. Analysing the circuit,

$$\text{Assume } I_S = 5 \times 10^{-16} \text{ A} \quad (\text{Standard for BJT})$$

$$I_C = I_S (e^{\frac{V_{in}}{V_T}} - 1) = (5 \times 10^{-16}) (e^{\frac{V_{in}}{V_T}} - 1) \text{ A}$$

$$V_{out} = -R_L (5 \times 10^{-16}) (e^{\frac{V_{in}}{V_T}} - 1) \text{ V}$$

Take an example signal  $V_{in}$  let  $V_{in}$  start at zero and goes to 10 mV at time t  $\rightarrow$  Doubtful considering that  $V_{BE}$  should be  $> 0.7V$ .

After time t in  $V_{out}$ ,

$$\begin{aligned} V_{out} &= -R_L I_S (e^{\frac{10\text{mV}}{V_T}} - 1) \\ &= -R_L (5 \times 10^{-16}) (e^{10/25} - 1) \\ &\approx -R_L (2.35 \times 10^{-16}) \text{ V} \end{aligned}$$


Therefore, for any reasonable gain in the output,  $R_L$  must be impractically large.  $\rightarrow$  Not a usable amplifier.

- I-V Characteristics of a BJT :-



- By the above graph we can see why our  $I_c$  was very low in our calculations.

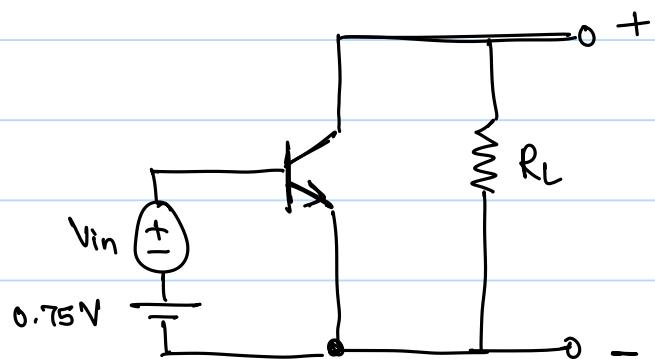- To combat this, maybe we can introduce a battery in series with  $V_{in}$ .



- If  $V_{in} = 0$ ,  $V_{BE} = 0.75V$ , which can produce a significant amount of current,

$$\begin{aligned}
 I_c &= I_s (e^{\frac{V_{BE}}{V_T}} - 1) \\
 &= (5 \times 10^{-5}) (e^{\frac{750}{26}} - 1) \\
 &\approx \underline{1.7 \text{ mA}}
 \end{aligned}$$

When  $V_{in}$  goes to 10 mV,

$$I_C = (5 \times 10^{-5}) (e^{\frac{760}{123}} - 1)$$
$$\approx 2.48 \text{ mA}$$

$$\Delta I_C = 2.48 - 1.7 = 0.78 \text{ mA} \rightarrow \text{significant}$$

Therefore, we can use a practical value of resistance to create a significant gain in the output.


$$\text{If gain} = 10, \quad \Delta V_{out} = 10 \Delta V_{in}, \quad \Delta V_{in} = 10 \text{ mV}$$
$$\Rightarrow \Delta V_{out} = 100 \text{ mV}$$

$$\Delta V_{out} = R_L \Delta I_C = 100 \text{ mV}$$

$$R_L = \frac{100 \text{ mV}}{\Delta I_C} = \frac{100}{0.78} \approx 128 \Omega$$

An  $R_L$  of 128  $\Omega$  will give us a gain of 10 in this case.

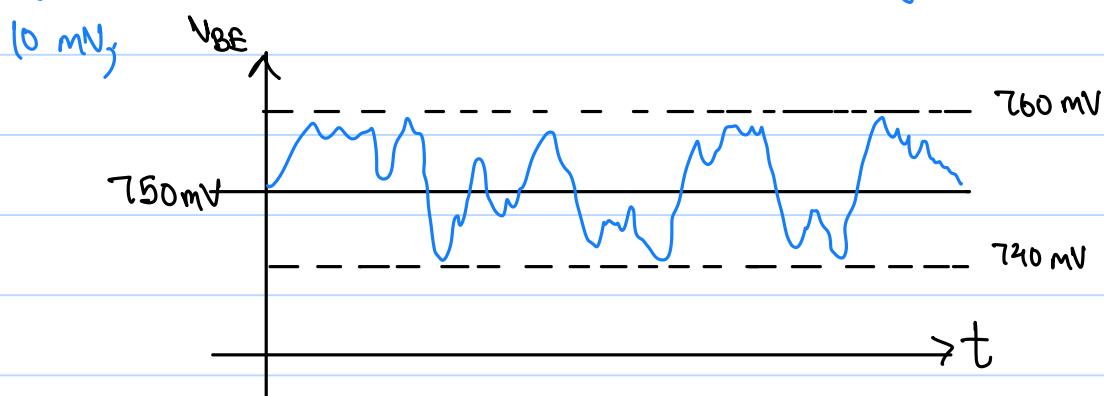If we use this model with a  $V_{in}$  signal that varies by 10 mV,




We will get a gain of 10, ie, an output signal of amplitude 100 mV

- This process of adding a voltage source so that the transistor can amplify, is called **biasing the transistor**
- Biasing is done to move the transistor into the forward active region before applying the input voltage.
- The base values of  $V_{BE}$ ,  $I_C$ ,  $I_B$ ... is defined as **operating point**.

In the prev. situation,  $V_{BE} = 0.75V$  and  $I_C = 1.7mA$  is our operating point.

→ Observations :-

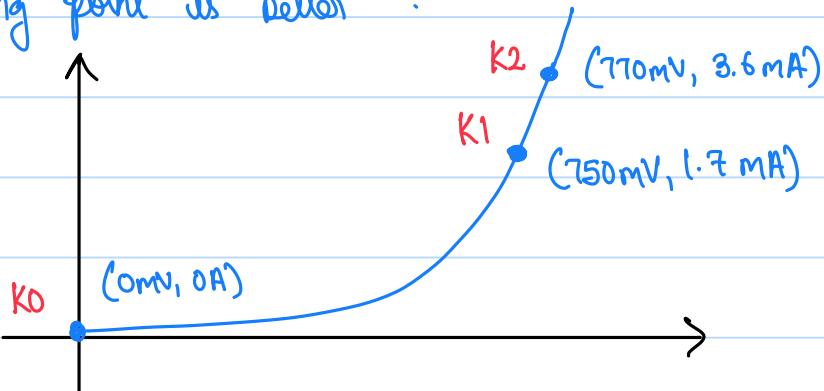- ① A bipolar transistor can act as a voltage dependent current source, since its collector current is exponentially related to the base-emitter voltage.
- ② The operating point determines how the transistor responds.
- ③ Which operating point is "better"?



Obviously  $K_0$  is a bad OP as seen before, but which is

Better among K1 and K2?

In K2,

At  $V_{in} = 0 \text{ mV}$ ,

$$I_c = I_s (e^{\frac{770}{23}} - 1) \approx 3.6 \text{ mA}$$

At  $V_{in} = 10 \text{ mV}$

$$I_c = I_s (e^{\frac{780}{23}} - 1) \approx 5.3 \text{ mA}$$

$$\therefore \Delta V_{in} = 10 \text{ mV} \Rightarrow \Delta I_c = 5.3 - 3.6 = 1.7 \text{ mA}$$

If  $\Delta V_{out} = 100 \text{ mV}$


$$R_L = \frac{\Delta V_{out}}{\Delta I_c} = \frac{100}{1.7} = 58.823$$

Therefore, the case K2 requires a lesser resistance requirement, ie, has a stronger response to the change

- An increase in the biasing voltage of  $V_{BE}$  results in an increase in the sensitivity of the amplifier.
- This increase in sensitivity is denoted by Transconductance.

° Transconductance:

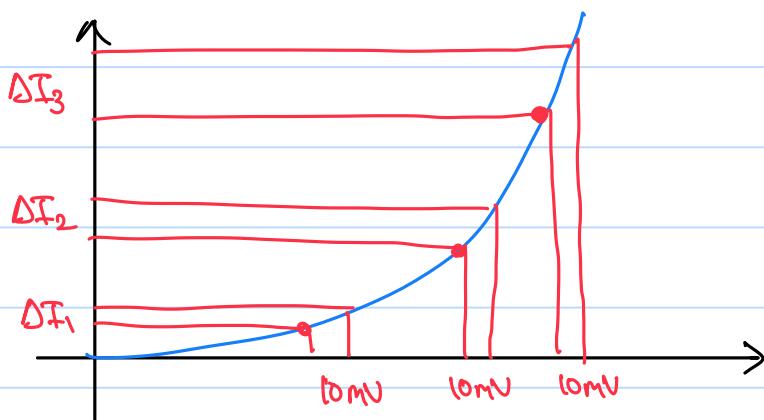- In the forward active region, if we plot  $I_c$  vs  $V_{BE}$



We see that  $\Delta I_1 < \Delta I_2 < \Delta I_3$

$\Rightarrow$  Slope of the relation is increasing ( $\frac{dI_c}{dV_{BE}}$ )

- The slope  $\frac{dI_c}{dV_{BE}}$  is termed as transconductance. ( $g_m$ )

In the scenario we have  $\Delta I_1 = 0.78 \text{ mA}$  and  $\Delta I_2 = 17 \text{ mA}$  each for a  $\Delta V_{in}$  of  $10 \text{ mV}$ . Assume this  $\Delta V_{in}$  to be small, calculate the transconductance at OP 1 and OP 2.

$$g_m = \frac{dI_c}{dV_{BE}} \approx \frac{\Delta I_c}{\Delta V_{BE}} \quad (\text{for small } \Delta V_{BE})$$

$$g_{m1} = \frac{0.78 \mu\text{A}}{10 \mu\text{V}} = 0.078 \text{ A/V} = 0.078 \text{ S} \quad (\text{Siemens})$$

$$g_{m2} = \frac{1.7 \text{ mA}}{10 \mu\text{V}} = 0.17 \text{ A/V} = 0.17 \text{ S}$$

- Since wekt  $I_c = I_s (e^{\frac{V_{BE}}{V_T}} - 1)$

$$g_m = \frac{d}{dV_{BE}} I_s (e^{\frac{V_{BE}}{V_T}} - 1) = I_s \frac{d}{dV_{BE}} e^{\frac{V_{BE}}{V_T}}$$

$$g_m = \frac{I_s}{V_T} e^{\frac{V_{BE}}{V_T}}$$

Transconductance in itself is exponentially dependent on  $V_{BE}$

$$\approx g_m = \frac{I_c}{V_T}$$

- If  $I_c = 1\text{mA}$  at room temp,  $g_m = 0.04\text{S}$ .

• The very first circuit made for amplification failed because of **low transconductance**. The biasing step increased the transconductance.

- If  $g_m = 0 \rightarrow$  No Amplification.

- $g_m > 0 \Rightarrow$  need certain  $I_c \Rightarrow$  need certain  $V_{BE}$
- 
- Form the desired OP

Using the new formula, calculate transconductance of OP1 and OP2 in the given scenario.

$$g_{m1} = \frac{I_{c1}}{V_T} = \frac{1.7\text{mA}}{26\text{mV}} \quad g_{m2} = \frac{I_{c2}}{V_T} = \frac{3.6\text{mA}}{26\text{mV}}$$

$$= 0.0653 \text{ S} \quad = 0.1384 \text{ S}$$

$$\text{Old } g_{m1} = 0.078$$

$$\text{Old } g_{m2} = 0.17 \text{ S}$$


- Therefore, from this discussion, we get the fact that the response of the amplifier is stronger, greater the biasing voltage.

- Tradeoff is power consumption from the biasing voltage source.



- The approximation in the derivative can be taken if  $V_{BE}$  is a small

fraction of  $V_T$ .


- IV Characteristics :-

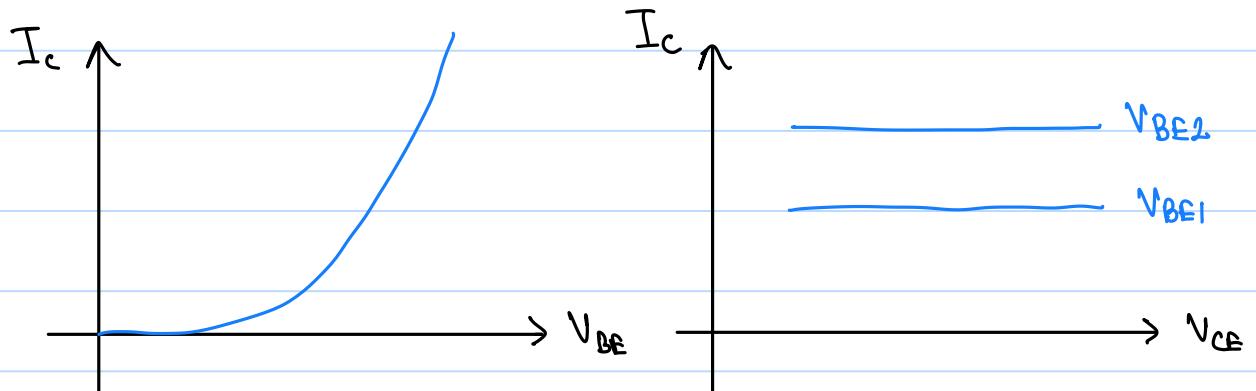

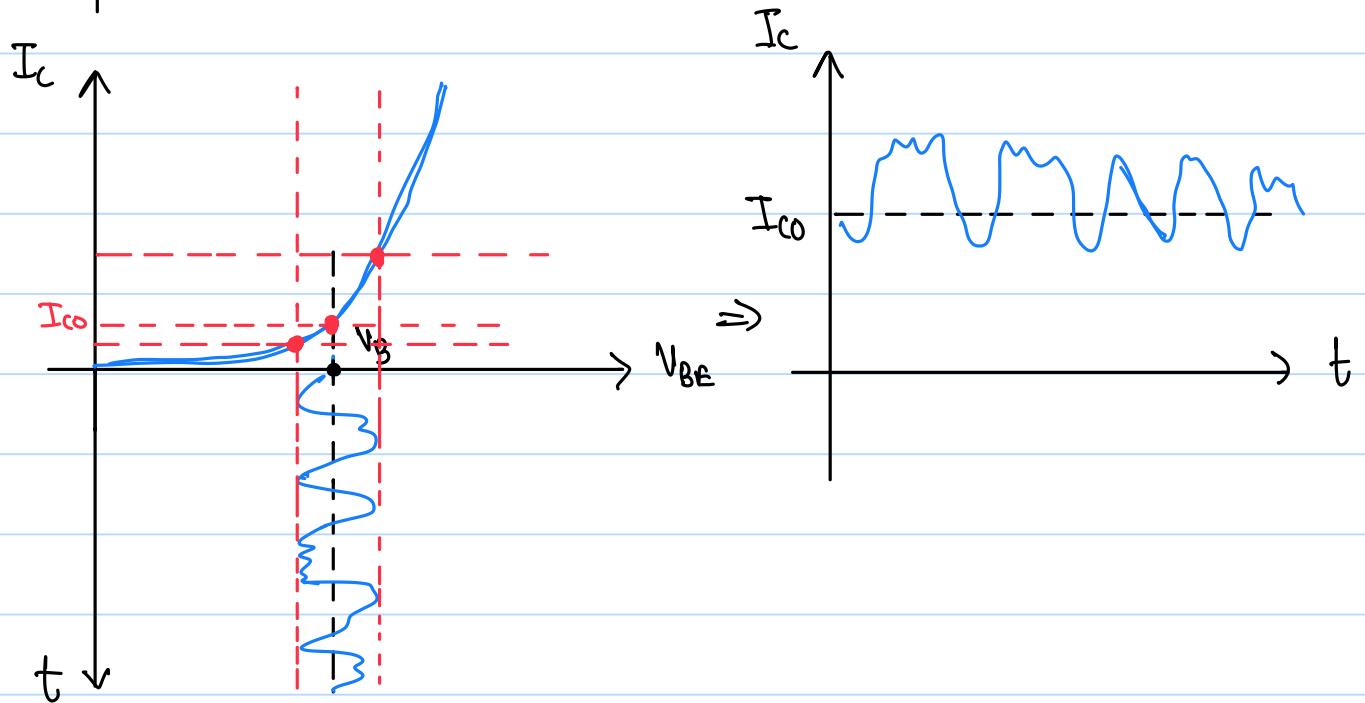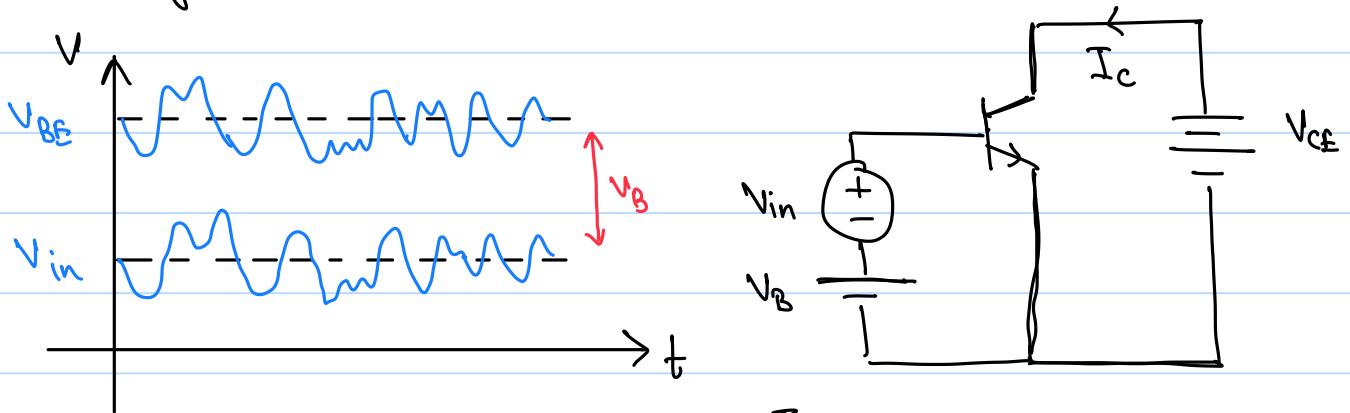- Combining Time Response w/ IV Characteristics :-



→ Simple BJT Models :-

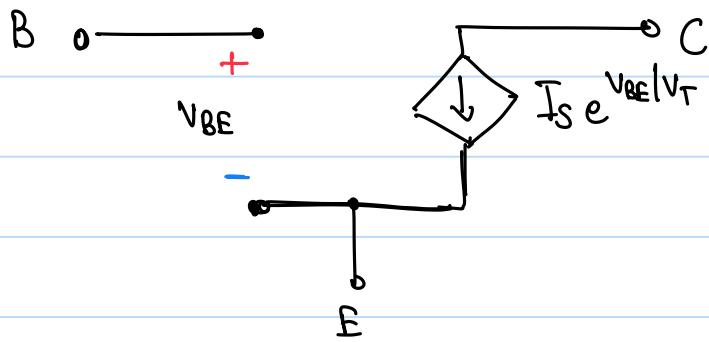


The current source goes directly over the base into the emitter due to the presence of base current

(Not very accurate ob.)

- To model the base current, w.r.t,


$$I_B = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}}$$

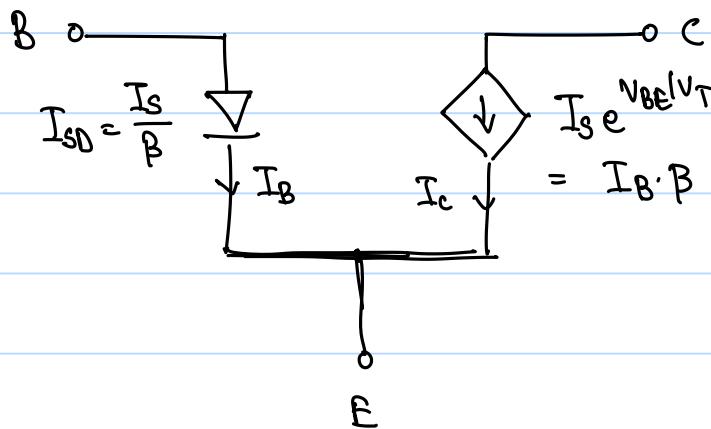We can model this behaviour with a diode of gen. sat current  $\frac{I_S}{\beta}$ .




- This model is valid only for forward active biasing.

Example:

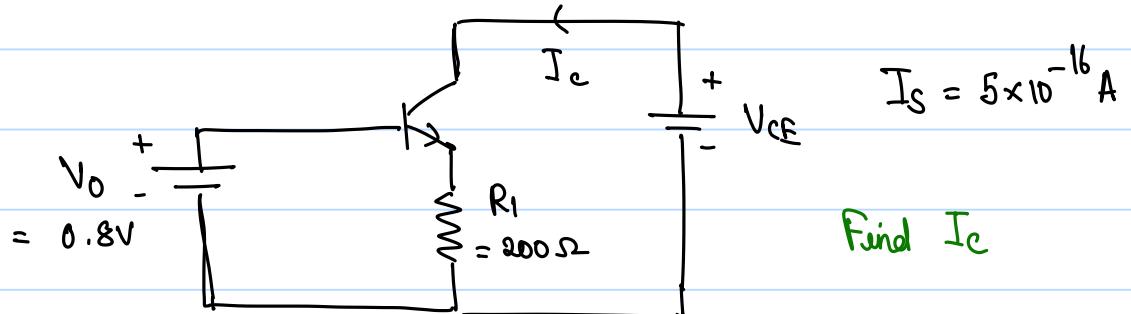

Applying the model,

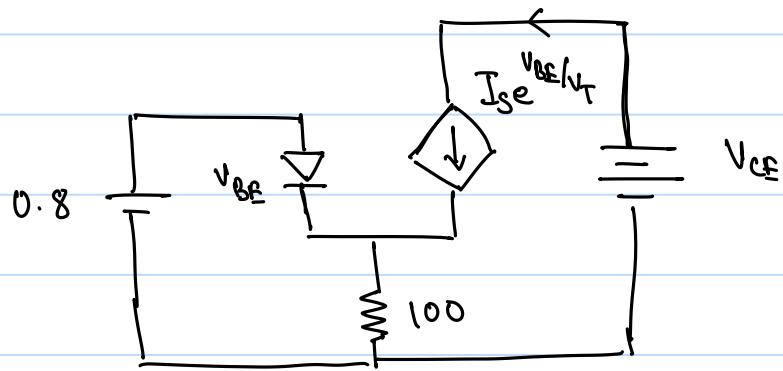

Let  $I_E \approx I_c$ . By KVL,


$$V_o = V_{BE} + R_1 I_E \approx V_{BE} + R_1 I_c$$

w.k.t  $V_{BE} = V_T \ln \frac{I_c}{I_S}$

$$\Rightarrow V_o = V_T \ln \frac{I_c}{I_S} + R_1 I_c$$

We can solve this by iteration by assuming a value for  $I_c$  in  $V_T \ln I_c / I_S$  and solving for  $I_c$ 's new value.

Example :

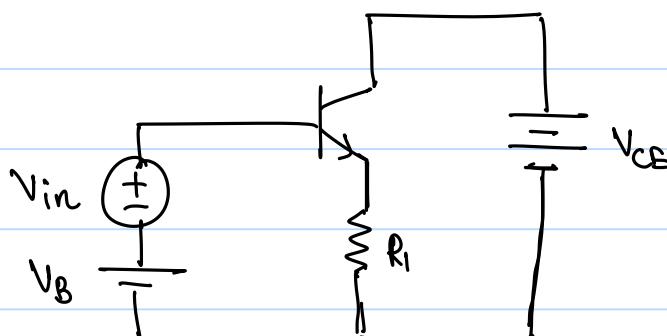

$$V_{in} = V_m \sin \omega t$$

Find  $I_c$


from prev. qn., we can see that

$$V_{in} + V_o = V_T \ln \frac{I_c}{I_S} + R_1 I_c$$

$$= V_m \sin \omega t + V_0 = V_T \ln \frac{I_c}{I_s} + R_i I_c$$

Here  $I_c$  is a function of time, ie, it is not constant. Hence we cannot use the iterative method.

If we use a simpler situation,

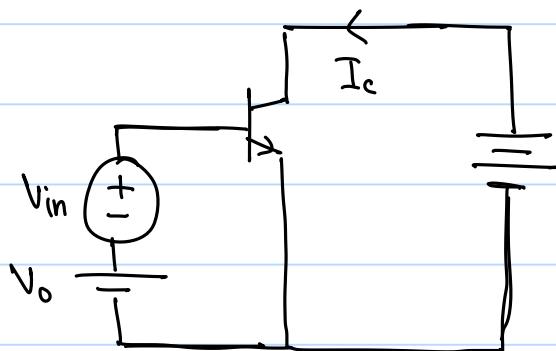

By KVL,

$$V_{in} + V_o = V_{CE}$$

$$= V_{in} + V_o = V_T \ln \frac{I_c}{I_s}$$

$$= I_c = I_s e^{\frac{V_{in} + V_o}{V_T}} =$$

$$= I_c = I_s \exp(V_m \sin \omega t + V_o / V_T)$$

$$= I_s \underbrace{\exp(V_o / V_T)}_{\text{const}} \exp(V_m \sin \omega t / V_T)$$

Therefore, the behaviour of  $I_c$  is complicated in general case / large signal models. (exponential of a sinusoid)

## Small Signal Operation :

The signal perturbs the operating point by only a small amount, ie,

$$V_m \ll V_{bias}$$

$$I_c = I_s \exp(V_o/V_T) \exp(V_m \sin \omega t / V_T)$$

$$\approx I_s \exp(V_o/V_T) \left( 1 + \frac{V_m \sin \omega t}{V_T} \right) \quad V_m \ll V_T$$


OP current

$$= I_c = I_{c0} + \frac{I_{c0}}{V_T} V_m \sin \omega t$$


$\rightarrow g_m$



- In small signal operations,
  - $I_c$  varies sinusoidally
  - $I_c = I_{c0} + g_m V_m \sin \omega t$  → Can be observed using Time and IV Analyser.

## Small Signal Model:

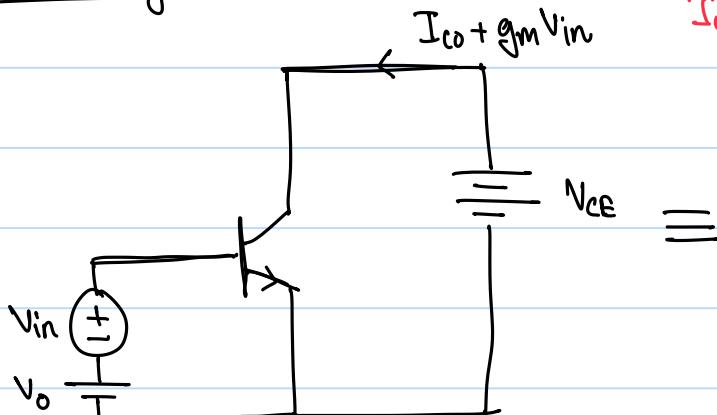

Small signal operation

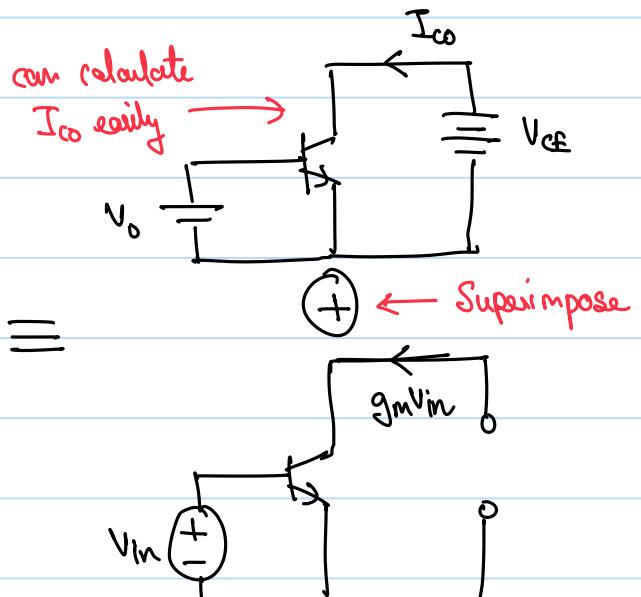

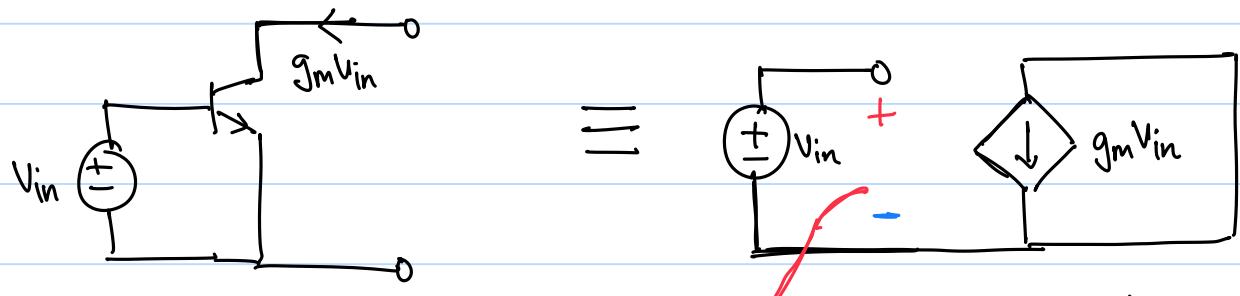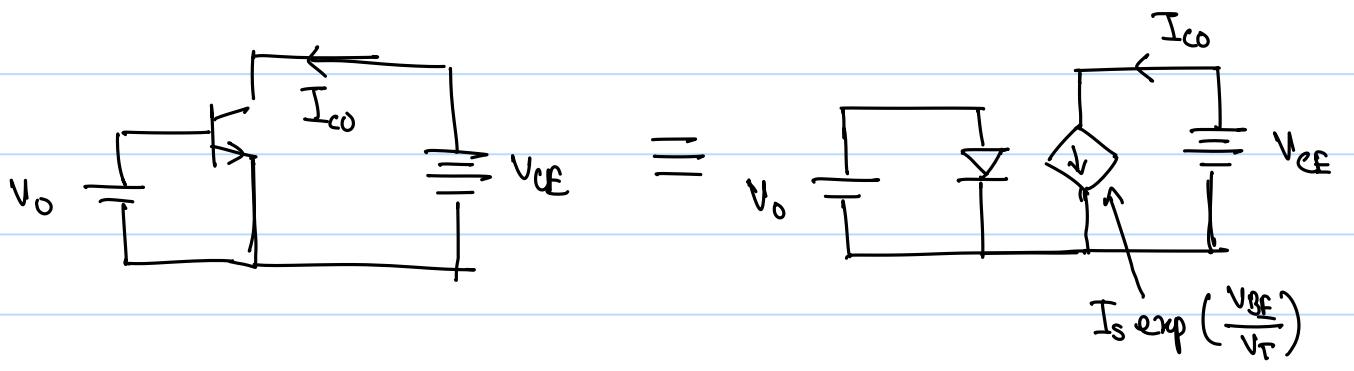


Small Signal Model

The base region  
is open

To model base current,

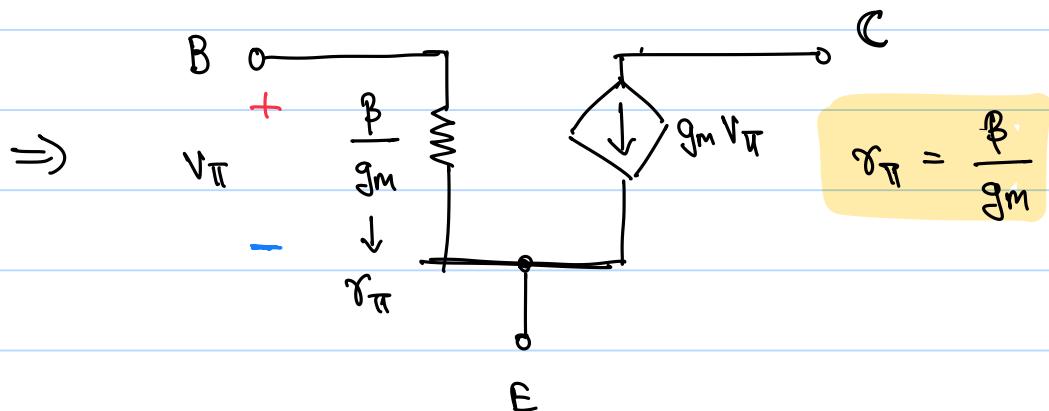
$$I_B = I_c/\beta = I_{C0}/\beta + g_m V_{in}/\beta$$



Small Signal Model

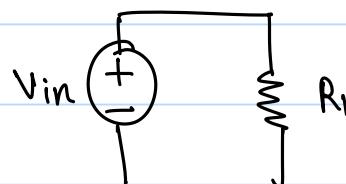Example:

Find the small signal model of a linear resistor




since there  
is no diff R  
in the solution

$$I = \frac{V_{in}}{R_1} \Rightarrow \Delta I = \frac{\Delta V_{in}}{R_1} \rightarrow \text{ie, it's the same model}$$

- In our small signal model, all the constant voltage sources are set to zero, ie, short circuited.
- Similarly all constant current sources are opened.

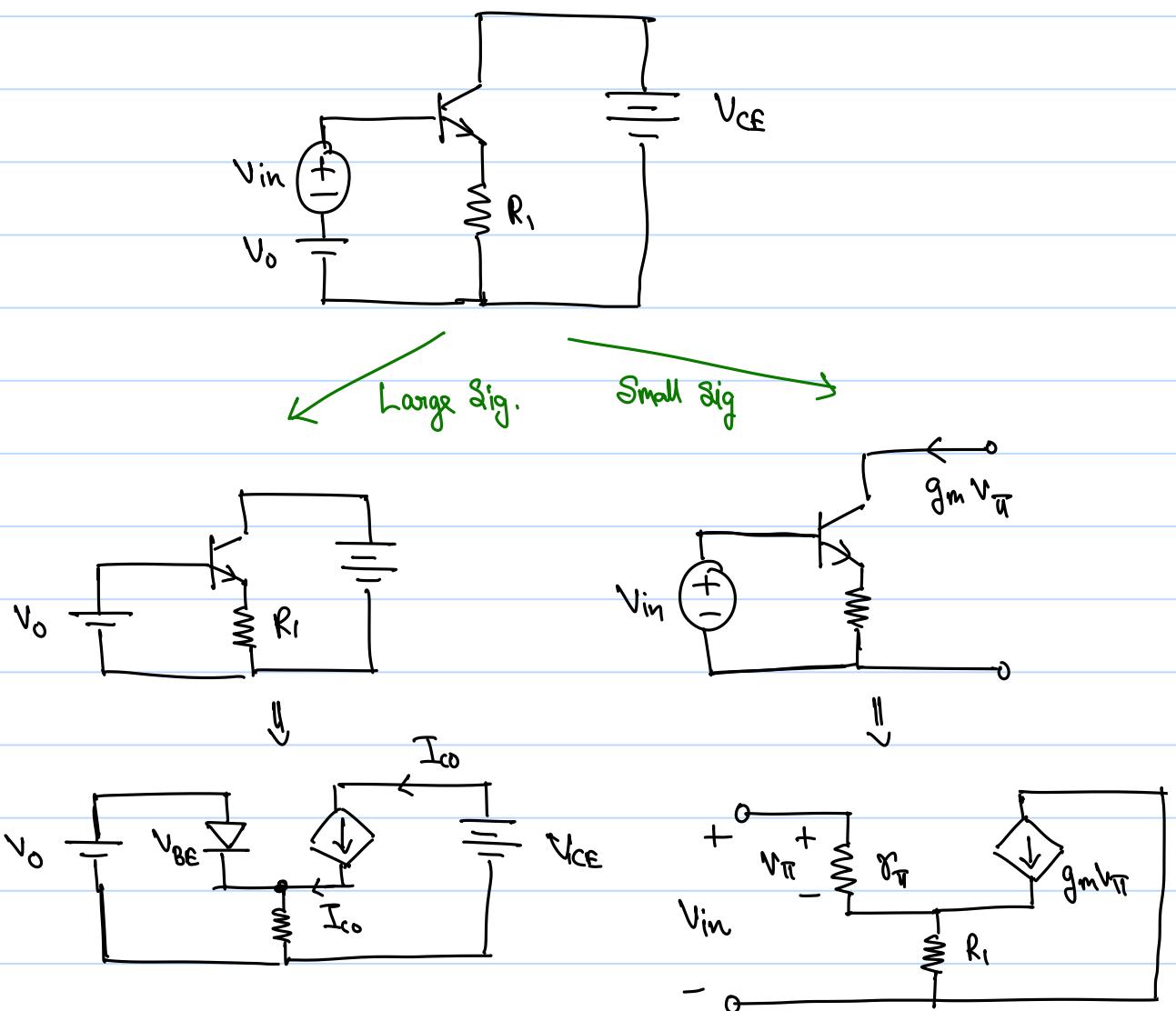Example: Coming back to a prev. scenario,



By KVh,

$$V_o = V_{BE} + R_1 I_{co}$$

$$V_o = V_T \ln \frac{I_{co}}{I_s} + R_1 I_{co}$$

By KVL,


$$V_{\pi} = \Delta V_{BE}$$

$$g_m V_{\pi} = \Delta I_c$$

$$V_{in} = V_{\pi} + R_1 g_m V_{\pi}$$


$$= V_{\pi} (1 + g_m R_1)$$

## Example 2:

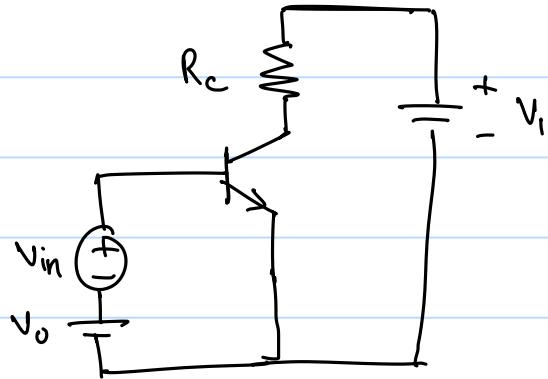


Model this circuit.

Large sig.      Small sig.

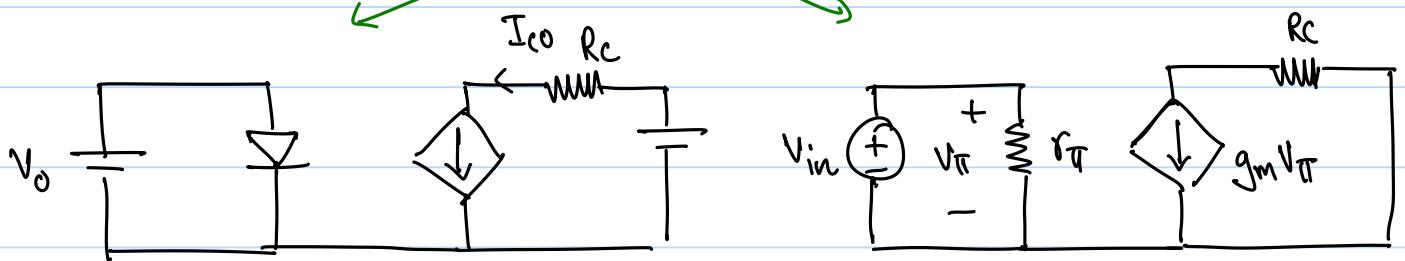


→ Early Effect :-

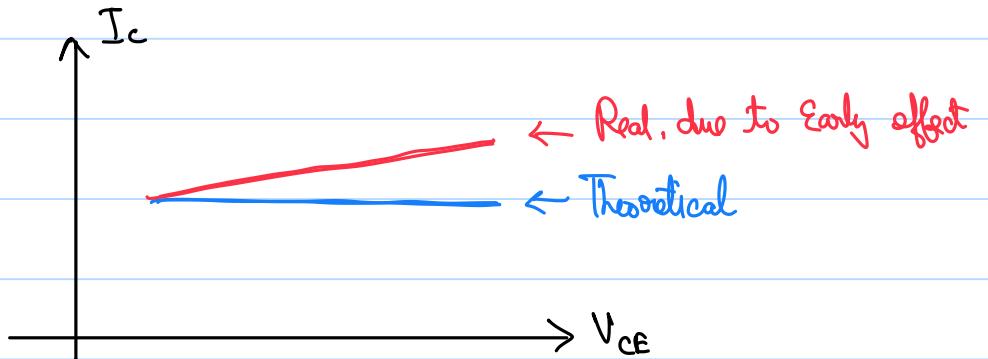

° We have seen that  $I_c$  does not depend on  $V_{CE}$ , but in reality there is some linear relation b/w them.

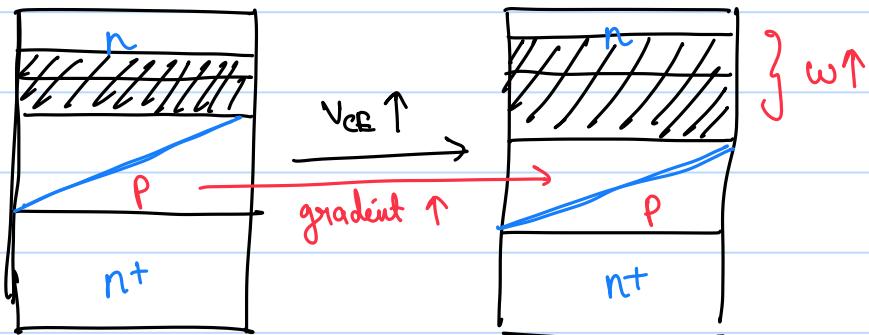° This is due to the width of the CBJ depletion region in reverse bias.



Also,  $I_S = \frac{A q n i^2 D_n}{N_A V_B}$   $\rightarrow$  Decreases w/  $V_{CE} \uparrow$

To take into account that linear relation,

$$I_C = I_S \left( e^{\frac{V_{BE}}{V_T} + 1} \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

Where  $V_A$  is termed as Early Voltage, a transistor dependent quantity.

- Early Effect in Small Signal Operation :-

Note: In all models till now, it was assumed that the transistor is always in fwd. active mode.

- To create a small signal model, apply a voltage change and calculate the current changes across the circuit. Then model those changes w/ appropriate devices.


$$\begin{aligned} g_m &= \frac{dI_C}{dV_{BE}} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right) \\ &= g_m = \frac{I_C}{V_T} \quad \rightarrow \text{g}_m \text{ is still affected by Early effect. That effect is in } I_C. \end{aligned}$$

$$\pi_T: I_B = \frac{I_C}{\beta} \Rightarrow \Delta I_B = \frac{\Delta I_C}{\beta}$$


$$\Rightarrow \pi_T = \frac{\beta}{g_m}$$

Still our previous small signal model is wrong as  $V_{CE}$  is not taken into account anywhere.


- Including Early Effect in the circuit,

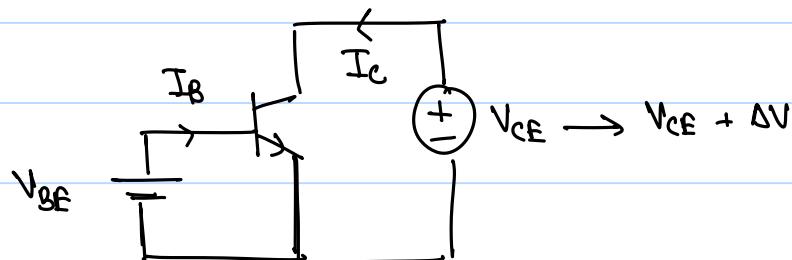
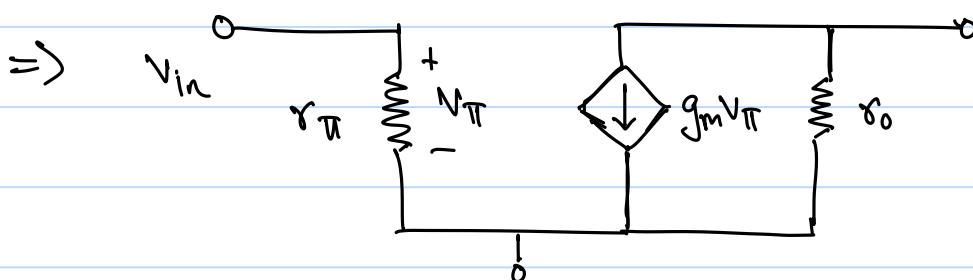
$$\Delta I_c \text{ (due to EE)} = I_s e^{\frac{V_{BE}}{V_T}} \left( \frac{\Delta V}{V_A} \right) \rightarrow \text{Linear dependence on } \Delta V$$



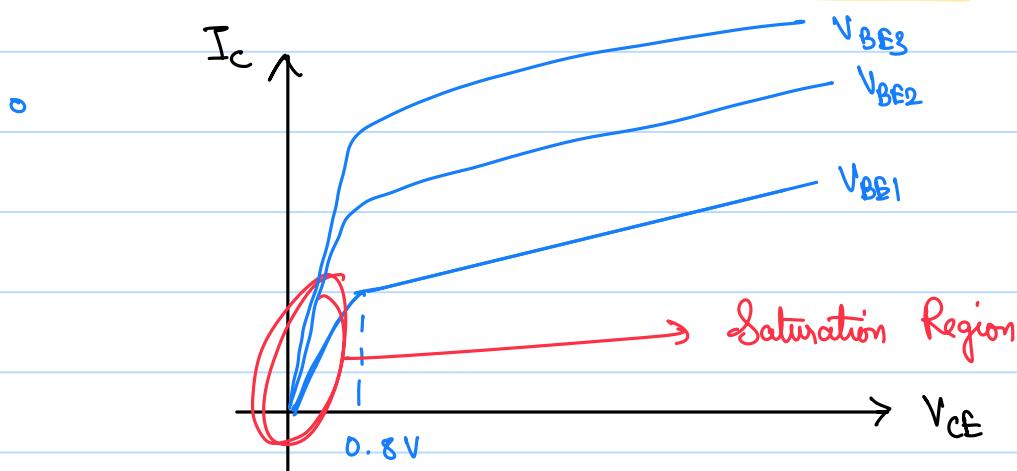
$$r_o = \frac{V_A}{I_s e^{\frac{V_{BE}}{V_T}}} \approx \frac{V_A}{I_c}$$



When  $V_{CE}$  drops below 0.7V, the transistor enters saturation mode.

- Light Saturation :  $V_{CE} \in (0.5V, 0.8V)$
- Deep Saturation :  $V_{CE} < 0.5V$

Example:

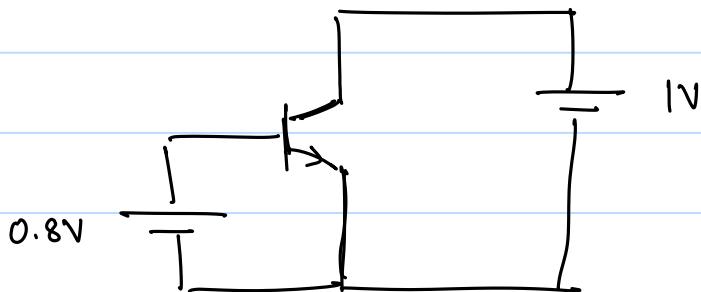

$$I_S = 5 \times 10^{-16} A, \beta = 100, V_A = 5V, I_C = ?, g_m = ?, r_\pi = ?, r_o = ?$$

$$I_C = I_S (\exp(V_{BE}/V_T)) (1 + \frac{V_{CE}}{V_T}) = 13.8 \text{ mA}$$


$$g_m = \frac{I_C}{V_T} = \frac{13.8}{26} = \underline{0.53 \text{ S}}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.53} = \underline{1900 \Omega}$$


$$r_o = \frac{V_A}{I_C} = \frac{5}{13.8 \times 10^{-3}} = \underline{362 \Omega}$$

In the above example, note that  $g_m r_o \gg 1$  - keep in mind for later.


→ PNP Transistor:-

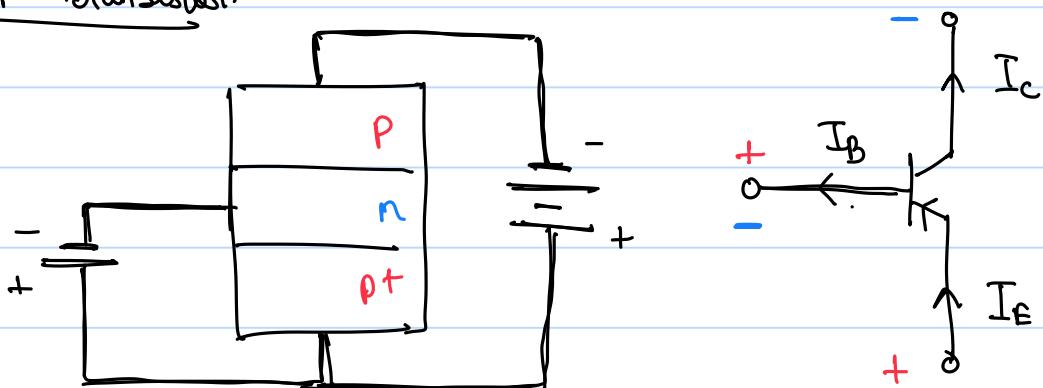

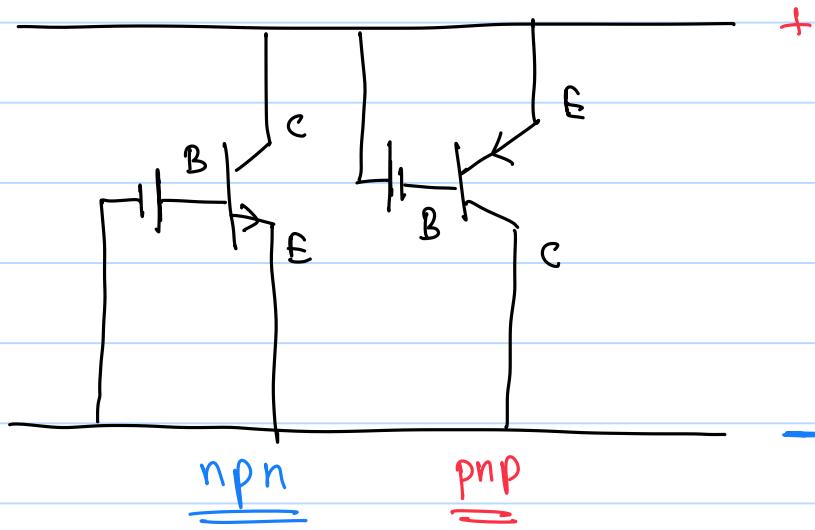- Fund Active Region:  $V_{EB} > 0$ ,  $V_{Ec} < V_{EB}$ .




- Visualization :-

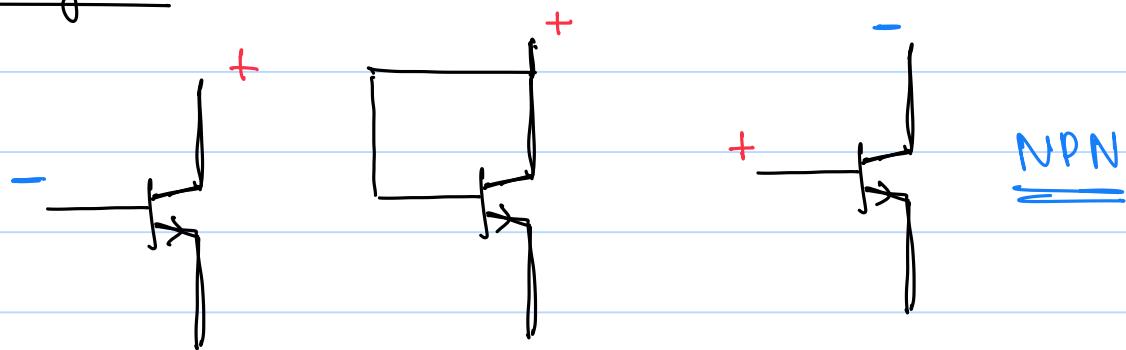

Active

Edge of Saturation

Saturation

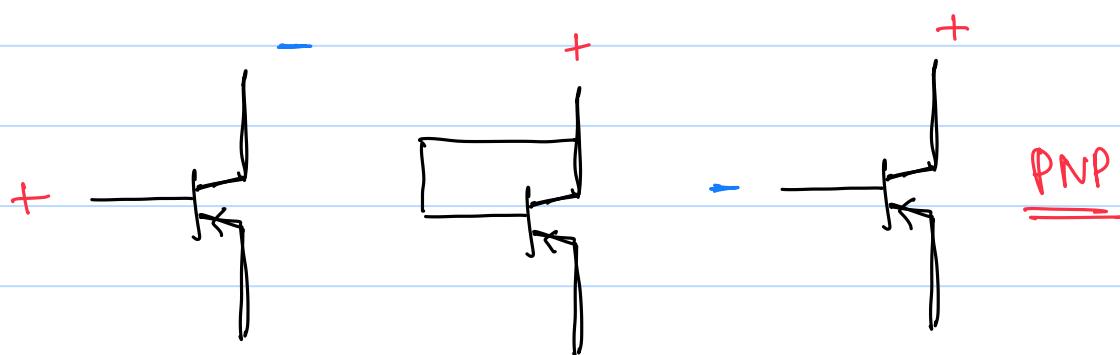


Active

Edge of Saturation


Saturation

° Large signal Model :-

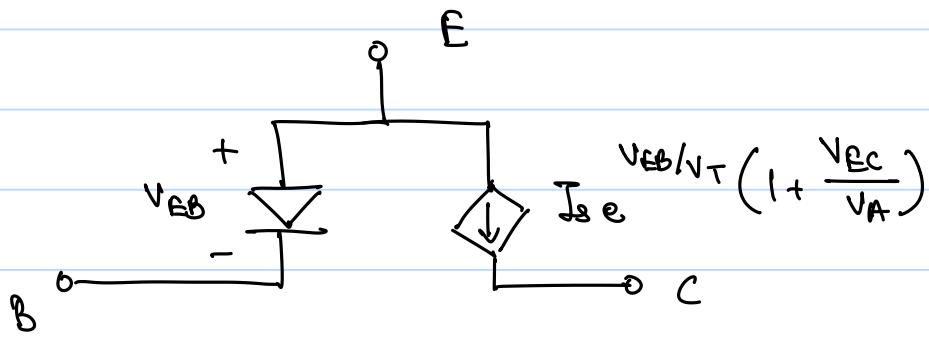

° Small Signal Model :-

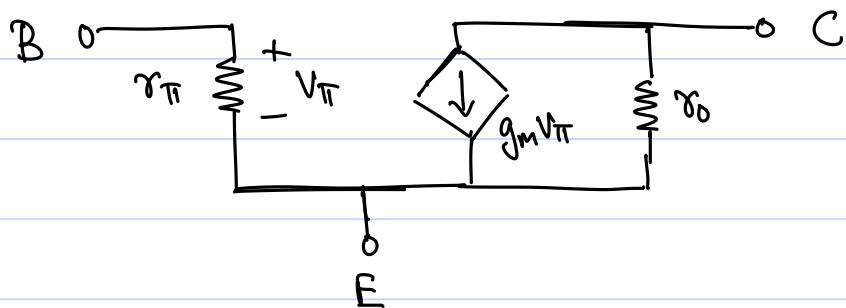- The effects of small signal approximation is identical to npn.




→ Amplifier Design :

- 1) Topology
- 2) Biasing
- 3) Small signal Properties

° Amplifier Characteristics :-

• Voltage Gain :

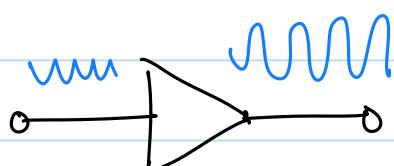
$$A_V = \frac{\text{o/p Amplitude}}{\text{i/p Amplitude}}$$



- Power Consumption :-


Biasing circuitry need external power.

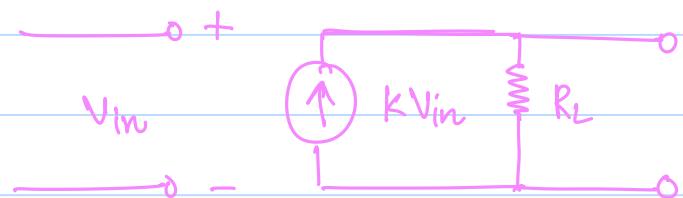Note: We designed an amplifier in the beginning,




$$A_v = \frac{V_o}{V_i} = \underline{K R_L}$$

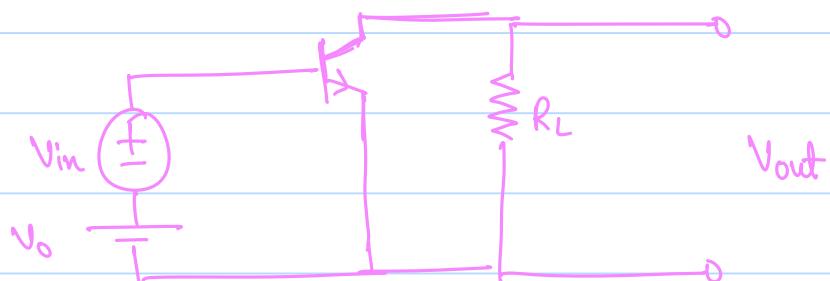We also noted that a BJT can be used to create the voltage dependent current source, as below




But, all this time, we assumed that the BJT is in **fixed bias mode**, which is not guaranteed.

=>

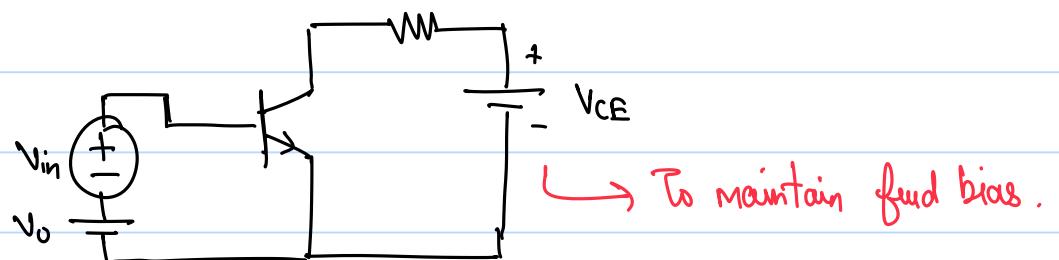


This circuit is termed as having a **common emitter topology**.


→ Common Emitter Topology :-

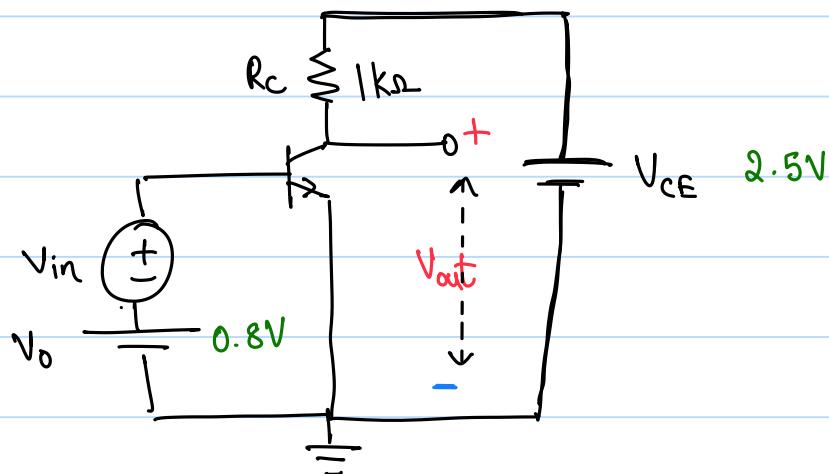

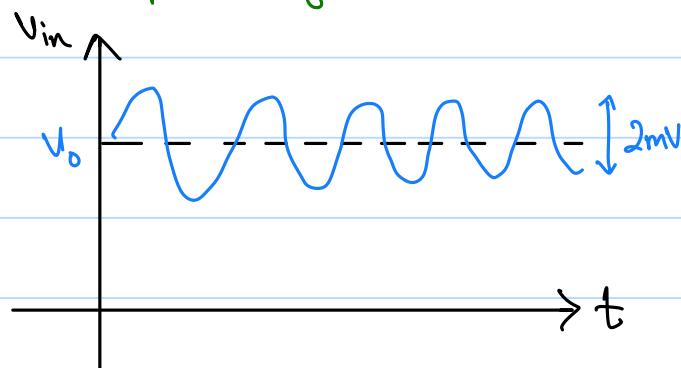
Let  $V_{in}$  have an amplitude of 2mV,  $I_{CO} = 1\text{mA}$



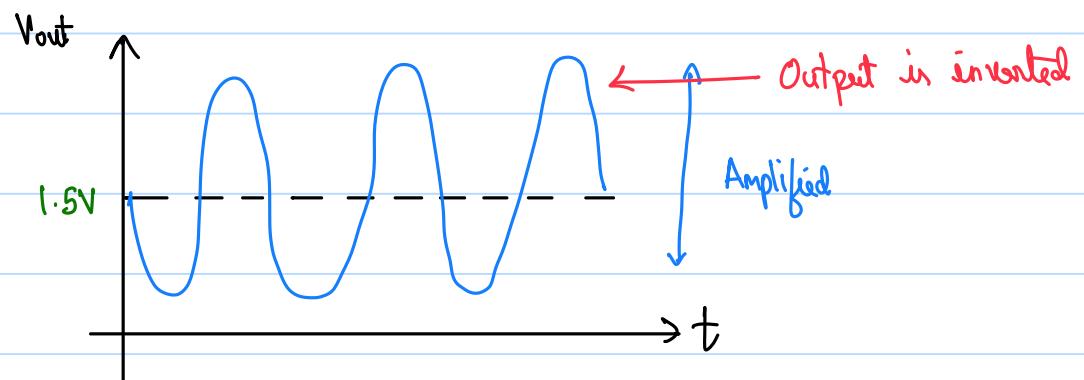
At operating point,  $V_0 = 2.5 - (1\text{mA} \times 1\text{k}\Omega) = 1.5\text{V}$



Simplified Diagram,

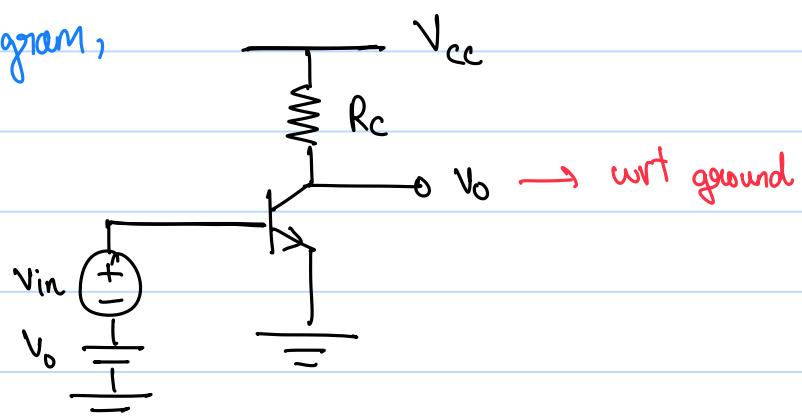

° Small signal Voltage gain calculation,

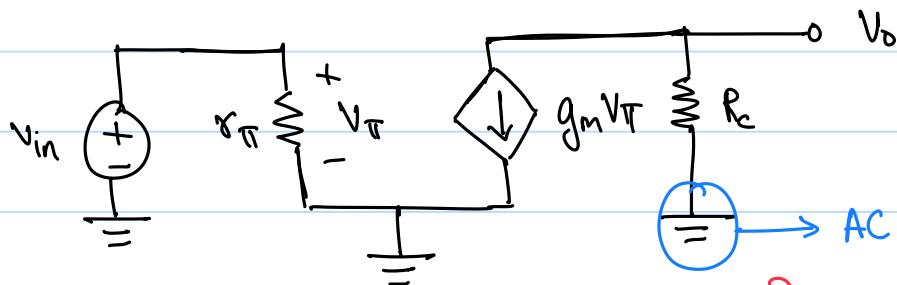

AC ground, since it appeared due to small signal analysis.

Here  $V_{in} = V_\pi$ ,

$$V_o = -R_c \cdot I_c$$


$$\Rightarrow V_o = -R_c g_m V_{in}$$

$$\Rightarrow A_v = -\underline{g_m R_c}$$

Neglecting Early effect.

$$\Rightarrow A_v = -g_m X \quad X - \text{Total resistance b/w collector and AC ground}$$

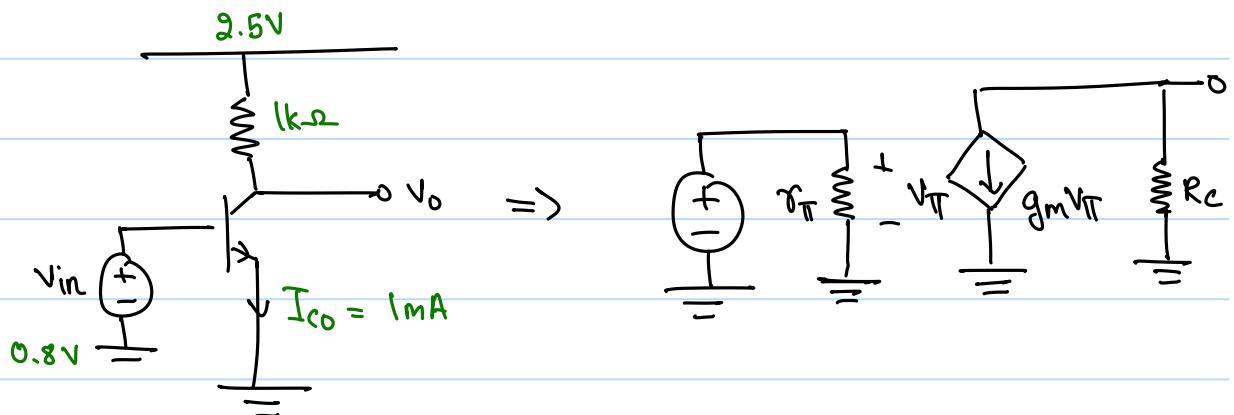Example: Find gain if  $V_{cc} = 2.5V$ ,  $\Delta V_{in} = 2mV$ ,  $I_{CO} = 1mA$ ,  $R_c = 1k\Omega$ ,  $V_o = 0.8V$



$$g_m = \frac{I_{CO}}{V_T} = \frac{1}{26} = 0.038 S$$

$$V_{out} = -R_c g_m V_\pi = -R_c g_m V_{in}$$

$$\Delta V_{\text{out}} = -R_c g_m \Delta V_{\text{in}}$$


$$\Rightarrow \text{gain} = -R_c g_m$$

$$= -(1 \times 10^3)(0.038)$$

$$= \underline{\underline{-38}}$$

Example 2: Suppose we want to double the gain, does doubling  $R_c$  work?

If new  $R_c = 2k\Omega$ ,

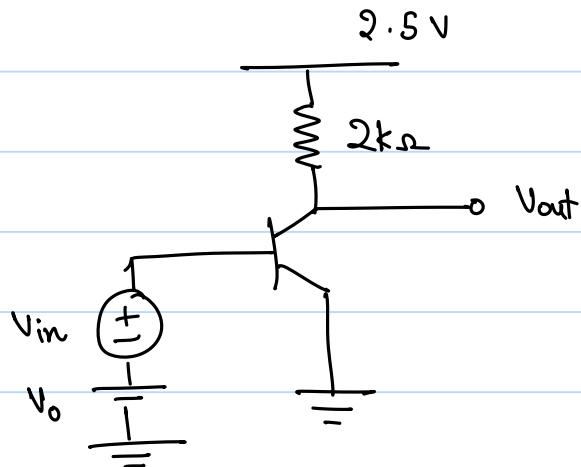

At operating point,

$$V_{CE} = 2.5 - R_c I_C$$

$$= 2.5 - (2 \times 10^3)(1 \times 10^{-3})$$

$$= 0.5 \text{ V} < 0.8 \text{ V}$$

$\rightarrow V_{CE}$  is less than  $V_{BE}$   
 $\rightarrow$  Saturation region

- Therefore in this design there is an upper limit on the gain we can get just by increasing  $R_c$ .


Example: What if we double  $g_m$  by doubling  $I_c$ ?

$I_c R_c$  doubles  $\Rightarrow$  Reduces  $V_{CE}$   $\rightarrow$  Same reason as before.

- Therefore, there is a strict upper limit on gain.

- Inclusion of Early Effect :-

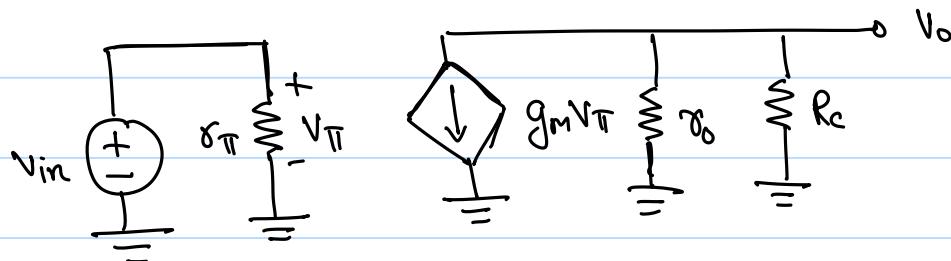- Early Effect changes our small signal model.



The total resistance seen from the output is  $r_o \parallel R_c$ .

$$\Rightarrow \text{gain} = g_m \left( \frac{R_c r_o}{R_c + r_o} \right) \rightarrow \text{Reduction in Gain}$$

- We know,  $g_m = \frac{I_c}{V_T}$ ,  $r_o = \frac{V_a}{I_c}$

$$\Rightarrow g_m r_o = \frac{I_c}{V_T} \times \frac{V_a}{I_c} = \frac{V_a}{V_T}$$

$$\Rightarrow g_m r_o = \frac{V_a}{V_T} \rightarrow \text{Intrinsic Gain of the Transistor}$$

- Intrinsic gain is the max possible gain of the transistor. ( $R_c \rightarrow \infty$ ).


◦ In a CE topology,

- 1) i/p applied to base
- 2) o/p taken from collector


◦ Impedances :-

- In the amplifier, there may be some impedances at the input and output.

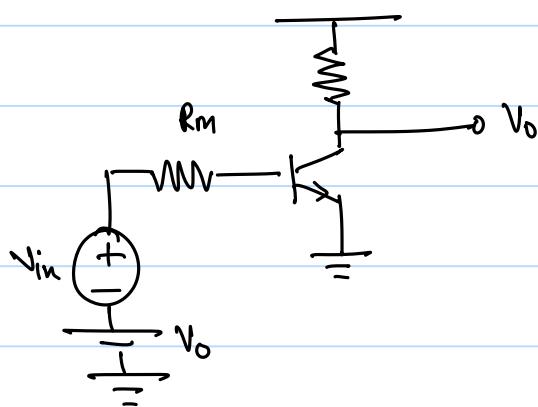Example: The input source has a series resistance of  $R_m$ .



SSM,

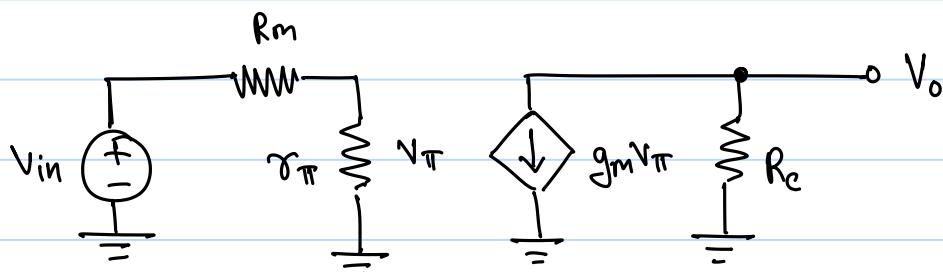

$$V_{\pi} = \frac{V_{in} \gamma_{\pi}}{R_m + \gamma_{\pi}}$$

$\left( \frac{\gamma_{\pi}}{R_m + \gamma_{\pi}} \right)$  - Attenuation factor

$$V_0 = - g_m V_{\pi} R_c$$

$$\Rightarrow \frac{V_0}{V_{in}} = - \frac{g_m R_c \gamma_{\pi}}{R_m + \gamma_{\pi}}$$

→ Reduced gain

- The resistance  $R_m$  causes an impedance at the i/p.
- Input Impedance: To calculate i/p impedance,
  1. Set all independent sources to zero
  2. Apply a small signal voltage source b/w the input terminals.  
Calculate the current supplied by the source.

$$R_m = \frac{V_{in}}{I_x}$$


$$I_x r_{\pi} = V_{in}$$

$$\Rightarrow R_m = r_{\pi} \quad \rightarrow \text{Does not depend on } R_C, R_O$$

- Output Impedance:-

Suppose at the output, we have a low impedance device attached.

Example:

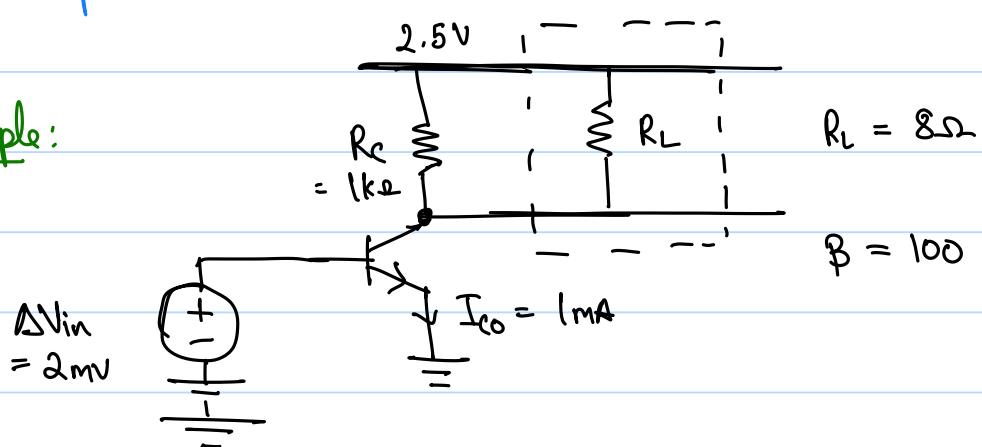


$$A_v = -g_m (R_C \parallel R_L)$$

$$= -(0.038) \left( \frac{1000 \times 8}{1000 + 8} \right) \approx -0.3 \rightarrow \text{Attenuation}$$

The output impedance is measured by


SSM:

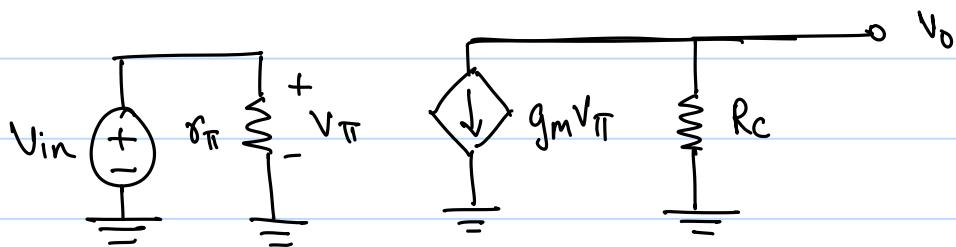

Let's find the Thevenin Equivalent of this circuit,


$$V_{out} = -R_C g_m V_{\pi}$$

$$R_{eq} = R_C$$

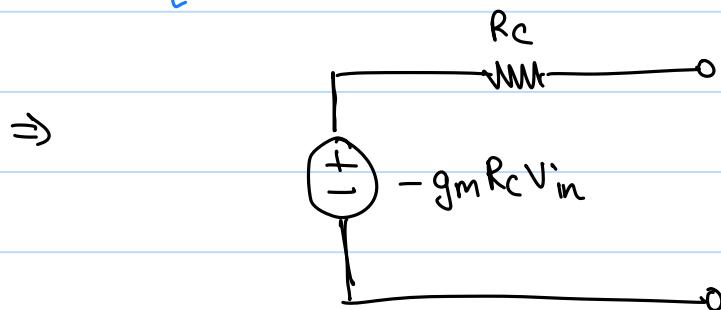

If load resistance is  $R_L$ , voltage delivered to the load is given by,
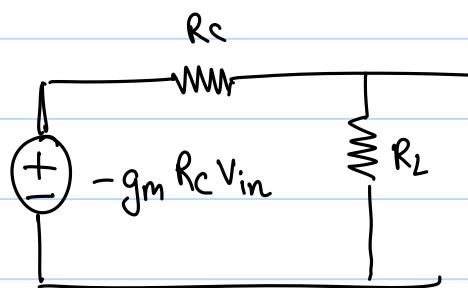
$$V_L = \frac{R_L}{R_L + R_C} (-g_m R_C V_{in})$$



$$\Rightarrow \text{gain} = -g_m R_C \frac{R_L}{R_L + R_C}$$

Attenuation factor

- Calculation of o/p impedance is ||| to i/p impedance, with  $V_{in} = 0$ .  
( $R_{out}$ )

- $R_{out} = R_C \text{ (or) } R_C \parallel r_o \rightarrow \text{Early Effect}$

- i/p and o/p impedances are observed when connecting circuitry to the i/p or o/p of the Amplifier.


- Gain Variation :-

The gain of an Amplifier is given by

$$A_V = g_m R_C = -\frac{I_C R_C}{V_T}$$

- This gain can vary due to

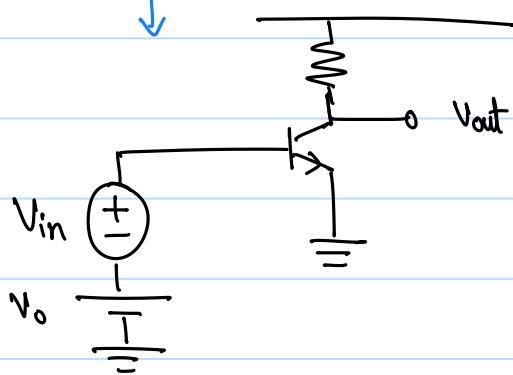- 1) Variation of temperature. ( $V_T$ )
- 2) Variation of process (Manufacturing,  $R_C$ )
- 3) Variation due to signal amplitude




If  $V_{in}$  is a large signal, there will be significant variation in  $I_C$ , which affects the gain.

$\Rightarrow$  gain  $\propto$  instantaneous  $V_{in}$


↳ This causes non-linear behaviour / distortion in o/p.

- To fix this, we have **emitter degeneration**

→ CE stage w/ Emitter Degeneration :-

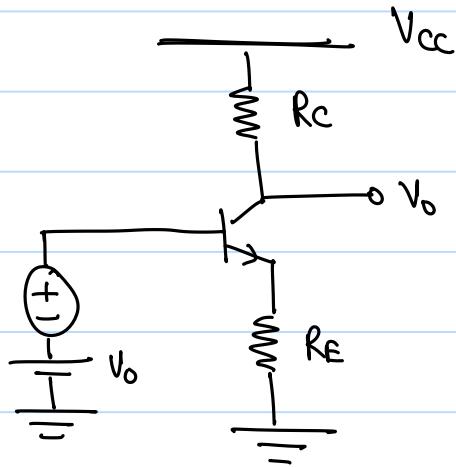

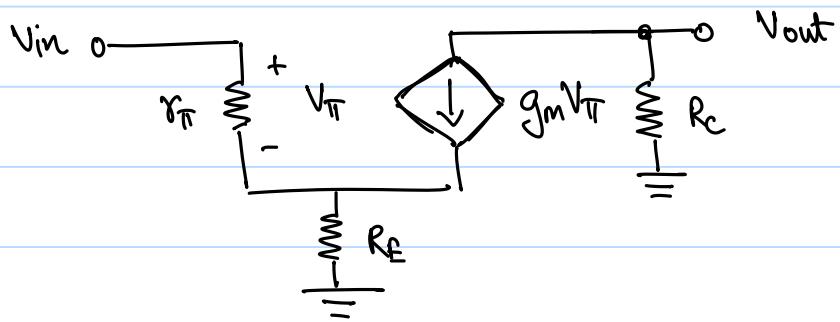° Gain of this design can be calculated as follows,



By KCL,

$$g_m V_{TI} + \frac{V_{out}}{R_C} = 0$$

$$V_{TI} = -\frac{V_{out}}{g_m R_C}$$

KCL at Emitter node,

$$\frac{V_{TI}}{r_{pi}} + g_m V_{TI} = I_E$$

$$\Rightarrow \text{Voltage across } R_E = \left( \frac{V_{TI}}{r_{pi}} + g_m V_{TI} \right) R_E$$

$$= \left( -\frac{V_{out}}{g_m R_C r_{pi}} - \frac{g_m V_{out}}{g_m R_C} \right) R_E$$

By KVL

$$V_{in} = V_{\pi} + \left( \frac{-V_{out}}{g_m R_c r_{\pi}} - \frac{V_{out}}{R_E} \right) R_E$$

$$V_{in} = -\frac{V_{out}}{g_m R_c} - \frac{V_{out} R_E}{g_m R_c r_{\pi}} - \frac{V_{out} R_E}{R_E}$$

$$\Rightarrow \frac{1}{A_V} = - \left( \frac{1}{g_m R_c} + \frac{R_E}{g_m R_c r_{\pi}} + \frac{R_E}{R_E} \right)$$

$$= - \left( \frac{1}{g_m R_c} + \frac{R_E}{\beta R_c} + \frac{R_E}{R_E} \right)$$

$$\Rightarrow A_V = \frac{\beta g_m R_c}{\beta + (\beta+1) g_m R_E}$$

$$= \frac{R_c}{\frac{1}{g_m} + \left( \frac{\beta+1}{\beta} \right) R_E}$$

$$\Rightarrow A_V = \frac{R_c}{\frac{1}{g_m} + R_E} \quad \beta \gg 1$$

- If  $R_E$  is large enough, variation in  $g_m$  will not affect overall gain. ( $R_E$  dominates over  $g_m$ ).