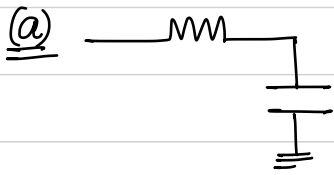


Assignment 1 (AEC)

Solutions.

Q1: Transient and AC analysis of RC (theory part):

$$V(t) = \underbrace{V(t=\infty)}_{\text{voltage at } t=\infty} + \left[\underbrace{V(t=0) - V(t=\infty)}_{\text{voltage at } t=0^+} \right] e^{-t/\tau} \quad (\text{For any 1st order / single pole systems})$$



$V(t=0^+)$: Capacitor acts as short circuit
 $\hookrightarrow = 0$


$V(t=\infty)$: Capacitor steady state achieved

$$i = \frac{C dV_{out}}{dt}$$

$$i = 0 \text{ means } V_{out} = V_p$$

$$\tau = RC$$
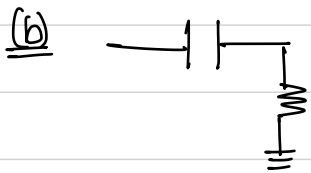
$$\text{pole} = -\frac{1}{RC} \quad (\text{make net impedance } \infty)$$




$$V_{out}(t=0^+) = V_p$$

$$V_{out} = V_p e^{-t/RC}$$

$$V_{out}(t=\infty) = 0$$

zero = 0 (i must be 0, means $\frac{1}{sC} = \infty$ happens if $s=0$)

$$\text{pole} = -\frac{1}{RC}$$

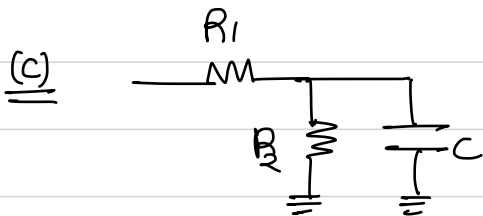

$$t=0^+, \quad R_2 \parallel \frac{1}{sC} \sim \frac{1}{sC} \quad (s \sim \infty \text{ means } \frac{1}{sC} \sim 0)$$

$$V_{out}(t=0^+) \Rightarrow 0$$


$$t \rightarrow \infty, \quad R_2 \parallel \frac{1}{sC} \sim R_2 \quad (s \sim 0 \text{ means } \frac{1}{sC} \sim \infty)$$

$$V_{out}(t=\infty) = \frac{R_2}{R_1 + R_2} V_p$$


$$\tau = (R_1 \parallel R_2)C$$

$$\text{pole} = -\frac{1}{(R_1 \parallel R_2)C}$$

Bodeplot:

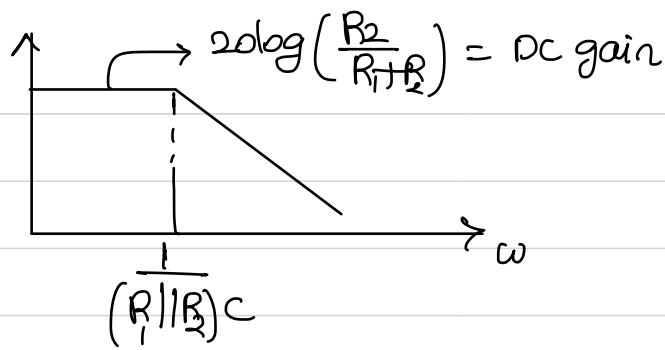


(d)

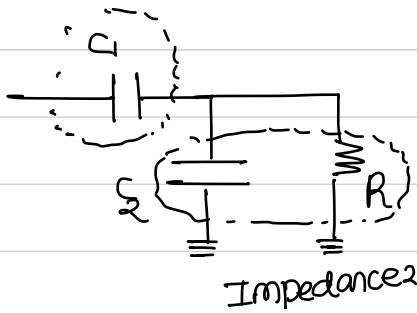


at $t = 0^+$

$\frac{1}{sC_2} || R \sim \frac{1}{sC_2}$ (equivalent to capacitance at $s \rightarrow \infty$ means $\frac{1}{sC_2} \rightarrow 0$)

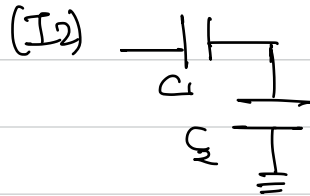

at $t \rightarrow \infty$

$\frac{1}{sC_2} || R \sim R$ (equivalent to Resistance at $s \rightarrow 0$ means $\frac{1}{sC_2} \rightarrow \infty$)

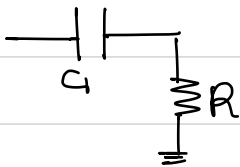

$$Z = R(C_1 + C_2)$$

For calculating zeros:

$$Z_1 = 1/sC_1$$


$$Z_2 = \frac{1}{sC_2} || R$$


make $Z_1 = \infty$ without making Z_2 to ∞

(∞) make $Z_2 = 0$ without making Z_1 to 0

zero, at $s = 0$

pole, at $s = -\frac{1}{R(C_1 + C_2)}$

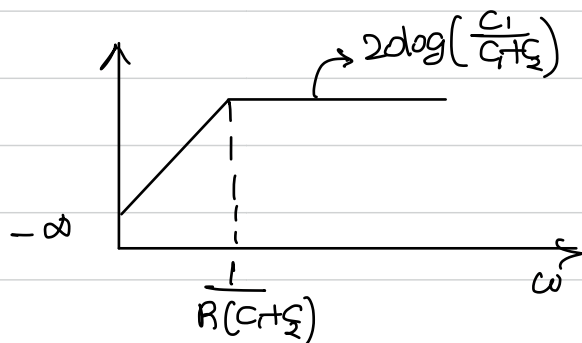


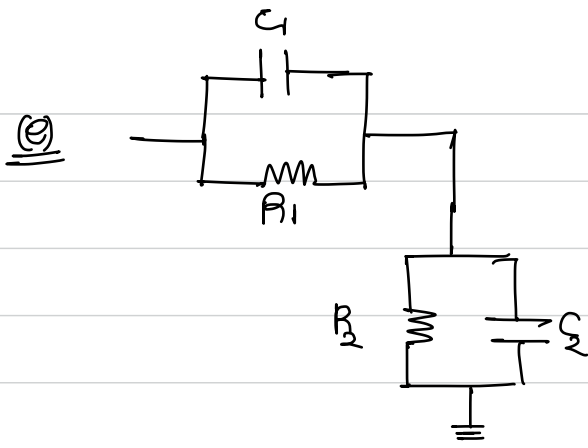

at $t=0^+$, $s \rightarrow \infty$ means

Resistance || capacitance ($1/s$)
 \sim capacitance ($1/s$)


Circuit will look like:

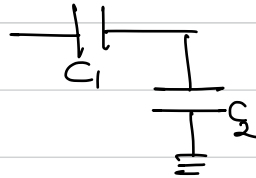

$$V_{out} = \frac{C_1}{C_1 + C_2} V_P$$

at $t=\infty$ ($s=0$) means

Resistance || capacitance ($1/s$)
 \sim Resistance

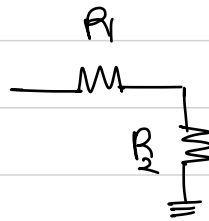

$$V_{out} = \frac{R_2}{R_1 + R_2} V_P$$


zeros: make $Z_1 = \infty$ means at $s = -\frac{1}{R_1 C_1}$



make $Z_2 = 0$ means at $s = \infty$

pole: (make input, ground)
 find output impedance

pole at $s = \frac{1}{[R_1 || R_2] (C_1 + C_2)}$
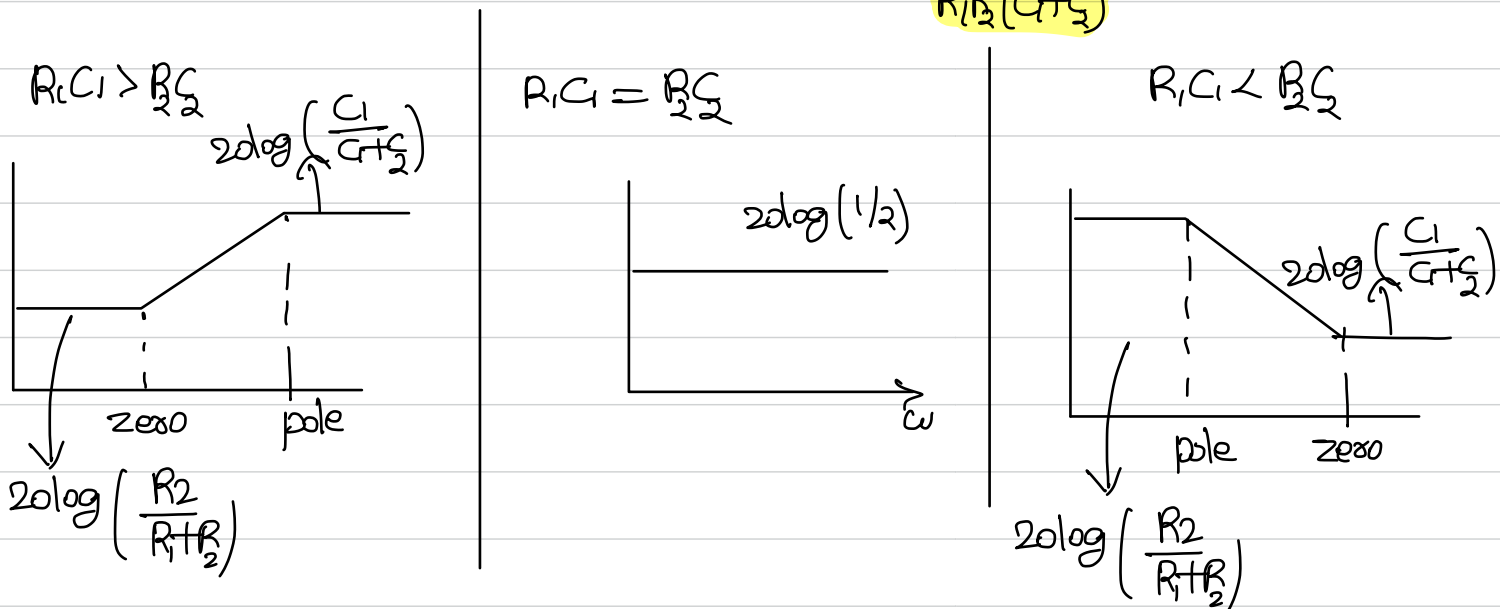
$$\Rightarrow \frac{-(R_1 + R_2)}{R_1 R_2 (C_1 + C_2)}$$



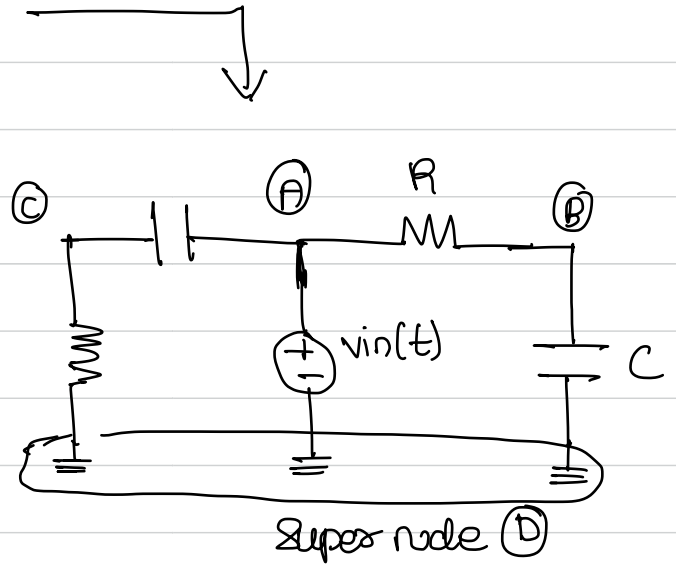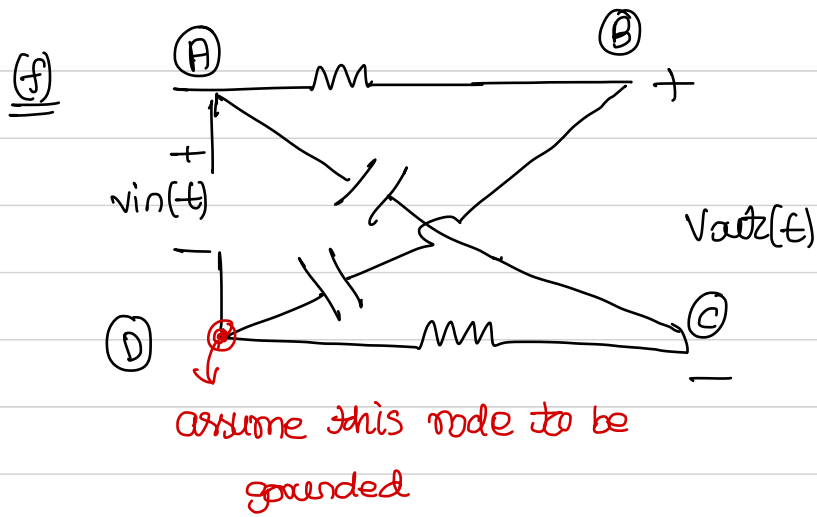

$$V_{out}(t) = V(B) - V(C)$$

$$V(B) = v_{in}(1 - e^{-t/RC}) \quad (\text{LPF})$$

$$V(C) = v_{in}e^{-t/RC} \quad (\text{HPF})$$

$$V_{out}(t) = v_{in} - 2v_{in}e^{-t/RC}$$

AC analysis:

$$V_B(s) = \frac{1}{1 + j\omega RC} v_{in}(s)$$


$$V_C(s) = \frac{j\omega RC}{1 + j\omega RC} v_{in}(s)$$

$$V_{out}(s) = \frac{1 - j\omega RC}{1 + j\omega RC} v_{in}(s)$$


$$\text{pole} = \frac{-1}{RC}$$

$$\text{zero} = \frac{1}{RC}$$

Bode magnitude plot vs ω :

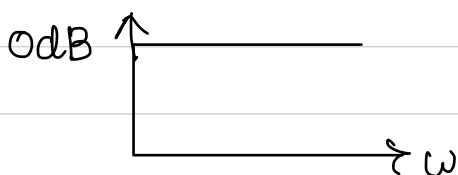

phase plot vs ω

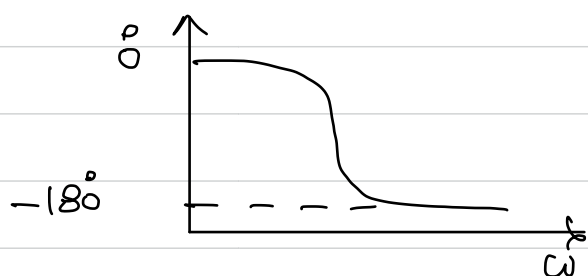

$$\text{phase} = -2 \tan^{-1}(\omega RC)$$