
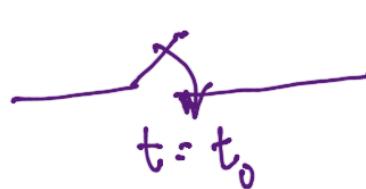
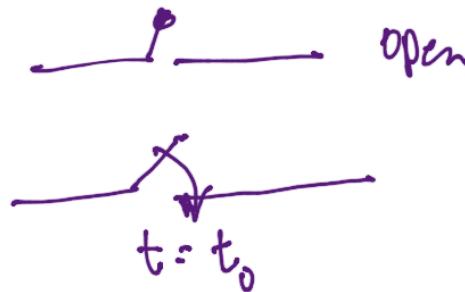
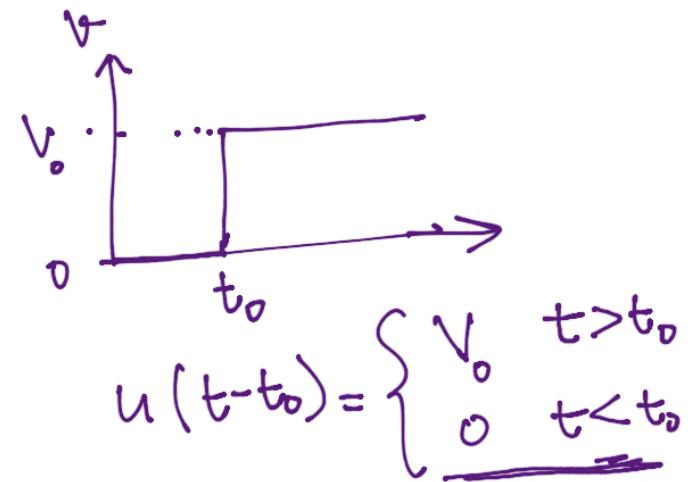
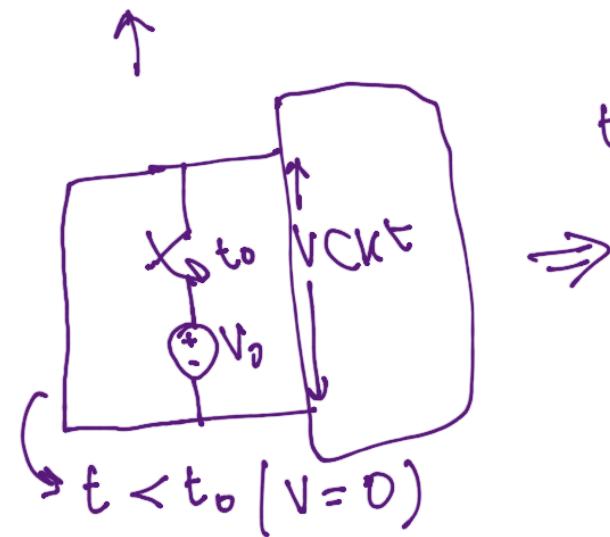


Unit Step Function

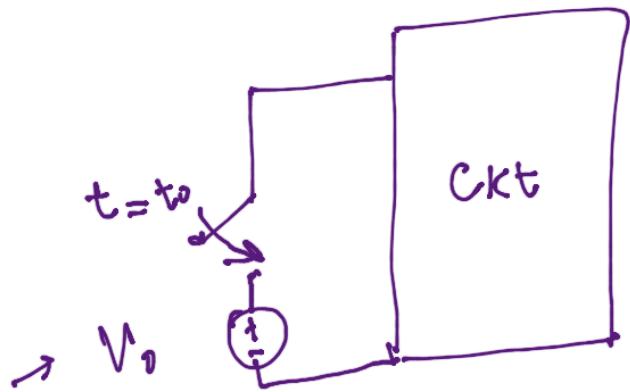



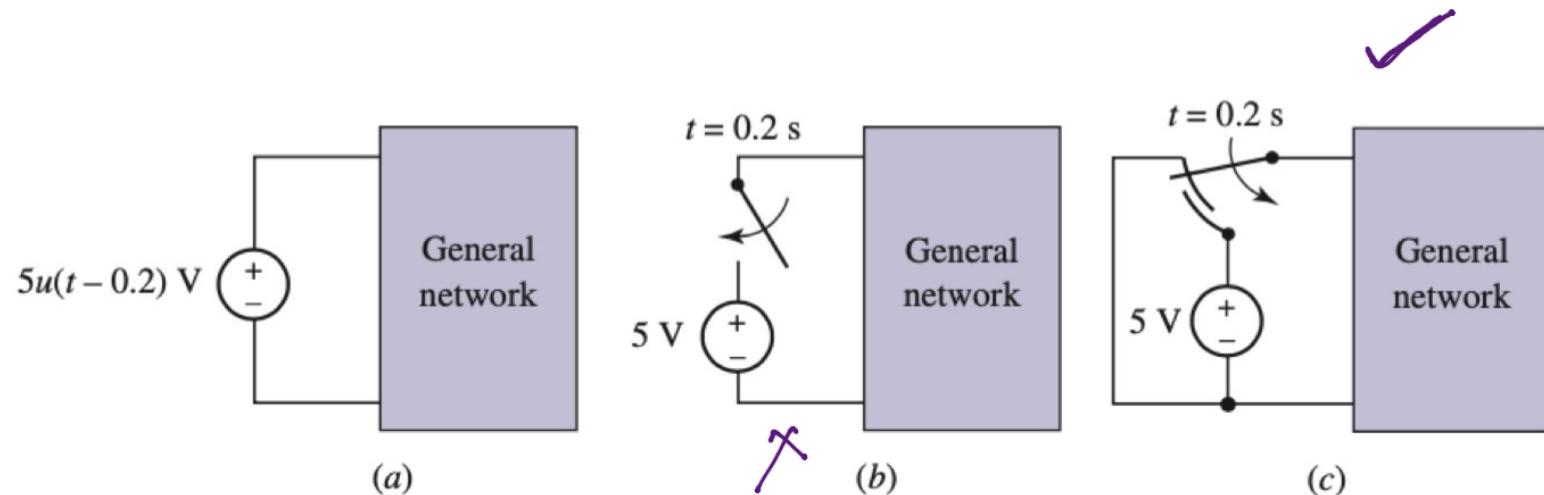


FIGURE 8.28 (a) A voltage-step forcing function is shown as the source driving a general network. (b) A simple circuit which, although not the exact equivalent of part (a), may be used as its equivalent in many cases. (c) An exact equivalent of part (a).


Current Source

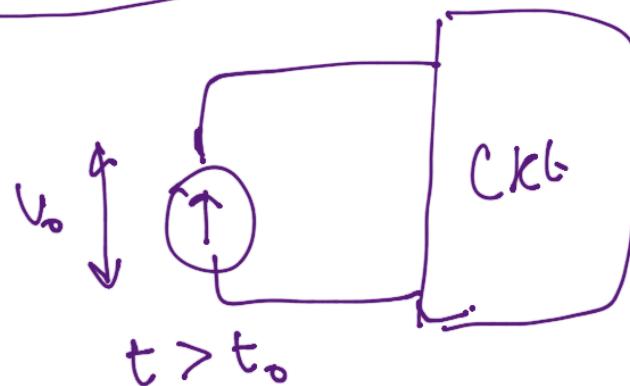



Approx.

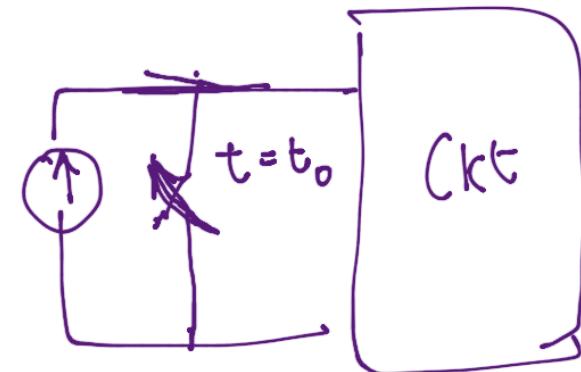

$$t < t_0$$

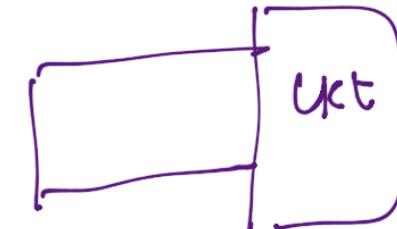

$$\bar{I} = 0$$

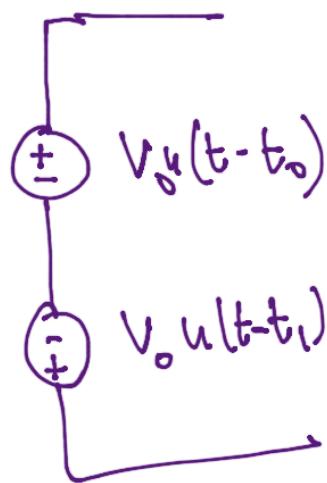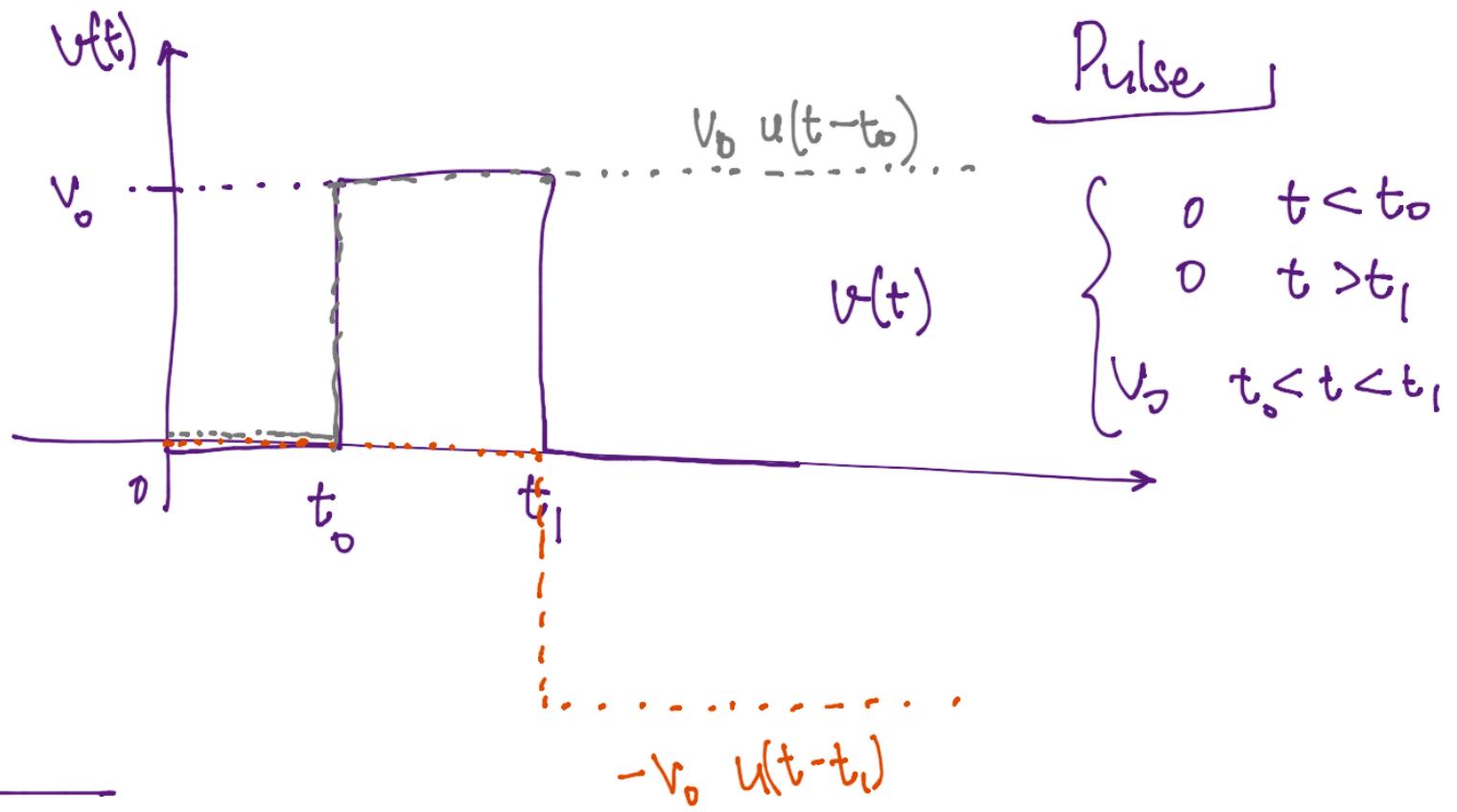

General Solution : Natural Response

+ Forced Response

First order

$$\frac{di}{dt} + Pi = Q$$

↑
Forcing function.

$$\Rightarrow di + Pi dt = Q dt \quad \text{--- (1)}$$

Integrating factor $e^{\int P dt}$ $= e^{Pt} = C$ $\left\{ \begin{array}{l} P = \text{const.} \\ L, C, R \end{array} \right.$

(1) * Int. factor

$$(e^{Pt} di + Pi e^{Pt} dt) = Q C dt$$

$$\Rightarrow \int \underline{d(i e^{Pt})} = \int Q e^{Pt} dt \Rightarrow$$

After integration

$$\Rightarrow i_c = \int Q e^{pt} dt + A$$

Solution

$$i = e^{-pt} \underbrace{\int Q e^{pt} dt}_{I} + A e^{-pt}$$

$$II \quad A e^{-pt} = \text{Natural response} = i_n$$

$$\underline{p} \quad RC, \frac{L}{R}$$

$$i_n \rightarrow 0 \quad \text{at} \quad t \rightarrow \infty$$

$$I \quad i_f = -C \int Q e^{pt} dt$$

Forced response.

$$2) \underline{Q = \text{const.}} \quad i_f = -\frac{1}{p} Q e^{-pt} = \frac{Q}{p}$$

Steady state resp.
Particular solution

S_0 , if $V_s \rightarrow \text{const}$ (Source)

$$\boxed{i = \frac{Q}{P} + A e^{-Pt}}$$

$= i_f + i_n$

General $V_s, I_s \rightarrow \text{not const.}$

$$i = \tilde{i}_f + \tilde{i}_n$$


$$\boxed{i = \tilde{c} e^{-Pt} \int Q e^{Pt} dt + A e^{-Pt}}$$

$b - R$

Ex 8.8

$$i_n = A e^{-t/\tau}$$

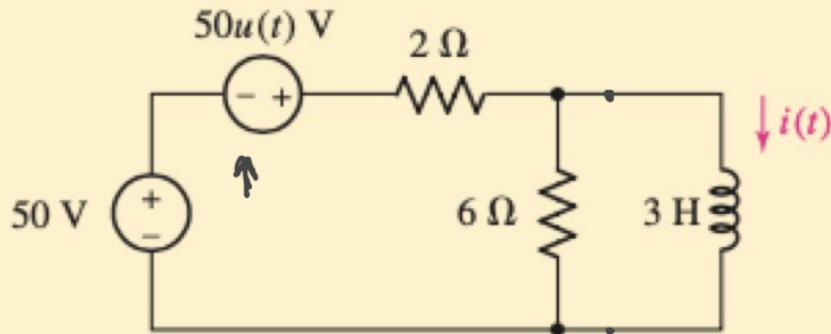Determine $i(t)$ for all values of time in the circuit of Fig. 8.37.




■ FIGURE 8.37 The circuit of Example 8.8.

R-L type circuit

Step 1

P or τ

R_{eq}

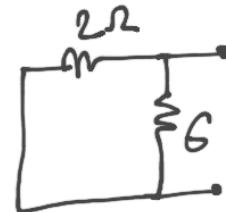


$$\frac{2}{R_{eq}} = \frac{12}{8} = \frac{3}{2} = 1.5$$

$$L = 3H \Rightarrow \tau = \frac{L}{R_{eq}} = \frac{3}{3 \times 1.5} = 2 \text{ sec}$$

Step 2

Natural response

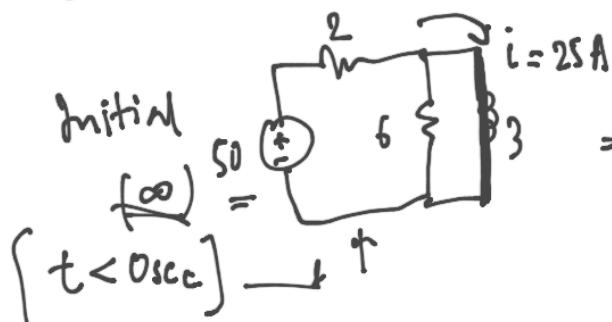

i_0 (initial condition)


$$i_n = A e^{-t/2}$$

Apply initial condition
to complete solution
Nat.

Satisfy the

to find response
not just the natural response *

Forced response

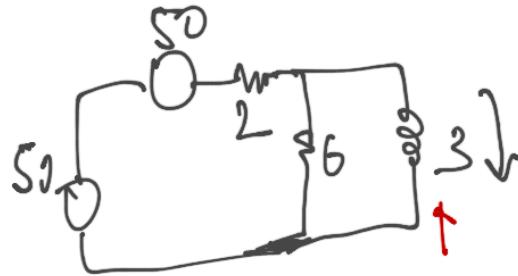

Forced response
L → wire.

$$V_s = 50 + 50 = 100 \quad |$$

$$R_s = 2 \Omega$$

$$= \frac{100}{2} = 50 \text{ A}$$

$$i_f = 50 \text{ A}$$

$$i = i_f + i_n - t/2$$

$$i = 50 + A e^{-t/2}$$

Check

$$t \rightarrow \infty$$

$$i = 50 \text{ A}$$

$$t = 0$$

$$25 = 50 + A e^0 \Rightarrow A = \frac{25 - 50}{1} = -25$$

$$i = 50 - 25 e^{-t/2}$$

Steps for Finding Solution (R-C)

L-R:

R-C

$\frac{L}{R} = \tau$

$\dots v$

$L \rightarrow S \cdot C$

$i_L(0) -$

\dots

$C \rightarrow S \cdot C$

$\frac{V}{R}$

\dots

$i_L(\infty)$

$= i_L(\delta)$

\dots

$A = ?$

- With all independent sources zeroed out, simplify the circuit to determine R_{eq} , C_{eq} , and the time constant $\tau = R_{eq}C_{eq}$.
- Viewing C_{eq} as an open circuit, use dc analysis methods to find $v_C(0^-)$, the capacitor voltage just prior to the discontinuity.
- Again viewing C_{eq} as an open circuit, use dc analysis methods to find the forced response. This is the value approached by $f(t)$ as $t \rightarrow \infty$; we represent it by $f(\infty)$.
- Write the total response as the sum of the forced and natural responses: $f(t) = f(\infty) + Ae^{-t/\tau}$. \leftarrow Total response
- Find $f(0^+)$ by using the condition that $v_C(0^+) = v_C(0^-)$. If desired, C_{eq} may be replaced by a voltage source $v_C(0^+)$ [a short circuit if $v_C(0^+) = 0$] for this calculation. With the exception of capacitor voltages (and inductor currents), other voltages and currents in the circuit may change abruptly.
- $f(0^+) = f(\infty) + A$ and $f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-t/\tau}$, or total response = final value + (initial value - final value) $e^{-t/\tau}$.

Time const.

Initial

Forced response

$\left\{ \begin{array}{l} C \rightarrow 0 \cdot C \\ L \rightarrow S \cdot C \end{array} \right.$

$\left\{ \begin{array}{l} i_f = V/R \\ \dots \end{array} \right.$

$\left\{ \begin{array}{l} i_f = V/R \\ \dots \end{array} \right.$


Find constants

Steps for find Solution (R - L)

1. With all independent sources zeroed out, simplify the circuit to determine R_{eq} , L_{eq} , and the time constant $\tau = L_{\text{eq}}/R_{\text{eq}}$.
2. Viewing L_{eq} as a short circuit, use dc analysis methods to find $i_L(0^-)$, the inductor current just prior to the discontinuity.
3. Again viewing L_{eq} as a short circuit, use dc analysis methods to find the forced response. This is the value approached by $f(t)$ as $t \rightarrow \infty$; we represent it by $f(\infty)$.
4. Write the total response as the sum of the forced and natural responses: $f(t) = f(\infty) + Ae^{-t/\tau}$.
5. Find $f(0^+)$ by using the condition that $i_L(0^+) = i_L(0^-)$. If desired, L_{eq} may be replaced by a current source $i_L(0^+)$ [an open circuit if $i_L(0^+) = 0$] for this calculation. With the exception of inductor currents (and capacitor voltages), other currents and voltages in the circuit may change abruptly.
6. $f(0^+) = f(\infty) + A$ and $f(t) = f(\infty) + [f(0^+) - f(\infty)] e^{-t/\tau}$, or total response = final value + (initial value - final value) $e^{-t/\tau}$.

Switching Circuit

HW

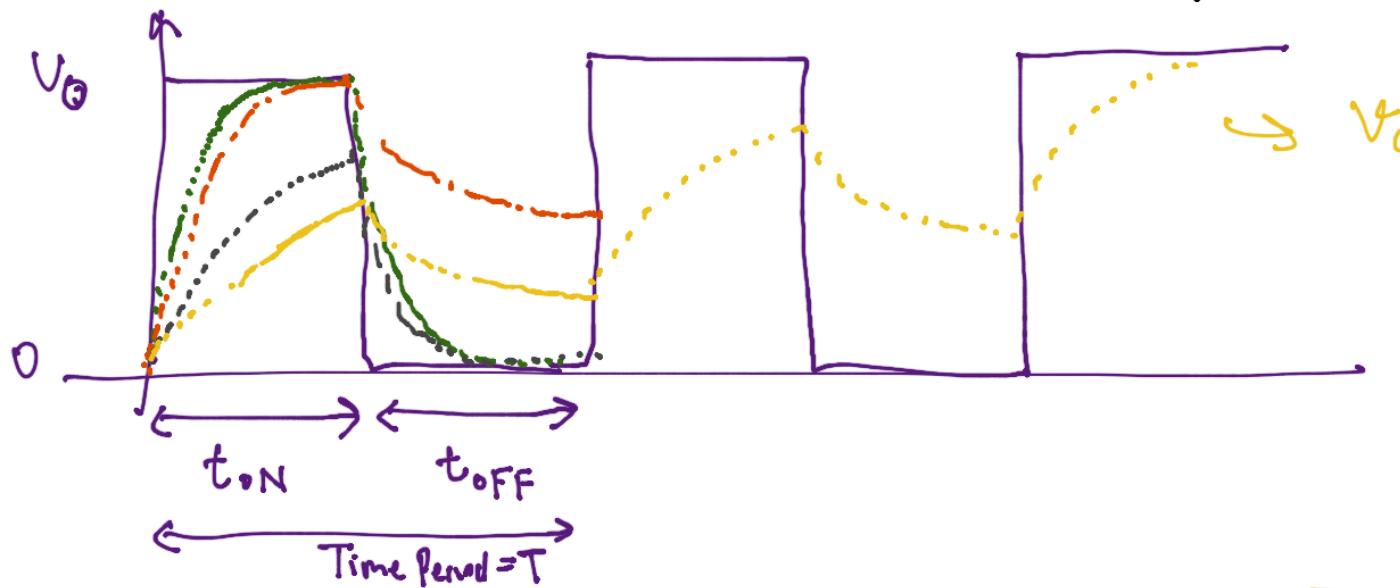

R-C

τ = Time const..

t_{OFF} & t_{ON} → varying :

$$t_{OFF}, t_{ON} \gg \tau$$

$$t_{ON} \gg \tau ; t_{OFF} < \tau$$


$$t_{ON} < \tau ; t_{OFF} \gg \tau$$

$$t_{ON} < \tau , t_{OFF} < \tau$$

Ex 8.10


(R-C type)

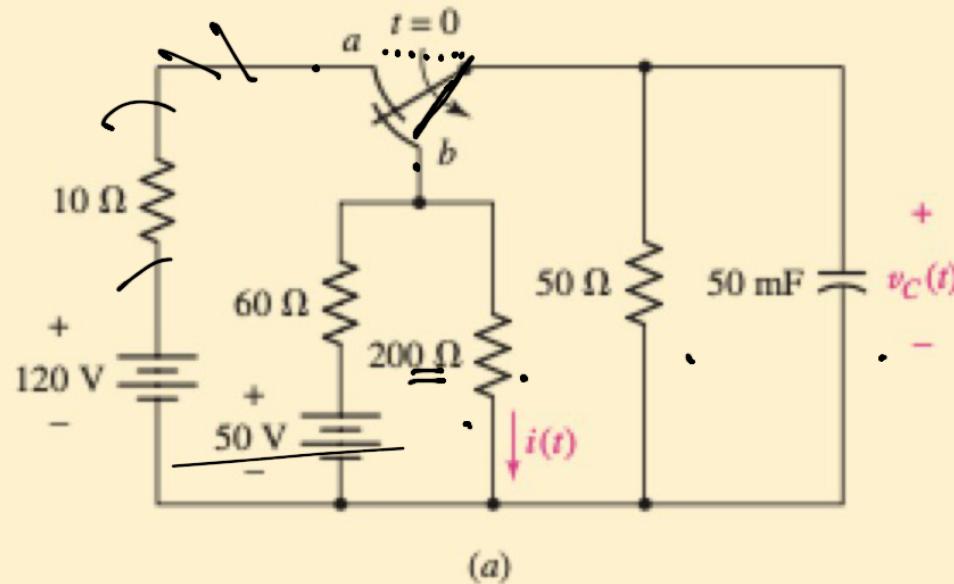Find the capacitor voltage $v_C(t)$ and the current $i(t)$ in the 200Ω resistor of Fig. 8.42 for all time.



$t < 0$

initial condition:

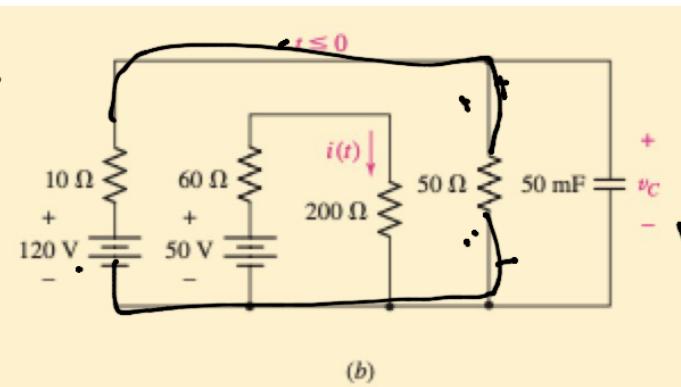

$$v_C(0) =$$

$$t \rightarrow \infty C: 0 \cdot C$$


$$v_C(0) = \frac{120}{60} * 50 = 100V$$

$$v_C(0^-) = v_C(0^+)$$

$$\uparrow = 100V$$

$\nexists 200\Omega : i(0^-) \neq i(0^+)$

$t > 0 \quad i(0^+)$

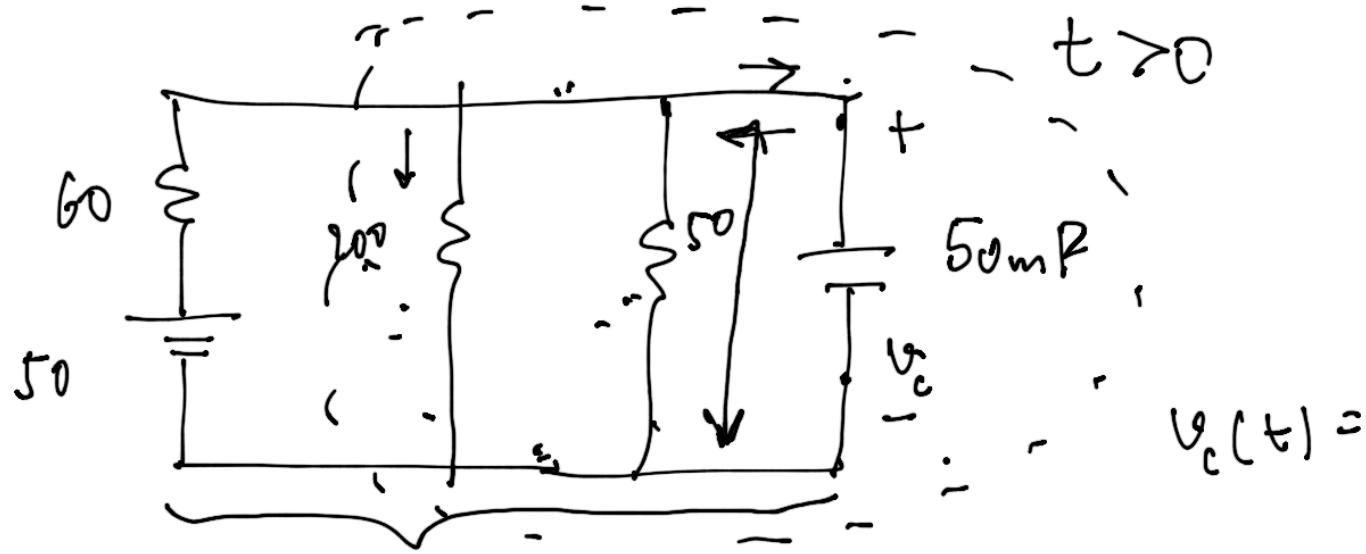

$$1. \quad \tau = (60 || 200) || 50 * 50m$$

$$= 1.2 \text{ sec.}$$

$$v_{cn} = A e^{-t/1.2}$$

$$2. \quad \text{Cap } (t \rightarrow \infty) \rightarrow 0 \cdot C$$

$$v_{cf} = \frac{V * R}{R + (200 || 50)} = \frac{50V + (200 || 50)}{60 + (200 || 50)} \cdot$$

$$= 20V$$

$$3. \quad v_c = v_{cf} + v_{cn} = 20 + A e^{-t/1.2} = v_c$$

Find A using initial

$$(t=0) \quad V_C = 100 = 20 + A e^0$$

$$A = 80$$

$$V_C = 20 + 80 e^{-t/1.2}$$

i (at condition)

$$\frac{i}{50} = \frac{1}{60 + 50/1.2} * \frac{50}{200 + 50} = 0.1 A$$

(without cap)

Act has Active i & v will have = (forced + natural response) $-t/1.2$

$$T = 1.2 \quad i = i_f + i_n = 0.1 + K e^{-t/1.2}$$

$$t > 0 \quad V_C = \dots \quad 0.5 = 0.1 + K e^0$$
$$K = ?$$

Example