


Fundamentals of Electronics

ECE 101



Exercise: Simplify the following Boolean function

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

 

$$A'B'C'D' + A'B'CD' = A'B'D'$$

$$AB'C'D' + AB'CD' = AB'D'$$

$$A'B'D' + AB'D' = B'D'$$

$$A'B'C' + AB'C' = B'C'$$

$$F = B'D' + B'C' + A'CD'$$

Prime Implicant A prime implicant is a product term obtained by combining the maximum possible number of adjacent squares in the map.

- A single 1 on a map represents a prime implicant if it is not adjacent to any other 1's.
- Two adjacent 1's form a prime implicant, provided that they are not within a group of four adjacent squares.
- Four adjacent 1's form a prime implicant if they are not within a group of eight adjacent squares, and so on.


The **essential prime implicants** are found by looking at each square marked with a 1 and checking the number of prime implicants that cover it.

The prime implicant is essential if it is the only prime implicant that covers the minterm


- The procedure for finding the simplified expression from the map requires that we first determine all the essential prime implicants.
- The simplified expression is obtained from the logical sum of all the essential prime implicants, plus other prime implicants that may be needed to cover any remaining minterms not covered by the essential prime implicants.
- Occasionally, there may be more than one way of combining squares, and each combination may produce an equally simplified expression.

 Example:

$$F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$



 Essential prime implicants
 BD and $B'D'$



The simplified expression is obtained from the logical sum of the two essential prime implicants and any two prime implicants

Logical sum of all the essential prime implicants, plus other prime implicants that may be needed to cover any remaining minterms not covered by the essential prime implicants.

$$\begin{aligned} F &= BD + B'D' + CD + AD \\ &= BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD \\ &= BD + B'D' + B'C + AB' \end{aligned}$$

Prime Implicant A prime implicant is a product term obtained by combining the maximum possible number of adjacent squares in the map.

The **essential prime implicants** are found by looking at each square marked with a 1 and checking the number of prime implicants that cover it.

The prime implicant is essential if it is the only prime implicant that covers the minterm

- The procedure for finding the simplified expression from the map requires that we first determine all the essential prime implicants.
- The simplified expression is obtained from the logical sum of all the essential prime implicants, plus other prime implicants that may be needed to cover any remaining minterms not covered by the essential prime implicants.
- Occasionally, there may be more than one way of combining squares, and each combination may produce an equally simplified expression.



PRODUCT-OF-SUMS SIMPLIFICATION

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$$


$$F = B'D' + B'C' + A'C'D$$

$$F' = AB + CD + BD'$$

$$F = (A' + B')(C' + D')(B' + D)$$

  

(a) $F = B'D' + B'C' + A'C'D$

 

(b) $F = (A' + B')(C' + D')(B' + D)$

K-map for PRODUCT-OF-SUMS representation

$$F(x, y, z) = \Pi(0, 2, 5, 7)$$


$$F = x'z + xz'$$

$$F' = xz + x'z'$$

$$F = (x' + z')(x + z)$$

$$F = (A' + B' + C')(B + D)$$

$$F' = ABC + B'D'$$

 

To build a K-map of F from POS, mark 0's in the squares representing the minterms of F.

Don't care conditions

Sometimes, functions have unspecified outputs for some input combinations, such functions are called incompletely specified functions.

In such case, we generally don't care what value is assumed by the function for the unspecified minterms.

They are called as don't care conditions.

These don't-care conditions can be used on a map to provide further simplification of the Boolean expression.

Generally, these minterms are marked by 'X' in the K-map.

In choosing adjacent

Example:

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

which has the don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$

		y			
		00	01	11	10
wx	yz				
		m_0	m_1	m_3	m_2
00	$w'x'$	X	1	1	X
		m_4	m_5	m_7	m_6
01		0	X	1	0
11		m_{12}	m_{13}	m_{15}	m_{14}
		0	0	1	0
10	w	m_8	m_9	m_{11}	m_{10}
		0	0	1	0
		z			
		yz			

$$F = yz + w'x'$$

$$F(w, x, y, z) = yz + w'x' = \Sigma(0, 1, 2, 3, 7, 11, 15)$$

		y			
		00	01	11	10
wx	yz				
		m_0	m_1	m_3	m_2
00	$w'z$	X	1	1	X
		m_4	m_5	m_7	m_6
01		0	X	1	0
11		m_{12}	m_{13}	m_{15}	m_{14}
		0	0	1	0
10	w	m_8	m_9	m_{11}	m_{10}
		0	0	1	0
		z			
		yz			

$$F = yz + w'z$$

$$F(w, x, y, z) = yz + w'z = \Sigma(1, 3, 5, 7, 11, 15)$$

Don't care conditions

Sometimes, functions have unspecified outputs for some input combinations, such functions are called incompletely specified functions.

In such case, we generally don't care what value is assumed by the function for the unspecified minterms.

They are called as don't care conditions.

These don't-care conditions can be used on a map to provide further simplification of the Boolean expression.

Generally these minterms are marked by 'X' in the K-map.

In choosing adjacent

Decimal	Excess-3
-3	0000
-2	0001
-1	0010
0	0011
1	0100
2	0101
3	0110
4	0111
5	1000
6	1001
7	1010
8	1011
9	1100
10	1101
11	1110
12	1111

Decimal Digit	BCD 8421	2421	Excess-3	8, 4, -2, -1
0	0000	0000	0011	0000
1	0001	0001	0100	0111
2	0010	0010	0101	0110
3	0011	0011	0110	0101
4	0100	0100	0111	0100
5	0101	1011	1000	1011
6	0110	1100	1001	1010
7	0111	1101	1010	1001
8	1000	1110	1011	1000
9	1001	1111	1100	1111
Unused bit combinations	1010	0101	0000	0001
	1011	0110	0001	0010
	1100	0111	0010	0011
	1101	1000	1101	1100
	1110	1001	1110	1101
	1111	1010	1111	1110

Example:

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

which has the don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$

		y			
		00	01	11	10
wx	yz				
		m_0	m_1	m_3	m_2
00	$w'x'$	X	1	1	X
		m_4	m_5	m_7	m_6
01		0	X	1	0
11		m_{12}	m_{13}	m_{15}	m_{14}
		0	0	1	0
10	w	m_8	m_9	m_{11}	m_{10}
		0	0	1	0
		z			
		yz			

$$F = yz + w'x'$$

$$F(w, x, y, z) = yz + w'x' = \Sigma(0, 1, 2, 3, 7, 11, 15)$$


		y			
		00	01	11	10
wx	yz				
		m_0	m_1	m_3	m_2
00	$w'z$	X	1	1	X
		m_4	m_5	m_7	m_6
01		0	X	1	0
11		m_{12}	m_{13}	m_{15}	m_{14}
		0	0	1	0
10	w	m_8	m_9	m_{11}	m_{10}
		0	0	1	0
		z			
		yz			

$$F = yz + w'z$$


$$F(w, x, y, z) = yz + w'z = \Sigma(1, 3, 5, 7, 11, 15)$$

NAND Implementation



 
NAND and NOR gates are universal and relatively easier to implement



AND-invert

 




Invert-OR

   


NAND Implementation: Two level implementation

The implementation of Boolean functions with NAND gates requires that the functions be in sum-of-products form

$$F = AB + CD$$

   

 
Example: Implement the following Boolean function with NAND gates:



$$F(x, y, z) = (1, 2, 3, 4, 5, 7)$$


$$F = xy' + x'y + z$$

- Simplify the function and express it in sum-of-products form.
- Draw a NAND gate for each product term of the expression that has at least two literals. The inputs to each NAND gate are the literals of the term. This procedure produces a group of first-level gates.
- Draw a single gate using the AND-invert or the invert-OR graphic symbol in the second level, with inputs coming from outputs of first-level gates.
- A term with a single literal requires an inverter in the first level. However, if the single literal is complemented, it can be connected directly to an input of the second level NAND gate.

 

Multilevel NAND Implementation

$$F = A (CD + B) + BC'$$

 



Convert all AND gates to NAND gates with AND-invert graphic symbols.

Convert all OR gates to NAND gates with invert-OR graphic symbols.




Check all the bubbles in the diagram. For every bubble that is not compensated by another small circle along the same line, insert an inverter (a one-input NAND gate) or complement the input literal.

Multilevel NAND Implementation

$$F = (AB' + A'B)(C + D')$$

  


NOR Implementation

   


Example:

$$F = (A + B)(C + D)E'$$

 

NOR Implementation

$$F = (AB' + A'B)(C + D')$$

 

XOR Function

$$x \oplus y = xy' + x'y$$

$$(x \oplus y)' = xy + x'y'$$

$$(x \oplus y)' = (xy' + x'y)' = (x' + y)(x + y') = xy + x'y'$$

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$


$$x \oplus x = 0$$

$$x \oplus x' = 1$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

XOR is an Odd Function

 i.e. an odd number of variables
be equal to 1 to make function
equal to 1.




(b) Exclusive-OR with NAND gates

Parity Generation and Checking

Exclusive-OR functions are very useful in systems requiring error detection and correction codes

Even-Parity-Generator Truth Table


Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(a) 3-bit even parity generator

Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 


(b) 4-bit even parity checker

Combinational and Sequential Circuits

- **Combinational circuit:** Logic gates whose outputs at any time are determined from only the present combination of inputs
 - A combinational circuit performs an operation that can be specified logically by a set of Boolean functions.
- **Sequential circuit:** Contain storage elements in addition to logic gates.
 - Their outputs are a function of the inputs and the state of the storage elements.
 - The state of the storage elements is a function of previous inputs
 - The outputs of a sequential circuit depend not only on present values of inputs, but also on past inputs

Combinational Circuits

 


- A combinational circuit can be described by **m** Boolean functions
 - One for each output variable.
- Each output function is expressed in terms of the **n** input variables.
- **The aim here is:**
 - Analyze the behavior of a given logic circuit
 - Synthesize a circuit that will have a given behavior
- There are several combinational circuits that are employed extensively in the design of digital systems.
These circuits are available in integrated circuits and are classified as standard components.

Combinational Circuits

- **Examples are:** Adders, subtractors, comparators, decoders, encoders, and multiplexers.
- These components are available in integrated circuits as medium-scale integration (MSI) circuits.
- **The analysis of a combinational circuit requires that we determine the function that the circuit implements.**
- This task starts with a given logic diagram and culminates with a set of Boolean functions, a truth table, or, possibly, an explanation of the circuit operation.
- The diagram of a combinational circuit has logic gates with no feedback paths or memory elements .
- A feedback path is a connection from the output of one gate to the input of a second gate whose output forms part of the input to the first gate.
 - Feedback paths in a digital circuit define a sequential circuit and must be analyzed by special methods

Analysis

 

$$\begin{aligned} F_1 &= T_3 + T_2 = F'_2 T_1 + ABC = (AB + AC + BC)'(A + B + C) + ABC \\ &= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\ &= (A' + B'C')(AB' + AC' + BC' + B'C) + ABC \\ &= A'BC' + A'B'C + AB'C' + ABC \end{aligned}$$






Example:

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Decimal Digit	BCD 8421	2421	Excess-3	8, 4, -2, -1
0	0000	0000	0011	0000
1	0001	0001	0100	0111
2	0010	0010	0101	0110
3	0011	0011	0110	0101
4	0100	0100	0111	0100
5	0101	1011	1000	1011
6	0110	1100	1001	1010
7	0111	1101	1010	1001
8	1000	1110	1011	1000
9	1001	1111	1100	1111
Unused bit combinations	1010	0101	0000	0001
	1011	0110	0001	0010
	1100	0111	0010	0011
	1101	1000	1101	1100
	1110	1001	1110	1101
	1111	1010	1111	1110

How to create this circuit?

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

     

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Circuit Implementation


$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$$

$$= B'(C + D) + B(C + D)'$$

$$w = A + BC + BD = A + B(C + D)$$

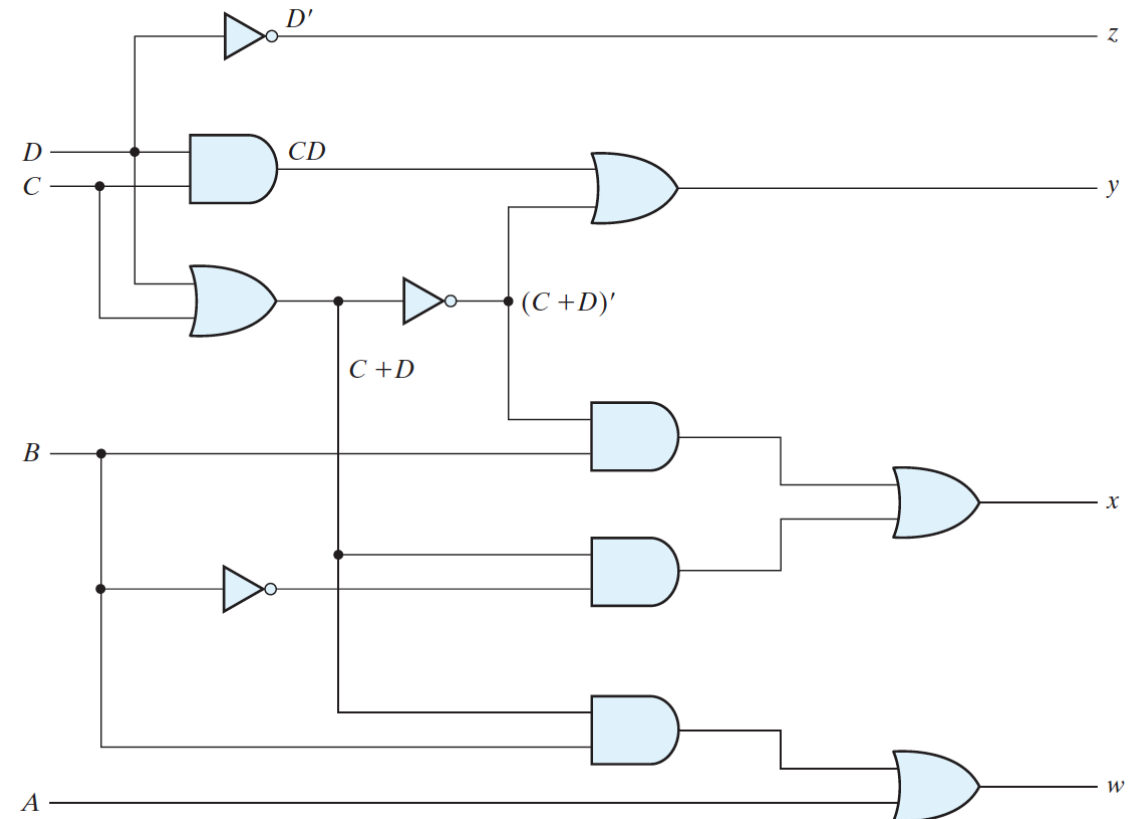


Binary Adder and Subtractor

Half Adder Needs two binary inputs and two binary outputs

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$


$$C = xy$$

 

 (b) $S = x \oplus y$
 $C = xy$

A combinational circuit that performs the addition of two bits is called a half adder .

One that performs the addition of three bits (two significant bits and a previous carry) is a full adder .



(a) $S = xy' + x'y$
 $C = xy$

Thank you