

LAB-1 REPORT

TABLE NO:-42

ROOM NO:-117

NAME:-SANTHOSH

ROLL NO:-2024102054

NAME:-AKSHAY

ROLL NO:-2024102014

OBJECTIVE:-

to compare the theoretical value and practical values of time constant, cutoff frequency, using the digital Storage oscilloscope

EQUIPMENT REQUIRED:

Breadboard, Resistors (various values), Capacitors (various values), Digital Storage Oscilloscope (DSO), Connecting wires

PROCEDURE:

Take a resistor and capacitor in which the capacitance is known and the resistance should be calculated by multimeter

Now take the DSO (digital storage oscillator) take the input as square wave for the first signal

Connect the potential difference between capacitor to the second signal which will be a exponential increase and decrease

The increasing curve represents charging of the capacitor and the decreasing curve represents the discharging of the capacitor

Now calculate the theoretical value of the time constant

$$\text{Time constant} = RC$$

Calculate the time at which the potential difference becomes 63rd percentage of its highest value by referring the initial time as zero



Compare the theoretical and practical value of the time constant


Perform it for 2 resistances and compare them

OBSERVATIONS AND RESULTS:

s.no	R(in Ω)	C(in μf)	Time const (theoretical) (in μs)	Time Const (practical) (in μs)	Cutoff Freq (theoretical) (In k hz)	Cutoff Freq (practical) (in k hz)
1)	10000	0.1	1000	800	0.16	0.15
2)	11600	0.001	11.6	14.7	13.7	10.8
3)	46600	0.001	46.6	58	3.41	2.7

DSO IMAGES AND CALCULATIONS

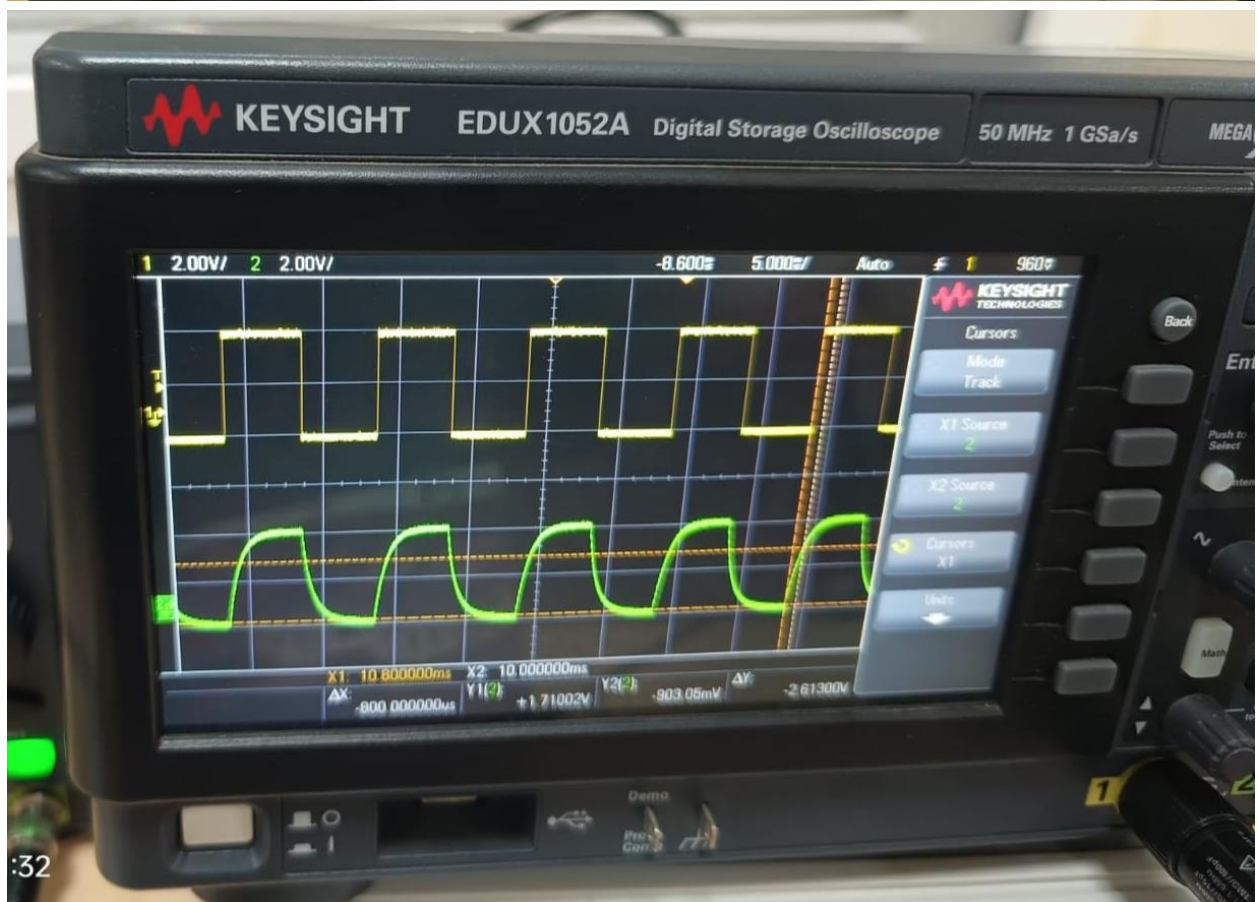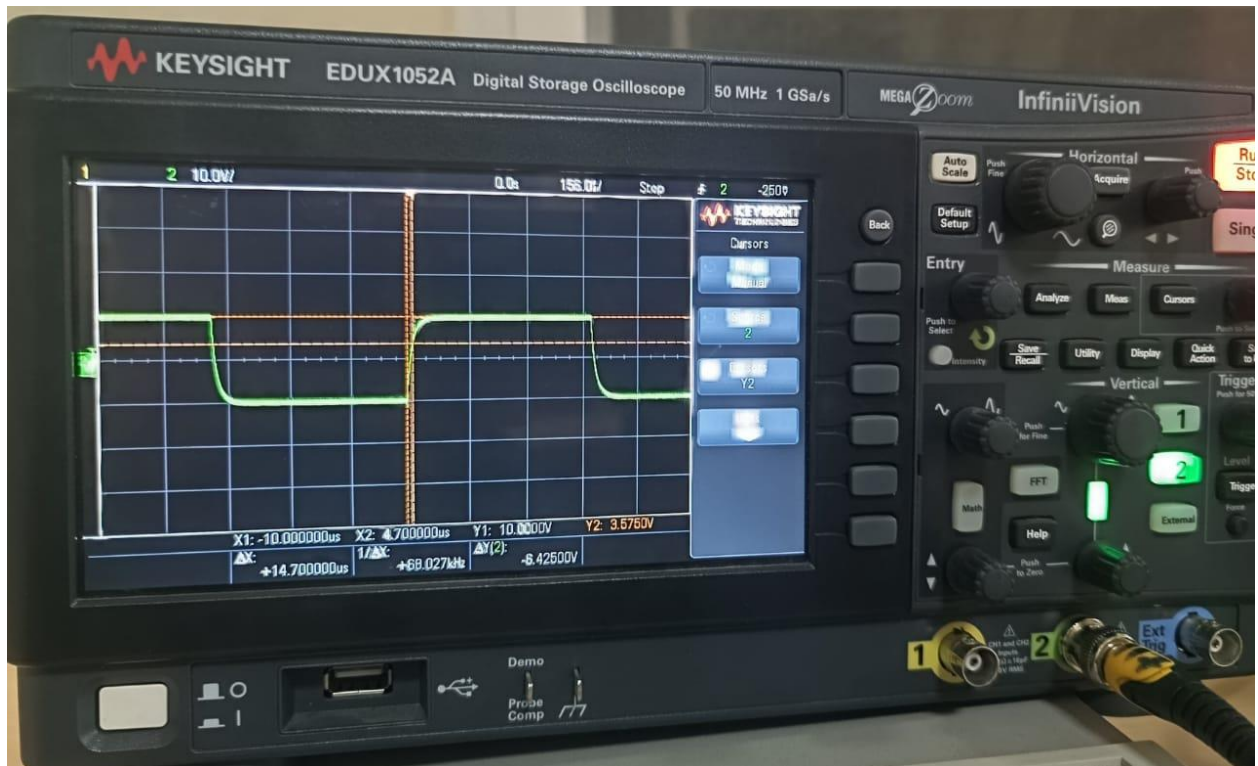

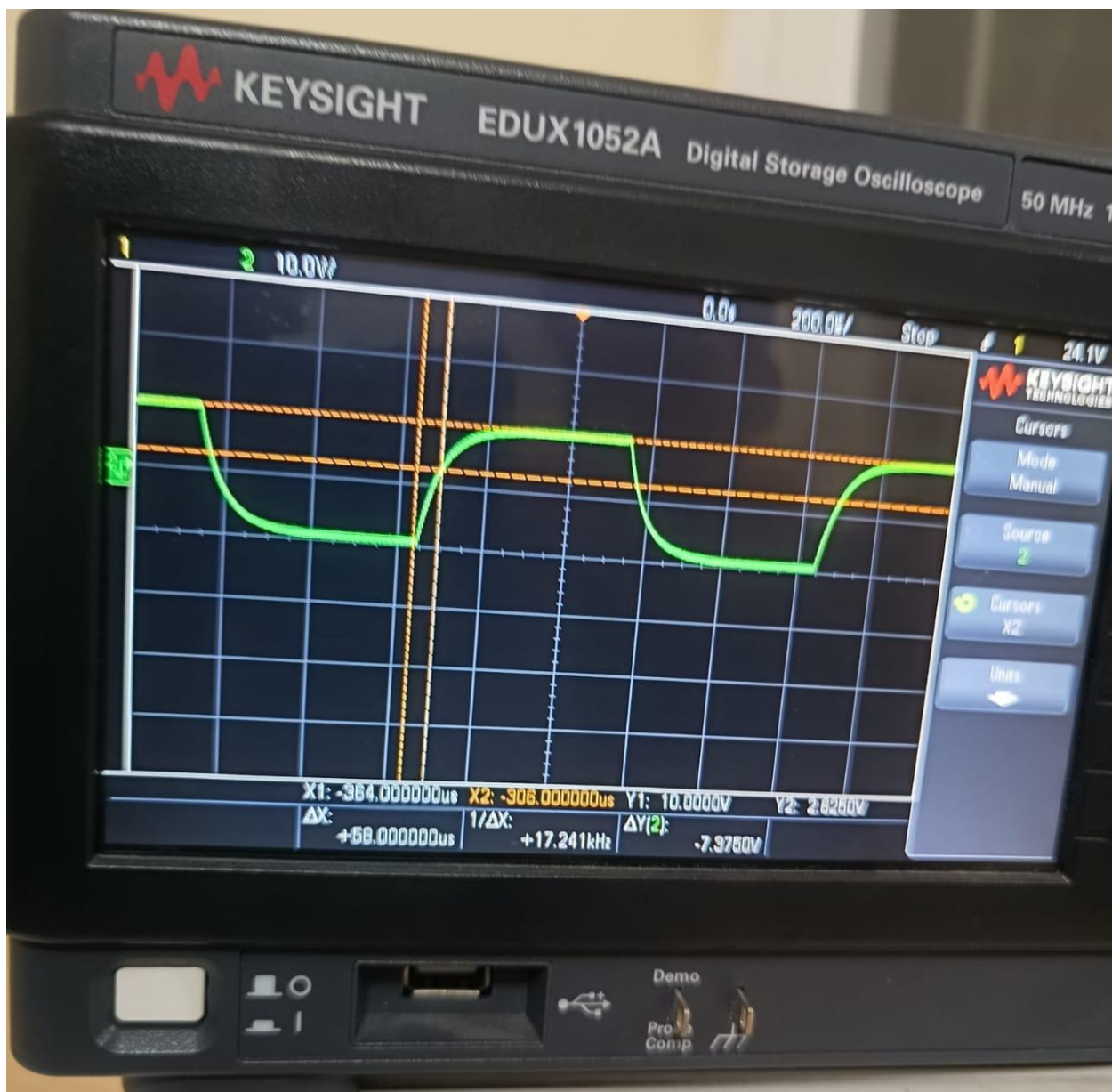

$$R = 10 \times 10^3 \Omega$$

$$C = 10^{-7} \text{ F} = 0.1 \mu\text{F}$$

$$T = RC = (10 \times 10^3 \Omega)(10^{-7} \text{ F})$$

$$= 10^{-3} \text{ sec}$$

$$f = \frac{1}{2\pi RC}$$

$$= \frac{1}{(2)(3.14)(10^{-3})}$$

$$= 0.16 \times 10^3$$

$$= 1.6 \times 10^2$$

$$\text{cut off frequency} = 1.6 \times 10^2$$

$$\text{Experimental} = 150 \text{ Hz}$$

Experimental

$$\text{Time constant} = 0.8 \times 10^{-3} \text{ sec}$$

Calculated

$$\text{Time constant} = 10^{-3} \text{ sec}$$

S.V. Santosh C.H. Akshay

$$11.6 \times 10^3 \Omega$$

$$46.6 \times 10^3 \Omega$$


$$46.6 \times 10^3 \Omega$$

$$\begin{array}{r} 10.4 \\ 9.7 \\ \hline \end{array}$$

$$\begin{array}{r} 21.1 \times 0.63 \\ 13.293 \\ 9.700 \\ \hline 3.593 \end{array}$$

$$\begin{array}{r} 27.62 \\ 7.56 \\ \hline \end{array}$$

$$20.12$$

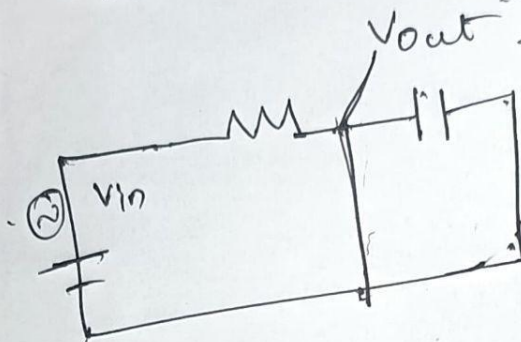

$$\tau = \frac{1}{RC}$$

$$\tau = RC$$

$$\begin{array}{r} 4.25 \\ 4.23 \\ \hline 9.68 \end{array}$$

$$\begin{array}{r} 19.25 \\ 6.09 \\ \hline \end{array}$$

$$\begin{aligned} C &= 0.001 \text{ Mf} \\ &= 10^{-3} \text{ Mf} \\ &= 10^{-3} \times 10^{-6} \text{ f} \\ &= 10^{-9} \text{ f} \\ C &= 1 \text{ nF} \end{aligned}$$

$$t = \frac{V}{C}$$

$$q = CE \left[1 - e^{-\frac{t}{RC}} \right]$$

$$= CE \left[1 - \frac{1}{e} \right]$$

$$q = 0.63 CE$$

$$V = \frac{q}{C} = 0.63 E$$

$$\tau = 46.6 \times 10^3 \times 10^{-9}$$

$$\tau = 46.6 \text{ ms}$$

$$20 \times 0.63$$

$$\begin{array}{r} 12.6 \times 2 \\ 12.6 - 10 \\ \hline 2.6 \end{array}$$

$$q = CE \left[1 - e^{-t/RC} \right]$$

$$t \rightarrow \infty$$

$$q = CE \left[1 - 0 \right]$$

$$q_{\text{max}} = CE$$

$$\frac{q_{\text{max}}}{C} = E$$

Experimental: 58 mV

Calculated: 46.6 mV

$$\begin{array}{r} 9.625 \\ 10.1 \\ \hline 19.625 \end{array}$$

Tany B

CONCLUSION:

There is a cutoff frequency which is calculated as $1/(2 \cdot \pi \cdot RC)$ after which the capacitor charges and discharges very quickly in which the maximum value cannot be reached the time constant also cannot achieve its exact value due to some errors in the instrument