

End-Sem: Analog Electronic Circuits (S25.EC2.103)

Max. Marks: 80

Time: 3:00 PM-6:00 PM

Date: 29/04/2025

NOTE: No query allowed during the exam. Write your assumptions (if any) for each question.

Q1. A curious student like you decides to try a new circuit topology wherein the input is applied to the drain and the output is sensed at the source (Fig.1). Assume $\lambda \neq 0$, determine the voltage gain of the circuit and discuss the result. [10 Marks]

 


Fig.1

 


Fig.2



Fig.3

Q2(a). Discuss Miller theorem/effect in the context of amplifiers. How it impacts the amplifier performances? Prove that Miller effect results in an increase in the input capacitance (Just for reference; Fig.2 and Fig.3). [5 Marks]

(b). What is open-circuit time constant approach technique? Estimate the upper 3dB cut-off frequency of the given amplifiers (in Fig.4 and Fig.5) using open-circuit time constant approach. [10 Marks]
Assume $C_{gsn}=4fF$, $C_{gdn}=0.4fF$, $C_{dbn}=4fF$, $C_{gdp}=0.4fF$, $C_{dbp}=4fF$. Also, take the voltage gain of amplifiers equal to -8. What are amplifier configurations in the given circuits (Fig.4 and Fig.5)?
[Hint: You may need to estimate the voltage gain at V_{o1} (Fig.5). Gain at this node will suffer from Miller effect. Just need to show gain at V_{o1} is ≤ 1]

 


Fig.4

 


Fig.5

Q 3(a). Consider the circuit shown in Fig.6. Calculate the maximum transconductance that M_1 can provide (without going into the triode region). Consider $V_{TH}=0.4V$ for NMOS. [5 Marks]

 


Fig.6

 


Fig.7

 


Fig.8

$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TH}}$$

$$= \frac{2I_{DS}}{1.4 - 100I_{DS}}$$

$$g_m = \frac{2I_{DS}}{V_{DSAT}} = \frac{2 \left(\frac{1}{2} K_n (V_{DSAT})^2 \right)}{V_{DSAT}}$$

$$g_m = K_n V_{DSAT} \quad g_m = K_n (V_{GS} - V_{TH})$$

(b). Consider the circuit depicted in Fig.7, where $W/L = 20/0.18$. Assuming the current flowing through R_2 is one-tenth of I_{D1} , calculate the values of R_1 and R_2 so that $I_{D1} = 0.5$ mA. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200 \mu\text{A/V}^2$ for NMOS. [5 Marks]

(c). The self-biased stage of Fig.8 must be designed for a drain current of 1 mA. If M_1 is to provide a transconductance of $1/(100\Omega)$, calculate the required value of R_D . Consider $V_{TH} = 0.4$ V for NMOS. [5 Marks]

Q4. The CS stage of Fig. 9 must provide a voltage gain of 10 with a bias current of 0.5 mA. Assume $\lambda_1 = 0.1 \text{ V}^{-1}$, and $\lambda_2 = 0.15 \text{ V}^{-1}$. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200 \mu\text{A/V}^2$ for the NMOS; $V_{TH} = -0.4$ V, $\mu_p C_{ox} = 100 \mu\text{A/V}^2$ for the PMOS. [Hint: $r_o = 1/\lambda I_D$] [2.5+2.5+5+5= 15 Marks]

(a). Compute the required value of $(W/L)_1$.

(b). if $(W/L)_2 = 20/0.18$, calculate the required value of V_b .

(c). if in the stage of Fig.9, M_2 has a long length so that $\lambda_2 \ll \lambda_1$. Calculate the voltage gain if $\lambda_1 = 0.1 \text{ V}^{-1}$, $(W/L)_1 = 20/0.18$, and $I_D = 1$ mA.

(d). if the circuit of Fig.9 is designed for a bias current of I_D with certain dimensions for M_1 and M_2 . If the width and the length of both transistors are doubled, how does the voltage gain change? Consider two cases: (i) the bias current remains constant, or (ii) the bias current is doubled.

 


Fig.9

Q5(a). The CG stage depicted in Fig.10 must provide an input impedance of 50Ω and an output impedance of 500Ω . Assume $\lambda = 0$. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200 \mu\text{A/V}^2$ for the NMOS. [2+2+2=6Marks]

- What is the maximum allowable value of I_D ?
- With the value obtained in (a), calculate the required value of W/L .
- Compute the voltage gain.

(b). The source follower (CD amplifier) shown in Fig.11 is biased through R_G . Calculate the voltage gain if $W/L = 20/0.18$ and $\lambda = 0.1 \text{ V}^{-1}$. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200 \mu\text{A/V}^2$ for the NMOS. [4 Marks]

 


Fig.10

 


Fig.11

Q6(a). Is there any trade-off between voltage gain and output voltage swing in MOS amplifier? Explain your answer through gain and voltage swing equations. You may consider resistive load common-source amplifier for your explanations. [5 Marks]

(b). Compare the common-source (CS), common-gate (CG), and common-drain (CD) amplifier configurations in terms of voltage gain, input impedance, output impedance, voltage swing, and frequency response in general. [5 Marks]


Q7. Draw a small-signal model of a common-source amplifier with NMOS active load, estimate voltage gain of this amplifier. Discuss the pros and cons of this amplifier. [5 Marks]

OR

 Q7. Find the output signal if the input is

- $V_{IN}=1V$ DC
- $V_{IN}=1V$ AC (very high frequency)

Assume the op-amp to be ideal. $R=100\ \Omega$, $C=1nF$ and $R'=500\ \Omega$



Note: Keep your answers to the point.

*****Best of luck*****

$$g_m = \sqrt{2 k_n I_{DQ}} = \sqrt{2 k_n \left(\frac{1}{2} k_n \right) (V_{DSAT})^2}$$

$$= k_n V_{DSAT}$$