

# ANALOG ELECTRONIC CIRCUITS

## LAB REPORT-7

**Name:** Ande Karthik


**Roll no:** 2023102009

**Team mate:** Radheshyam.M

**Roll no:** 2023102032

### Common Source Amplifier
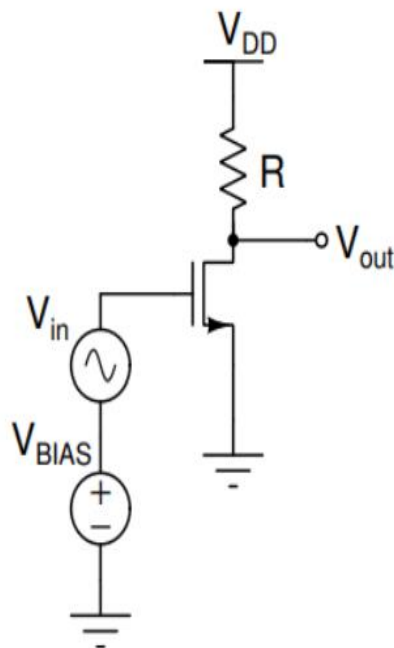
#### 1) Effect of Body Effect on gain of CS Amplifier:



We built a circuit with  $V_{DD} = 5V$ ,  $V_{BIAS} = 2.5V$ ,  $V_T = 1.8V$ ,  $R_L = 4.7k\Omega$ .

a)  $V_{DS} = 3.12V$

Find Drain current

$$I_{DS} = \frac{V_{DD} - V_{DS}}{R_L}$$

And also find  $g_m$  and

$$\mu_n C_{ox} \frac{W}{L}$$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \mu C_o \frac{W}{L} (V_{GS} - V_T)$$

Handwritten calculations:

$$V_{DD} = 5V, V_B = 2.5, V_T = 1.8V, R_L = 1K$$

$$\boxed{V_{DS} = 3.2}$$

$$I_D = \frac{V_{DD} - V_{DS}}{R_L}$$

$$I_D = \frac{5 - 3.2}{1000} = 1.8 \times 10^{-3}$$

$$I_D = \frac{1}{2} \times \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$3.6 \times 10^{-3} = K (0.7)^2$$

$$7.346 \times 10^{-3} = K$$

$$K = 0.007346$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$


$$= K \times 0.7$$

$$\boxed{g_m = 0.0051422}$$



$G_m = 5.15\text{m}$ (approx.)

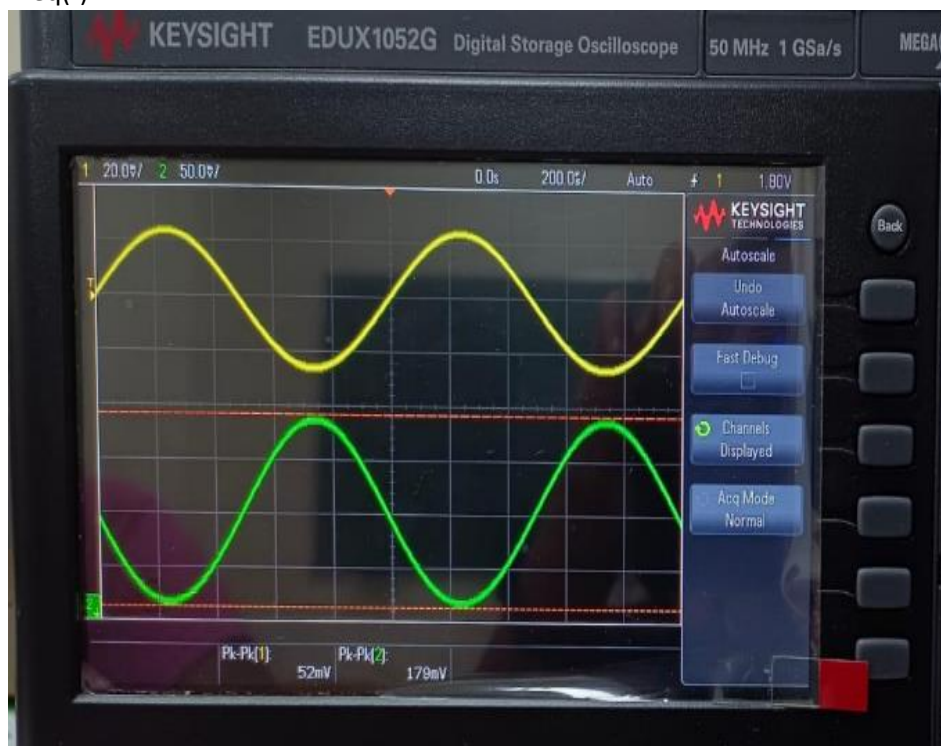b)  
We have applied an AC signal  
 $V_{in} = 50\text{m V}_{pp}$ (peak to peak)  
 $\text{Freq}(f) = 1\text{k Hz}$



$V_{out} = 180\text{mV}$  (peak to peak)

$$\text{Gain} = \frac{180 \text{ mV}}{50 \text{ mV}} = 3.6 = 3.6$$

$$g_m R_L = 3.6$$

$$\boxed{g_m = 3.6 \text{ m}} = 3.6 \times 10^{-3}$$

The measured value of  $g_m$ , which is 5.15 mA/V, is quite close to the calculated value of  $g_m$ , which is 3.62 mA/V.

There are several possible factors that could contribute to this small difference, such as process variations, temperature effects, and parasitic resistances and capacitances.

c)


$V_{in} = 50 \text{ mV}$  (peak to peak)

Calculate gain and  $G_m$  effective

Check is it matching with previously calculated  $g_m$  ...?
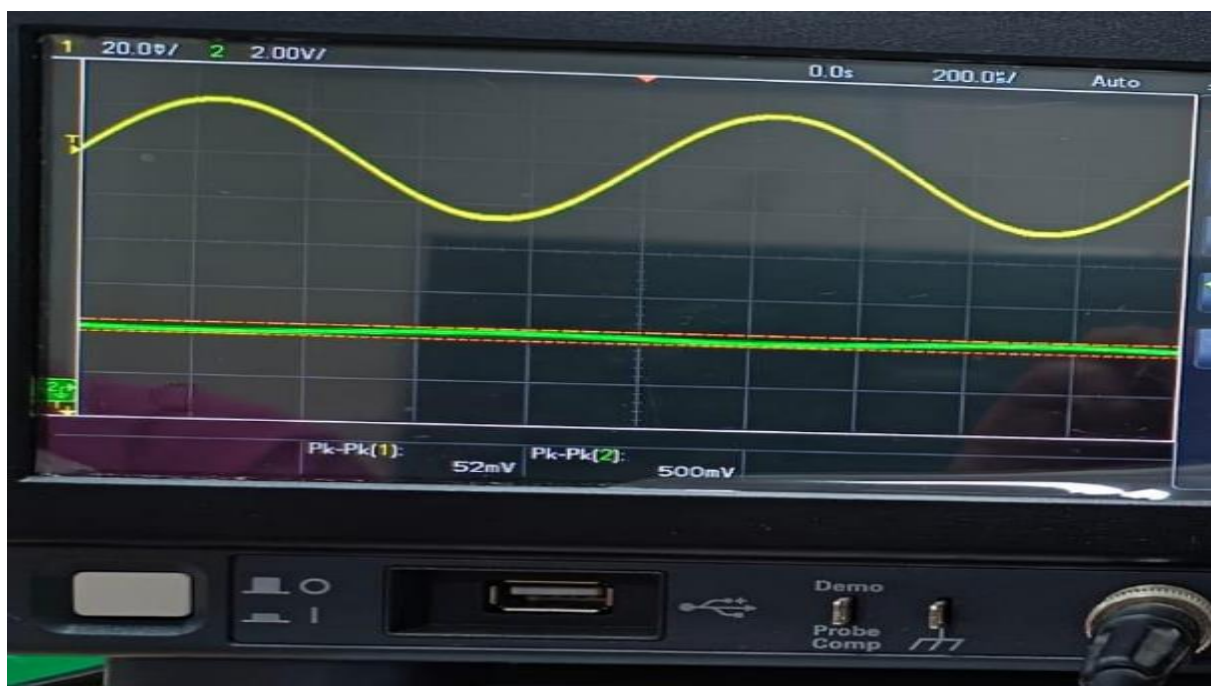
$$A_v = \frac{v_{out}}{v_{in}} = g_m \times R_L$$







Body Voltage (V <sub>ss</sub> )	V <sub>out</sub>	Gain =(V <sub>out</sub> /V <sub>in</sub> )	G <sub>m</sub> (effective)
0	280mV	5.5	0.00119
0.4	177mV	3.3	0.0007
-0.4	500mV	9.7	0.002

$$(C) g_{m(effective)} = g_m + g_{mb}$$

This is because if we consider body effect i.e.,  $V_B > V_S$ .

More  $V_{GS}$  is required for channel formation i.e.,  $V_T$  increases.

This is reciprocated in eqn:

$$V_T = V_{T0} + \gamma \left[ \sqrt{2\phi_s + V_{SB}} - \sqrt{2\phi_s} \right]$$

$$\phi_s = 2V_T \ln \left( \frac{N_A}{n_T} \right)$$

$V_T$  = Thermal Voltage

When  $V_{SB} = 0$

$$V_T = V_{T0}$$


when we consider body effect,  $V_T$  is of func<sup>n</sup> of  $V_{SB}$ .

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

$I_D$  is a function of  $V_T$   
Indirectly,  $I_D$  is a function of  $V_{SB}$

$\frac{\partial I_D}{\partial V_{SB}}$  is finite value

$\therefore$  We can say
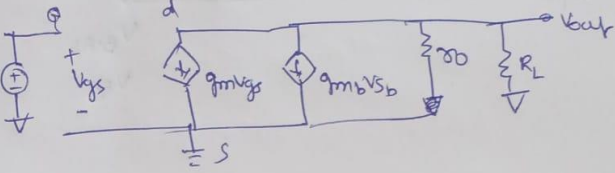
$$I_{D2} = -g_{mb}V_{SB}$$


$$\frac{V_{out}}{R_L} + \frac{V_{out}}{r_o} + g_m V_{SB} + g_m V_{in} = 0$$

$$V_{out} \left( \frac{1}{R_L} + \frac{1}{r_o} \right) = -(g_m V_{SB} + g_m V_{in})$$

$\therefore$  as  $V_S = 0$

$$\frac{V_{out}}{V_{in}} = \frac{-(g_{mb} + g_m)}{\frac{1}{r_o} + \frac{1}{R_L}}$$

$r_o$  is very high if we ignore CLM.

$$A_v = -(g_{mb} + g_m) R_L$$

$$\therefore g_m (\text{effective}) = g_m + g_{mb}$$

When the body voltage is increased in an NMOS (n-channel MOSFET), the conductivity of the channel increases. As the body voltage is raised, the p-substrate reaches a higher potential. This positive charge accumulation at the bottom of the substrate causes more electrons to be attracted out of the n+ regions. Consequently, a lower threshold voltage ( $V_{th}$ ) is required to fill the channel with electrons and enable conduction.

Since transconductance ( $g_m$ ) is directly proportional to the difference between the gate-to-source voltage ( $V_{gs}$ ) and the threshold voltage


( $V_{th}$ ), an increase in  $g_m$  is observed. This is because the decreased  $V_{th}$  leads to a larger  $V_{gs} - V_{th}$  value, resulting in higher transconductance.

On the other hand, if the body voltage is decreased ( $V_{bs} < 0$ ), the n+ regions and the p-substrate are in reverse bias. This reverse biasing causes electrons to be pushed further into the n+ regions, resulting in an increased threshold voltage. Consequently, a higher  $V_{th}$  is needed to fill the channel with electrons and allow conduction, leading to a reduction in transconductance ( $g_m$ ).

## 2) Effect of BIAS points on Gain of common source Amplifier:

a)

Vbias=1.5 V

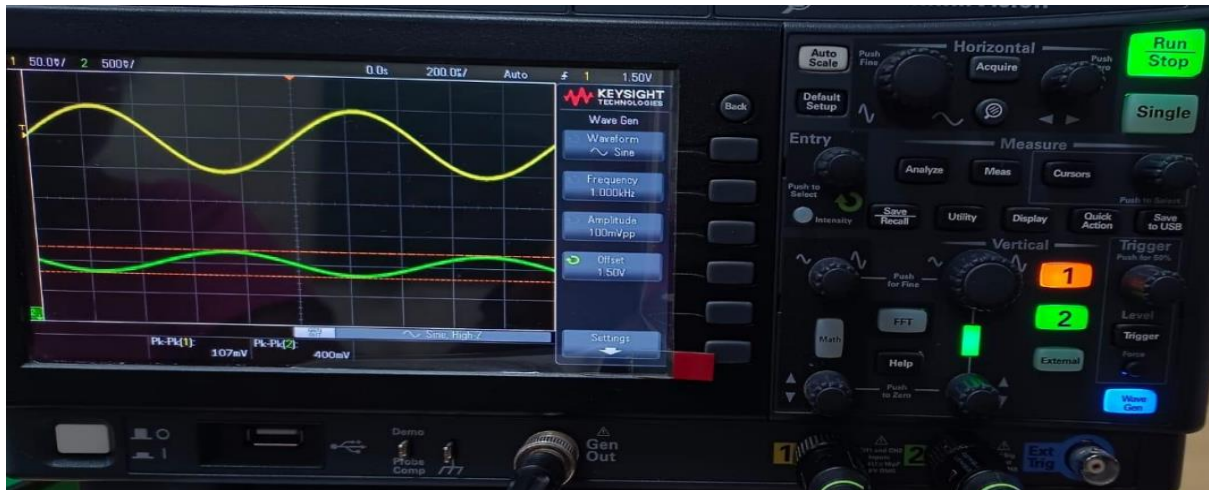


Vbias=1.8 V





Vbias=2.5 V

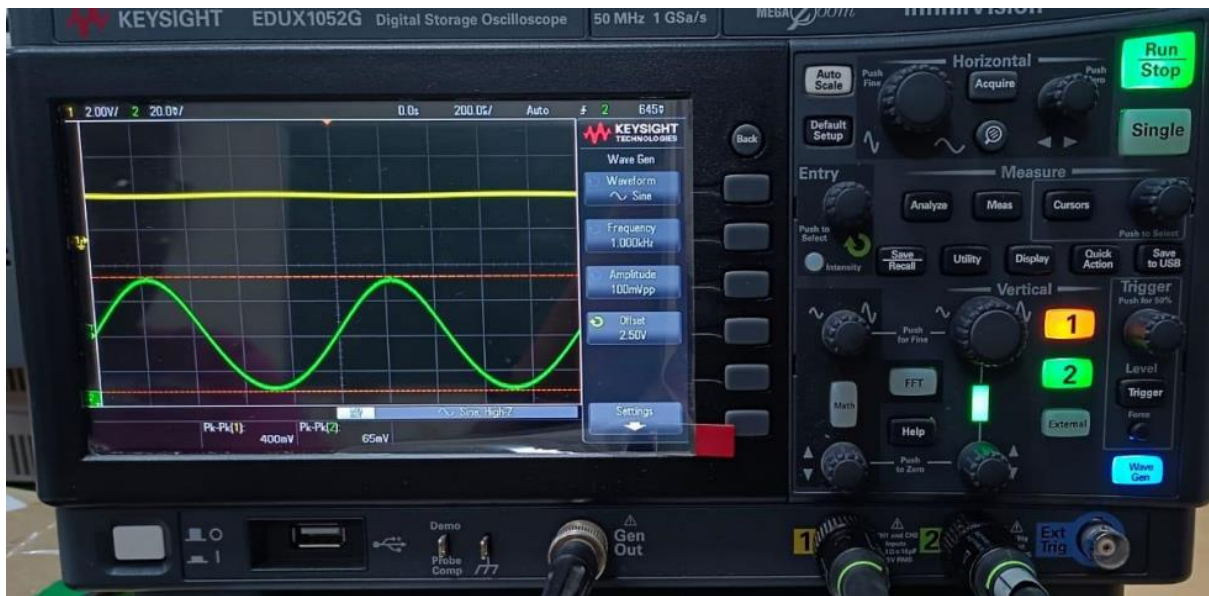

b)

When Vbias=1.8V .



At this point, the device is just turning on and is on the verge of entering the saturation mode. As a result, the drain current  $I_d$  is slightly greater than zero.

The measured value of the output voltage ( $V_{out}$ ) is 1mV. The gain of the amplifier is calculated as the ratio of  $V_{out}$  to the input voltage ( $V_{in}$ ), which is 1mV divided by 100mV, resulting in a gain of 0.01. And  $g_m = \text{gain} / R_D = 2.125 \mu A/V$

Vbias=2.5




The device is turned on, and the gate-to-source voltage  $V_{gs}$  exceeds the threshold voltage  $V_{th}$  (1.8V). As a result, the device enters the saturation mode.

$V_{out}=100\text{mV}$ ,  $\text{gain}=V_{out}/V_{in}=100/100=1 \Rightarrow$

$\text{gain}=1$  And  $g_m=\text{gain}/R_d=1/4.7\text{k}=0.212\text{mA/V} \Rightarrow g_m=0.212\text{mA/V}$

Vbias=3.1V

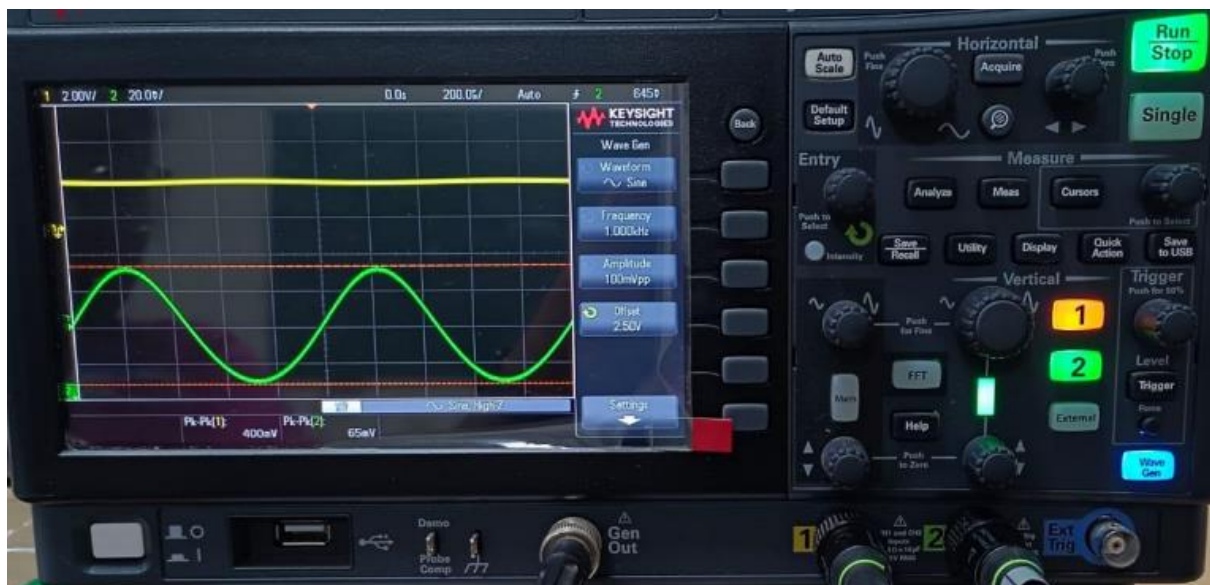

In the given scenario, the measured value of  $V_{ds}$  (drain-to-source voltage) is 3.92V. Since  $V_{ds}$  is greater than  $V_{bias}-V_{th}$ , the device remains in saturation mode, and no clipping of the output is observed.

$V_{out}=200\text{mV}$ ,  $\text{gain}=V_{out}/V_{in}=200\text{mV}/100\text{mV}=2 \Rightarrow \text{gain}=2,$

$$g_m = \text{gain}/R_d = 2/4.7 = 0.4255 \text{ mA/V} \Rightarrow g_m = 0.4255 \text{ mA/V}$$

$$V_{\text{bias}} = 4 \text{ V}$$




The measured value of  $V_{ds}$  (drain-to-source voltage) is 2.93V. Since  $V_{ds}$  is still greater than  $V_{gs} - V_{th}$ , the device continues to operate in saturation mode, and no clipping of the output signal is observed.

$$V_{out} = 300 \text{ mV}, \text{ gain} = V_{out}/V_{in} = 300 \text{ mV}/100 \text{ mV} = 3 \Rightarrow$$

$$\text{gain} = 3, g_m = \text{gain}/R_d = 3/4.7 \text{ k} = 0.6382 \text{ mA/V} \Rightarrow g_m = 0.6382 \text{ mA/V}$$

c)

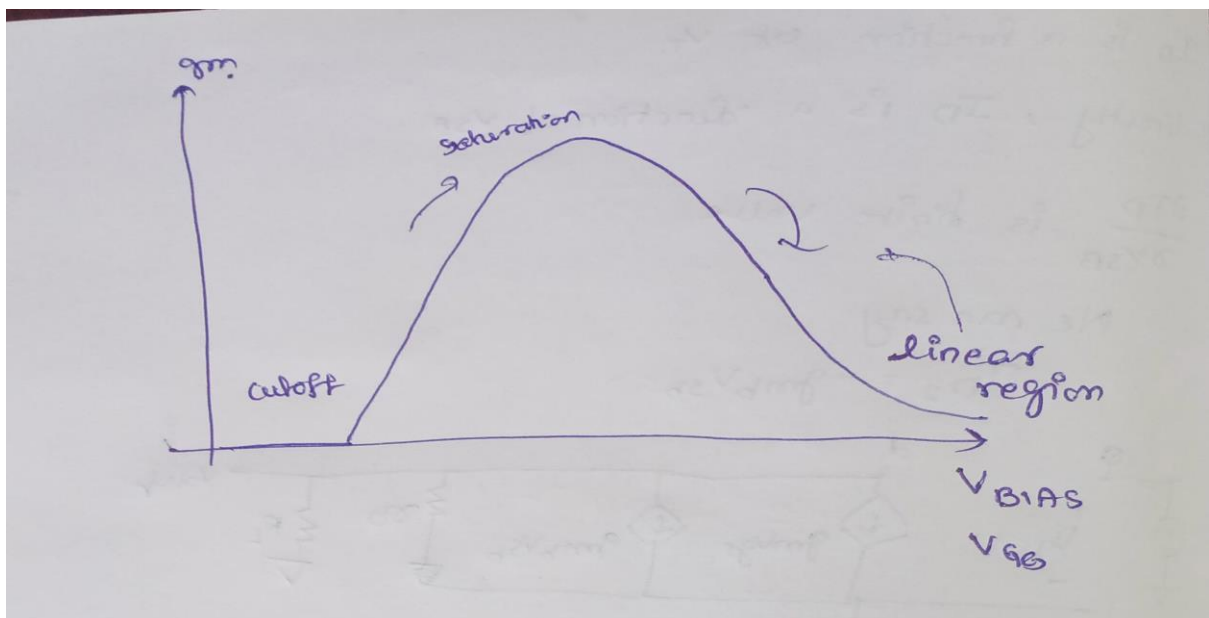



d)

Vbias(V)	Vout	Gain	gm
0.9	8mV	0.08	0.017
1.5	480mV	3.73	0.795m
1.8	480mV	4.40	0.936m
2.5	63mV	0.16	0.034m
3.1	15.7mV	0.03	0.0066
4	7.6mV	0.01	0.0026

Upto Vbias=2V MOSFET is in SATURATION MODE. After 2V the MOSFET goes to LINEAR/TRIODE MODE .



Till 2V the MOSFET acts as voltage dependent current source.







Due to linear region after 2V gain is decreasing because MOSFET acts as voltage dependent RESISTOR in TRIODE MODE.
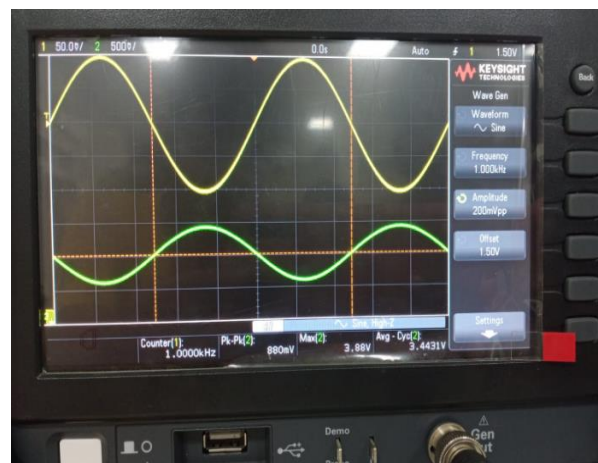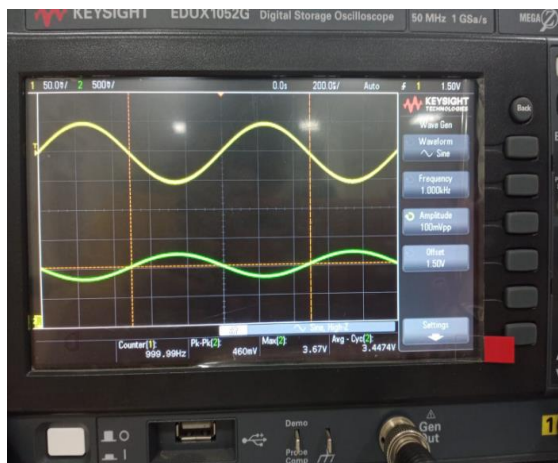
### **3) Effect of small signal input swing on gain of common source Amplifier :**

a)

CHANGING VALUES OF Vin for constant BIAS voltage:



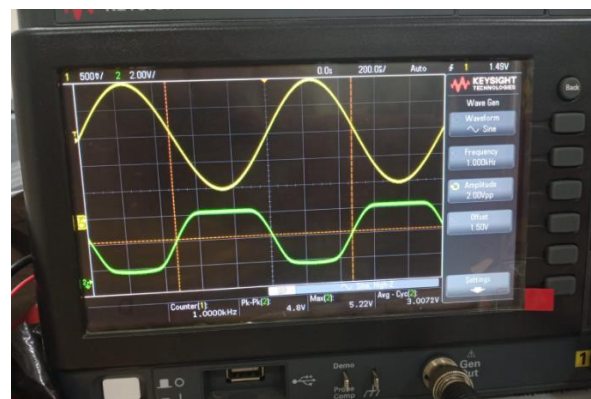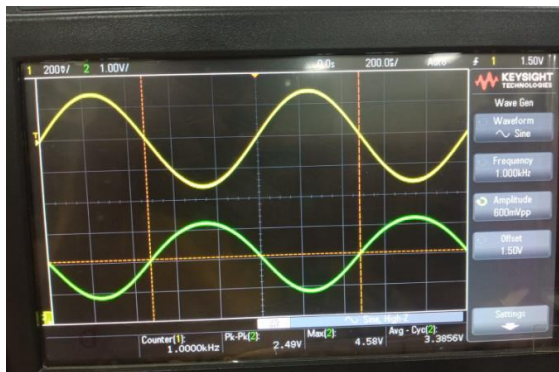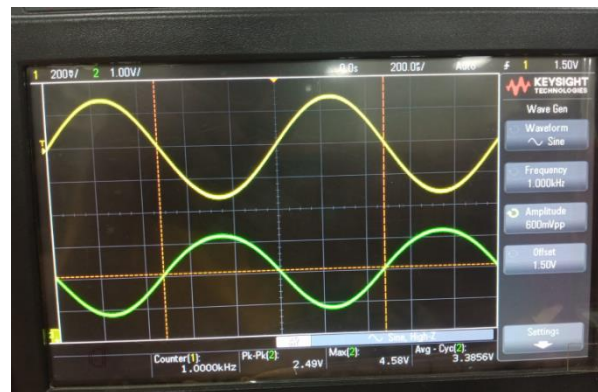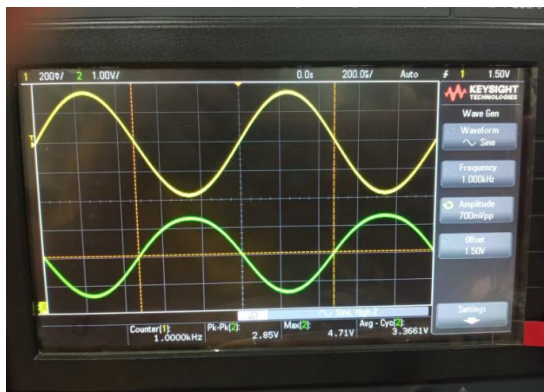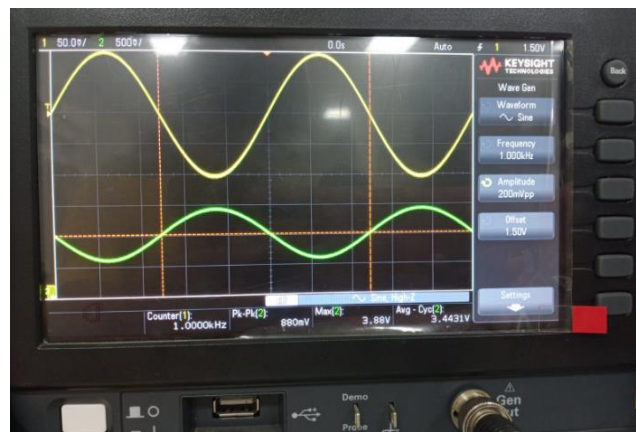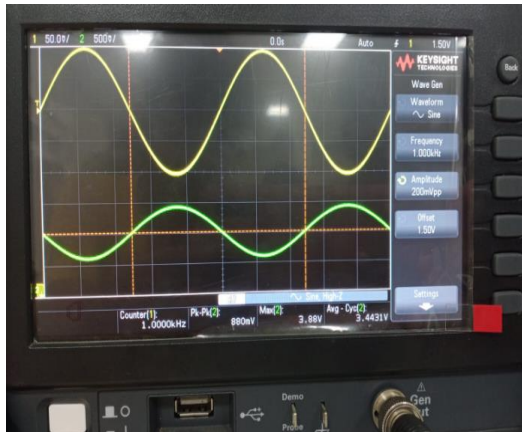

V(input)	V(output)	Gain	Gm
100mV	480mV	4.8	1.021m
200mV	900mV	4.5	0.958m
300mV	1.33V	4.43	0.945m
400mV	1.71 V	4.27	0.909m
500mV	2.17V	4.34	0,923m
600mV	2.57V	4.28	0.91m
700mV	2.6V	3.57	0.895m



900mV	3.14V	3.48	0.874m
1V	4V	4	0.85m
1.2V	4.4V	3.66	0.778m
1.3V	4.5V	3.46	0.73m
1.4V	4.6V	3.28	0.69m
1.5V	4.7V	3.14	0.66m


Clipping is observed in the output signal when the input voltage  $V_{in}$  exceeds a threshold between 1.2V and 1.3V. Beyond this threshold, the output signal exhibits distinct clipping, indicating that the device is entering the cutoff region and cannot fully amplify the input signal.

When observing the gain with respect to  $V_{gs}$  (gate-to-source voltage), it is noticed that the gain generally increases as  $V_{gs}$  increases when the device is operating in the saturation region. This implies that the overall gain of the amplifier increases in a consistent manner. However, it is important to note that linearity in the gain is maintained only when  $V_{gs}$  is greater than  $V_{th}$  (threshold voltage).

On the other hand, when  $V_{gs}$  is less than  $V_{th}$ , the gain continues to increase, but linearity is not preserved on the negative side of the output signal.

This is due to clipping, where the output signal is unable to fully amplify the input signal and gets truncated, resulting in distortion and a loss of linearity. While the gain increases steadily with increasing  $V_{gs}$  in the saturation region, linearity is only maintained up to  $V_{gs}$  exceeding  $V_{th}$ . For  $V_{gs}$  less than  $V_{th}$ , there is an increase in gain but with the presence of clipping, leading to a loss of linearity on the negative side of the output signal.

#### 4)CS Amplifier with external coupling:

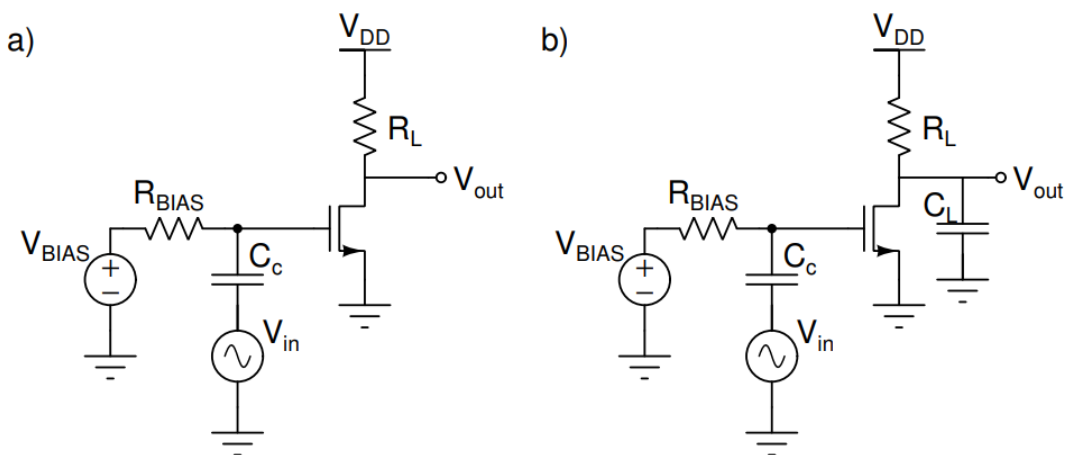

**Figure 2:** CS amplifier with external coupling capacitance and resistor

a)

In the circuit, an external coupling capacitance  $C_c$  of 10 $\mu$ F and a bias resistor  $R_{bias}$  of 100 ohms are connected.


The coupling capacitance  $C_c$  is used to block any DC component of the signal, allowing only the AC component to pass through. It helps to prevent any unwanted DC bias from affecting the subsequent stages of the circuit.

The bias resistor  $R_{bias}$  is employed to establish a DC bias point in the circuit. It ensures that the amplifier operates within the desired range and provides a stable operating point for the active components.

b)

$V_{in}(V_{pp})=100\text{mV}$ ,  $V_{bias}=2.5\text{V}$  and  $V_{DD}=5\text{V}$

MEASURED gain:

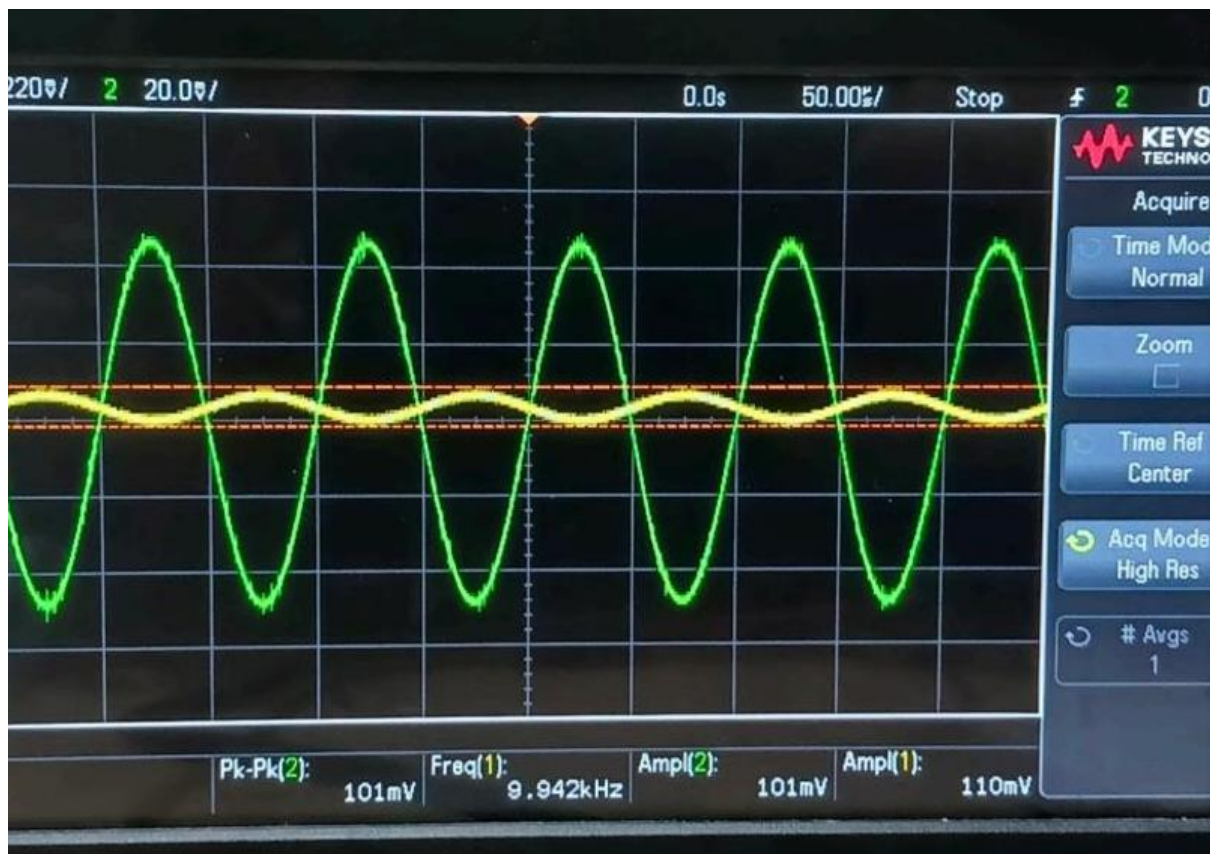

$$g_m = \text{gain}/R = 1.0891/4.7\text{k} = 0.2317\text{mA/V}$$

$$\text{Gain} = V_{out}/V_{in} = 110/101 = 1.089$$


In the current configuration with the addition of external coupling, there is only a slight increase in  $g_m$ . This can be attributed to the effect of the external coupling on the circuit.

By connecting the  $V_{bias}$  and small input signal separately, the small AC signal is prevented from passing towards the  $V_{bias}$  side branch due to the presence of the bias resistor  $R_{bias}$ . Additionally, the DC bias voltage  $V_{bias}$  is blocked from passing through the coupling capacitor  $C_c$ . As a result, a proper mixing of the DC and AC signals is achieved, which leads to a slight increase in transconductance ( $g_m$ ).

In summary, the introduction of external coupling in the circuit results in a small increase in  $g_m$ . This can be attributed to the isolation of the AC and DC components of the signal, allowing for a more accurate mixing of the signals and enhancing the transconductance.


c)

MEASURED VALUE OF  $V_{DS}$ :

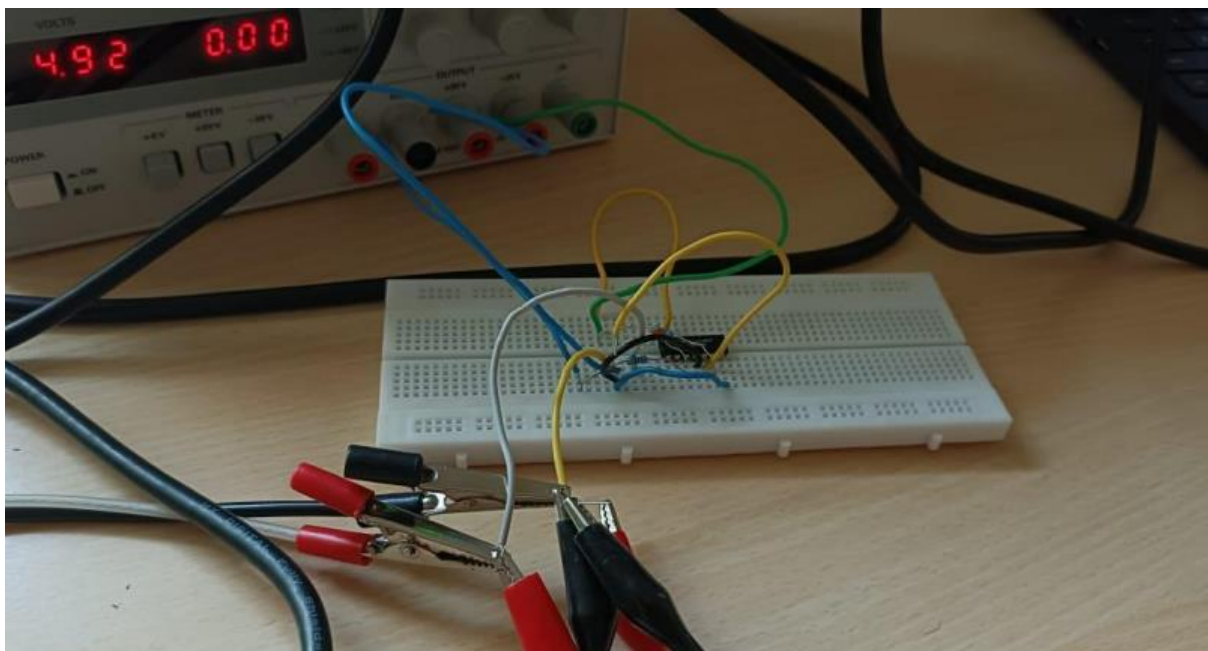

Measured  $V_{DS}$  = 4.42 which is close to previous observed value which was 4.4v.

d) LOAD CAPACITANCE  $C_L$  = 470pF

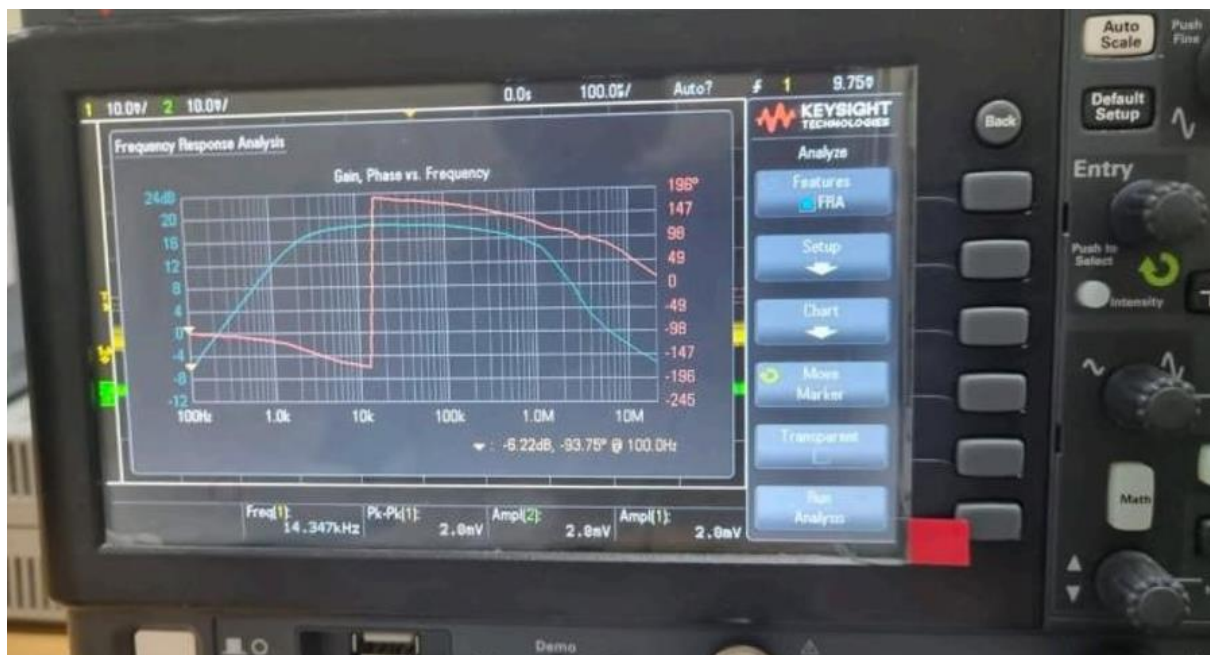

And -3db cut-off frequencies are  $F_1=588\text{Hz}$  and  $F_2=100\text{KHz}$



(C)  $V_{DS} = 4.42V$

$$I_{DS} = \frac{V_{DD} - V_{DS}}{R} = \frac{5 - 4.42}{4.7K} = 0.123 mA$$

$$I_{DS} = 0.123 mA$$


And  $g_m = 0.2382 mA/V$

$$\text{As } g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$


$$= 0.2382 = \mu_n C_{ox} \frac{W}{L} (2.5 - 1.8)$$

$$\therefore \mu_n C_{ox} \frac{W}{L} = 0.331 mA/V^2$$

\* Calculation of poles:

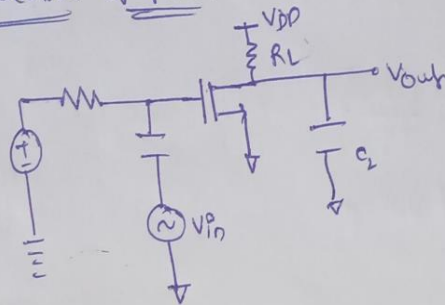


Small signal:

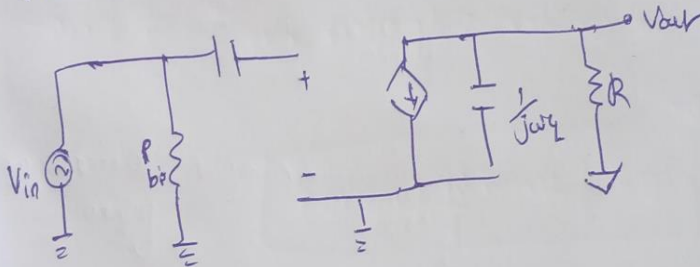



\* calculation of poles:

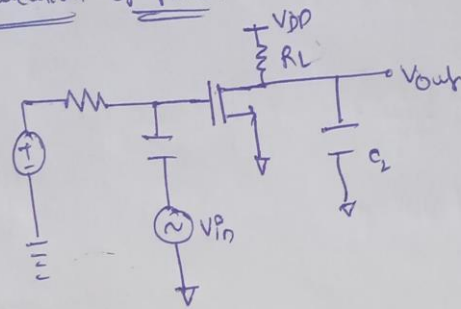

Small signal:

