


Lecture 1 – Introduction and Number systems

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 1 (first half)


Introductions

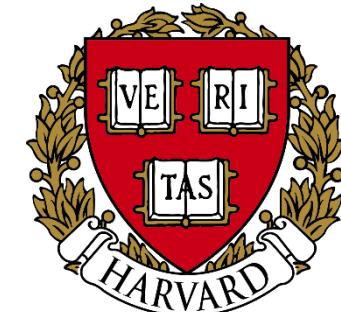- B. Tech in IIT Roorkee (2009):
- After B. Tech.:
 - Design Engineer, Analog Devices India (2011)
- Joined KAUST as M.S. in 2011
- Continued as Ph.D. from Jan 2013
- Postdoc in Harvard University up to Jan 2018
- Asst. Prof., CVEST, IIITH
- Total of 90+ research papers and 11 patents in the last 10 years



Courses

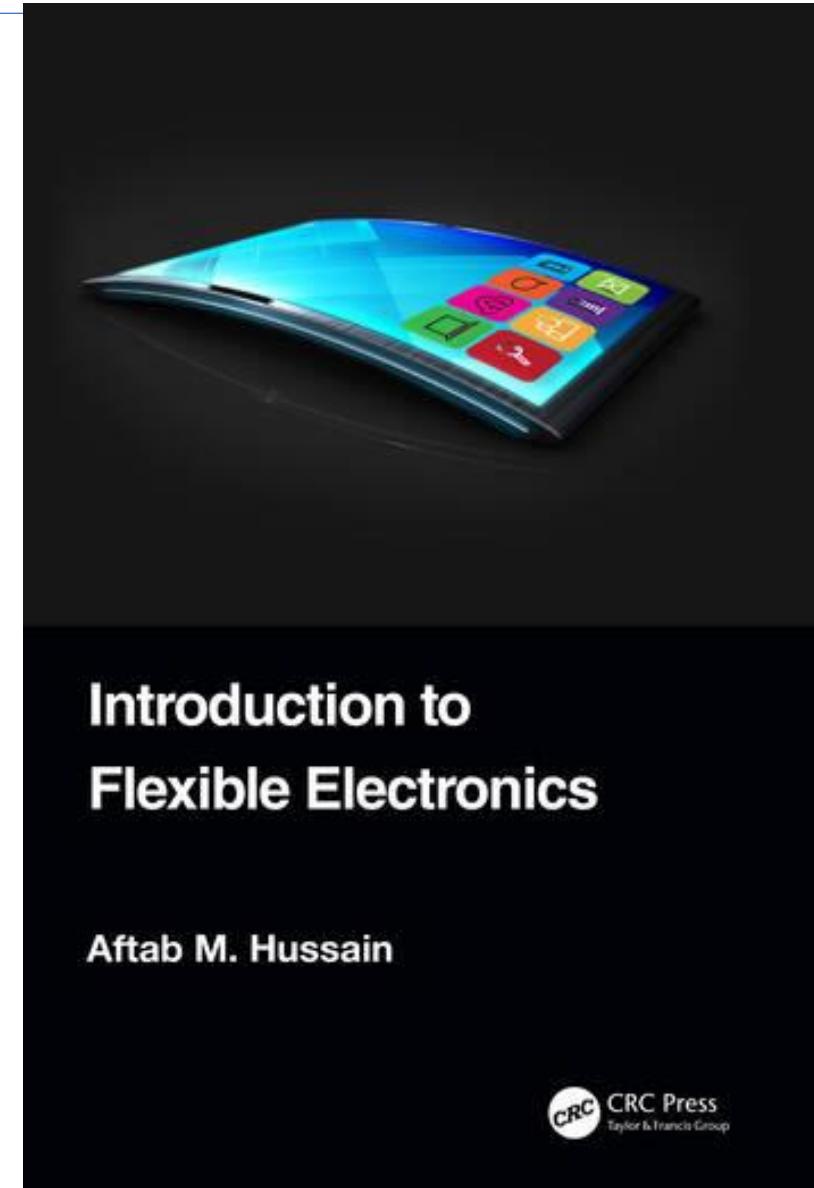- Digital Systems and Microcontrollers (DSM) [UG1 core]
 - Digital logic
 - Basic digital circuits
 - Basics of microcontrollers
- Embedded Systems Workshop [CS UG2 core]
- Communications and Controls in IoT [ECE UG2 elective]
- Flexible Electronics [Open Elective]
 - Materials for flexible electronics
 - Processes and applications



About the course


- Name: Digital Systems and Microcontrollers (DSM)
- Textbook:
 - M. Morris Mano and Michael D. Ciletti, “Digital Design”
- Logistics:
 - Three 1-hour lectures per week
 - One 3-hour lab per week
 - One 1-hour tut per week
- Faculty: Dr. Aftab M. Hussain (lectures B)
Dr. Ubaidulla P (lectures A)
Dr. Harikumar Kandath (labs)

About the course

Quizzes (x2)	10
Midsem	20
Lab reports (x9)	15
Lab exam	20
End semester	35
Total	100



About the course

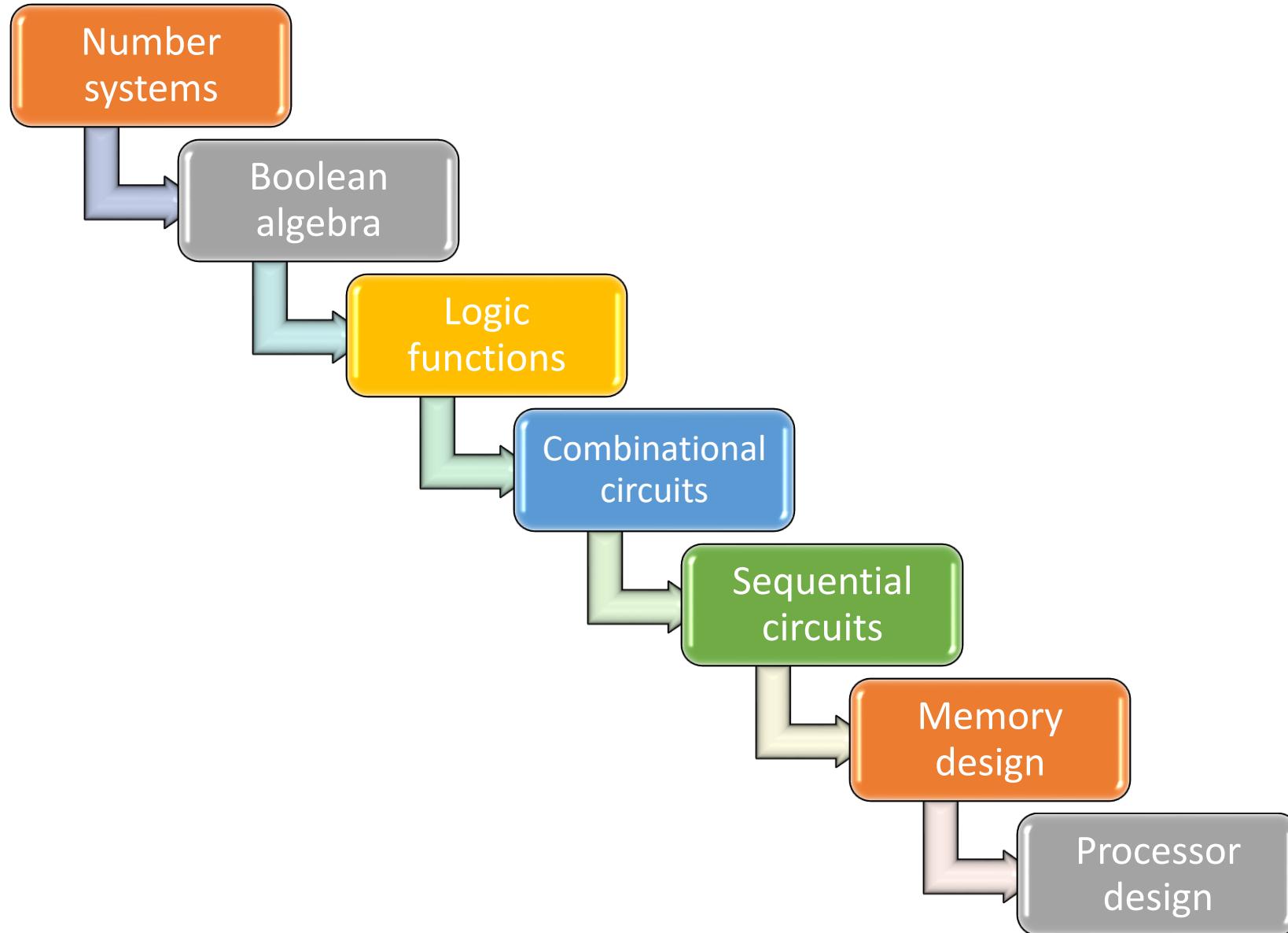

Here... We... Go...

Counting

- Lets learn counting...

0 1 2 3 4 5 6 7 8 9 **10**

- 1 四 2 三
7 3 = 5 9 七
五 八 6 六 4
八 8 九

Counting

- Lets learn counting...

0 1 2 3 4 5 6 7 8 9 **10**

- The place-value system:

- Put symbols in specific places/positions to denote their “power”
- The *base* or the *radix* of the decimal number system is 10

1 0 6 6

$10^3 \ 10^2 \ 10^1 \ 10^0$

1000 100 10 1

$$1 \times 1000 + 0 \times 100 + 6 \times 10 + 6 \times 1 = 1066$$

1 9 4 0

$10^3 \ 10^2 \ 10^1 \ 10^0$

1000 100 10 0

$$1 \times 1000 + 9 \times 100 + 4 \times 10 + 0 \times 1 = 1940$$

The “power” of the radix

- Many everyday things are because of the radices of the ancient past:
 - 24 hours in a day
 - 60 minutes in an hour
 - 60 seconds in a minute
 - 360° in a circle
- Things not dependent on the radix:
 - Days in a year
 - The value of pi (or other constants)

Various number systems

- Octal number system
 - The base or radix is 8
 - The symbols are: 0, 1, 2, 3, 4, 5, 6, 7
- Hexadecimal number system
 - The base or radix is 16
 - The symbols are: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F
- Binary number system
 - The base or radix is 2
 - The symbols are: 0, 1
- We denote the base of the number using a suffix subscript: $(10395)_{10}$
- In general a number $(a_4a_3a_2a_1a_0)_r = a_4r^4 + a_3r^3 + a_2r^2 + a_1r^1 + a_0r^0$

Conversions to decimal

- Octal number system
 - $(110)_8 = 1*8^2 + 1*8^1 + 0*8^0 = (72)_{10}$
 - $(777)_8 =$
- Hexadecimal number system
 - $(110)_{16} = 1*16^2 + 1*16^1 + 0*16^0 = (272)_{10}$
 - $(BAD)_{16} =$
- Binary number system
 - $(110)_2 = 1*2^2 + 1*2^1 + 0*2^0 = (6)_{10}$
 - $(101010)_2 =$

Conversions from decimal

- Algorithm:
 - Divide by radix
 - Save the remainder
 - Repeat
 - Arrange remainders in reverse order
- Octal number system
 - 912
 - 75
- Hexadecimal number system
 - 1729
 - 133
- Binary number system
 - 21
 - 10

Conversions from Oct/Hex to Binary

- From Oct/Hex to binary, we can take a short cut because the bases are $(2)^3$ and $(2)^4$ respectively
- For octal: take each digit and convert it individually into *three* bits
- For hex: take each digit and convert it individually into *four* bits
- Octal number system
 - $(433)_8$
 - $(70)_8$
- Hexadecimal number system
 - $(DEAD)_{16}$
 - $(FEED)_{16}$

Conversions from Binary to Oct/Hex

- The reverse course can be taken for converting binary to oct or hex
 - For octal: take *three* bits and convert it individually into a symbol
 - For hex: take *four* bits and convert it individually into a symbol
-
- Octal number system
 - $(110101011)_2$
 - $(1010111101)_2$
 - Hexadecimal number system
 - $(11101011)_2$
 - $(110000110)_2$
 - $(101011111)_2$

Lecture 2 – Binary numbers and representations

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 1 (second half)

Addition

- Octal number system
 - $(73)_8 + (157)_8$
 - $(57)_8 + (23)_8$
- Hexadecimal number system
 - $(AA)_{16} + (BB)_{16}$
 - $(BAD)_{16} + (DAD)_{16}$
- Binary number system
 - $(1101)_2 + (111)_2$
 - $(10101)_2 + (100)_2$

Subtraction

- Octal number system
 - $(172)_8 - (167)_8$
 - $(32)_8 - (21)_8$
- Hexadecimal number system
 - $(BB)_{16} - (AA)_{16}$
 - $(DAD)_{16} - (BAD)_{16}$
- Binary number system
 - $(1101)_2 - (111)_2$
 - $(10101)_2 - (100)_2$

Multiplication

- Binary number system

$$\begin{array}{r} 1010 \\ \times 1011 \\ \hline 1010 \\ 1010 \\ 0000 \\ 1010 \\ \hline 1101110 \end{array}$$

→ **Multiplicand**
→ **Multiplier**
→ **Partial product 1**
→ **Partial product 2**
→ **Partial product 3**
→ **Partial product 4**

- Examples:

- $(111)_2 * (110)_2$
- $(1011)_2 * (1010)_2$

The “decimal” point

- The powers of radix decrease after the decimal point

- Binary to decimal:


- $(1.011)_2 = 1*2^0+0*2^{-1}+1*2^{-2}+1*2^{-3}$
 $= 1+0.25+0.125$
 $= 1.375$

- $(0.1101)_2$

- Decimal to binary:

- $(0.75)_{10} = 0.75*2= 1.50$
 $0.5*2 = 1.00$
 $=(0.11)_2$

- $(0.625)_{10}$

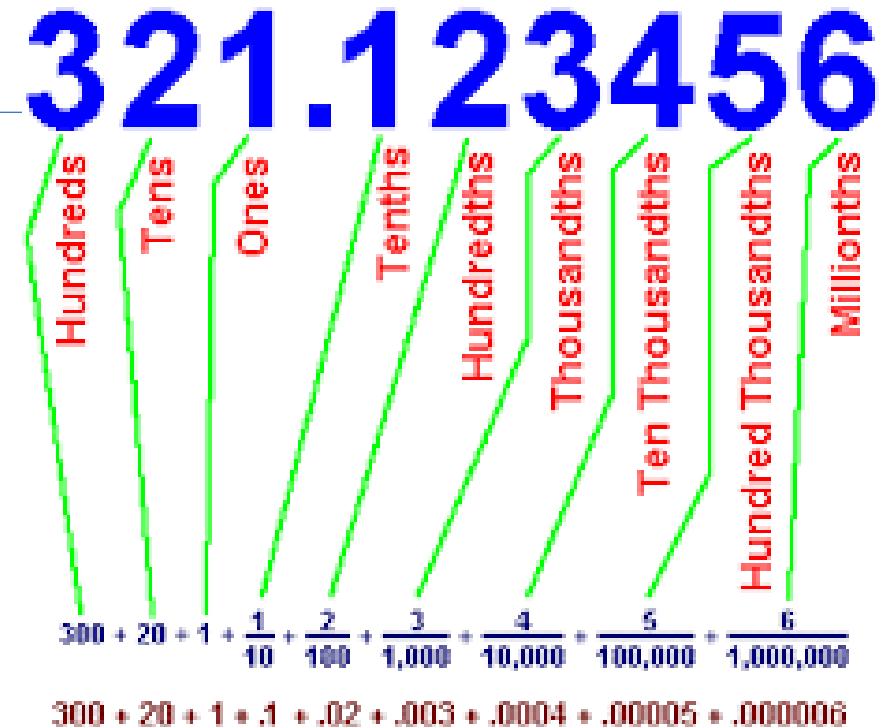

Complements of numbers

- Complement operations are run on a single number in any given base
- Complements are used in digital computers to simplify the subtraction operation and for logical manipulation
- Simplifying operations leads to simpler, less expensive circuits to implement the operations
- There are two types of complements for each base- r system:
 1. The radix complement [r 's complement] – called the 10's complement in decimal, 2's complement in binary and so on
 2. The diminished radix complement [$(r-1)$'s complement] – called the 9's complement in decimal, 1's complement in binary and so on

Diminished radix complement

- Given a number N in base r having n digits, the $(r - 1)$'s complement of N , i.e., its diminished radix complement, is defined as $(r^n - 1) - N$
- For decimal numbers, the 9's complement of N is $(10^n - 1) - N$
- In this case, $10^n - 1$ is a number represented by n 9s
- For example, if $n = 4$, we have $10^4 = 10,000$ and $10^4 - 1 = 9999$
- It follows that the 9's complement of a decimal number is obtained by subtracting each digit from 9
- Examples:
 - 1242
 - 9981

Diminished radix complement

- For binary numbers, the 1's complement of N is $(2^n - 1) - N$.
- Again, $(2^n - 1)$ is a binary number represented by n 1s
- For example, if $n = 4$, we have $2^4 = (1000)_2$ and $2^4 - 1 = (1111)_2$. Thus, the 1's complement of a binary number is obtained by subtracting each digit from 1
- However, when subtracting binary digits from 1, we can have either $1 - 0 = 1$ or $1 - 1 = 0$, which causes the bit to change from 0 to 1 or from 1 to 0, respectively
- Therefore, **the 1's complement of a binary number is formed by changing 1's to 0's and 0's to 1's.**
- Examples:
 - 11100101
 - 10000

Lecture 3 – Binary Subtraction

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 2

Radix complement

- The r 's complement of an n -digit number N in base r is defined as $r^n - N$ for $N \neq 0$ and as 0 for $N = 0$
- Comparing with the $(r - 1)$'s complement, we note that the r 's complement is obtained by adding 1 to the $(r - 1)$'s complement, since $r^n - N = [(r^n - 1) - N] + 1$
- Thus, the 10's complement of decimal 2389 is $7610 + 1 = 7611$ and is obtained by adding 1 to the 9's complement value
- The 2's complement of binary 101100 is $010011 + 1 = 010100$ and is obtained by adding 1 to the 1's-complement value
- Examples:
 - $(66772)_{10}$
 - $(10011)_2$

Some notes on Complements

- If the original number N contains a radix point, the point should be removed temporarily in order to form the r 's or $(r - 1)$'s complement
- The radix point is then restored to the complemented number in the same relative position
- Example: 9's complement and 10's complement of $(82.314)_{10}$
- It is also worth mentioning that **the complement of the complement restores the number to its original value**
- To see this relationship, note that the r 's complement of N is $r^n - N$, so that the complement of the complement is $r^n - (r^n - N) = N$ and is equal to the original number
- $(r-1)$'s complement of N is $r^n - 1 - N$, so that the complement of the complement is $(r^n - 1) - (r^n - 1 - N) = N$ and is equal to the original number

Subtraction with Radix complements

- The usual method of borrowing taught in elementary school for subtraction is less efficient when subtraction is implemented with digital hardware
- Lets assume we have to perform $M-N$ in base r
- Here is the algorithm using Radix complement:
 1. Take radix complement of N : $r^n - N$
 2. **Add** this to M : $r^n - N + M = r^n + (M - N) = r^n - (N - M)$
 3. If you get a carry in the $(n+1)$ th digit, then the result is positive, discard the carry and you are done
 4. If you **do not** get a carry in the $(n+1)^{\text{th}}$ digit, then the result is **negative**. Take the radix complement of the number to get the answer, then put a negative sign
- 10's complement subtraction:
 - $(9812)_{10} - (3142)_{10}$
 - $(1423)_{10} - (7336)_{10}$

Subtraction with Diminished radix complements

- The usual method of borrowing taught in elementary school for subtraction is less efficient when subtraction is implemented with digital hardware
- Lets assume we have to perform $M-N$ in base r
- Here is the algorithm using Diminished radix complement:
 1. Take diminished radix complement of N : $r^n - 1 - N$
 2. **Add** this to M : $r^n - 1 - N + M = r^n + (M - N - 1) = (r^n - 1) - (N - M)$
 3. If you get a carry in the $(n+1)^{\text{th}}$ digit, then the result is positive, ***add the carry to the result*** and you are done
 4. If you ***do not*** get a carry in the $(n+1)^{\text{th}}$ digit, then the result is **negative**. Take the diminished radix complement of the number to get the answer, then put a negative sign
- 9's complement subtraction:
 - $(6552)_{10} - (3145)_{10}$
 - $(2142)_{10} - (9667)_{10}$

Binary subtraction with complements

- Perform the following subtractions using 2's complement method:
 - $(110001)_2 - (010100)_2$
 - $(010110)_2 - (100)_2$
 - $(10)_2 - (100000)_2$
 - $(100001)_2 - (110100)_2$
- Perform the following subtractions using 1's complement method:
 - $(110001)_2 - (010100)_2$
 - $(100100)_2 - (011101)_2$
 - $(1)_2 - (10100)_2$
 - $(11010)_2 - (110111)_2$

Subtraction using complements

Radix Subtraction

- Find Radix Complement of Y
- Add Y complement to X

Extra Leading Digit

- Drop extra digit

No Extra Digit

- Take Radix Complement
- Attach Negative

Reduced Radix Subtraction

- Find Reduced Radix Complement of Y
- Add Y complement to X

Extra Leading Digit

- Drop extra digit
- Add extra digit to result

No Extra Digit

- Take Reduced Radix Complement
- Attach Negative

Representing negative binary

- In ordinary arithmetic, a negative number is indicated by a minus sign and a positive number by a plus sign
- Because of hardware limitations, computers must represent everything with binary digits
- It is customary to represent the sign with a bit placed in the leftmost position of the number
- The convention is to make the sign bit 0 for positive and 1 for negative
- This can be done using:
 1. Signed magnitude representation
 2. Signed complement representation
 1. Signed 1's complement representation
 2. Signed 2's complement representation

Lecture 4 – Binary representation

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 2

Signed magnitude representation

- In this notation, the number consists of a magnitude and a symbol (+ or -) or a bit (0 or 1) indicating the sign
- This is similar to the representation of signed numbers used in ordinary arithmetic
- For example, the string of bits 01001 represents +9, and 11001 represents -9 in signed magnitude representation
- In signed-magnitude, -9 is obtained from +9 by changing only the sign bit in the leftmost position from 0 to 1
- Weird: +0 is represented as 0000 and minus 0 is represented as 1000. So, two representations for zero – inefficient and may cause errors

Signed complement representation

- When arithmetic operations are implemented in a computer, it is more convenient to use a different system, referred to as the *signed complement* system, for representing negative numbers
- In this system, a negative number is indicated by its complement
- Whereas the signed-magnitude system negates a number by changing its sign, the signed-complement system negates a number by taking its complement
- Since positive numbers always start with 0 (plus) in the leftmost position (in all representations), it follows that the complement will always start with a 1, indicating a negative number
- In signed-1's-complement, -9 is obtained by taking the 1's complement of all the bits of +9, including the sign bit
- The signed-2's-complement representation of -9 is obtained by taking the 2's complement of the positive number, including the sign bit

Reading and Writing signed complements

- Write into memory the following numbers in signed 2's complement representation in 4 bits:
 - +3
 - -7
 - 0
- We read these numbers from memory knowing its in signed 2's complement representation in 4 bits:
 - $(1100)_2$
 - $(1111)_2$
 - $(0000)_2$
 - $(1000)_2$

Interpretations for 4 bit binary numbers

Decimal	Signed-2's Complement	Signed-1's Complement	Signed Magnitude
+7	0111	0111	0111
+6	0110	0110	0110
+5	0101	0101	0101
+4	0100	0100	0100
+3	0011	0011	0011
+2	0010	0010	0010
+1	0001	0001	0001
+0	0000	0000	0000
-0	—	1111	1000
-1	1111	1110	1001
-2	1110	1101	1010
-3	1101	1100	1011
-4	1100	1011	1100
-5	1011	1010	1101
-6	1010	1001	1110
-7	1001	1000	1111
-8	1000	—	—

Signed addition

- Here is some magic: if the numbers are represented in memory in 2's complement form, we just need to add the two numbers, the sign takes care of itself!
- Bigger magic: the result is also in 2's complement representation
- The sign bit is to be included in the addition and if there is a carry, it is discarded
- Examples in 4-bit signed 2's complement representation:
 1. $3+1$
 2. $1+(-7)$
 3. $(-8)+5$
 4. $7+(-3)$
- In order to obtain a correct answer, we must ensure that the result has a sufficient number of bits to accommodate the sum
- If we start with two n -bit numbers and the sum occupies $n + 1$ bits, we say that an overflow occurs

Signed subtraction

- Subtraction of two signed binary numbers when negative numbers are in 2's-complement form is simple and can be stated as follows:
 - Take the 2's complement of the subtrahend (including the sign bit) and add it to the minuend (including the sign bit)
 - A carry out is discarded, if any
- This works because: $M - N = M + (-N)$
- Examples in 4-bit signed 2's complement representation:
 1. 3-5
 2. 6-2
 3. 1-7

Lecture 5 – Binary Codes

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST

Chapter 2

Binary codes

- Any discrete element of information that is distinct among a group of quantities can be represented with a binary code (i.e., a pattern of 0's and 1's)
- The codes must be in binary because, in today's technology, only circuits that represent and manipulate patterns of 0's and 1's can be manufactured economically for use in computers
- However, it must be realized that binary codes merely change the symbols, not the meaning of the elements of information that they represent
- If we inspect the bits of a computer at random, we will find that most of the time they represent some type of coded information rather than binary numbers
- An n -bit binary code can represent up to 2^n distinct elements of the set that is being coded

Binary Coded Decimal (BCD)

- The code most commonly used for the decimal digits is the straight binary assignment and is called *binary-coded decimal* (BCD)
- A binary code will have some unassigned bit combinations if the number of elements in the set is not a multiple power of 2
- The 10 decimal digits form such a set
- A binary code that distinguishes among 10 elements must contain at least four bits, but 6 out of the 16 possible combinations remain unassigned

Binary-Coded Decimal (BCD)

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Binary Coded Decimal (BCD)

- A number with k decimal digits will require $4k$ bits in BCD
- Decimal 396 is represented in BCD with 12 bits as 0011 1001 0110, with **each group of 4 bits representing one decimal digit**
- A BCD number greater than 10 looks different from its equivalent binary number, even though both contain 1's and 0's
- Moreover, **the binary combinations 1010 through 1111 are not used and have no meaning in BCD**

Binary-Coded Decimal (BCD)

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

ASCII code

- Many applications of digital computers require the handling not only of numbers, but also of other characters or symbols, such as the letters of the alphabet
- The standard binary code for the alphanumeric characters is the American Standard Code for Information Interchange (ASCII), which uses seven bits to code 128 characters
- The seven bits of the code are designated by b_1 through b_7 , with b_7 the most significant bit
- The letter A, for example, is represented in ASCII as 1000001
- The ASCII code also contains 94 graphic characters that can be printed and 34 nonprinting characters used for various control functions
- The graphic characters consist of the 26 uppercase letters (A through Z), the 26 lowercase letters (a through z), the 10 numerals (0 through 9), and 32 special printable characters, such as %, *, and \$

ASCII code

$b_4b_3b_2b_1$	$b_7b_6b_5$								
	000	001	010	011	100	101	110	111	
0000	NUL	DLE	SP	0	@	P	`	p	
0001	SOH	DC1	!	1	A	Q	a	q	
0010	STX	DC2	"	2	B	R	b	r	
0011	ETX	DC3	#	3	C	S	c	s	
0100	EOT	DC4	\$	4	D	T	d	t	
0101	ENQ	NAK	%	5	E	U	e	u	
0110	ACK	SYN	&	6	F	V	f	v	
0111	BEL	ETB	'	7	G	W	g	w	
1000	BS	CAN	(8	H	X	h	x	
1001	HT	EM)	9	I	Y	i	y	
1010	LF	SUB	*	:	J	Z	j	z	
1011	VT	ESC	+	;	K	[k	{	
1100	FF	FS	,	<	L	\	l		
1101	CR	GS	-	=	M]	m	}	
1110	SO	RS	.	>	N	^	n	~	
1111	SI	US	/	?	O	-	o	DEL	

Representing fractions (real numbers)

- We need to operate with fractions all the time
- This means we need a method to store/represent them in binary
- The simplest way is to have a “fixed” point representation where the binary point is assumed to be fixed at a certain location
- For example, for an 4-bit system, if given fixed-point representation is II.FF, then you can store minimum value is 00.01 (0001) and maximum value is 11.11 (1111)
- Remember the point is not actually stored – it is assumed to be there
- There are three parts of a fixed-point number representation: the sign field, integer field, and fractional field – which means we can also have signed magnitude fixed point numbers and signed complement fixed point numbers

Fixed point representation

- The advantage of using a fixed-point representation is performance and ease of arithmetic
- The disadvantage is relatively limited range of values that they can represent
- So, it is usually inadequate for numerical analysis as it does not allow enough numbers and accuracy
- For instance, using 32-bit format: the 1 bit sign bit, 15 bits for integer, and 16 bits for the fractional part, the smallest positive number is $2^{-16} \approx 0.000015$, and the largest positive number is ≈ 32768

Smallest	0	0000000000000000	0000000000000001
	Sign bit	Integer part	Fractional part
Largest	0	1111111111111111	1111111111111111
	Sign bit	Integer part	Fractional part

Floating point representation

- This representation does not reserve a specific number of bits for the integer part or the fractional part
- Instead it reserves a certain number of bits for the number (called the mantissa) and a certain number of bits to say where within that number the decimal place sits (called the exponent)
- We convert the number to be stored as $N = M * r^e$ and store M and e as binary
- Clearly, a large mantissa and small exponent can give both high precision and high range
- The exponent field needs to represent both positive and negative exponents. To do this, a *bias* is added to the actual exponent in order to get the stored exponent
- For instance, using 32-bit format: the 1 bit sign bit, 8 bits for signed exponent, and 23 bits for the fractional part. Smallest is 1.18×10^{-38} and the largest is 3.40×10^{38}

Read more [here](#)

(IEEE Standard 754 Floating point)

1	00000101	10101100000000000000000000000000
Sign bit	Exponent part	Mantissa part

$$-53.5 = (-110101.1)_2 = (-1.101011) \times 2^5$$

Floating Point Components			
	Sign	Exponent	Fraction
Single Precision	1 [31]	8 [30–23]	23 [22–00]
Double Precision	1 [63]	11 [62–52]	52 [51–00]

Laid out as bits, floating point numbers look like this:

Single: SEEEEEEE EFFFFFFF FFFFFFFF FFFFFFFF

Double: SEEEEEEE EEEEEEFF FFFFFFFF FFFFFFFF FFFFFFFF FFFFFFFF FFFFFFFF FFFFFFFF FFFFFFFF

	Denormalized	Normalized	Approximate Decimal
Single Precision	$\pm 2^{-149} \text{ to } (1-2^{-23}) \times 2^{-126}$	$\pm 2^{-126} \text{ to } (2-2^{-23}) \times 2^{127}$	$\pm \approx 10^{-44.85} \text{ to } \approx 10^{38.53}$
Double Precision	$\pm 2^{-1074} \text{ to } (1-2^{-52}) \times 2^{-1022}$	$\pm 2^{-1022} \text{ to } (2-2^{-52}) \times 2^{1023}$	$\pm \approx 10^{-323.3} \text{ to } \approx 10^{308.3}$

Lecture 6 – Boolean algebra

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST


Chapter 2

Binary logic

- Binary logic deals with variables that take on two discrete values and with operations that assume logical meaning
- The two values the variables assume may be called by different names (*true* and *false*, *yes* and *no*, etc.), but for our purpose, it is convenient to think in terms of bits and assign the values 1 and 0
- Binary logic consists of binary variables and a set of logical operations
- The variables are designated by letters of the alphabet, such as A , B , C , x , y , z , etc., with each variable having two and only two distinct possible values: 1 and 0

Boolean algebra

- The system for formalization of binary logic came much before their applications in electronics/computers
- Boolean algebra was introduced by George Boole in his first book *The Mathematical Analysis of Logic* (1847)
- In the 1930s, while studying switching circuits, Claude Shannon observed that one could also apply the rules of Boole's algebra in this setting, and he introduced switching algebra as a way to analyze and design circuits by algebraic means in terms of logic gates.

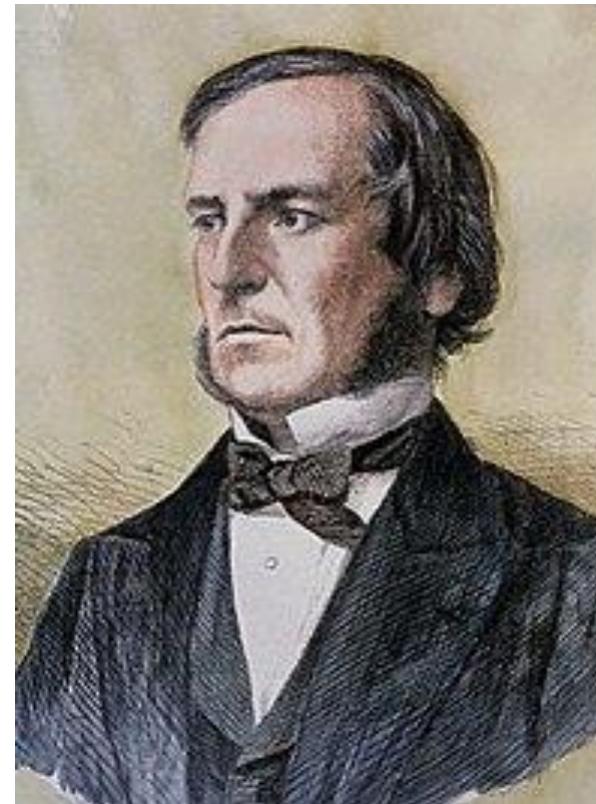

George Boole



Claude Shannon

Basic operations

- **NOT:** This operation is represented by a prime (sometimes by an overbar). For example, $x' = z$ (or $\bar{x} = z$); meaning that z is what x is not
- In other words, if $x = 1$, then $z = 0$, but if $x = 0$, then $z = 1$
- The NOT operation is also referred to as the complement operation, since it changes a 1 to 0 and a 0 to 1, i.e., the result of complementing 1 is 0, and vice versa
- **AND:** This operation is represented by a dot or by the absence of an operator
- For example, $x \cdot y = z$ or $xy = z$
- The logical operation AND is interpreted to mean that $z = 1$ if and only if $x = 1$ and $y = 1$; otherwise $z = 0$
- **OR:** This operation is represented by a plus sign. For example, $x + y = z$, meaning that $z = 1$ if $x = 1$ or if $y = 1$ or if both $x = 1$ and $y = 1$. If both $x = 0$ and $y = 0$, then $z = 0$

Basic operations

- An easy way to remember this is to make a table of all possible values of the variables and the results of these operations

AND		
x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT		
x	x'	
0	1	
1	0	

Binary logic

- Binary logic is different from binary numbers although it uses some of the same symbols
- In binary logic, we assume that variables can have ONLY two values – no other values are possible
- In binary numbers variables can have higher values or fraction or negative values, however, that is not the case in binary logic
- For example: in binary numbers, $(1+1 = 10)_2$, however, in binary logic, $1+1 = 1$ because two trues make a true
- There are formal rules and proofs for many of the statements we make in binary logic
- In modern circuits, logic gates are used to perform binary logic using a variety of complex architectures

Formalization of Boolean algebra

- Boolean algebra, like any other deductive mathematical system, may be defined with a set of elements, a set of operators, and a number of unproved axioms or postulates
- A *operator* defined on a set S of elements is a rule that assigns, to each pair of elements from S , a unique element from S
- As an example, consider the relation $a * b = c$. We say that $*$ is an operator if it specifies a rule for finding c from the pair (a, b) and also if $a, b, c \in S$

Postulates of Boolean algebra – Closure

- A set S is closed with respect to an operator if, for every pair of elements of S , the operator specifies a rule for obtaining an element of S
- For example, the set of natural numbers $N = \{1, 2, 3, 4, c\}$ is closed with respect to the operator $+$ by the rules of arithmetic addition, since, for any $a, b \in N$, there is a unique $c \in N$ such that $a + b = c$
- The set of natural numbers is *not* closed with respect to the operator $-$ by the rules of arithmetic subtraction, because $2 - 3 = -1$ and $2, 3 \in N$, but $(-1) \notin N$
- The Boolean logic structure is closed with respect to NOT, AND and OR logic operations

Postulates of Boolean algebra – Associative law

- The operator * on a set S is said to be associative whenever $(x * y) * z = x * (y * z)$ for all $x, y, z, \in S$
- In case of real numbers, the multiplication and addition operations are associative while subtraction and division are not
- Similarly in binary logic, the operators AND and OR are associative
- Thus, x AND $(y$ AND $z)$ is the same as $(x$ AND $y)$ AND z
- Also, x OR $(y$ OR $z)$ is the same as $(x$ OR $y)$ OR z

Postulates of Boolean algebra – Commutative law

- The operator * on a set S is said to be commutative whenever $x * y = y * x$ for all $x, y \in S$
- In case of real numbers, the multiplication and addition operations are commutative, while subtraction and division are not
- Similarly in binary logic, the operators AND and OR are commutative
- Thus, x AND y is the same as y AND x
- Also, x OR y is the same as y OR x

Postulates of Boolean algebra – Identity

- A set S is said to have an identity element with respect to an operation $*$ on S if there exists an element $e \in S$ with the property that $e * x = x * e = x$ for every $x \in S$
- *Example:* The element 0 is an identity element with respect to the operator $+$ on the set of integers $I = \{\dots, -3, -2, -1, 0, 1, 2, 3, \dots\}$, since $x + 0 = 0 + x = x$ for any $x \in I$
- The set of natural numbers, N , has no identity element, since 0 is excluded from the set
- In Boolean logic, 0 is the identity element for OR operation and 1 is the identity element for AND operation

Postulates of Boolean algebra – Distributive

- If $*$ and $\#$ are two operators on a set S , $*$ is said to be distributive over $\#$ whenever $x * (y \# z) = (x * y) \# (x * z)$
- In normal algebra, multiplication is distributive over addition: $x(y+z) = xy + xz$
- In Boolean logic, The operator AND (\cdot) is distributive over OR ($+$); that is, $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
- Also, the operator OR ($+$) is distributive over AND (\cdot); that is, $x + (y \cdot z) = (x + y) \cdot (x + z)$
- This is counter intuitive!
- An easy way to prove the distributive law is to make a table of all possible values of the variables and their results

Postulates of Boolean algebra – Distributive

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

x	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Lecture 7 – Binary Logic

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST

Chapter 2

Postulates of Boolean algebra – Duality principle

- The *duality principle* states that every algebraic expression deducible from the postulates of Boolean algebra remains valid if the operators and identity elements are interchanged, i.e., AND is changed to OR and vice versa
- In a two-valued Boolean algebra, the identity elements and the elements of the set S are the same: 1 and 0
- Thus, if the *dual* of an algebraic expression is desired, we simply interchange OR and AND operators and replace 1's by 0's and 0's by 1's



(a) $x + 0 = x$

(b) $x \cdot 1 = x$

(a) $x + x' = 1$

(b) $x \cdot x' = 0$

(a) $x + x = x$

(b) $x \cdot x = x$

(a) $x + 1 = 1$

(b) $x \cdot 0 = 0$

Theorems of Boolean algebra

- Theorem: $x + x = x$

$$\begin{aligned}x + x &= (x + x) \cdot 1 \\&= (x + x) \cdot (x + x') \\&= x + x \cdot x' \\&= x + 0 \\&= x\end{aligned}$$

- Its dual: $x \cdot x = x$

Theorems of Boolean algebra

- Theorem: $x + 1 = 1$

$$\begin{aligned}x + 1 &= 1 \cdot (x + 1) \\&= (x + x') \cdot (x + 1) \\&= x + x' \cdot 1 \\&= x + x' \\&= 1\end{aligned}$$

- Its dual: $x \cdot 0 = 0$

Theorems of Boolean algebra

- Theorem: $x + xy = x$ (absorption theorem)

$$\begin{aligned}x + xy &= x \cdot 1 + xy \\&= x \cdot (1 + y) \\&= x \cdot 1 \\&= x\end{aligned}$$

- Its dual: $x \cdot (x + y) = x$

Theorems of Boolean algebra

- Theorem: $(x + y)' = x' \cdot y'$ (first DeMorgan's theorem)
- A simple way to prove the theorem is to prove that $(x+y)$ and $x'y'$ are complements of each other so that $(x+y)'$ is the same as $x'y'$
- So, we need to prove that $(x + y) + x'y' = 1$ and $(x + y) \cdot x'y' = 0$. If they are both true, then $(x + y)' = x'y'$

$$\begin{aligned}(x + y) + x'y' &= x + y + x'y' \\&= x + (y + x')(y + y') \\&= x + (y + x') \cdot 1 \\&= x + y + x' \\&= y + (x + x') \\&= y + 1 \\&= 1\end{aligned}$$

Theorems of Boolean algebra

- Theorem: $(x + y)' = x' \cdot y'$ (first DeMorgan's theorem)
- A simple way to prove the theorem is to prove that $(x+y)$ and $x'y'$ are complements of each other so that $(x+y)'$ is the same as $x'y'$
- So, we need to prove that $(x + y) + x'y' = 1$ and $(x + y) \cdot x'y' = 0$. If they are both true, then $(x + y)' = x'y'$

$$\begin{aligned}(x + y) \cdot x'y' &= x \cdot x' \cdot y' + y \cdot x' \cdot y' \\&= (x \cdot x') \cdot y' + x' \cdot (y \cdot y') \\&= 0 \cdot y' + x' \cdot 0 \\&= 0 + 0 \\&= 0\end{aligned}$$

- Because both are true together, the theorem is proved

Operator precedence

- The operator precedence for evaluating Boolean expressions is (1) parentheses, (2) NOT, (3) AND, and (4) OR. This is similar to BODMAS
- In other words, expressions inside parentheses must be evaluated before all other operations
- The next operation that holds precedence is the complement, and then follows the AND and, finally, the OR
- As an example, consider one of DeMorgan's theorems
- The left side of the expression is $(x + y)'$. Therefore, the expression inside the parentheses is evaluated first and the result then complemented
- The right side of the expression is $x'y'$, so the complement of x and the complement of y are both evaluated first and the result is then ANDed

Boolean functions

- In normal algebra, we define functions on real number variables using addition, subtraction, exponents, etc.
- A Boolean function described by a Boolean expression consists of binary variables, the constants 0 and 1, and the logic operation symbols
- For a given value of the binary variables, the function can be equal to either 1 or 0 (closure on the Boolean set)
- As an example, consider the Boolean function: $F = x + y \cdot z$
- A Boolean function expresses the logical relationship between binary variables and is evaluated by determining the binary value of the expression for all possible values of the variable (truth table of the function)

Boolean functions

- A Boolean function can be represented in a truth table
- The number of rows in the truth table is 2^n , where n is the number of variables in the function
- An easy way for obtaining binary combinations for the truth table are by counting the binary numbers from 0 through $(2^n - 1)$
- For example, there are eight possible binary combinations for assigning bits to the three variables x , y , and z

Boolean functions

- There is only one way that a Boolean function can be represented in a truth table
- However, when the function is in algebraic form, it can be expressed in a variety of ways, all of which have equivalent logic
- Here is a key fact that motivates our use of Boolean algebra: By manipulating a Boolean expression according to the rules of Boolean algebra, it is sometimes possible to obtain a simpler expression for the same logic function, and thus reduce the complexity of the circuit representing that logic
- Consider, for example, the following Boolean functions:

$$F_1 = x'yz + xy'z + xyz$$

$$F_2 = x'yz + yz$$

- Can we simplify these?

Boolean functions

- A simplified function also has a simplified circuit implementation
- Therefore, the two circuits have the same outputs for all possible binary combinations of inputs (truth table)
- Thus, each circuit implements the same identical function, but the one with fewer components is preferable
- In general, there are many equivalent circuit representations of a logic function
- Finding the most economic representation of the logic is an important design task

Boolean functions

- The manipulation of Boolean algebra consists mostly of reducing an expression for the purpose of obtaining a simpler circuit
- Functions of up to five variables can be simplified by the map method which will be discussed later
- For complex Boolean functions and many different outputs, designers of digital circuits use computer minimization programs that are capable of producing optimal circuits
- The manual method available is a procedure employing the basic relations and other manipulation techniques that become familiar with use, but remain relatively less in use
- Example: Simplify $F = xy + x'z + yz$ (consensus theorem)

Lecture 8 – Boolean functions

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Complement of a function

- The complement of a function F is F' and is obtained from an interchange of 0's for 1's and 1's for 0's in the value of F (truth table method)
- The complement of a function may be derived algebraically through DeMorgan's theorems
- Example: $F = x + y'z$ what is F' ?
- But what if the function has more terms?
- DeMorgan's theorems can be extended to three or more variables
- The three-variable form of the first DeMorgan's theorem:
$$(x + y + z)' = x'y'z'$$
$$(xyz)' = x' + y' + z'$$
- The generalized form of DeMorgan's theorems states that the complement of a function is obtained by interchanging AND and OR operators and complementing each literal

Minterms

- A binary variable may appear either in its normal form (x) or in its complement form (x')
- Now consider two binary variables x and y combined with an AND operation
- Since each variable may appear in either form, there are four possible combinations: xy , $x'y$, xy' , $x'y'$
- Each of these four AND terms is called a *minterm*, or a *standard product*
- In a similar manner, n variables can be combined to form 2^n minterms
- The binary numbers from 0 to $2^n - 1$ are listed under the n variables. Each minterm is obtained from an AND term of the n variables, with each variable being primed if the corresponding bit of the binary number is a 0 and unprimed if a 1
- A symbol for each minterm is m_j , where the subscript j denotes the decimal equivalent of the binary number of the minterm designated

Maxterms

- In a similar fashion, n variables forming an OR term, with each variable being primed or unprimed, provide 2^n possible combinations, called *maxterms*, or *standard sums*
- Each maxterm is obtained from an OR term of the n variables, with each variable being unprimed if the corresponding bit is a 0 and primed if a 1, and
- Maxterms are denoted by M_j

Minterms and Maxterms

Minterms and Maxterms for Three Binary Variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

It is important to note that:

1. Each maxterm is the complement of its corresponding minterm and vice versa
2. Minterms are 1 for a unique combination of the variables, ie, $x'y$ is only one when x is 0 and y is 1, in all other cases, it is zero
3. Maxterms are 0 for a single unique combination of variables

Boolean functions

- Any Boolean function can be expressed algebraically from a given truth table by forming a minterm for each combination of the variables that produces a 1 in the function and then taking the OR of all those terms
- Example: $f_1 = m_1 + m_4 + m_7$
$$f_1 = x'y'z + xy'z' + xyz$$
- Thus, any Boolean function can be expressed as a sum of minterms (with “sum” meaning the ORing of terms)

x	y	z	Function f_1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Boolean functions

- Now consider the complement of a Boolean function
- It may be read from the truth table by forming a minterm for each combination that produces a 0 in the function and then ORing those terms

$$f_1' = m_0 + m_2 + m_3 + m_5 + m_6$$

- If we again take a complement, we get f_1 back:

$$f_1 = (m_0 + m_2 + m_3 + m_5 + m_6)'$$

$$f_1 = m'_0 m'_2 m'_3 m'_5 m'_6$$

$$f_1 = M_0 M_2 M_3 M_5 M_6$$

x	y	z	Function f_1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Boolean functions

- This shows a second property of Boolean algebra: Any Boolean function can be expressed as a product of maxterms (with “product” meaning the ANDing of terms)
- The procedure for obtaining the product of maxterms directly from the truth table is as follows: Form a maxterm for each combination of the variables that produces a 0 in the function, and then form the AND of all those maxterms

x	y	z	Function f_1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Boolean functions

- Are there infinitely many Boolean functions for two independent variables, x and y ?
- What are the total number of functions possible for two variables?
- For n variables?
- We can have 2^{2^n} functions for n binary variables!
- Thus, for two variables, $n = 2$, and the number of possible Boolean functions is 16
- Therefore, the AND and OR functions are only 2 of a total of 16 possible functions formed with two binary variables
- Let us find the other 14 functions and investigate their properties

Boolean functions

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

- Constant functions: 0 and 1
- AND and OR –the well-known logic functions
- Transfer functions: x and y
- Complement functions: x' and y'

Boolean functions

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	0	1	

- NAND and NOR –these are complementary functions to the usual AND and OR functions
- Take the AND/OR and then take the complement
- NAND is represented by \uparrow and NOR is represented by \downarrow
- $x \uparrow y = (x \cdot y)'$ and $x \downarrow y = (x + y)'$

Boolean functions

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	0	1	

- Exclusive OR (XOR) returns 1 only if one of x or y is 1, it is 0 if both are one
- This is represented by the symbol \oplus
- $x \oplus y = x'y + y'x$
- The complement of this is XNOR or Equivalence (is x=y?)

Boolean functions

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	0	1	

- Inhibition function: x but not y (F_2), and y but not x (F_4)
- x but not y: If y is LOW then what is x?
- It is represented by a /
- $x/y = xy'$

Boolean functions

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	1	1	0	0	1	1	
1	1	0	1	0	1	0	1	0	1	0	1	1	0	1	0	1	

- Implications: x implies y (F_{13}), or y implies x (F_{11})
- This tells us whether the variables x and y are following the *given* implication rule
- It is not for determining whether the two variables form an implication rule between them

Boolean functions

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x , but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y , but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \subset y$	Implication	If y , then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

Lecture 9 – Logic gates

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST

Logic gates!


- Logic gates are electronic circuits that operate on one or more input signals to produce an output signal
- Because Boolean world is binary in nature, we represent Boolean values as signals of two distinct voltage levels
- Voltage-operated logic circuits respond to these voltage levels that represent a binary variable equal to logic 1 or logic 0
- For example, a particular digital system may define logic 0 as a signal equal to 0 V and logic 1 as a signal equal to 5 V

Logic gates


- We represent the logic gates for basic Boolean operations as shown
- Logic gates can have more than two inputs (except for NOT gate of course!)




(a) Two-input AND gate

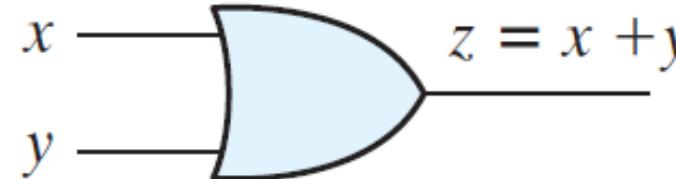


(b) Two-input OR gate

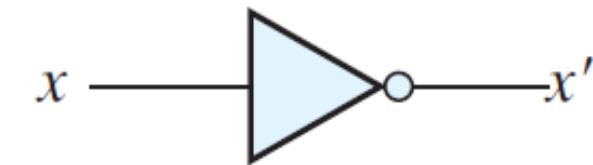


(c) NOT gate or inverter

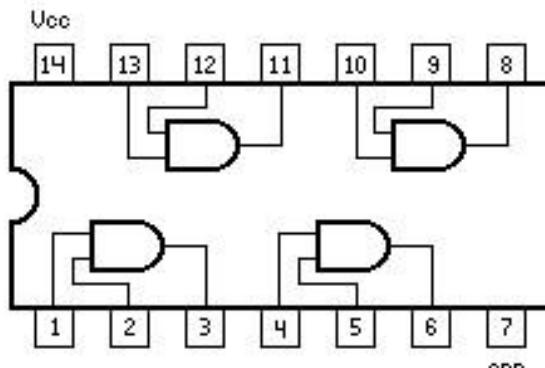

7408 (AND)

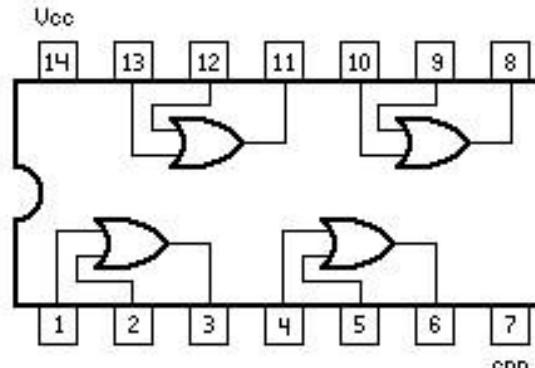

7432 (OR)

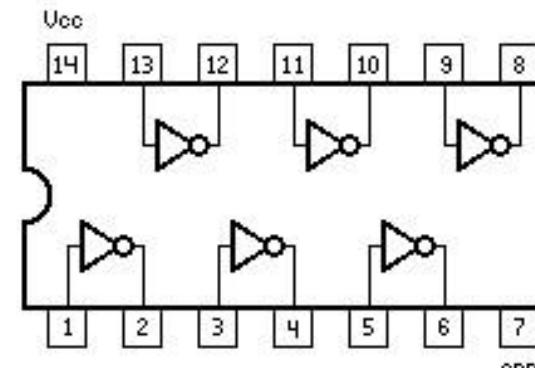


7404 (NOT)




Logic gates

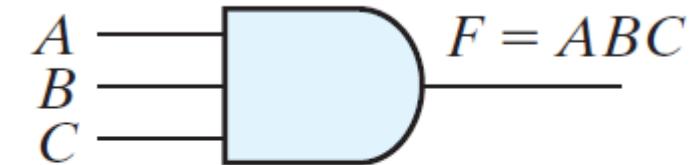- AND and OR gates may have more than two inputs
- The three-input AND gate responds with logic 1 output if all three inputs are logic 1. The output produces logic 0 if any input is logic 0
- The four-input OR gate responds with logic 1 if any input is logic 1; its output becomes logic 0 only when all inputs are logic 0



(a) Three-input AND gate

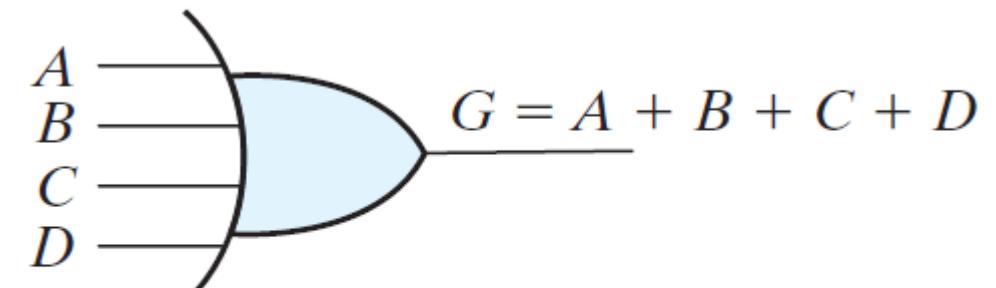

(b) Four-input OR gate

Logic gates

- Since Boolean functions are expressed in terms of AND, OR, and NOT operations, it is easier to implement a Boolean function with these type of gates
- Still, the possibility of constructing gates for the other logic operations is of practical interest
- Factors to be weighed in considering the construction of other types of logic gates are:
 1. The feasibility and economy of producing the gate with physical components
 2. The possibility of extending the gate to more than two inputs
 3. The basic properties of the binary operator such as commutativity and associativity
 4. The ability of the gate to implement Boolean functions alone or in conjunction with other gates

Logic gates

- Of the 16 functions for two variables x and y , two are equal to a constant and four are unary operators (transfer and complement)
- This leaves us with 10 functions for multiple input operations
- Out of these, four functions (two inhibitions and two implications) are not commutative or associative and thus are impractical to use as standard logic gates. Further, their logical definitions cannot be easily extended to multiple inputs
- Hence, the other six—AND, OR, NAND, NOR, exclusive-OR, and equivalence—are used as standard multi-input gates in digital design

Logic gates

AND




x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

OR



x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

Inverter

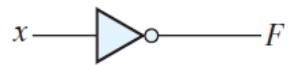

$$F = x'$$


x	F
0	1
1	0

Buffer



x	F
0	0
1	1

NAND

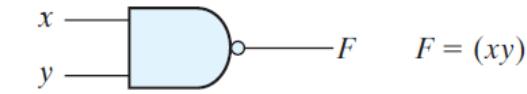

$$F = (xy)'$$

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

NOR



$$F = (x + y)'$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR
(XOR)



$$F = xy' + x'y \\ = x \oplus y$$

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

Exclusive-NOR
or
equivalence



$$F = xy + x'y' \\ = (x \oplus y)'$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

Multiple inputs

- The exclusive-OR and equivalence gates are both commutative and associative and can be extended to more than two inputs
- However, multiple-input exclusive-OR gates are difficult to make from the hardware standpoint
- The definition of the function must be modified when extended to more than two variables
- Multi-input Exclusive-OR is an *odd* function (i.e., it is equal to 1 if the input variables have an odd number of 1's), and XNOR is its complement

Multiple inputs

- A gate can be extended to have multiple inputs if the binary operation it represents is commutative and associative
- The AND and OR operations, defined in Boolean algebra, possess these two properties
- The NAND and NOR functions are commutative
- The difficulty is that the NAND and NOR operators are not associative
$$(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$$
- To overcome this difficulty, we define the multiple NOR (or NAND) gate as a complemented OR (or AND) gate. Thus, by definition, we have:

$$\begin{aligned}x \downarrow y \downarrow z &= (x + y + z)' \\x \uparrow y \uparrow z &= (xyz)'\end{aligned}$$


Boolean functions with gates

- We can represent any Boolean function using logic gates
- This forms the circuit for the function
- Examples:
 1. $F = x + y.z$
 2. $G = ABC + A'B' + AB'C'$
- Simplification of the function leads to a simpler circuit (less gates and smaller gates)

Logic circuits!

- Our first real circuit...
- Logic circuits are combinations of logic gates to make a particular logic function of our choice
- The logic function can be uniquely represented by a truth-table
- However, many algebraic expressions give the same truth-table and the best or most optimum way of making the circuit is to be found by designers
- Consider a statement: design a circuit to add two binary bits
- We go from having a logic function to getting the truth-table, then obtaining the circuit
- In this case, because of its simplicity, we know that
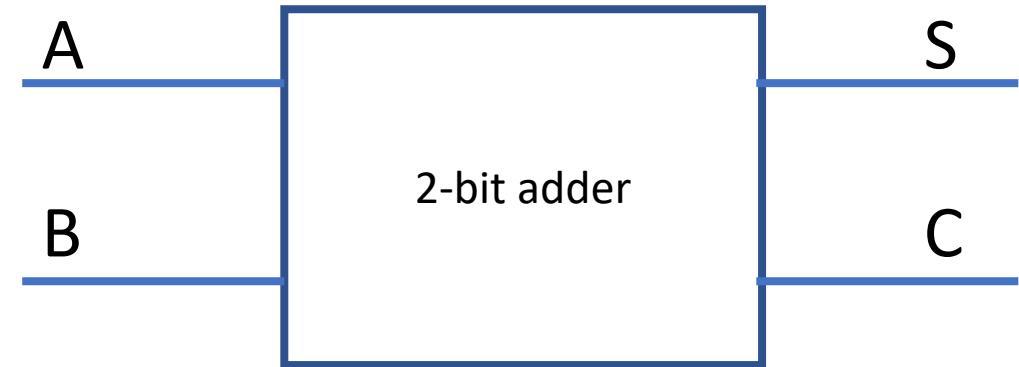
$$S = A \oplus B \text{ and } C = A \cdot B$$



A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Gate interconversions

- For a given function, many logic implementations can be done using the gates discussed
- But can we do ALL these implementations with a single logic function implemented over and over?
- These are the NAND and NOR gates –they are referred to as *Universal gates* for this property
- How do we prove this?
- If we can prove that we can get NOT, AND and OR from these gates, we can generate other logic functions using these basic functions

Gate interconversions

- Obtain NOT, AND and OR from NAND
- Obtain NOT, AND and OR from NOR
- Can we get NOT, AND and OR from NOT, AND or OR gates?

Logic circuits

- Let us say we wanted to continue adding, now we need to take care of the previous carry
- Thus, we need to add A, B and C to get a generic adding machine
- Still from observation, we can deduce that $S = A \oplus B \oplus C_0$
- But what is the algebraic expression for C_1 ?
- We know the sum of minterms, but is there an better way?



A	B	C_0	C_1	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Gate level minimization

- *Gate-level minimization* is the design task of finding an optimal gate-level implementation of the Boolean functions describing a digital circuit
- This task is well understood, but is difficult to execute by manual methods when the logic has more than a few inputs
- Fortunately, computer-based logic synthesis tools can minimize a large set of Boolean equations efficiently and quickly
- Nevertheless, it is important that a designer understand the underlying mathematical description and solution of the problem

Lecture 10 – K-maps

Gate level minimization

- Some history: although we use the term *Karnaugh map* (named after Maurice Karnaugh, 1953) for the map method, it dates back further
- In 1881, Allan Marquand published a paper criticizing “Mr. Venn” for his approach to visualization of logic problems using curvilinear shapes and proposed a method with non-intersecting squares
- Non-intersecting because he was concerned with two-state variables that are either *true* or *false*

XXXIII. *On Logical Diagrams for n terms.* By ALLAN MARQUAND, Ph.D., late Fellow of the Johns Hopkins University*.


IN the Philosophical Magazine for July 1880 Mr. Venn has offered diagrams for the solution of logical problems involving three, four, and five terms. From the fact that he makes use of circles, ellipses, and other curvilinear figures, the construction of diagrams becomes more and more difficult as new terms are added. Mr. Venn stops with the five-term diagram, and suggests that for six terms “the best plan would be to take two five-term figures.”

It is the object of this paper to suggest a mode of constructing logical diagrams, by which they may be indefinitely extended to any number of terms, without losing so rapidly their special function, viz. that of affording visual aid in the solution of problems.

Conceiving the logical universe as always more or less limited, it may be represented by any closed figure. For convenience we take a square. If then we drop a perpendicular from the middle point of the upper to the lower side of the square, the universe is prepared for a classification of its contents by means of a single logical term.


Gate level minimization

- Some history: although we use the term *Karnaugh map* (named after Maurice Karnaugh, 1953) for the map method, it dates back further
- In 1881, Allan Marquand published a paper criticizing “Mr. Venn” for his approach to visualization of logic problems using curvilinear shapes and proposed a method with non-interesting squares
- Non-intersecting because he was concerned with two-state variables that are either *true* or *false*

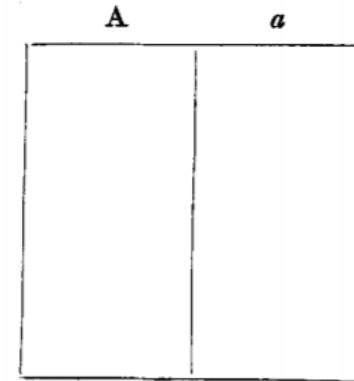


This represents a universe with its A and not-A “compartments.” The quantitative relation of the compartments being insignificant, they may for convenience be represented as equal.

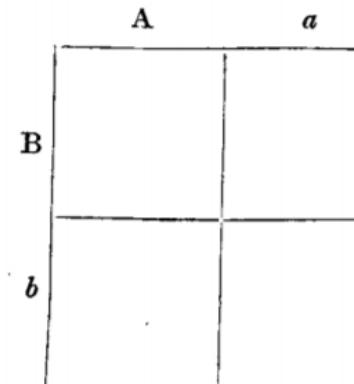The introduction of a second term divides each of the existing compartments. This may be done by a line drawn at right angles to our perpendicular and through its centre, thus :—




Gate level minimization

- **Gate-level minimization** is the task of finding an optimal gate-level implementation of the Boolean functions describing a digital circuit.
- The complexity of logic gate implementation of a Boolean function is directly related to the complexity of the algebraic expression from which the function is implemented.
- Algebraic simplification of Boolean expressions can be cumbersome
- Karnaugh map (K-Map) provides a systematic method to simplify Boolean expressions

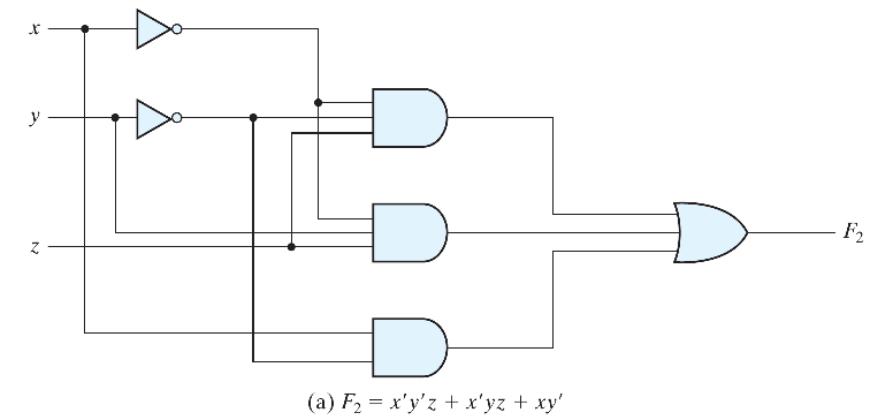

$$(a) F_2 = x'y'z + x'yz + xy'$$

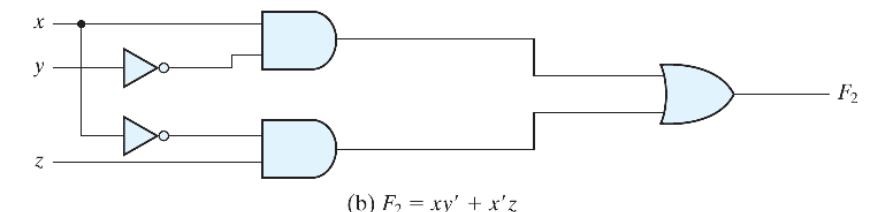


$$(b) F_2 = xy' + x'z$$

$$F_2 = x'y'z + x'yz + xy' = x'z(y' + y) + xy' = x'z + xy'$$

2 variable K-map


- There are four *minterms* for two variables – xy , $x'y$, xy' , $x'y'$; hence, the map consists of four squares, one for each *minterm*
- The map can be drawn to show the relationship between the squares and the two variables x and y
- The 0 and 1 marked in each row and column designate the values of variables
- In *minterm* form, variable x appears primed in row 0 and unprimed in row 1. Similarly, y appears primed in column 0 and unprimed in column 1

m_0	m_1
m_2	m_3

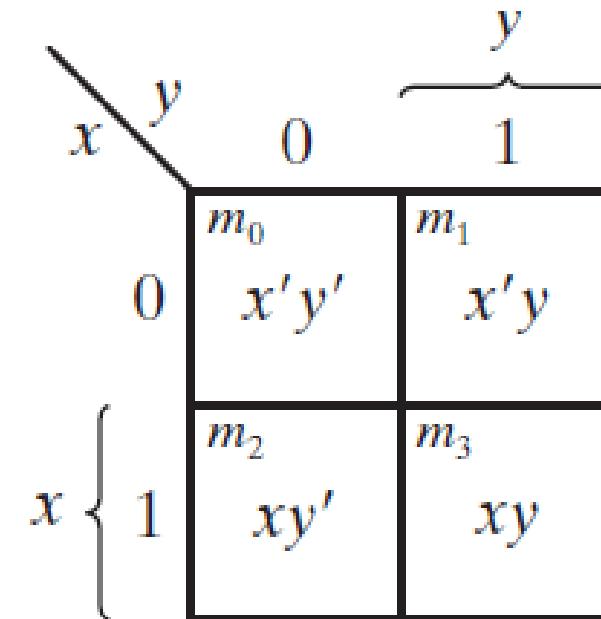


2 variable K-map

Example:

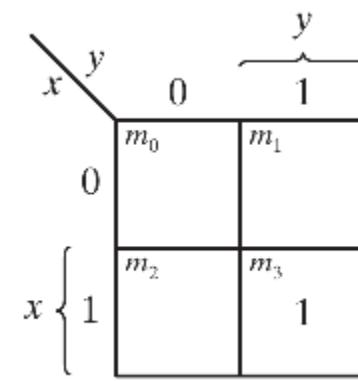

Map for $F = xy$

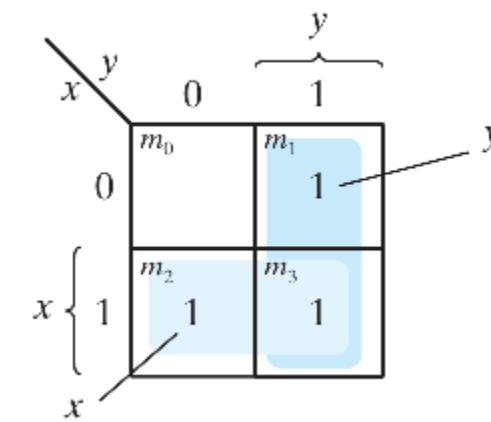


Map for $F = x+y$

3 variable K-map


- In 3 variable problems, there are eight **minterms** for three binary variables; therefore, the map consists of eight squares
- The map is marked with numbers in each row and each column to show the relationship between the squares and the three variables
- For example, the square assigned to m_5 corresponds to row 1 and column 01
- Each cell of the map corresponds to a unique **minterm**, so another way of looking at the square is $m_5 = xy'z$
- Note that there are four squares in which each variable is equal to 1 and four in which each is equal to 0

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

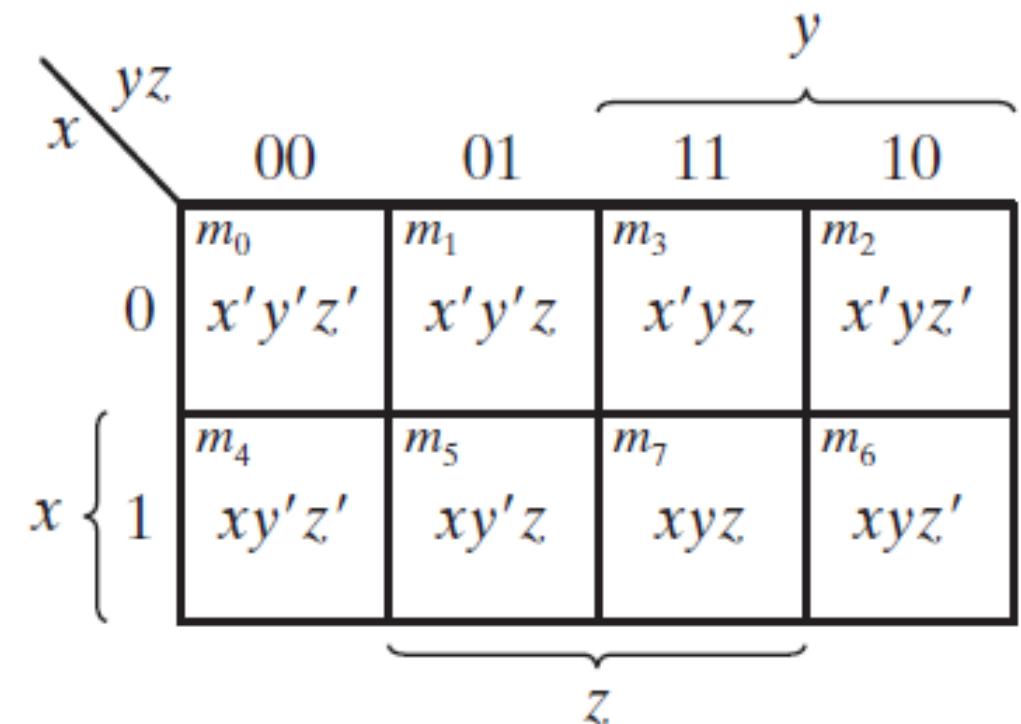


3 variable K-map

- Here is the magic: To understand the usefulness of the map in simplifying Boolean functions, we must recognize the basic property possessed by adjacent squares: **Any two adjacent squares in the map differ by only one variable**, which is primed in one square and unprimed in the other
- For example, m_5 and m_7 lie in two adjacent squares
- Variable y is primed in m_5 and unprimed in m_7 , whereas the other two variables are the same in both squares
- From the postulates of Boolean algebra, it follows that the sum of two **minterms** in adjacent squares can be simplified to a single product term consisting of only two literals- Eg: $xy'z + xyz = xz(y'+y) = xz$

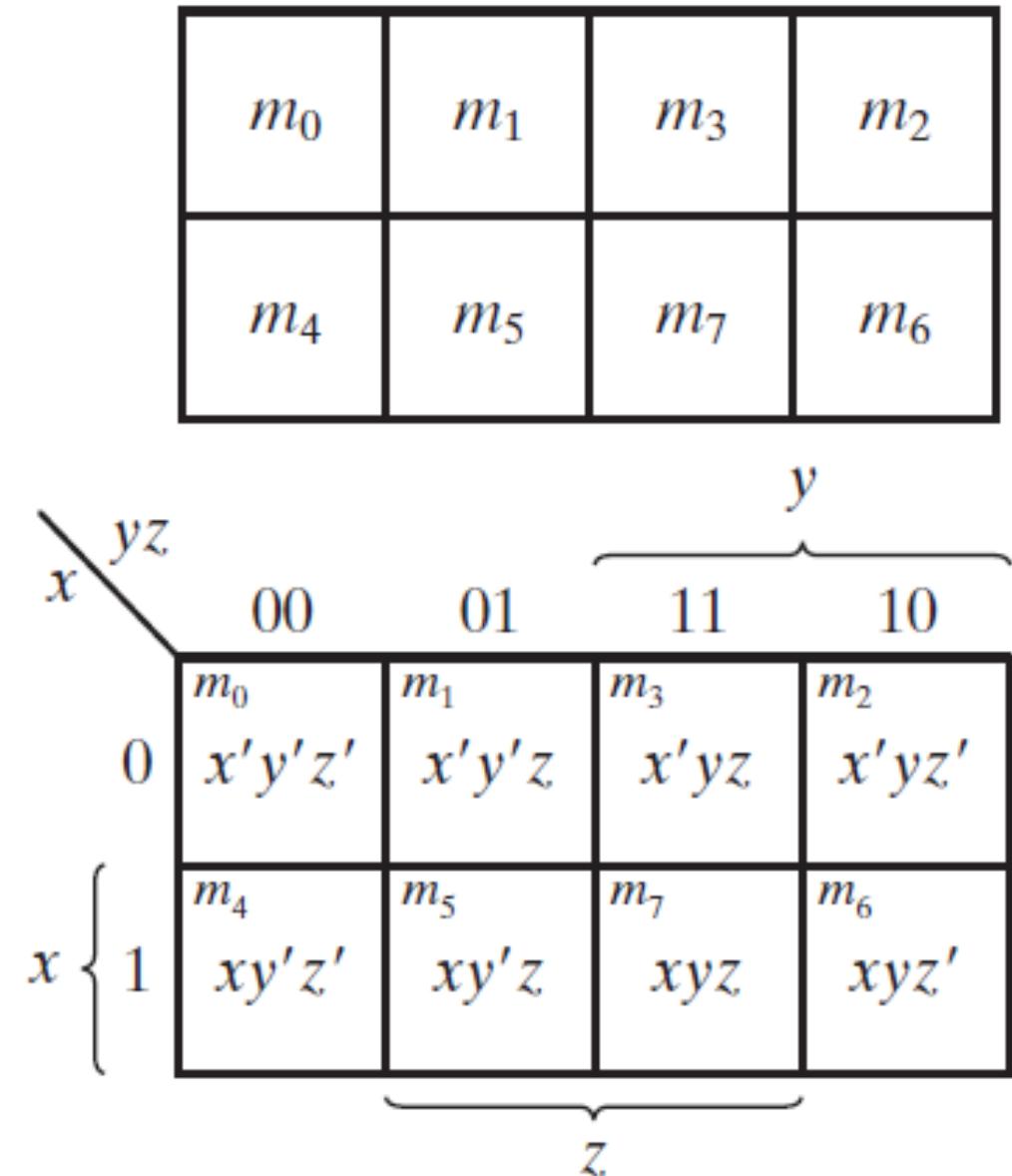


3 variable K-map

- Here is how we optimize the logic gate expression using maps:
 1. We look for a cluster of adjacent squares with the function value being 1 (or true):
 1. cluster of 8 squares (meaning the entire function is 1)
 2. A cluster of 4 squares (meaning one literal)
– eg: $xyz + xyz' + x'yz + x'yz' = xy + x'y = y$
 3. A cluster of 2 squares (meaning two literals ANDed)
 4. single square with all three variables ANDed (the minterm)
 2. We OR all the expressions related to the clusters
- Note that “adjacent” squares mean vertically or horizontally, not diagonally

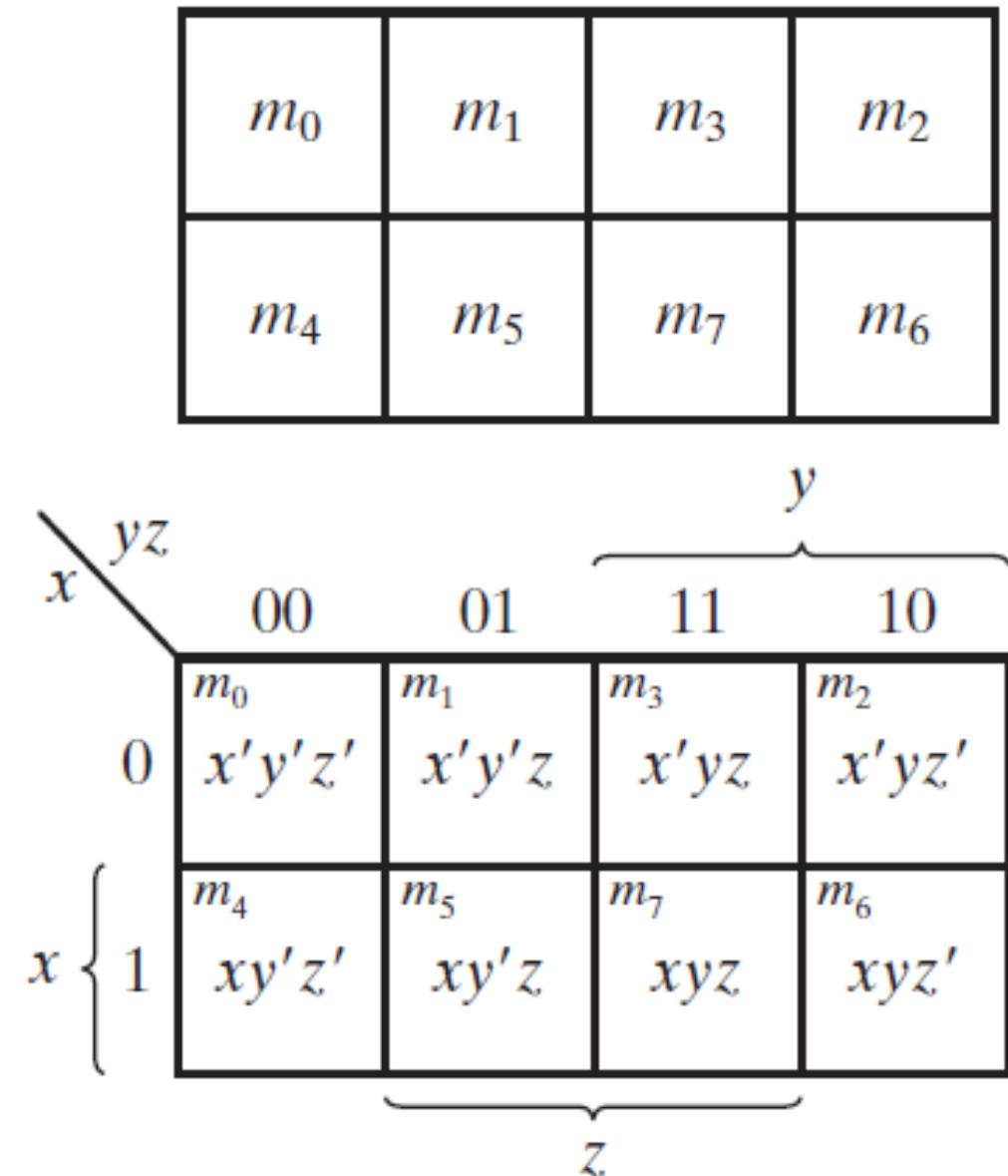


3 variable K-map

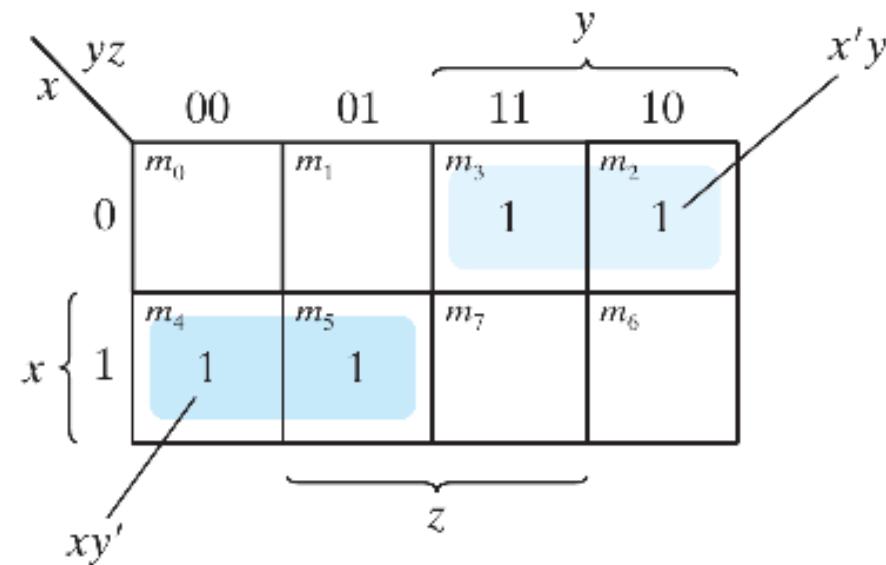Simplify the Boolean function: $F(x, y, z) = \Sigma(2, 3, 4, 5)$



$$F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$$

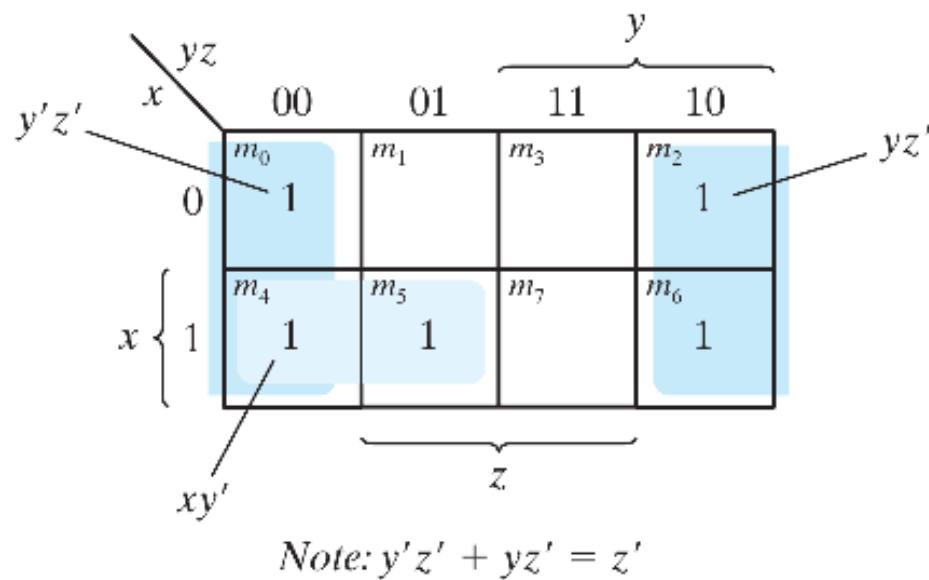Simplify the Boolean function: $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$



m_2 is adjacent to m_0
 m_6 is adjacent to m_4


$$F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$$

3 variable K-map

- Full adder:

A	B	C_0	C_1	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

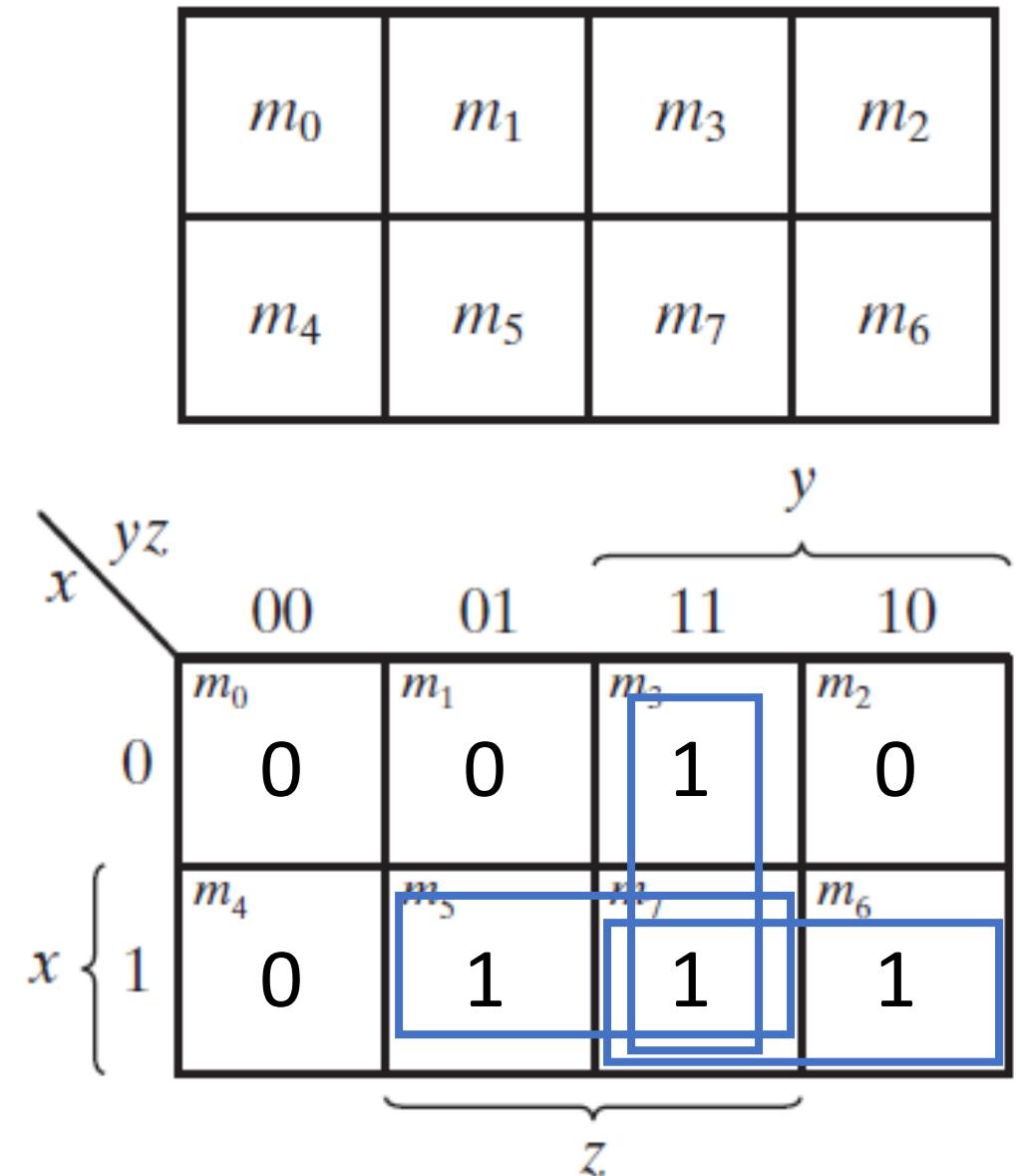
- Let $x = A$, $y = B$, $z = C_0$
 - Three clusters of 2 squares
 - Thus,
- $$C_1 = xy + yz + zx$$
- $$C_1 = AB + BC_0 + C_0A$$



3 variable K-map


- $F(x, y, z) = \sum(1, 2, 3, 5, 7)$
- We have one cluster of 4 squares
- This represents z
- One cluster of 2 squares
- This represents $x'y$
- Thus, $F = z + x'y$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

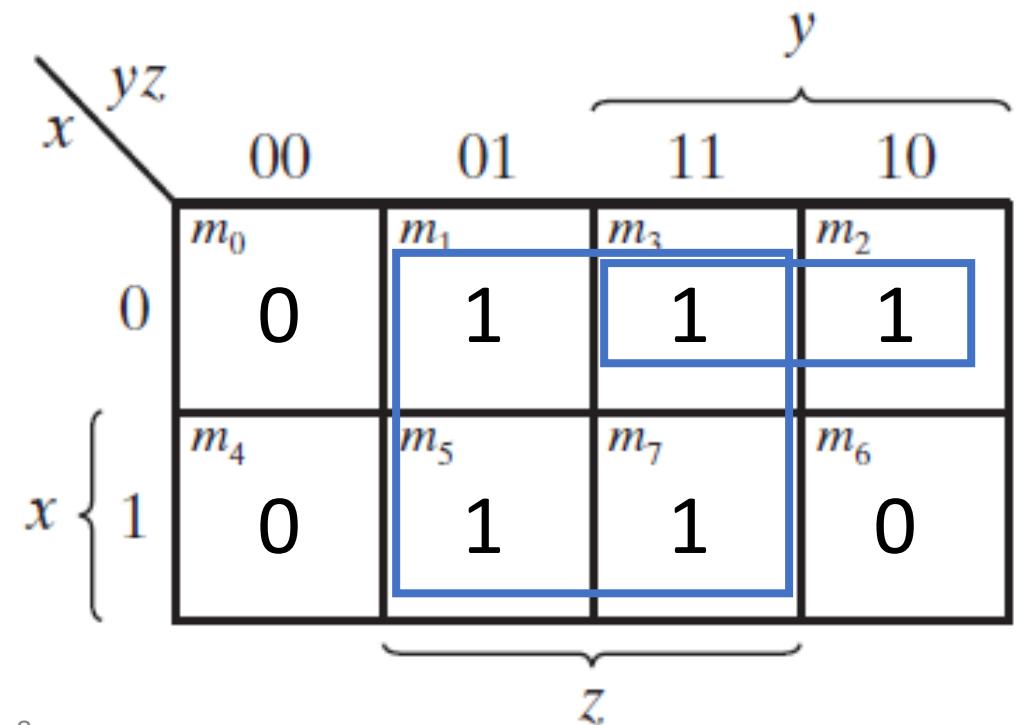

4 variable K-map


m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

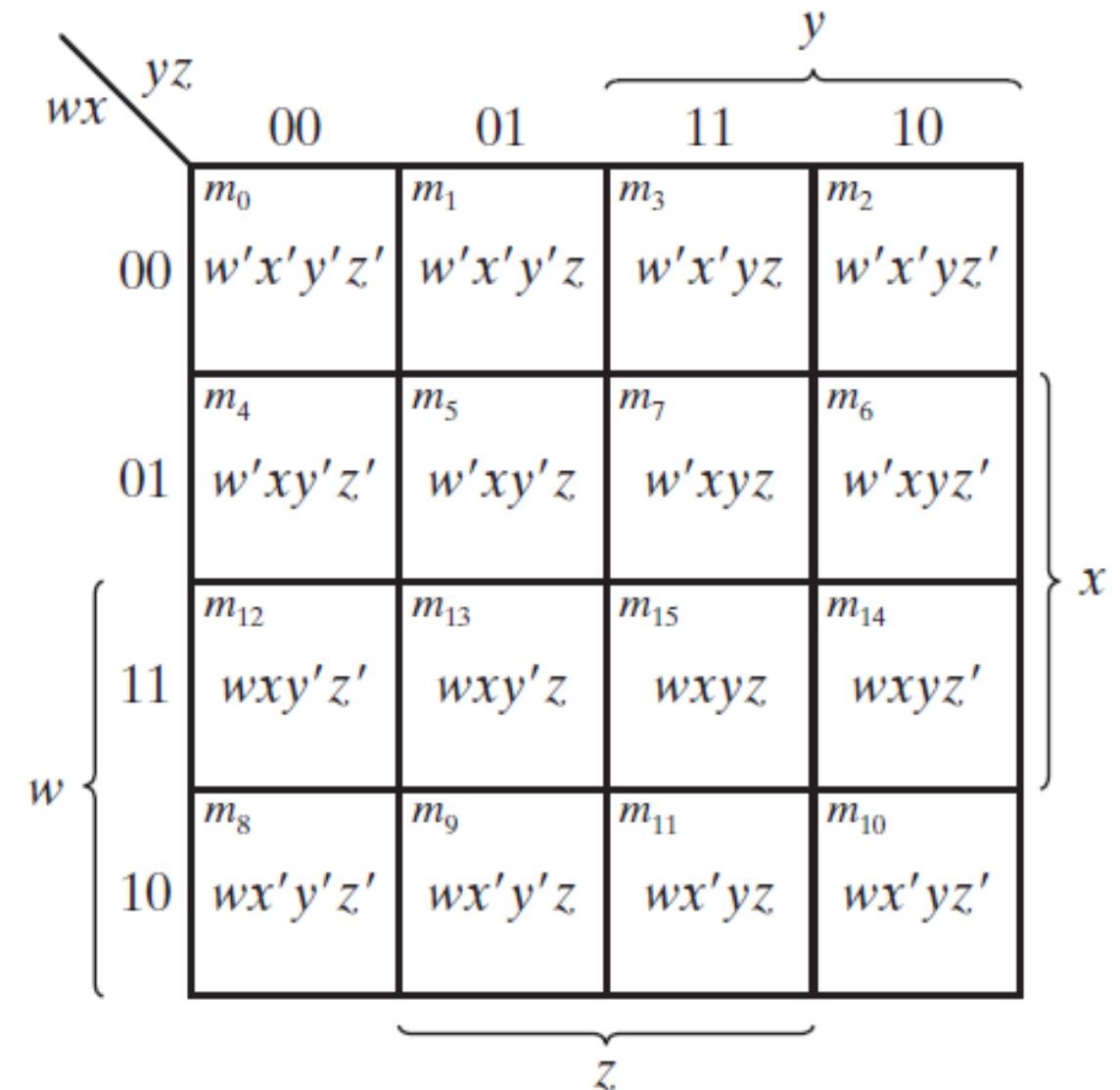

4 variable K-map


1. We look for a cluster of adjacent squares with the function value being 1 (or true):
 1. A cluster of 16 squares (meaning the entire function is 1)
 2. A cluster of 8 squares (meaning one literal)
 3. A cluster of 4 squares (meaning two literals ANDed)
 4. A cluster of 2 squares (meaning three literals ANDed)
 5. A single square with all the four variables ANDed (a minterm)
2. We OR all the expressions related to the clusters

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

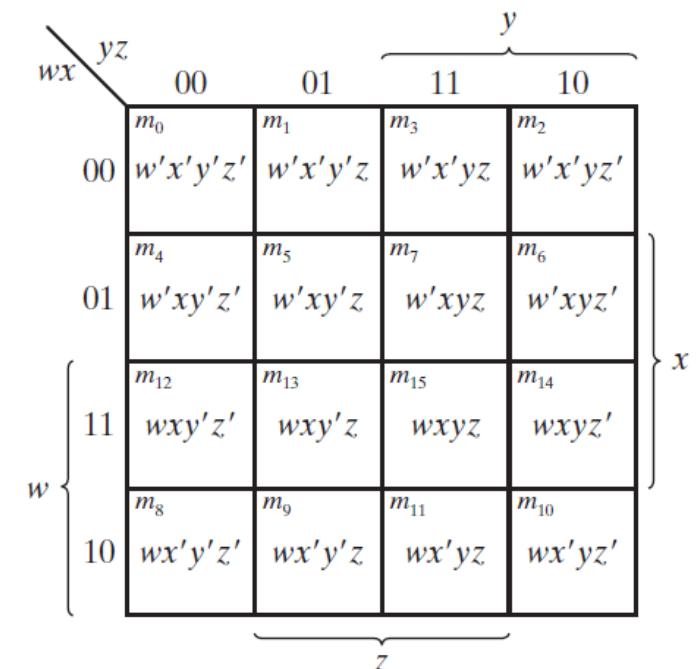

4 variable K-map

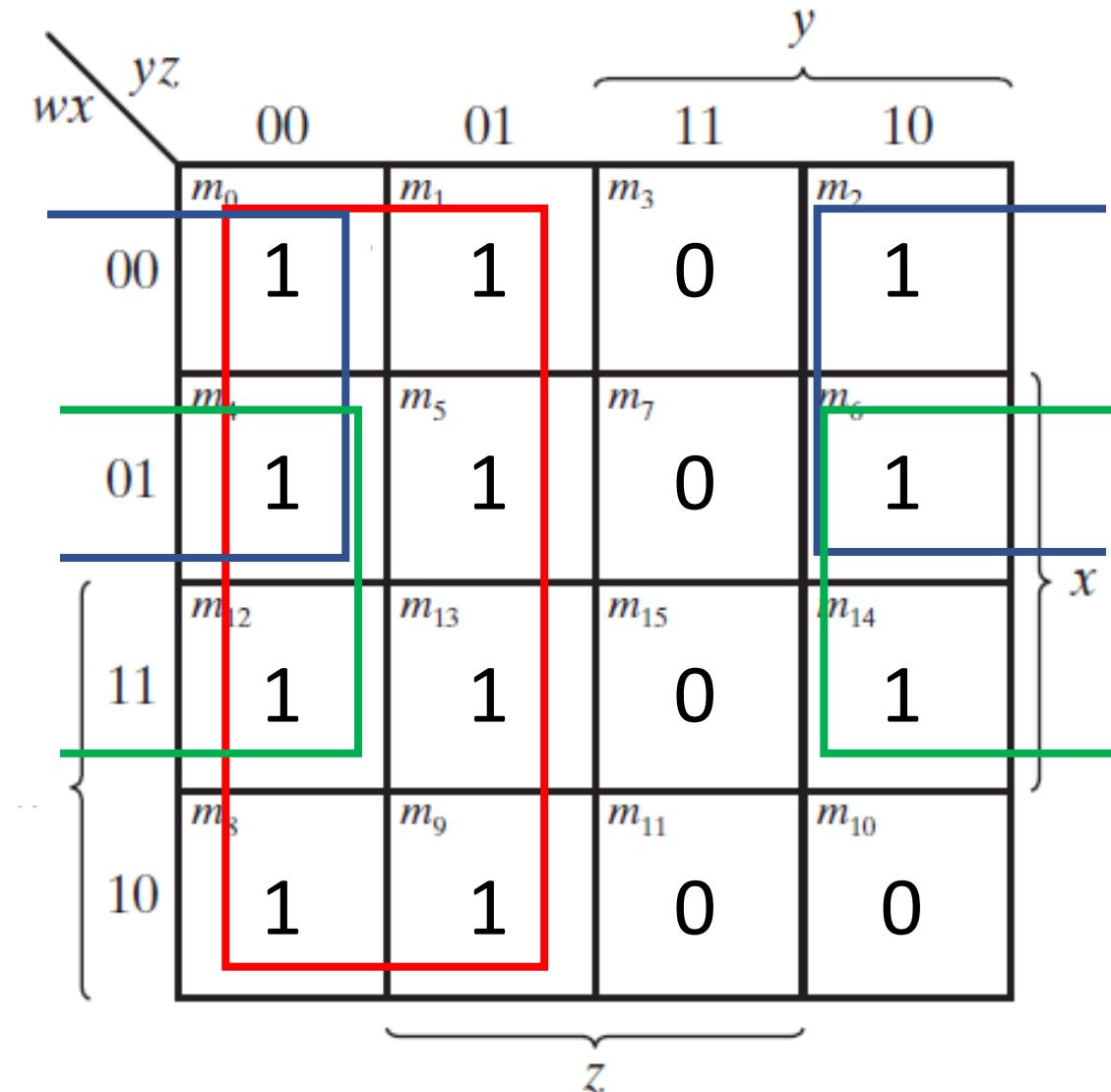- Simplify the function
 $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
- Cluster of 16? No
- Cluster of 8?
- It represents y'
- Cluster of 4?
- This represents $w'z'$
- This represents xz'
- Thus, the function is
 $F(w, x, y, z) = y' + w'z' + xz'$



Product of Sums


- The minimized Boolean functions derived from the K-map were expressed in *sum-of-products* form
- With a minor modification, the product-of-sums form can be obtained
- The 1's placed in the squares of the map represent the *minterms* of the function
- From this observation, we see that the complement of a function is represented in the map by the squares not marked by 1's
- *If we mark the empty squares by 0's and combine them into valid adjacent squares, we obtain a simplified sum-of-products expression of the complement of the function (i.e., of F')*
- The complement of F' gives us back the function F in product-of-sums form (a consequence of DeMorgan's theorem)

Product of Sums

- Simplify the following Boolean function into (a) sum-of-products form and (b) product-of-sums form:
 $F(w, x, y, z) = \sum(0, 1, 2, 5, 8, 9, 10)$


- Two clusters of four squares: $x'z'$ and $x'y'$
- One cluster of two squares: $w'y'z$
- Thus, the function is:

$$F = x'z' + x'y' + w'y'z$$

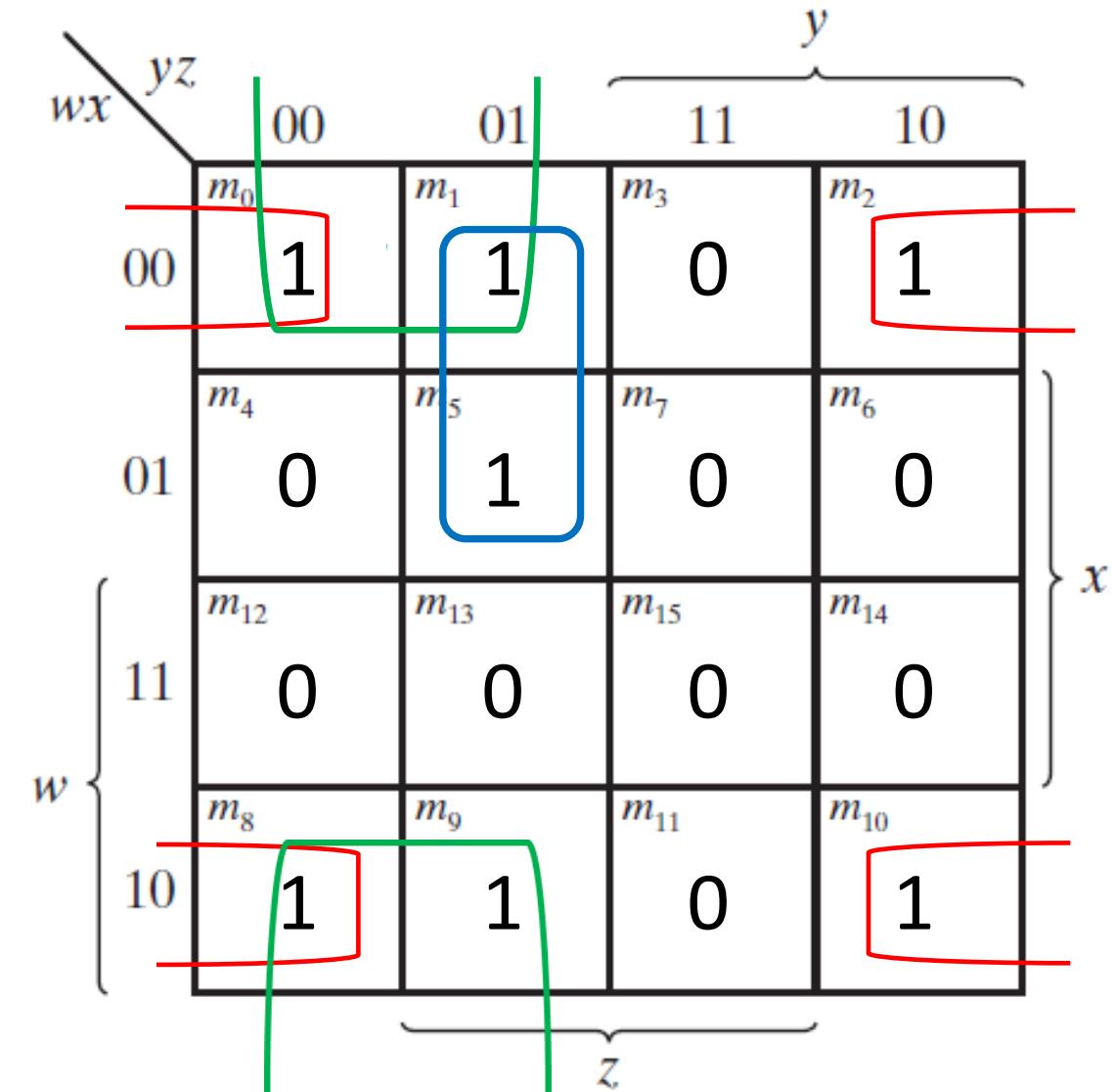


Product of Sums

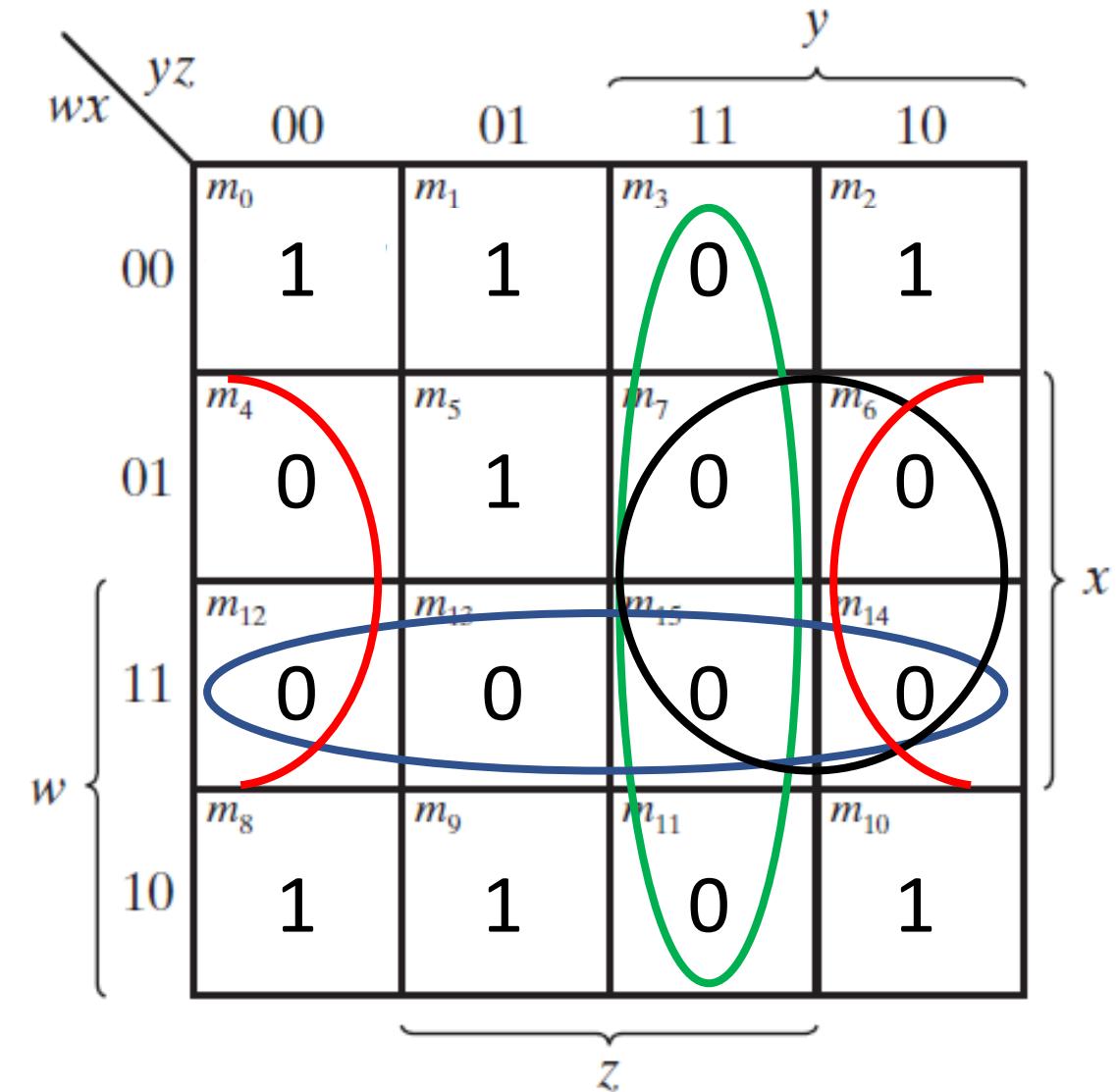- The original function is:
$$F = x'z' + x'y' + w'y'z$$
- Now, let us see the complement of the function: F'
- This can be obtained from clustering all the 0s together
- We have four clusters of four (*prime implicants*)
- Of these, the *essential prime implicants* are: yz , wx , xz'
- Thus, $F' = wx + yz + xz'$



Product of Sums

- The original function is:
$$F = x'z' + x'y' + w'y'z$$
- Thus, the complement function is
$$F' = wx + yz + xz'$$
- Now, we can obtain F back from F' using the DeMorgan's theorems
- Thus,
$$F = (w' + x')(y' + z')(x' + z)$$
- Hence, the actual simplest implementation of a function can be through its complement (product of sum)

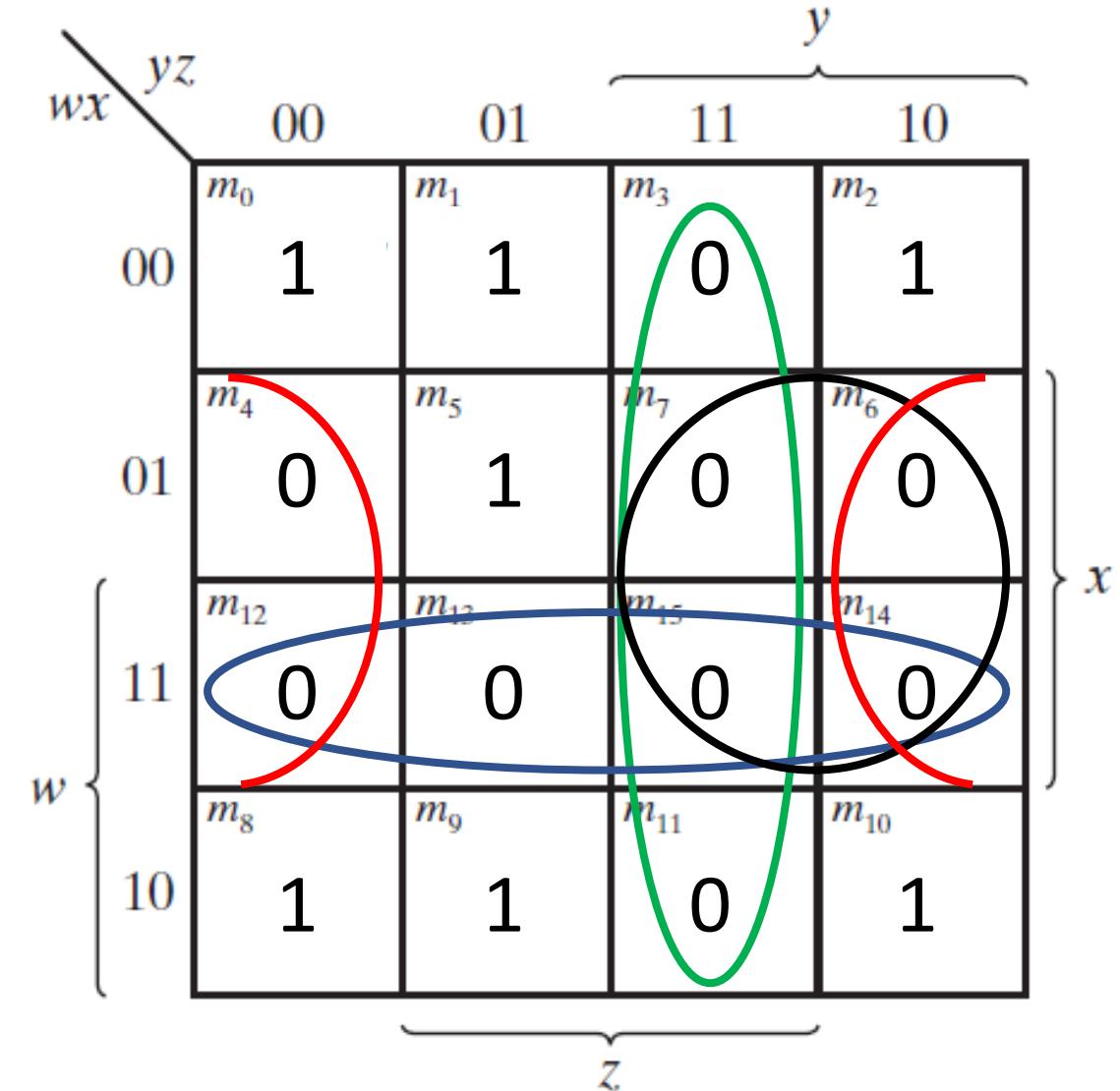


Lecture 11 – Logic implementation

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Timing diagrams

- With logic functions, it is always nice to visualize the various conditions giving a particular output
- One way of visualizing is the truth table, another way can be the timing diagram of a particular function
- Timing diagrams are useful to indicate the sequence of events in large combinational circuits


		AND		OR	
x	y	$x \cdot y$		x	y
0	0	0		0	0
0	1	0		0	1
1	0	0		1	0
1	1	1		1	1

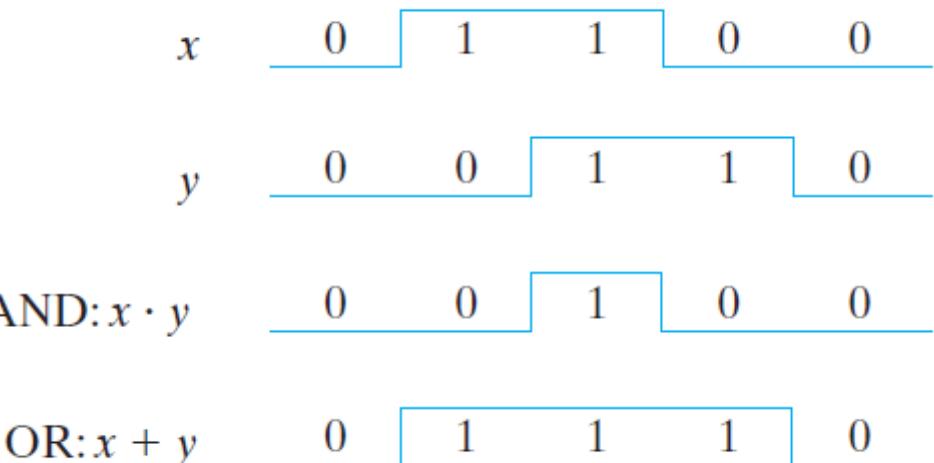

Timing diagrams


- The timing diagrams illustrate the idealized response of each gate to the four input signal combinations
- The horizontal axis of the timing diagram represents the time, and the vertical axis shows the signal as it changes between the two possible voltage levels
- In reality, the transitions between logic values occur quickly, but not instantaneously
- The low level represents logic 0, the high level logic 1

		AND		OR	
x	y	$x \cdot y$		x	y
0	0	0		0	0
0	1	0		0	1
1	0	0		1	0
1	1	1		1	1

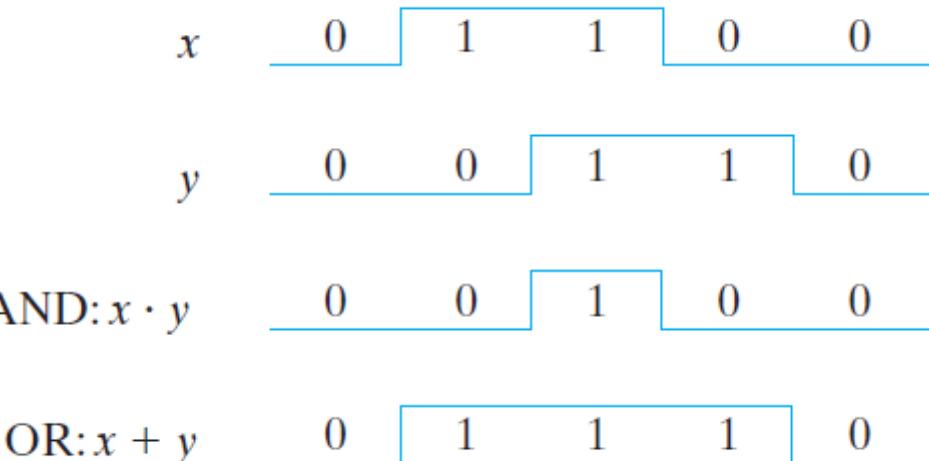


Implementing logic gates

- Typically, logic gates are implemented using transistors in CMOS architecture, where they act as switches, connecting VDD or GND to the output
- The switches are themselves driven using the logic states as inputs:
 - nMOS is on for logic 1 input and off for logic 0
 - pMOS is on for logic 0 input and off for logic 1
- When GND is connected, the output goes to logic 0
- When VDD is connected, the output goes to logic 1

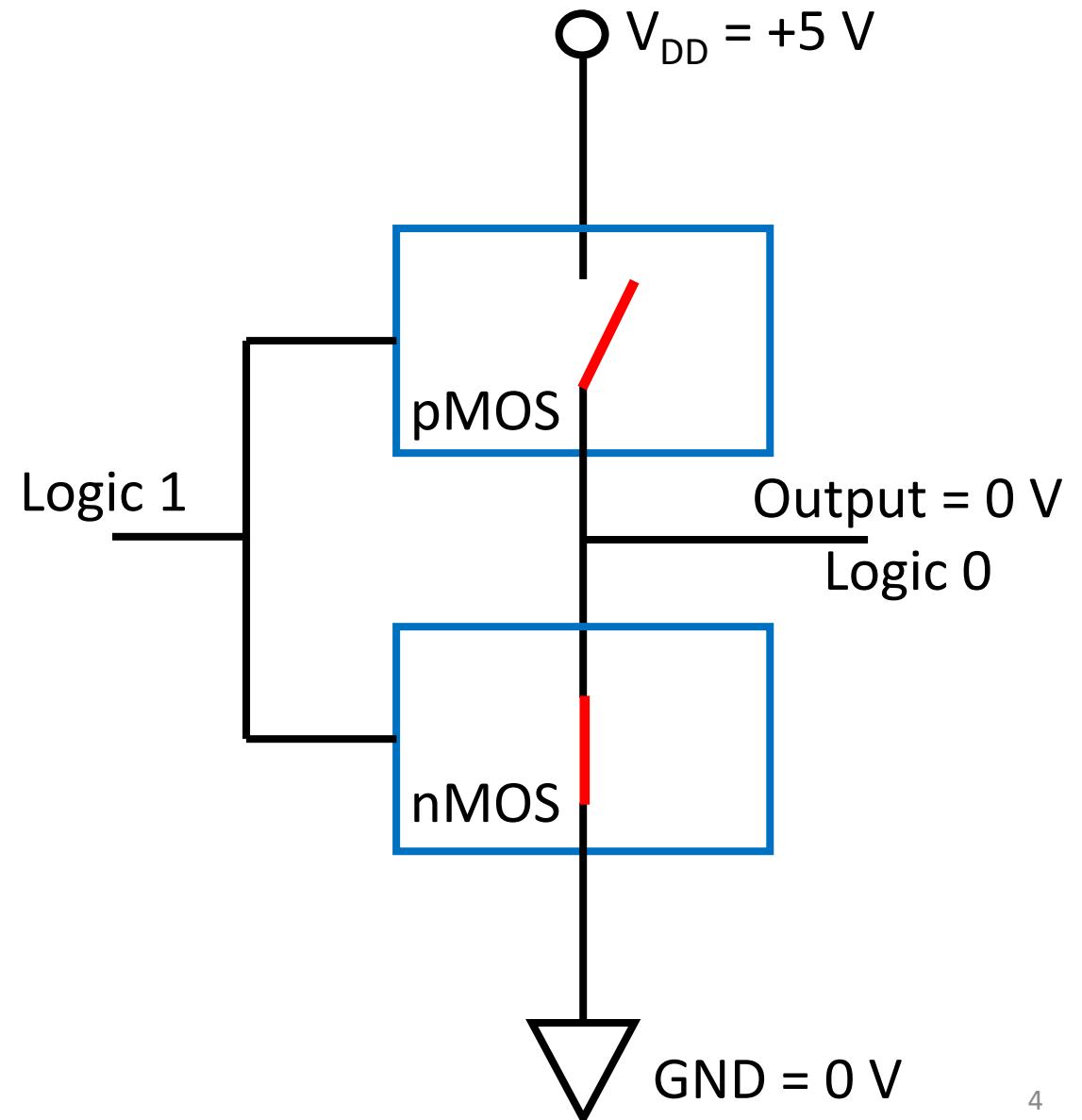


Implementing logic gates

- Typically, logic gates are implemented using transistors in CMOS architecture, where they act as switches, connecting VDD or GND to the output
- The switches are themselves driven using the logic states as inputs:
 - nMOS is on for logic 1 input and off for logic 0
 - pMOS is on for logic 0 input and off for logic 1
- When GND is connected, the output goes to logic 0
- When VDD is connected, the output goes to logic 1

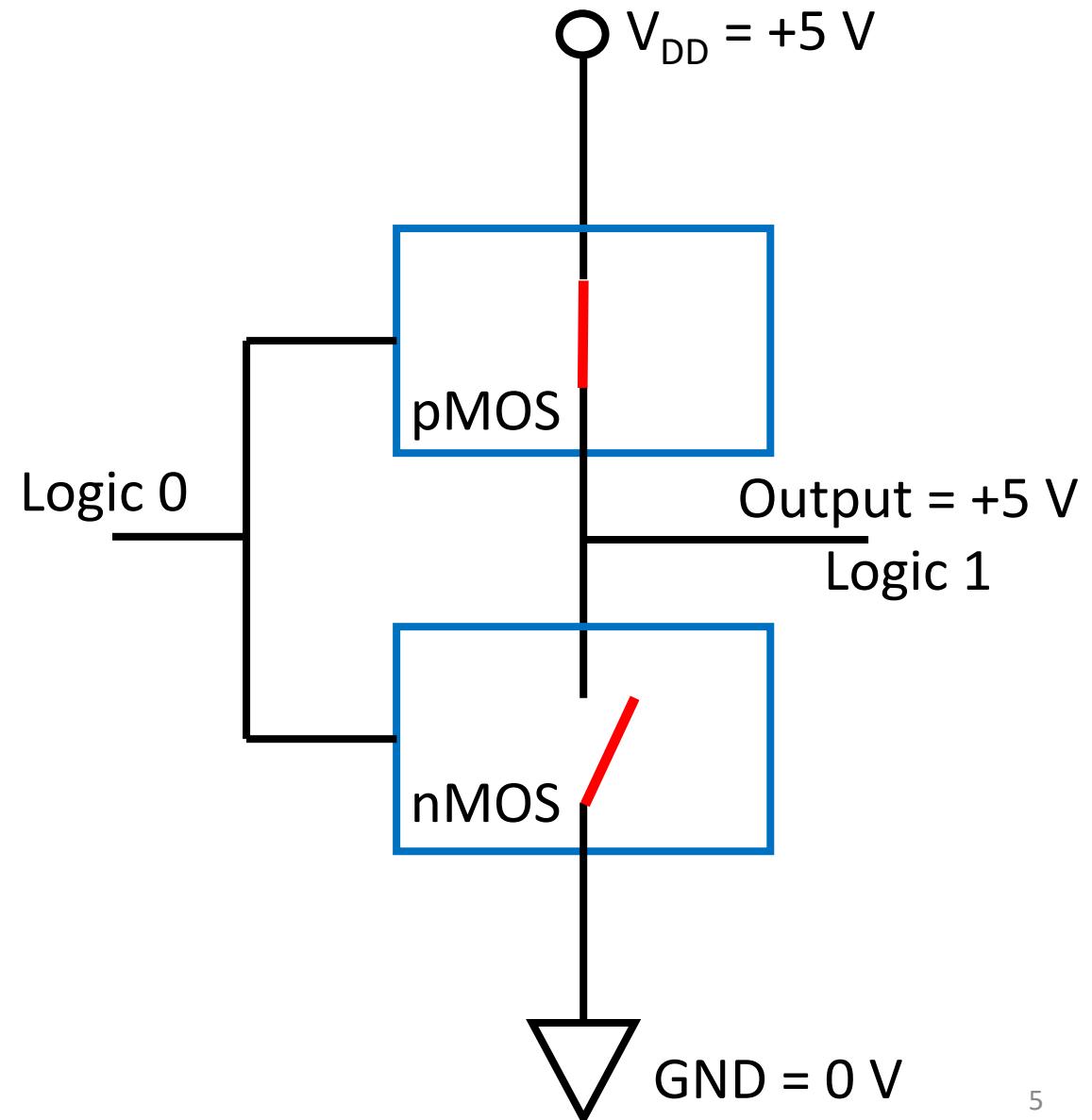


Implementing logic gates

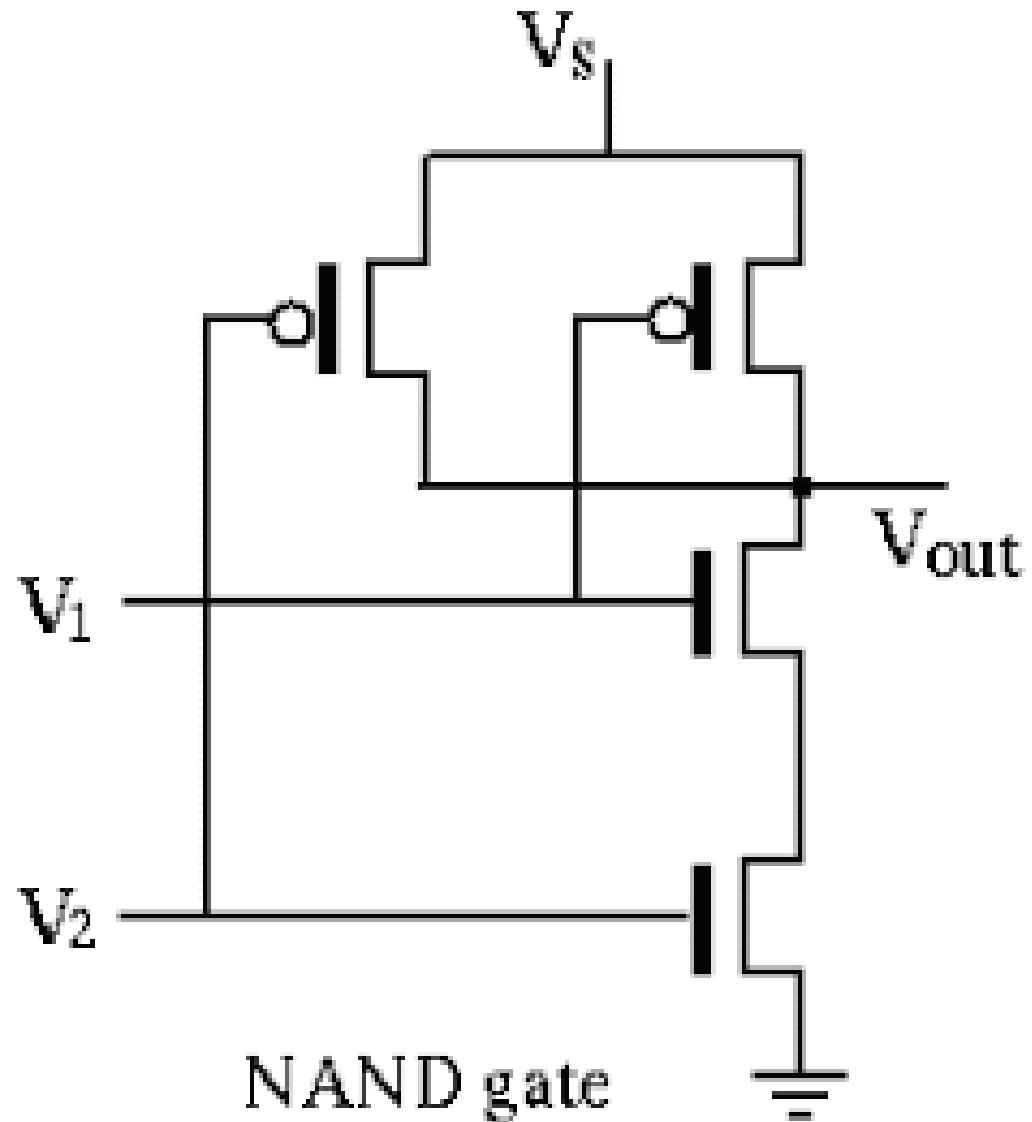


Implementing logic gates

AND gate

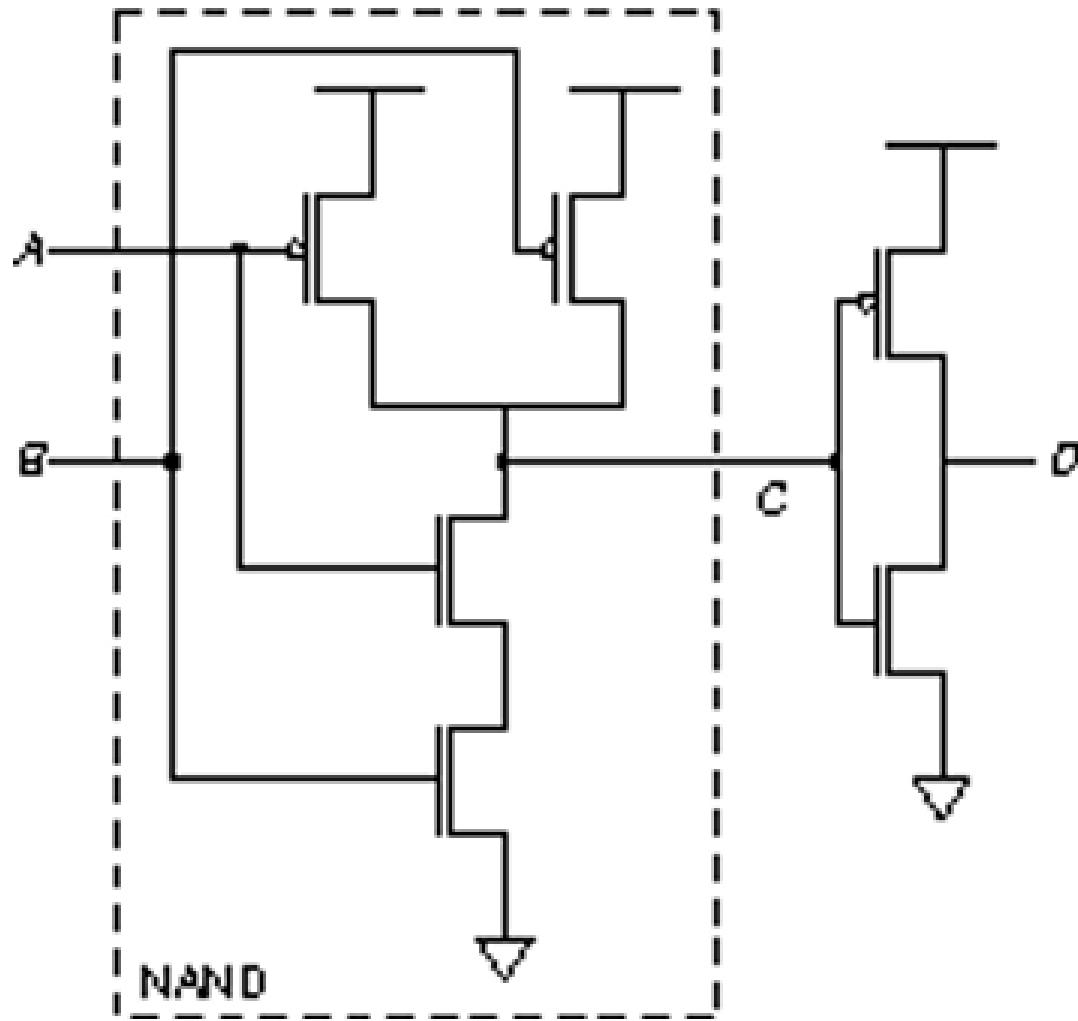


OR gate

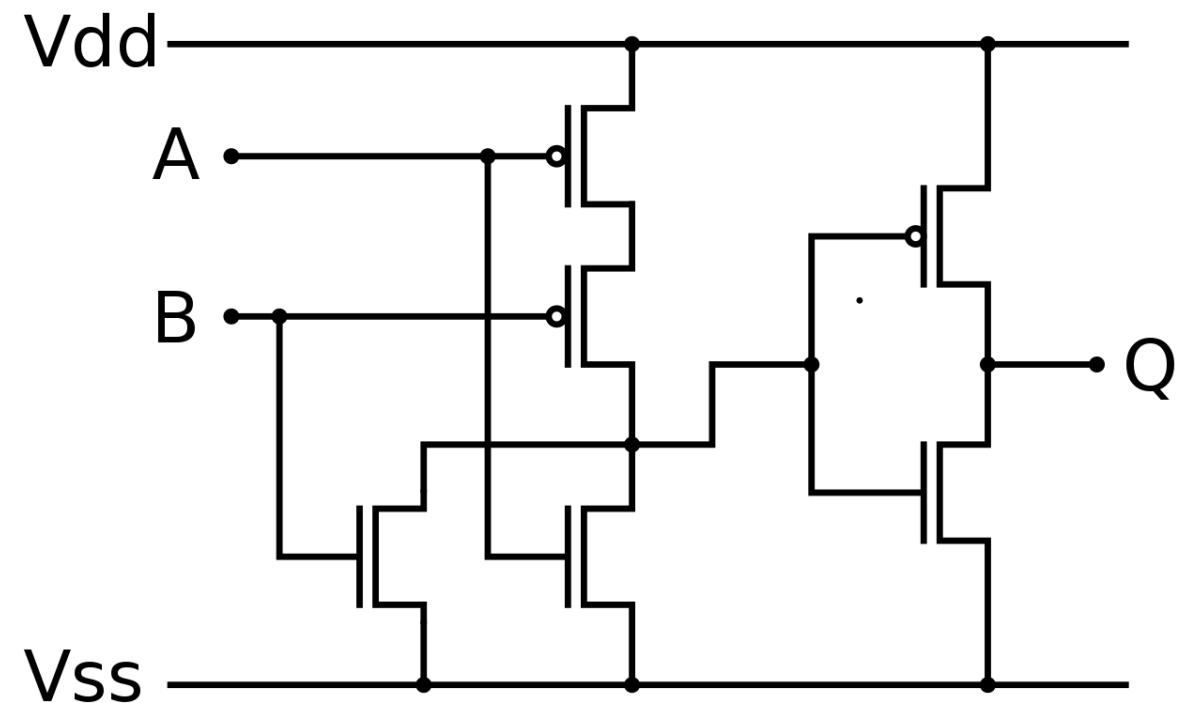


Implementing logic gates

3-input NAND gate

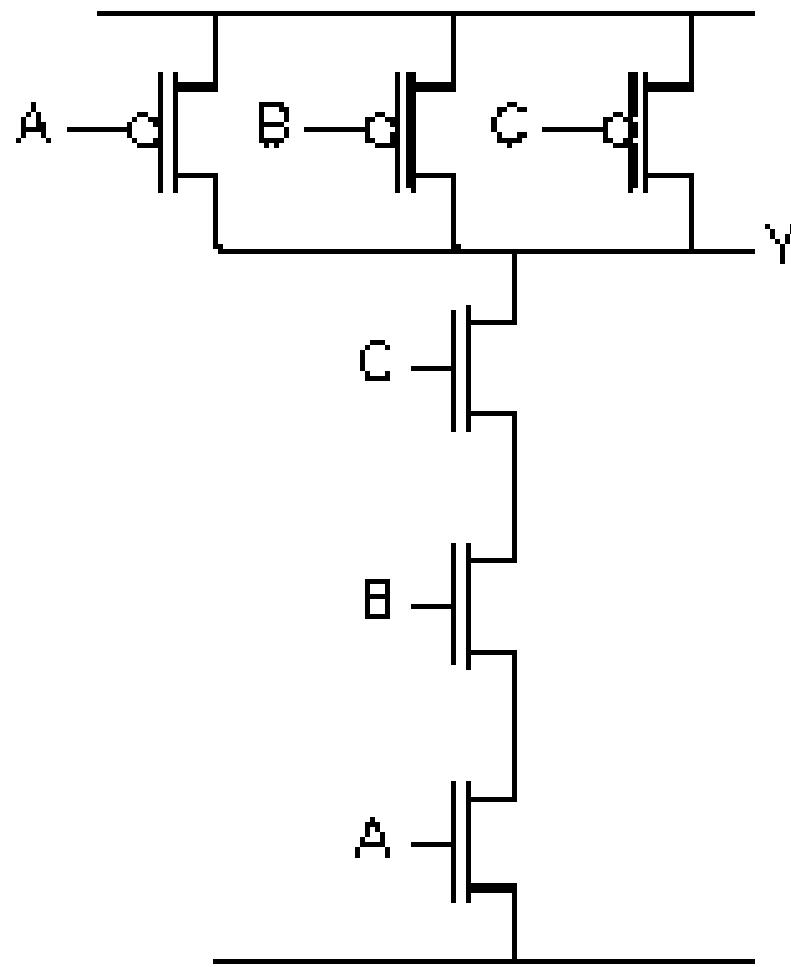

3-input NOR gate

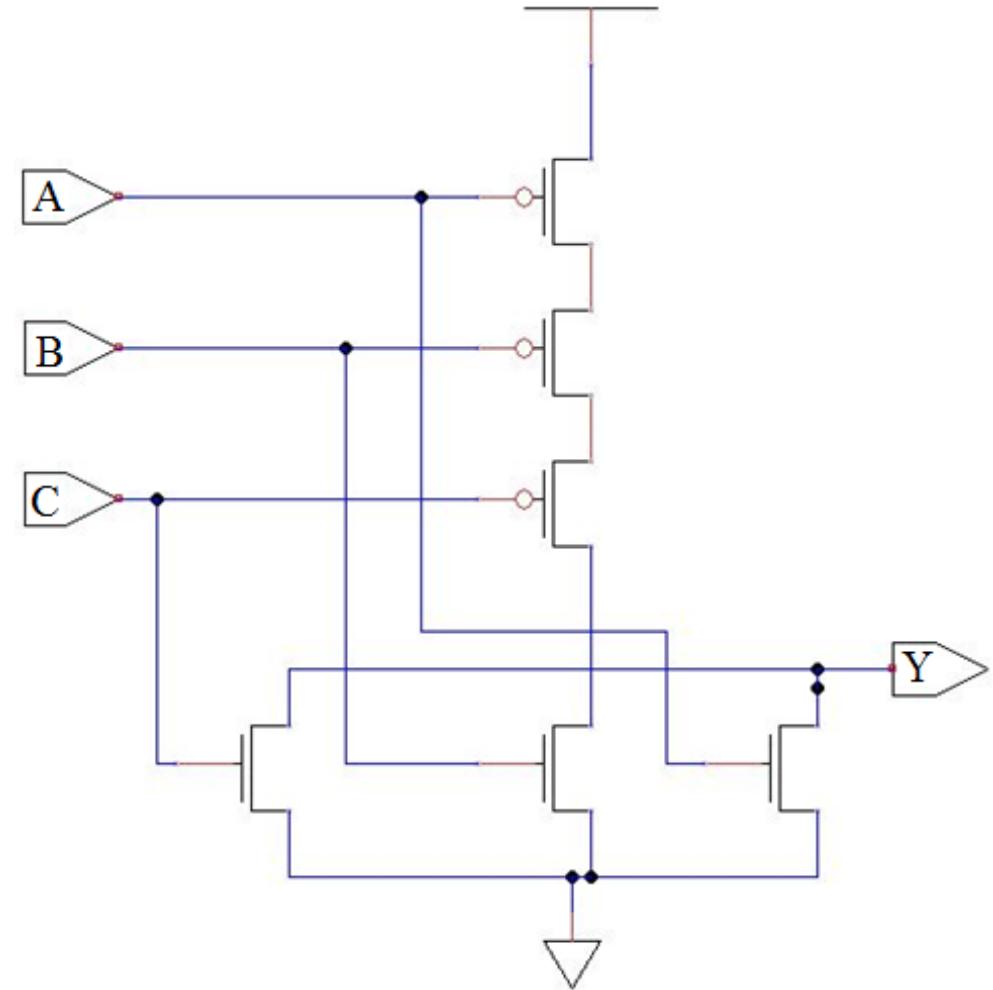

Circuit design

- The output binary functions listed in the truth table are simplified by any available method, such as algebraic manipulation, the map method, or a computer-based simplification program
- Frequently, there is a variety of simplified expressions from which to choose
- A practical designer must consider such constraints as the number of gates, number of inputs to a gate, propagation time of the signal through the gates, number of interconnections, limitations of the driving capability of each gate (i.e., the number of gates to which the output of the circuit may be connected), and various other criteria that must be taken into consideration when designing integrated circuits
- Since the importance of each constraint is dictated by the particular application, it is difficult to make a general statement about what constitutes an acceptable implementation
- In most cases, the simplification begins by satisfying an elementary objective, such as producing the simplified Boolean functions in a standard form
- Then the simplification proceeds with further steps to meet other performance criteria

Circuit design

- Say with everything else kept constant, we are most worried about the silicon area within which our design will fit
- To minimize the silicon real-estate needed, we have to reduce the number of transistors we use for a particular design – transistors are electronic switches that form the backbone of most of the modern day electronics
- A simple guide to remember:


Gate	Inputs	No of Transistors
NOT	1	2
NAND	N	2N
NOR	N	2N
AND	N	2N+2
OR	N	2N+2

The Other states

- This is REALLY important
- Apart from the two states of 0 and 1, there is a third state called the high impedance state denoted by Z
- When we say a particular pin is at HIGH or LOW state, we are assuming a driver behind it, i.e., the pin is *driven* to HIGH or LOW value
- This can be done through a transistor connecting the pin to either ground or Vcc
- However, if we do not connect a pin to either of HIGH or LOW, the pin is said to be in high impedance state or in Z state
- This concept is used extensively in the digital logic world to control buses

The Other states

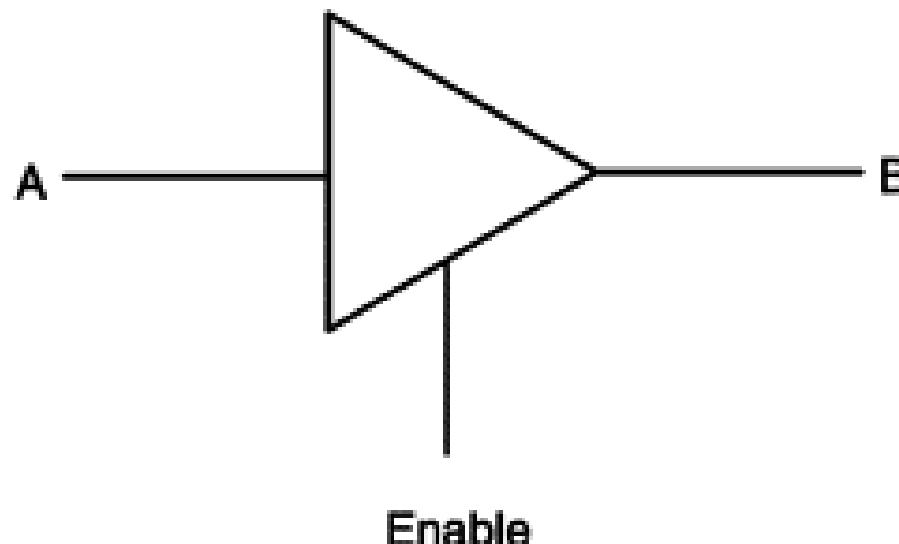- Most logic gates only output HIGH or LOW, the third state is generally obtained using tristate buffers
- These are used just before the bus connections



Enable	A	B
0	0	Z
0	1	Z
1	0	0
1	1	1

The Other states

- Another choice is that we can have either 0 or 1 (not both together, of course!)
- This is called the don't care state – or a condition in the logic function that follows that we do not care what the output in a particular case is, i.e., for a particular set of inputs
- This is represented as X
- This can be either 0 or 1 and both are equally acceptable while forming logic circuits for a given function

The Other states

- Consider a simple two variable statement: If A, then what is B?
- One way we can interpret this: we need to know the value of B when A is TRUE, but when A is FALSE, we DON'T CARE!
- If this is the case, we can make the truth table for the function as shown
- In this case, because X can take either 0 or 1 value, we can simply make the desired function using an AND gate or as transfer of B

A	B	F
0	0	X
0	1	X
1	0	0
1	1	1

The Other states

- Simplify the Boolean function

$$F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$$

- We have one cluster of four: yz and one cluster of two: $w'x'z$

- Thus, the function is

$$F = yz + w'x'z$$

		yz			
		00	01	y	
		m_0	m_1	m_3	m_2
w	00	0	1	1	0
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}
x					
z					

The Other states


- Now, consider the same function

$$F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$$

- which has the don't-care conditions

$$d(w, x, y, z) = \sum(0, 2, 5)$$

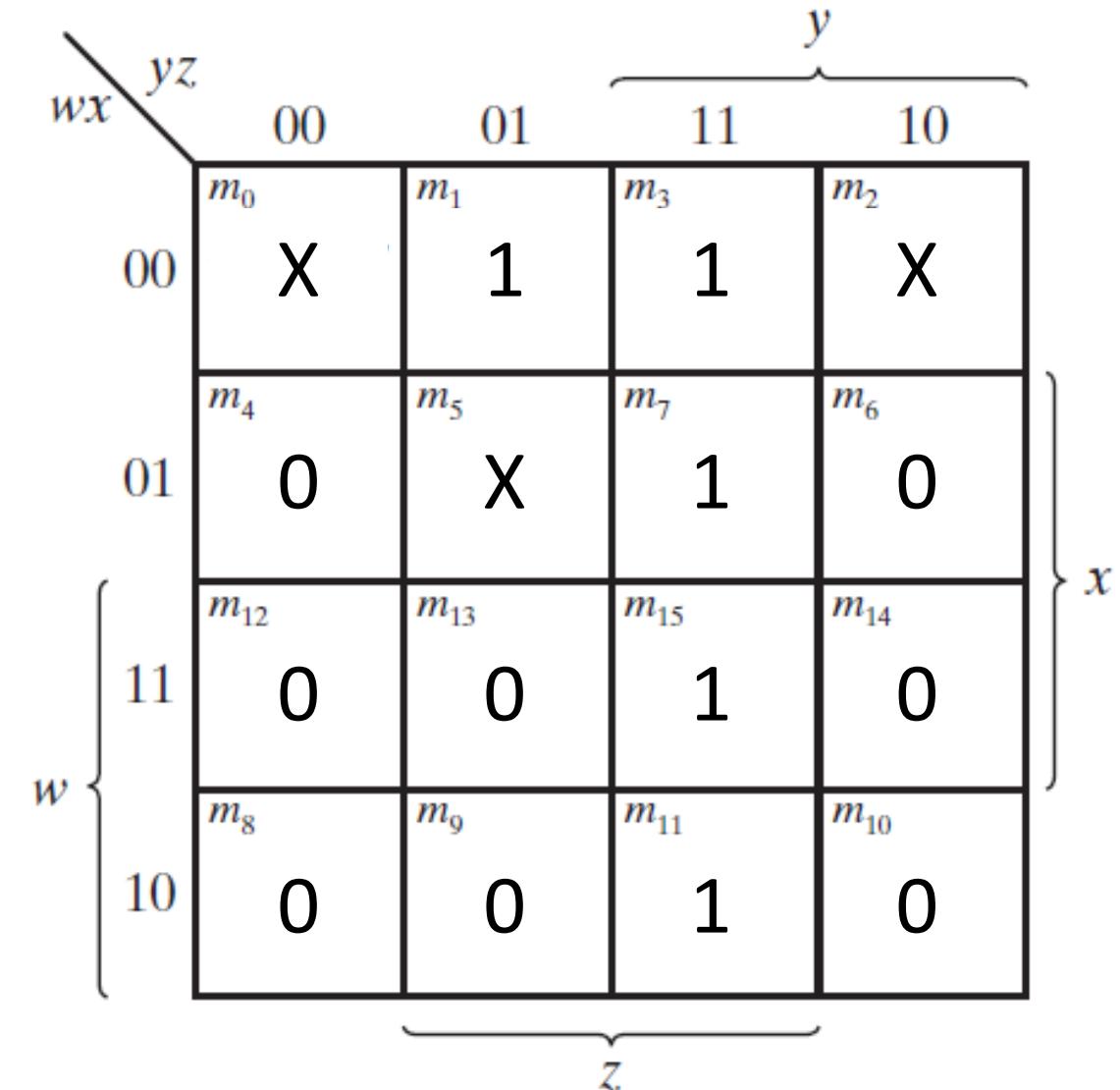- Now, we have two clusters of four squares: yz and $w'z$
- This is because m_5 can be 1, and it is ok if m_0 and m_2 are 0
- Thus, the function is $F = yz + w'z$
- The function can also be simplified as $F = yz + w'x'$



The Other states

- Functions $F = yz + w'z$ and $F = yz + w'x'$ are different functions
- However, both expressions include minterms 1, 3, 7, 11, and 15 that make the function F equal to 1
- The don't-care minterms 0, 2, and 5 are treated differently in each expression
- The first expression includes minterms 0 and 2 with the 1's and leaves minterm 5 with the 0's
- The second expression includes minterm 5 with the 1's and leaves minterms 0 and 2 with the 0's
- The two expressions represent two functions that are not equal but follow the logic statement

		yz			
		wx		00	01
				m_0	m_1
w	00	X		1	1
	01	m_4	m_5	X	1
	11	m_{12}	m_{13}	0	0
	10	m_8	m_9	0	0
		y		z	
		0	1	11	
				10	10

The Other states


- The key question is: Are these the simplest possible representations for the given function? $F = yz + w'z$ and $F = yz + w'x'$
- What if we look at the product of sum simplification?
- We can get a cluster of 8 squares: z'
- And a cluster of four squares: wy'
- Thus, the function can be represented as $F = z(w' + y)$

A Karnaugh map for a function of four variables (w, x, y, z). The variables are mapped to binary values as follows: w (vertical axis), x (inner vertical axis), y (outer horizontal axis), and z (inner horizontal axis). The map is a 4x4 grid of cells, each labeled with a minterm m_i or a don't care ('X'). The minterms are: $m_0 = X$, $m_1 = 1$, $m_3 = 1$, $m_2 = X$; $m_4 = 0$, $m_5 = X$, $m_7 = 1$, $m_6 = 0$; $m_{12} = 0$, $m_{13} = 0$, $m_{15} = 1$, $m_{14} = 0$; $m_8 = 0$, $m_9 = 0$, $m_{11} = 1$, $m_{10} = 0$. The map shows a cluster of 8 squares (minterms 0, 1, 3, 4, 5, 7, 12, 13) and a cluster of 4 squares (minterms 14, 15, 10, 11).

		yz	
		00	01
wx		00	01
m_0		X	
m_1		1	
m_3		1	
m_2		X	
m_4		0	
m_5		X	
m_7		1	
m_6		0	
m_{12}		0	
m_{13}		0	
m_{15}		1	
m_{14}		0	
m_8		0	
m_9		0	
m_{11}		1	
m_{10}		0	


ExOR gate

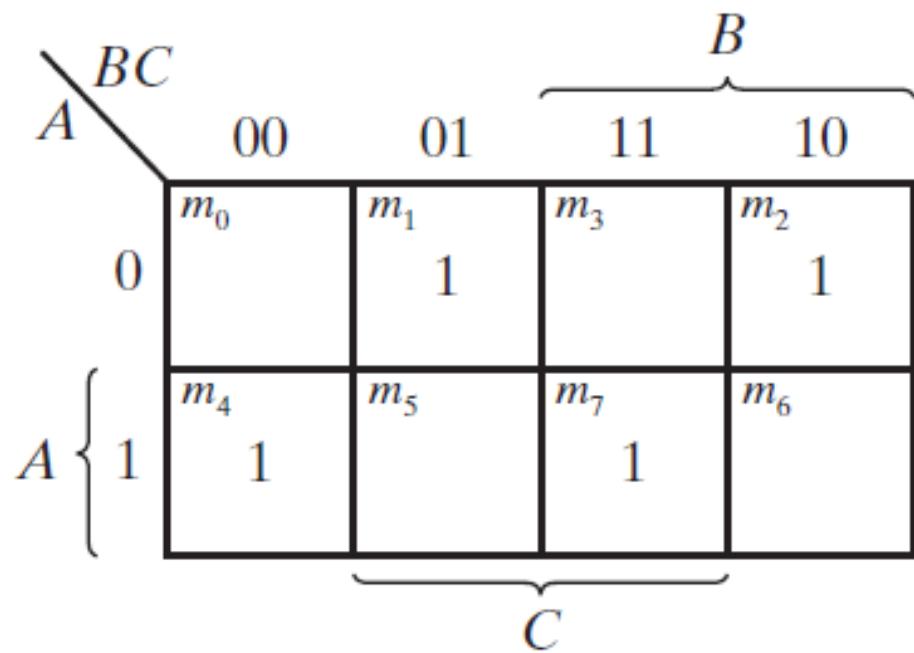- ExOR is weird because there is no easy way to simplify the function using K-maps



A K-map for a 2-variable ExOR function. The horizontal axis is labeled B and the vertical axis is labeled A . The axes are labeled BC at the top-left corner. The horizontal axis is divided into four cells labeled 00, 01, 11, and 10. The vertical axis is divided into two cells labeled 0 and 1. The cells are filled with minterms: m_0 , m_1 , m_3 , m_2 in the top row; and m_4 , m_5 , m_7 , m_6 in the bottom row. A bracket labeled C spans the width of the bottom row.

		B			
		00	01	11	10
A		m_0	m_1	m_3	m_2
A	0		1		1
	1	1		1	


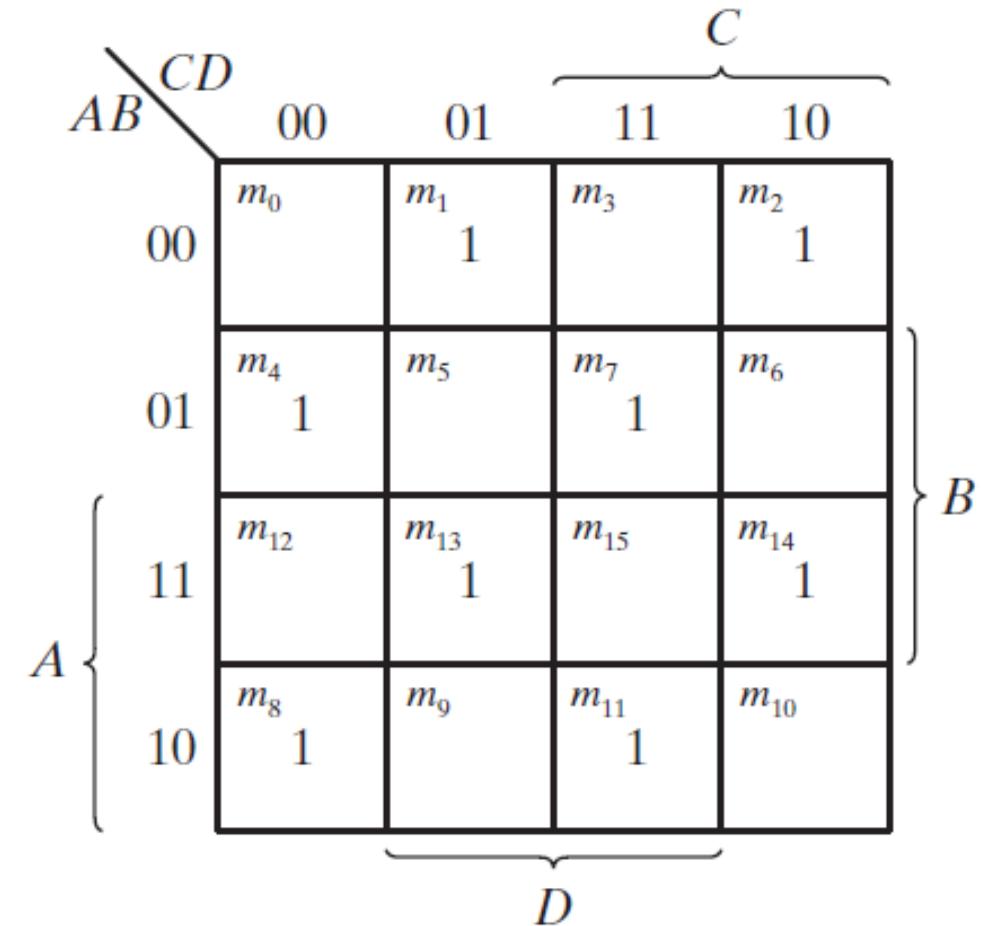


A K-map for a 4-variable ExOR function. The horizontal axis is labeled CD and the vertical axis is labeled A . The horizontal axis is divided into four cells labeled 00, 01, 11, and 10. The vertical axis is divided into four cells labeled 00, 01, 11, and 10. The cells are filled with minterms: m_0 , m_1 , m_3 , m_2 in the top row; m_4 , m_5 , m_7 , m_6 in the second row; m_{12} , m_{13} , m_{15} , m_{14} in the third row; and m_8 , m_9 , m_{11} , m_{10} in the bottom row. Brackets labeled C and D span the width of the top and bottom rows respectively. Brackets labeled B and A span the height of the first and last columns respectively.

		CD			
		00	01	11	10
A		m_0	m_1	m_3	m_2
A	0		1		1
	1	1		1	

ExOR gate

- ExOR is weird because there is no easy way to simplify the function using K-maps

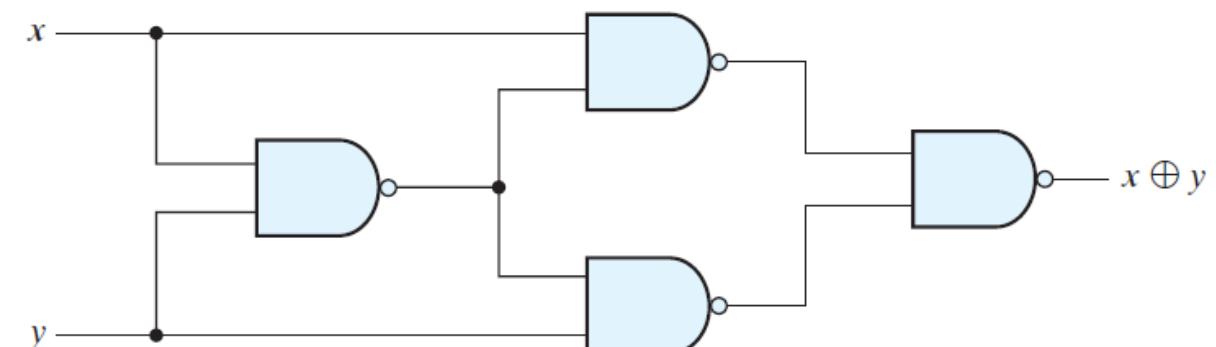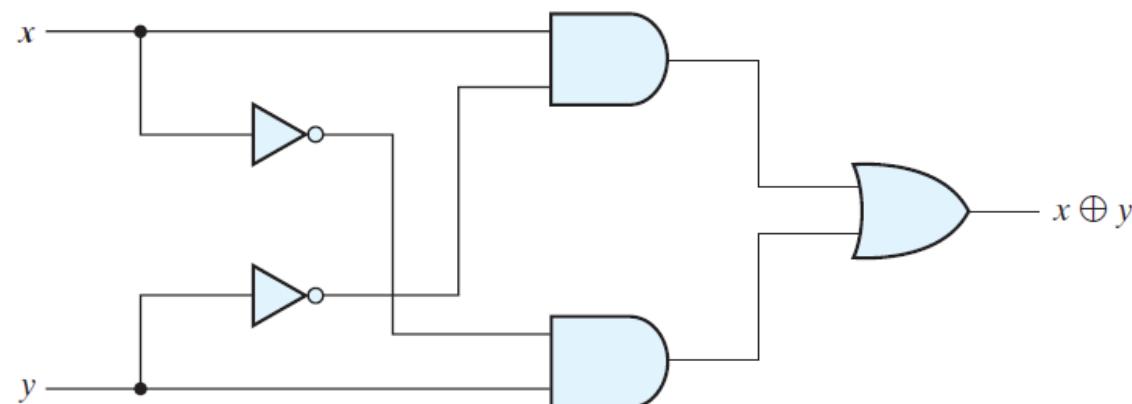


Lecture 12 – Combinational logic circuits

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST


Multiplexer

- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line
- The selection of a particular input line is controlled by a set of selection lines
- Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected
- A two-to-one-line multiplexer connects one of two 1-bit sources to a common destination
- The multiplexer acts like an electronic switch that selects one of two sources
- The block diagram of a multiplexer (also called MUX) is sometimes depicted by a wedge-shaped symbol

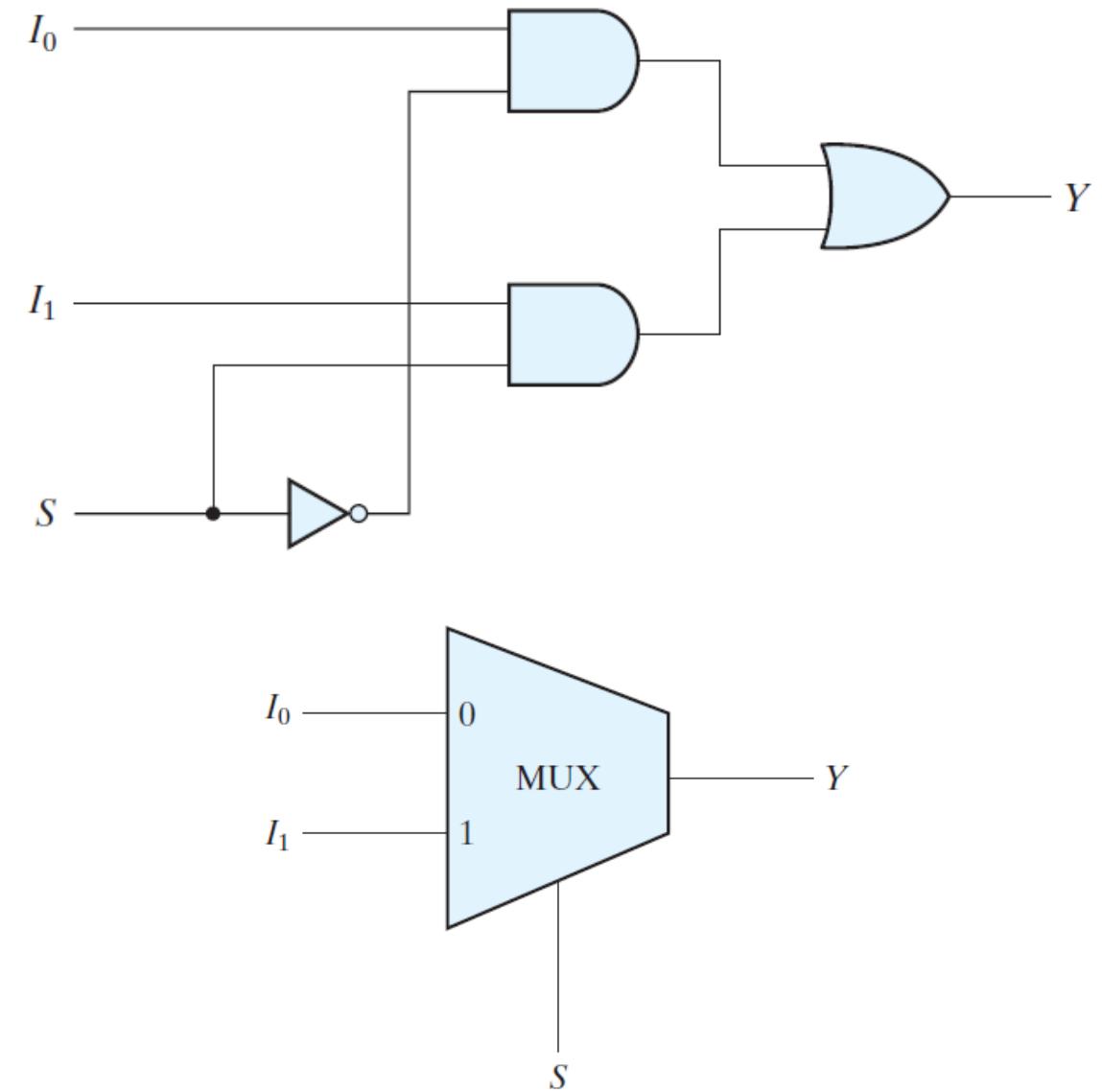


Multiplexer

- Similarly, we can make a four-to-one-line multiplexer
- Each of the four inputs, I_0 through I_3 , is applied to one input of an AND gate
- The outputs of the AND gates are applied to a single OR gate that provides the one-line output
- A multiplexer is also called a *data selector*, since it selects one of many inputs and steers the binary information to the output line
- In general, a 2^n -to-1-line multiplexer is constructed ANDing each input line with 2^n minterms
- The outputs of the AND gates are applied to a single OR gate

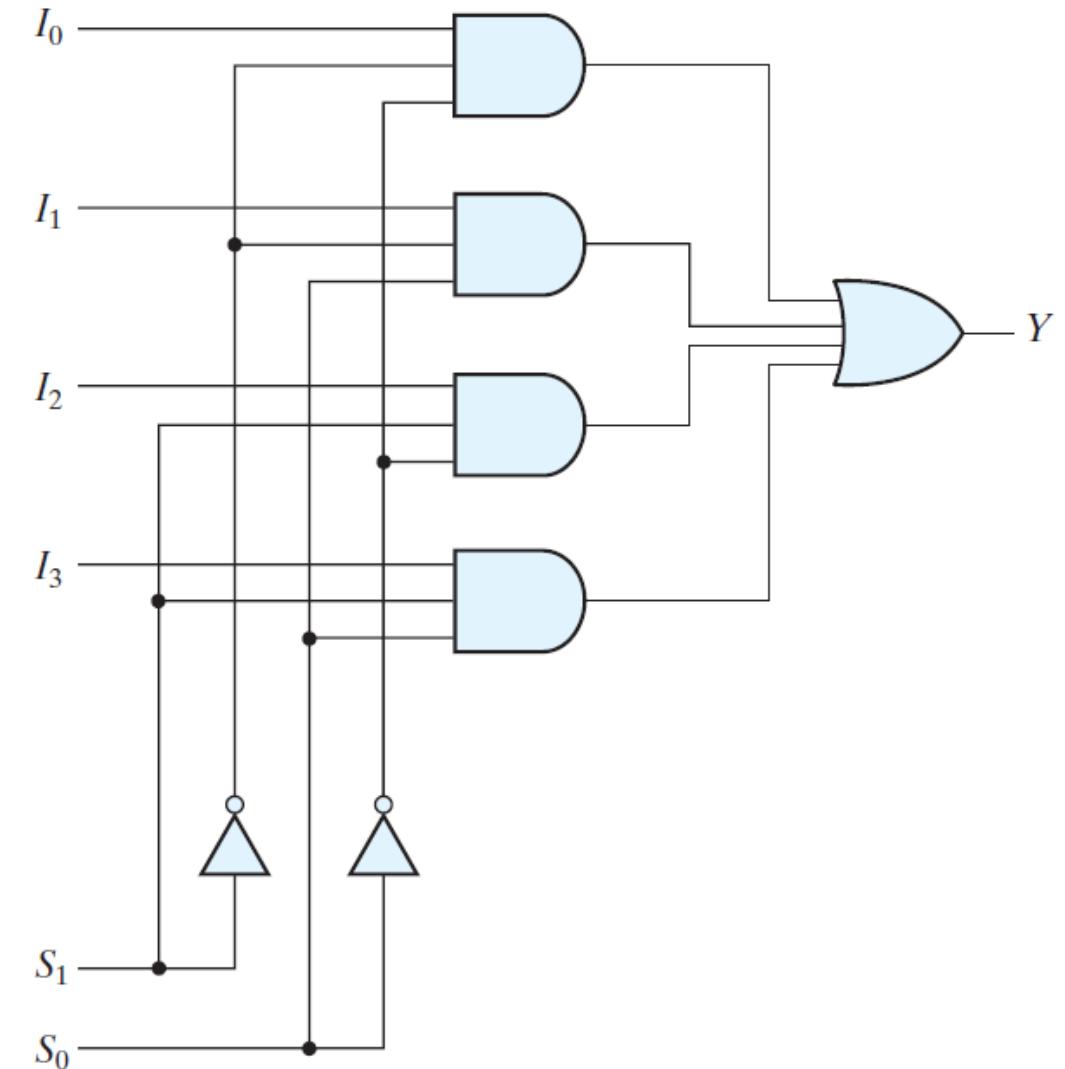


Multiplexer

- We can use MUXes to implement Boolean functions
- The minterms of a function are generated in a multiplexer by the circuit associated with the selection inputs
- The individual minterms can be selected by the data inputs, thereby providing a method of implementing a Boolean function of n variables with a multiplexer that has n selection inputs and 2^n data inputs, one for each minterm
- Example: implement EXOR

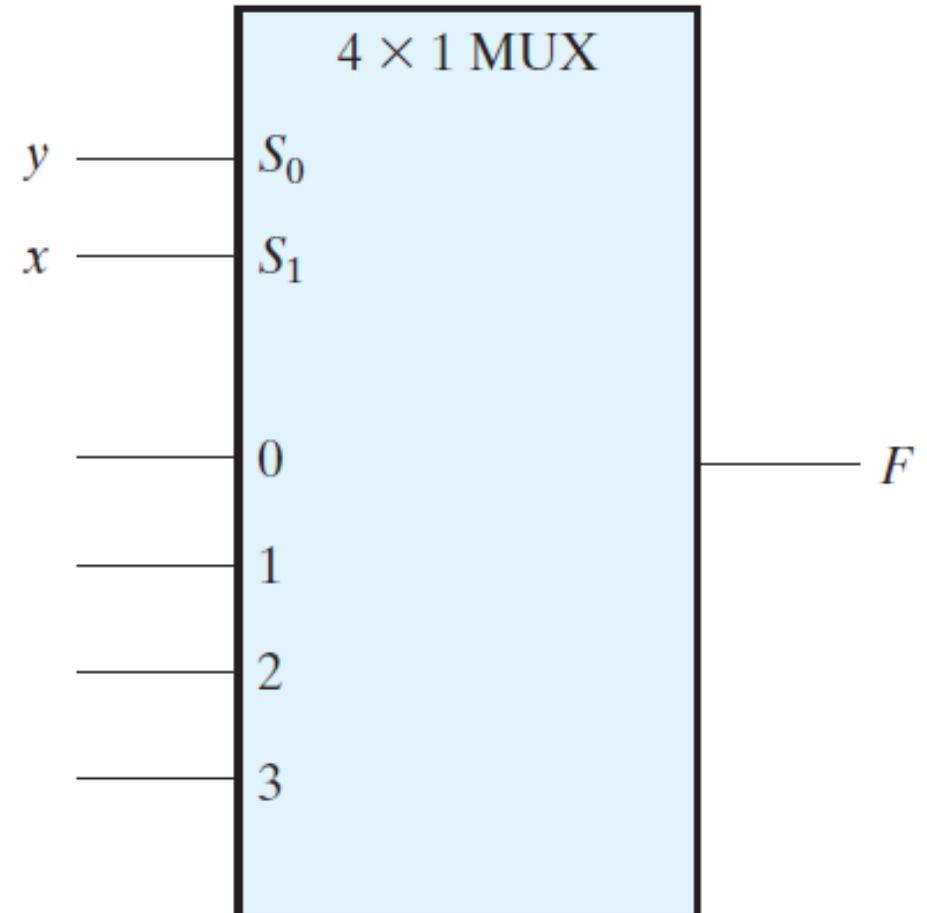

Multiplexer

- There is a neat trick to obtain a more efficient method for implementing a Boolean function of n variables with a multiplexer that has $n - 1$ selection inputs
- The first $n - 1$ variables of the function are connected to the selection inputs of the multiplexer
- The remaining single variable of the function is used for the data inputs
- Say we have a three variable function $F(x,y,z)$
- We take a 4to1 MUX (with two input select lines) and each data input of the multiplexer will be z , z' , 1, or 0

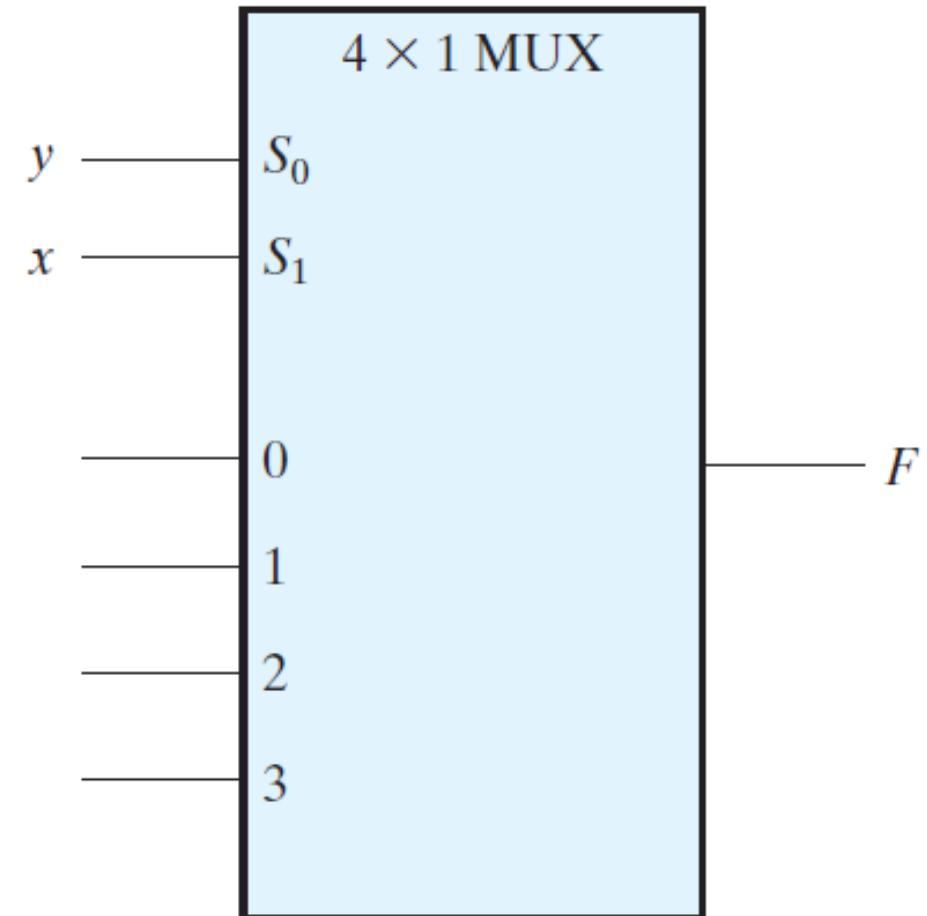


Multiplexer

- Consider the function:

$$F(x, y, z) = \sum(1, 4, 5, 6)$$

- This function of three variables can be implemented with a four-to-one-line multiplexer
- The two variables x and y are applied to the selection lines in that order; x is connected to the S_1 input and y to the S_0 input
- The values for the data input lines are determined from the truth table of the function
- When $xy = 00$, output F is equal to z because $F = 0$ when $z = 0$ and $F = 1$ when $z = 1$
- This requires that variable z be applied to data input 0
- In a similar fashion, we can determine the required input to data lines 1, 2, and 3 from the value of F when $xy = 01, 10$, and 11 , respectively

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

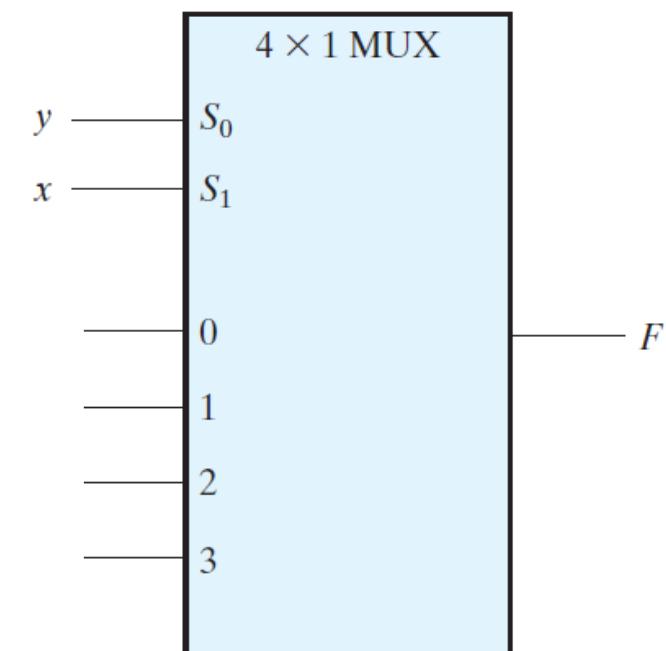

Multiplexer

- The general procedure for implementing any Boolean function of n variables with a multiplexer with $n - 1$ selection inputs and 2^{n-1} data inputs follows from the previous example
 1. To begin with, Boolean function is listed in a truth table
 2. Then the most significant $n - 1$ variables in the table are applied to the selection inputs of the multiplexer
 3. For each combination of the selection variables, we evaluate the output as a function of the last variable
 4. This function can be 0, 1, the variable, or the complement of the variable
 5. These values are then applied to the data inputs in the proper order


$$F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$$

Multiplexer

- The general procedure for implementing any Boolean function of n variables with a multiplexer with $n - 1$ selection inputs and 2^{n-1} data inputs follows from the previous example
- To begin with, Boolean function is listed in a truth table
 - Then the most significant $n - 1$ variables in the table are applied to the selection inputs of the multiplexer
 - For each combination of the selection variables, we evaluate the output as a function of the last variable
 - This function can be 0, 1, the variable, or the complement of the variable
 - These values are then applied to the data inputs in the proper order


$$F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$$

A	B	C	D	F
0	0	0	0	0 $F = D$
0	0	0	1	1
0	0	1	0	0 $F = D$
0	0	1	1	1
0	1	0	0	1 $F = D'$
0	1	0	1	0
0	1	1	0	0 $F = 0$
0	1	1	1	0
1	0	0	0	0 $F = 0$
1	0	0	1	0
1	0	1	0	0 $F = D$
1	0	1	1	1
1	1	0	0	1 $F = 1$
1	1	0	1	1
1	1	1	0	1 $F = 1$
1	1	1	1	1

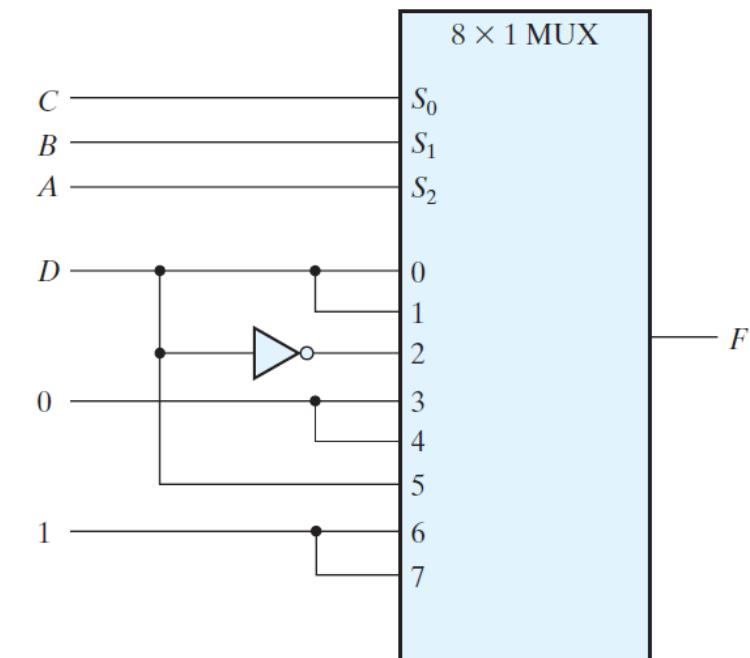

Demultiplexer

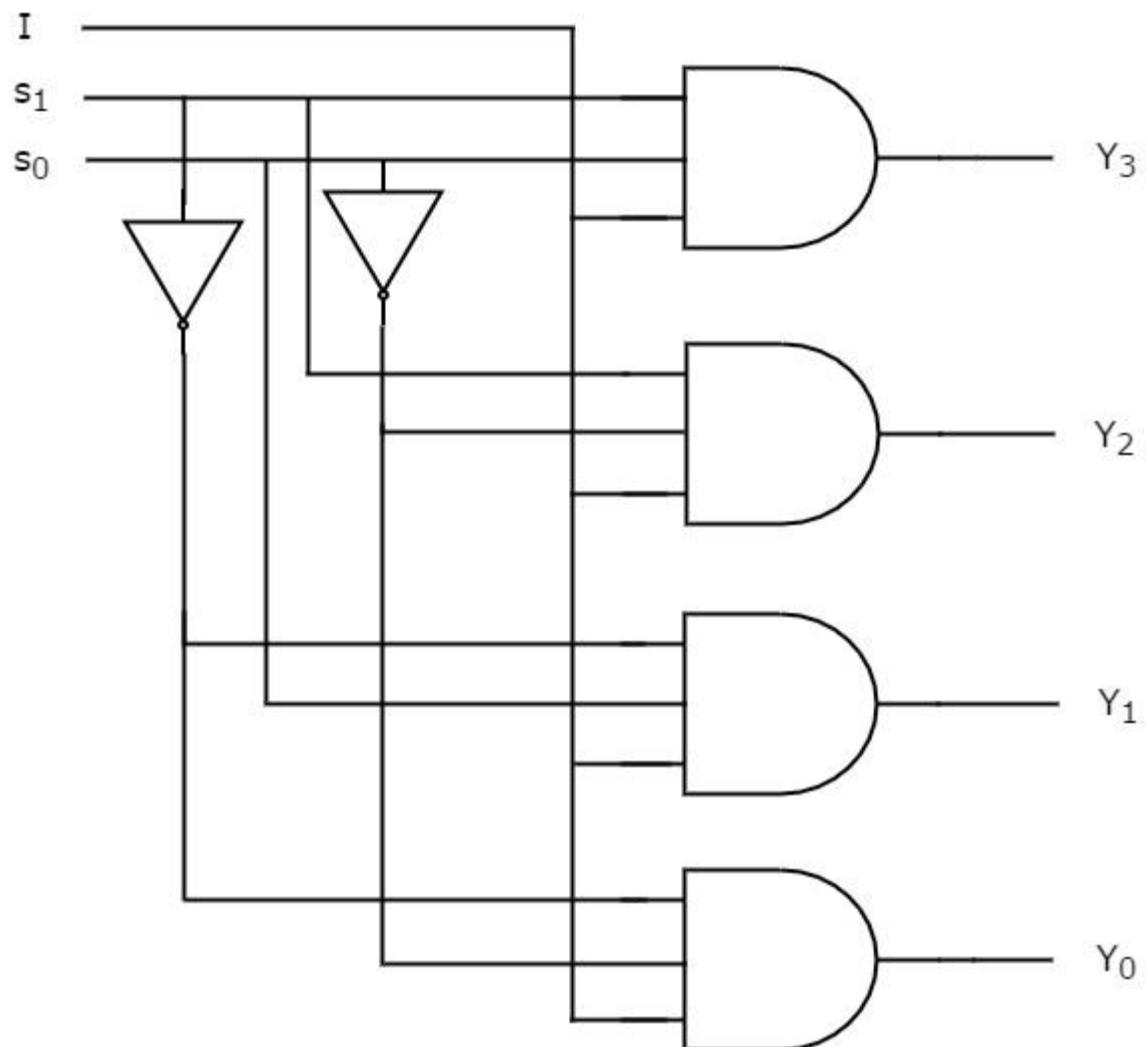- Demultiplexers do the exact opposite of MUX operation – take a single line input and direct it to an output line depending on the select line input
- 1to 2^n Demux will have n select lines
- We again make minterms from the available inputs and AND it with the single data line
- Based on the input signals the particular output is connected to the data line and all other outputs are zero




Combinational circuits

- Logic circuits for digital systems may be combinational or sequential
- A combinational circuit consists of logic gates whose outputs at any time are determined from only the present combination of inputs
- A combinational circuit performs an operation that can be specified logically by a set of Boolean functions
- In contrast, sequential circuits employ storage elements in addition to logic gates
- Their outputs are a function of the inputs and the state of the storage elements
- Because the state of the storage elements is a function of previous inputs, the outputs of a sequential circuit depend not only on present values of inputs, but also on past inputs, and the circuit behavior must be specified by a time sequence of inputs and internal states


Combinational circuits

- A combinational circuit consists of an interconnection of logic gates
- Combinational logic gates react to the values of the signals at their inputs and produce the value of the output signal, transforming binary information from the given input data to a required output data
- Each input and output variable exists physically as an analog signal whose values are interpreted to be a binary signal that represents logic 1 and logic 0

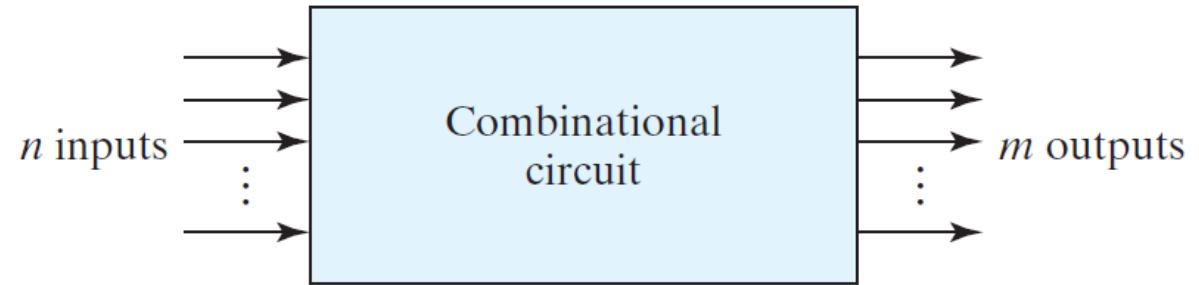

Combinational circuits

- For n input variables, there are 2^n possible combinations of the binary inputs
- For each possible input combination, there is one possible value for each output variable
- Thus, a combinational circuit can be specified with a truth table that lists the output values for each combination of input variables
- A combinational circuit also can be described by m Boolean functions, one for each output variable
- Each output function is expressed in terms of the n input variables

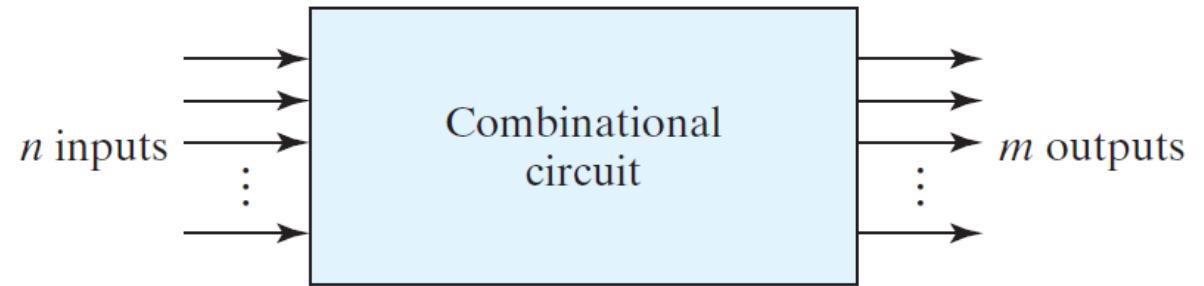

Circuit design

- The design of combinational circuits starts from the specification of the design objective and culminates in a logic circuit diagram or a set of Boolean functions from which the logic diagram can be obtained
- The procedure involves the following steps:
 1. From the specifications of the circuit, determine the required number of inputs and outputs and assign a symbol to each
 2. Derive the truth table that defines the required relationship between inputs and outputs
 3. Make the K-map, if necessary
 4. Obtain the simplified Boolean functions for each output as a function of the input variables
 5. Draw the logic diagram and verify the correctness of the design (manually or by simulation)


Here. We. Go.



The 7-Segment Decoder


7-segment decoder

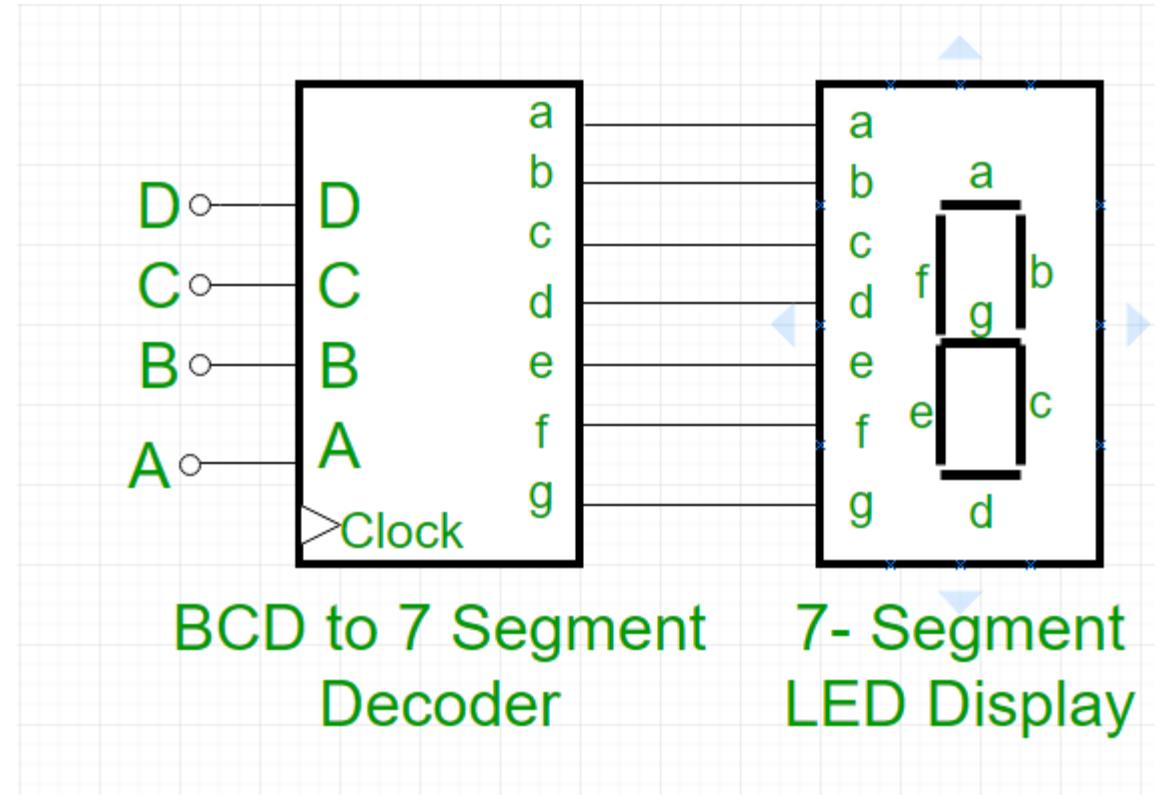- We discussed many ways of representing symbols using binary variables – signed magnitude, 2's complement, BCD, ASCII etc.
- Going from one representation may be considered as an encoding/decoding operation
- Consider the practical problem of displaying binary numbers using a 7-segment LED display
- For this, we need to “decode” the binary information into the display inputs




7-segment decoder

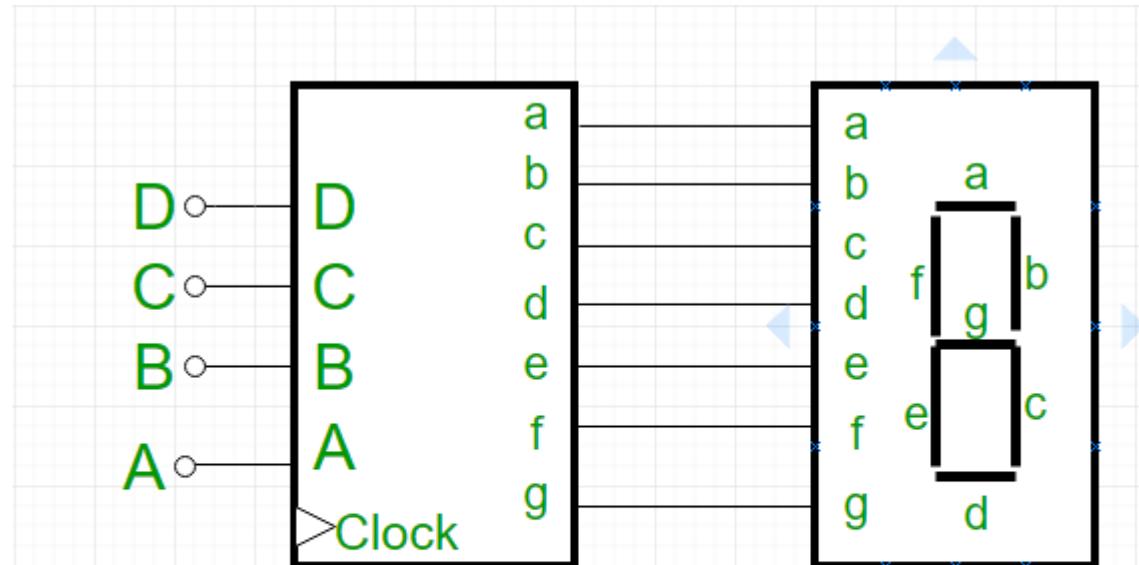- First, we realize that there are 4 inputs and 7 outputs!
- Thus, the truth-table will be a 16 row table with 7 different columns for 7 outputs
- Hence, there will be 7 different functions we will be implementing to make this decoder
- The other thing we need to realize is whether a particular output should be HIGH or LOW for the LED to glow?





BCD to 7 Segment
Decoder

7- Segment
LED Display

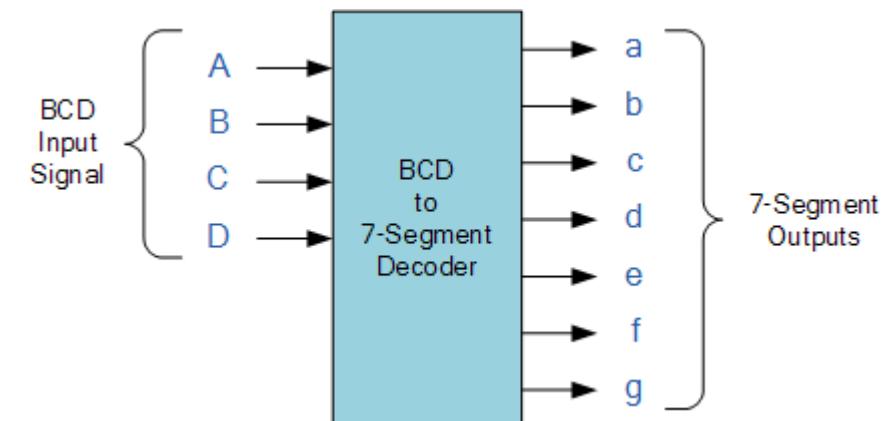


7-segment decoder

- The other thing we need to realize is whether a particular output should be HIGH or LOW for the LED to glow?
- To know the answer to this, we see that there are two types of 7-segment LED displays – common anode and common cathode
- The common cathode connects all LED cathodes to a common ground, thus, when input is high LED glows
- Conversely, the common anode connects all LED anodes to $+V_{cc}$, thus, when input is low, LED glows

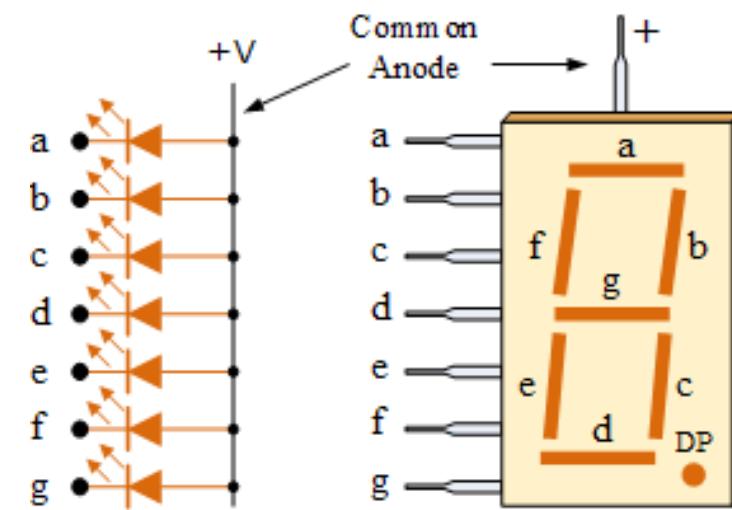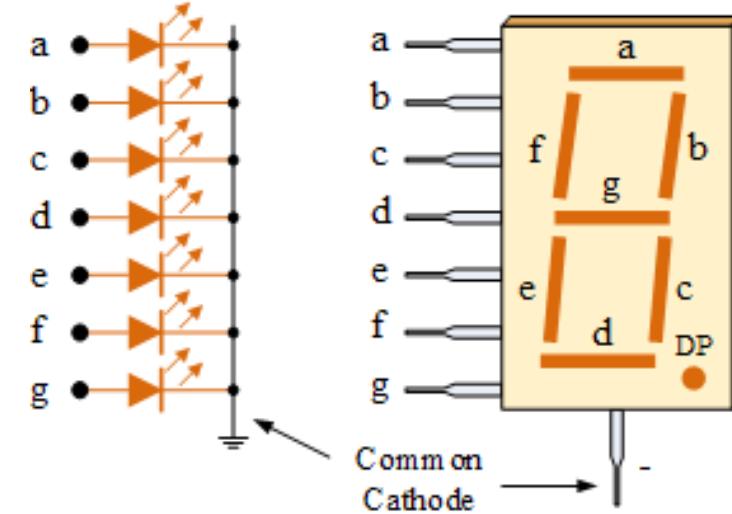

7-segment decoder

- Let us choose common cathode LED display to make the function
- Thus, we can make the truth-table
- Obviously, the BCD system only goes from 0 to 9, while we have 16 rows for 4 inputs
- What about the other rows?
- In the other rows, we fill all the outputs as don't care, because we are sure that these are not going to be input anyway (trust the engineer before you)
- Thus, we have six don't care conditions

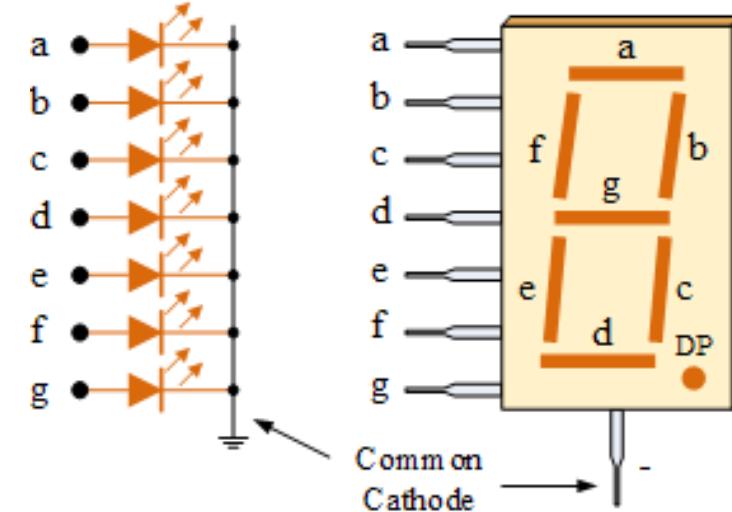


A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	1	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

Lecture 13 – Combinational logic circuits 2

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

7-segment decoder

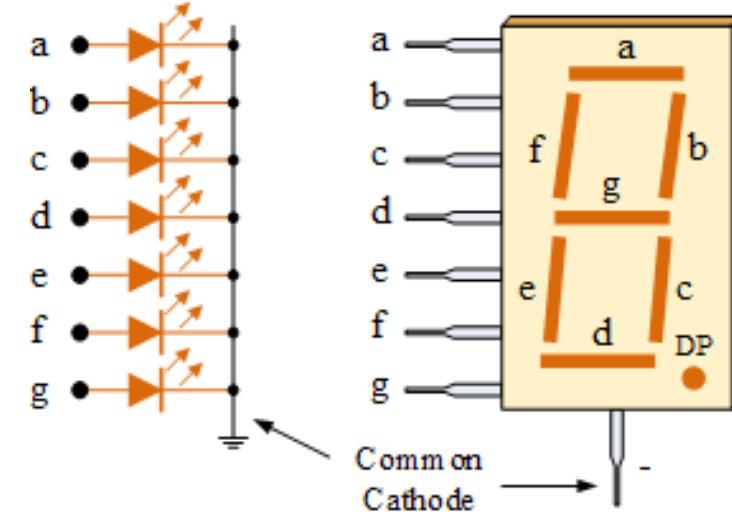
- Let us choose common cathode LED display to make the function
- Thus, we can make the truth-table
- Obviously, the BCD system only goes from 0 to 9, while we have 16 rows for 4 inputs
- In the other rows, we fill all the outputs as don't care, because we are sure that these are not going to be input anyway (trust the engineer before you)
- Thus, we have six don't care conditions



A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	1	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

7-segment decoder

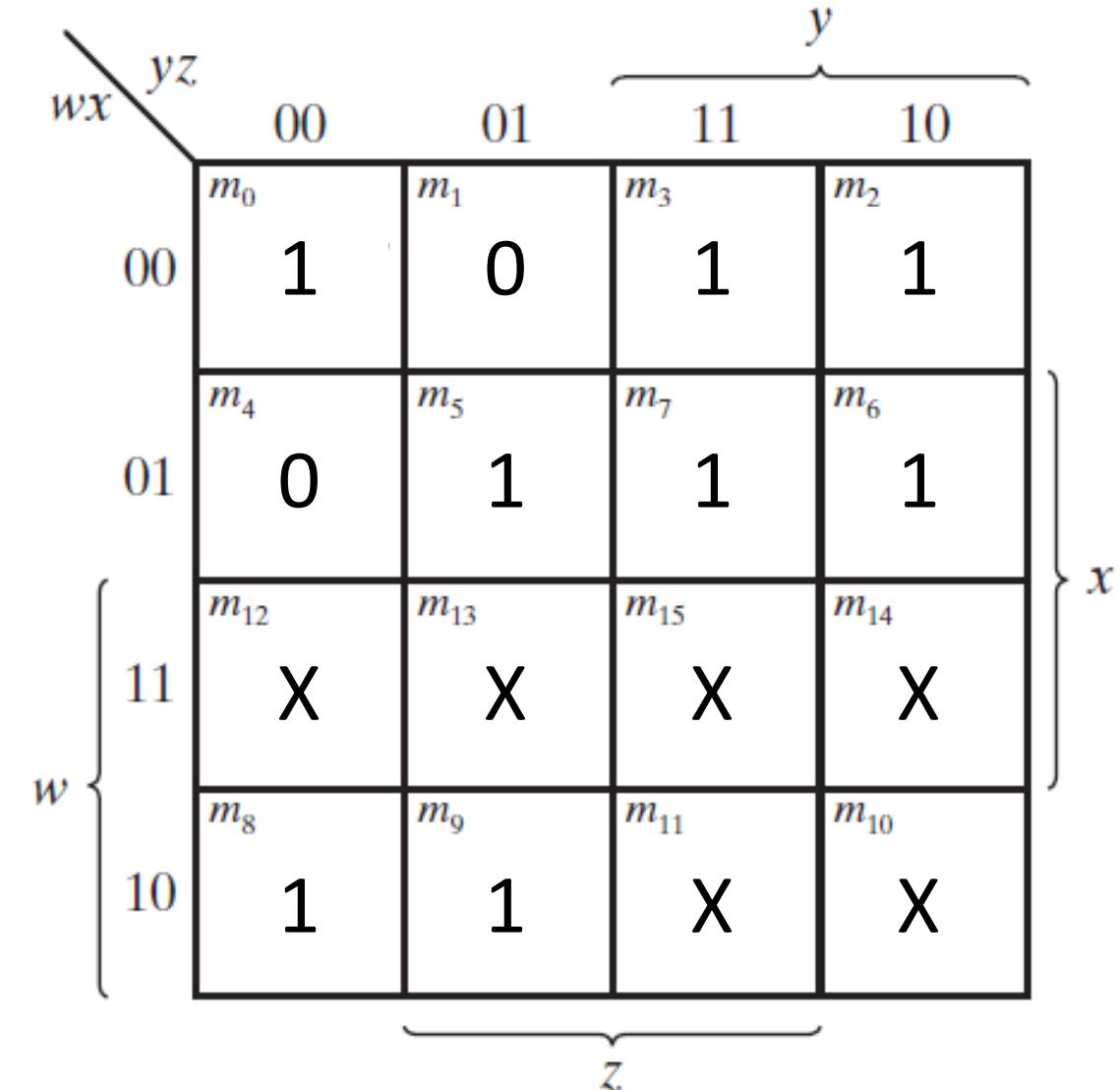
- Thus, the K-map for output a will look like this
- We have two clusters of 8: y and w
- Two clusters of four: xz and $x'z'$
- Thus, the logic function for a can be:
$$F_a = y + w + xz + x'z'$$
- Or we can have PoS as:
- One cluster of two: $xy'z'$
- One min-term: $w'x'y'z$
- Thus,
$$F_a = (x' + y + z)(w + x + y + z')$$
- This can be done for all the other outputs






7-segment decoder

- Thus, the K-map for output c will look like this
- We have only one zero, so we go the PoS route
- The max term cluster of two is represented by $yz'x'$
- In PoS form:

$$c = y' + z + x$$

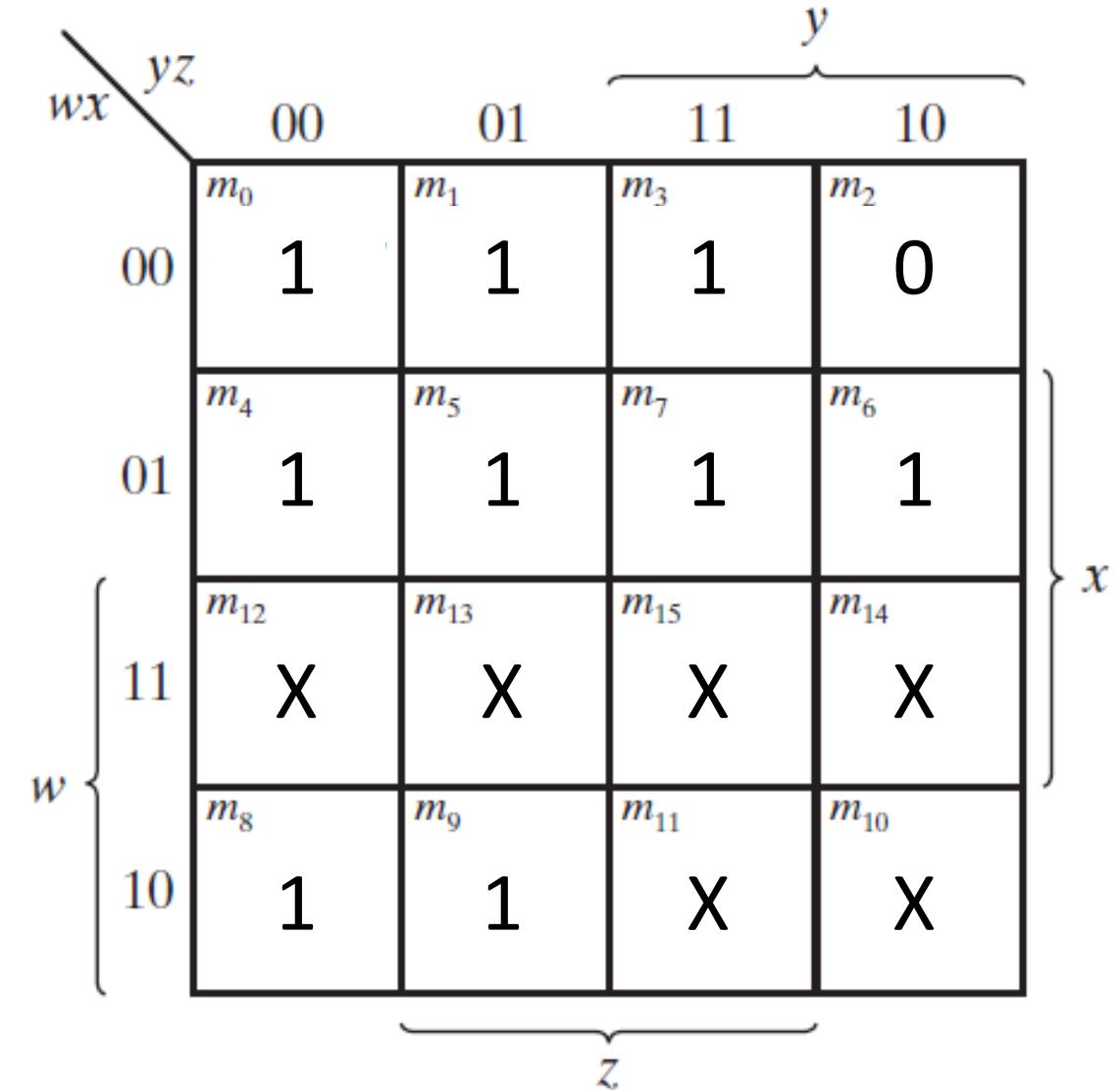

7-segment decoder

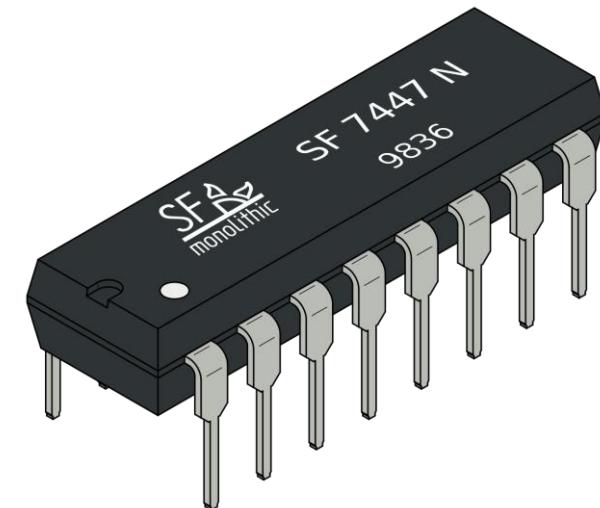
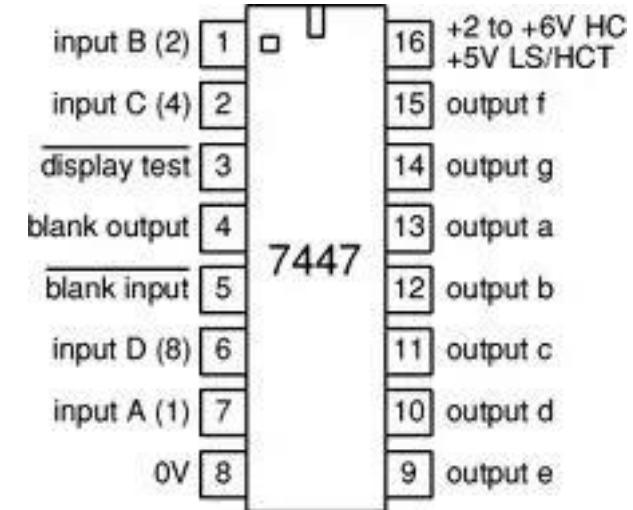
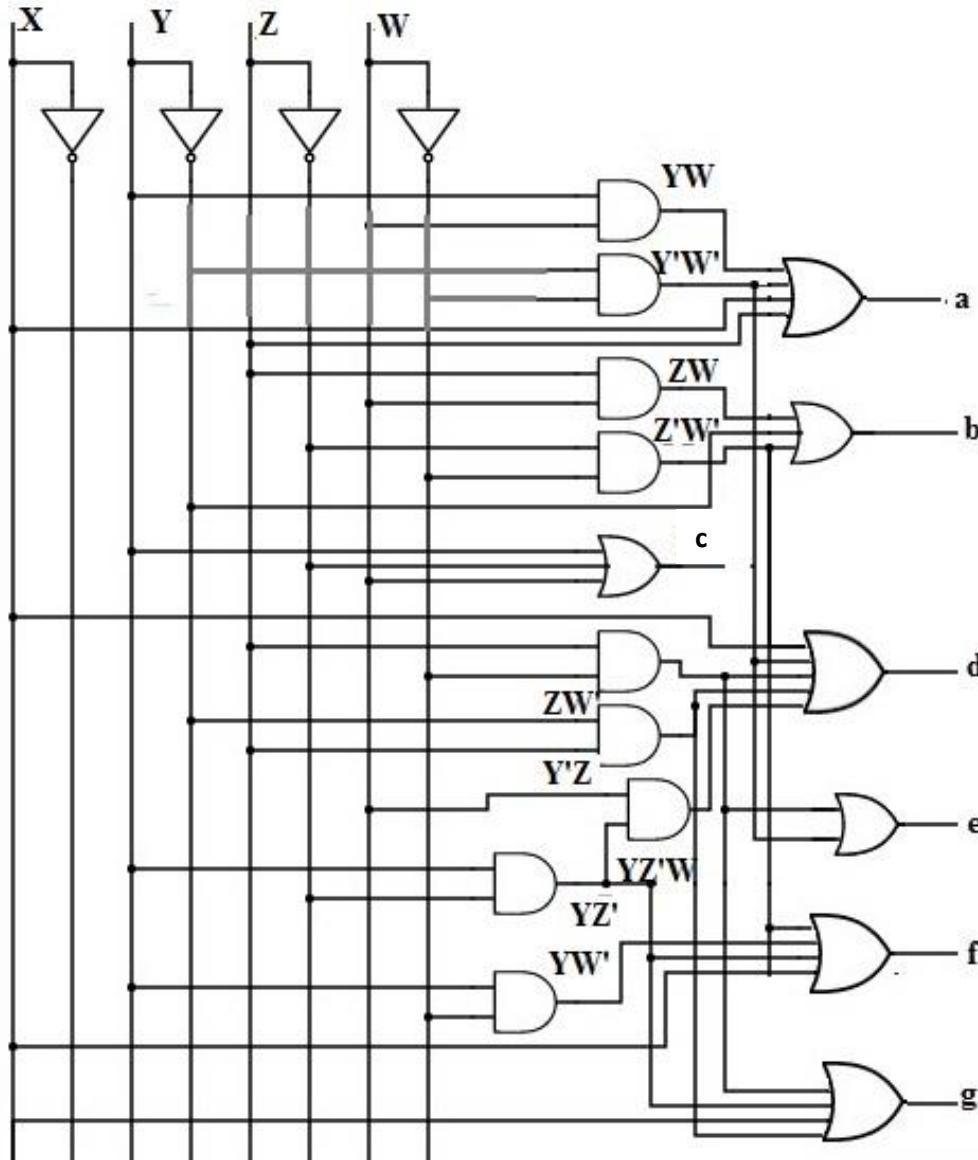




The Binary Adder


Binary adder

- Digital computers perform a variety of information-processing tasks
- Among the functions encountered are the various arithmetic operations
- The most basic arithmetic operation is the addition of two binary digits
- A combinational circuit that performs the addition of two bits is called a *half adder*.
- One that performs the addition of three bits (two significant bits and a previous carry) is a *full adder*

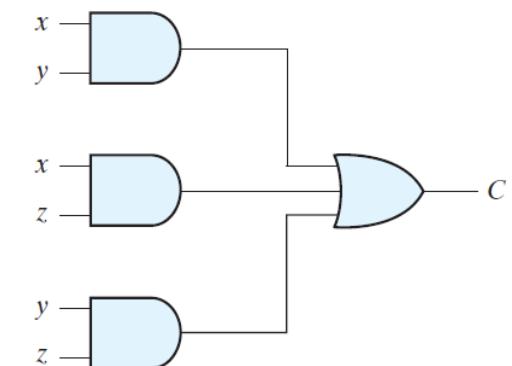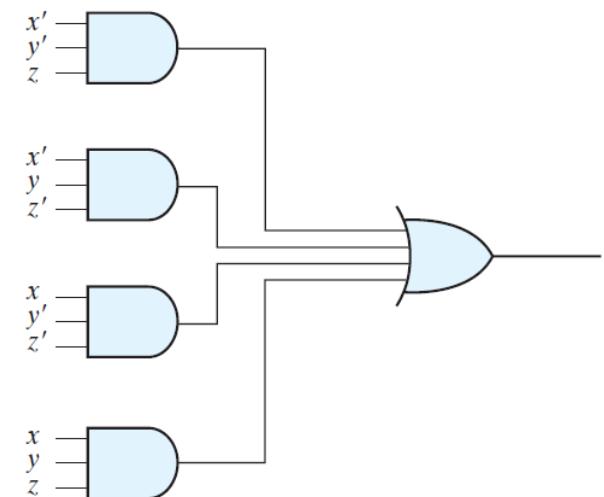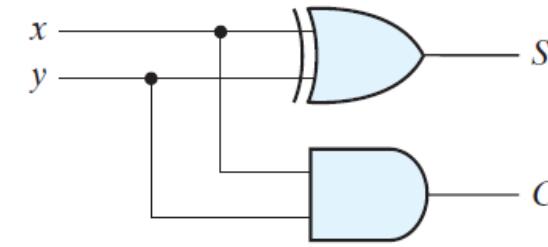


Binary adder

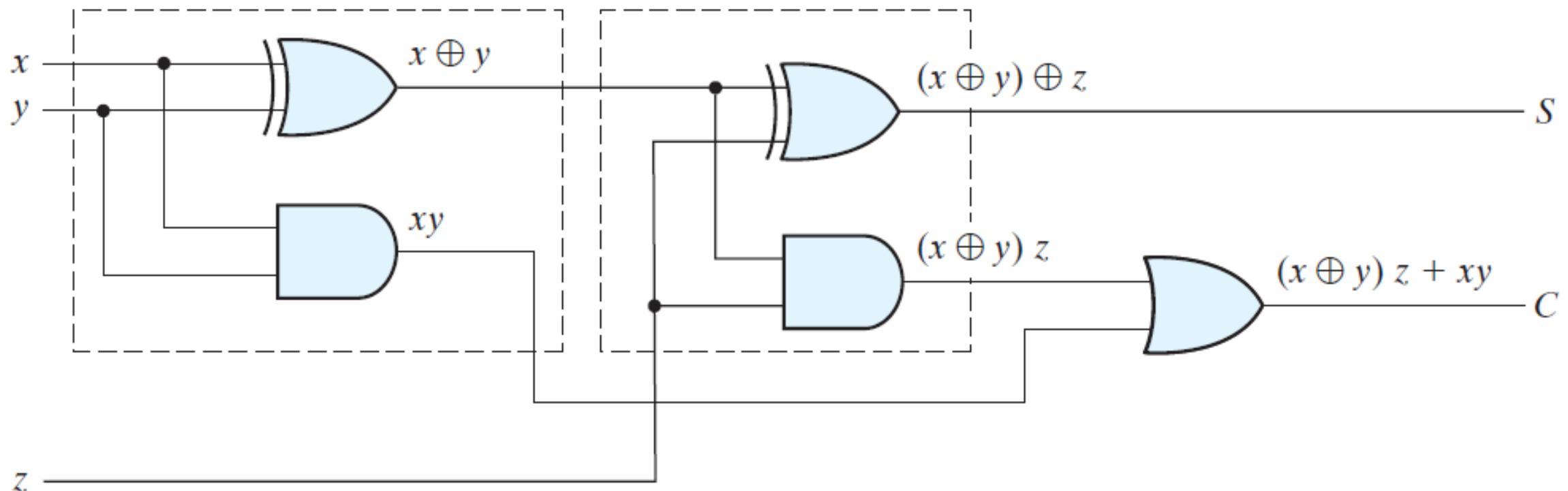- We can use two half adders to create a full adder




n-bit binary adder

- Addition of n -bit numbers requires a chain of n full adders or a chain of one-half adder and $n-1$ full adders
- Consider a four bit adder. The augend bits of A and the addend bits of B are designated by subscript numbers from right to left, with subscript 0 denoting the least significant bit
- The carries are connected in a chain through the full adders. The input carry to the adder is C_0 , and it ripples through the full adders to the output carry C_4 .
- The S outputs generate the required sum bits

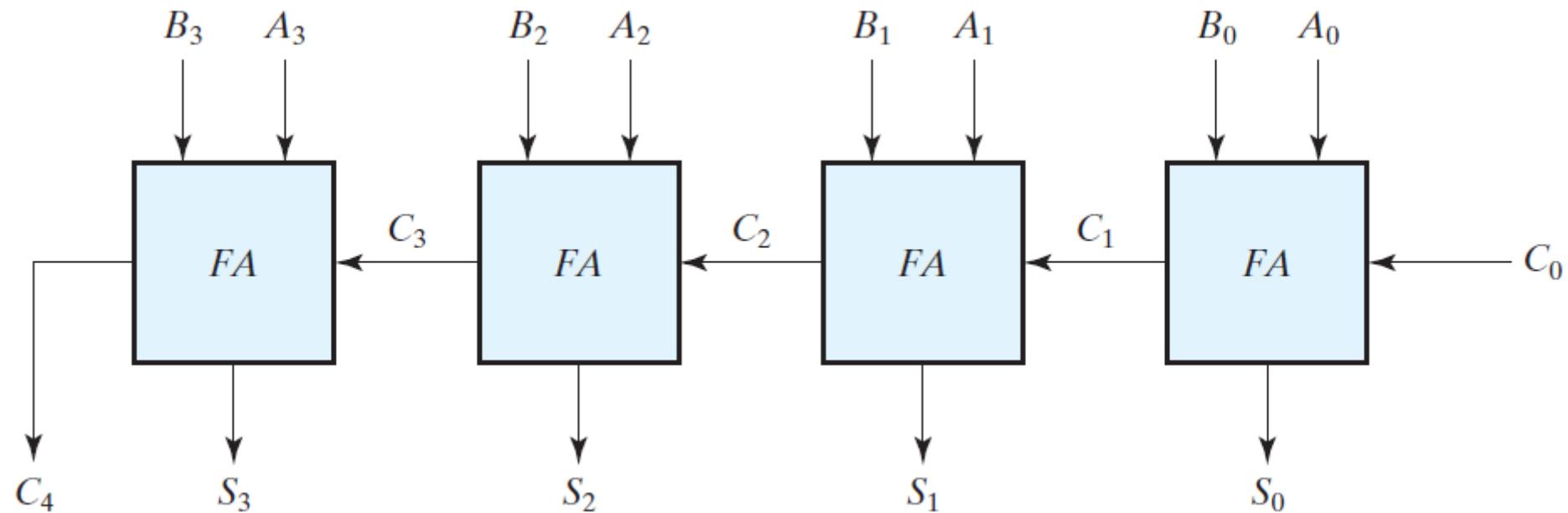

n-bit binary adder

- Can we make this circuit through the normal route?
- Note that the classical method would require a truth table (and K-map) with $2^9 = 512$ entries, since there are nine inputs to the circuit
- By using an iterative method of cascading a standard function, it is possible to obtain a simple and straightforward implementation

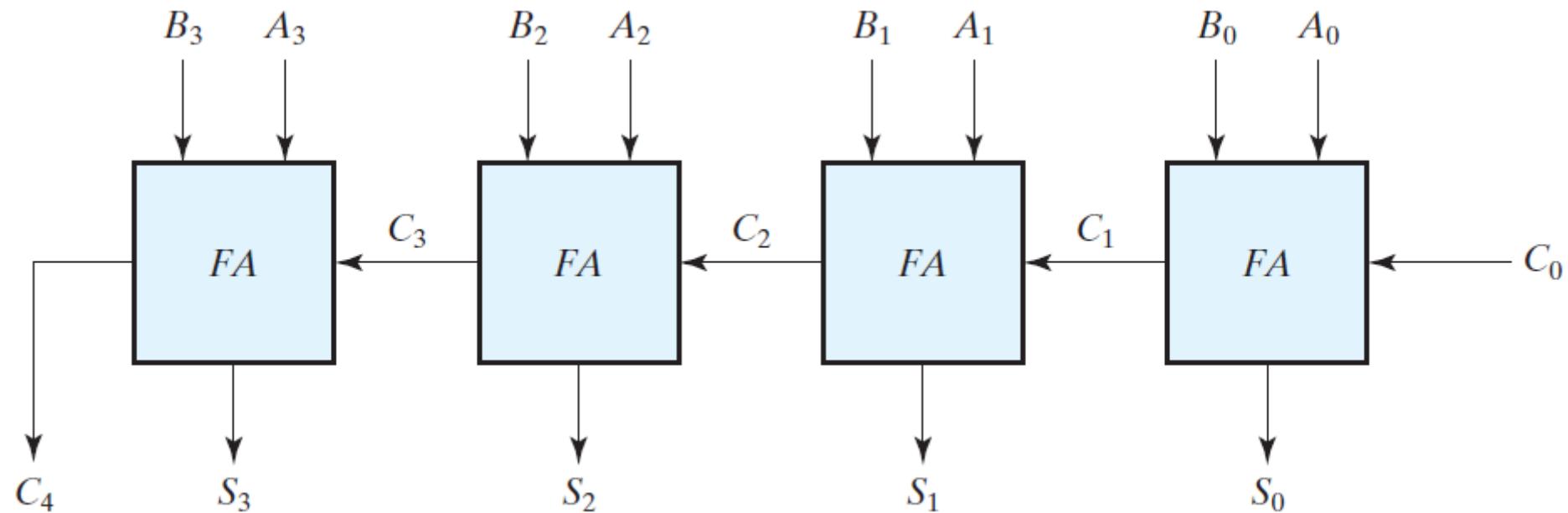


Lecture 14 – Combinational circuits 3

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 4


Carry propagation problem

- The addition of two binary numbers in parallel implies that all the bits of the augend and addend are available for computation at the same time
- As in any combinational circuit, the signal must propagate through the gates before the correct output sum is available in the output terminals
- The total propagation time is equal to the propagation delay of a typical gate, times the number of gate levels in the circuit
- The longest propagation delay time in an adder is the time it takes the carry to propagate through the full adders
- Since each bit of the sum output depends on the value of the input carry, the value of S_i at any given stage in the adder will be in its steady-state final value only after the input carry to that stage has been propagated

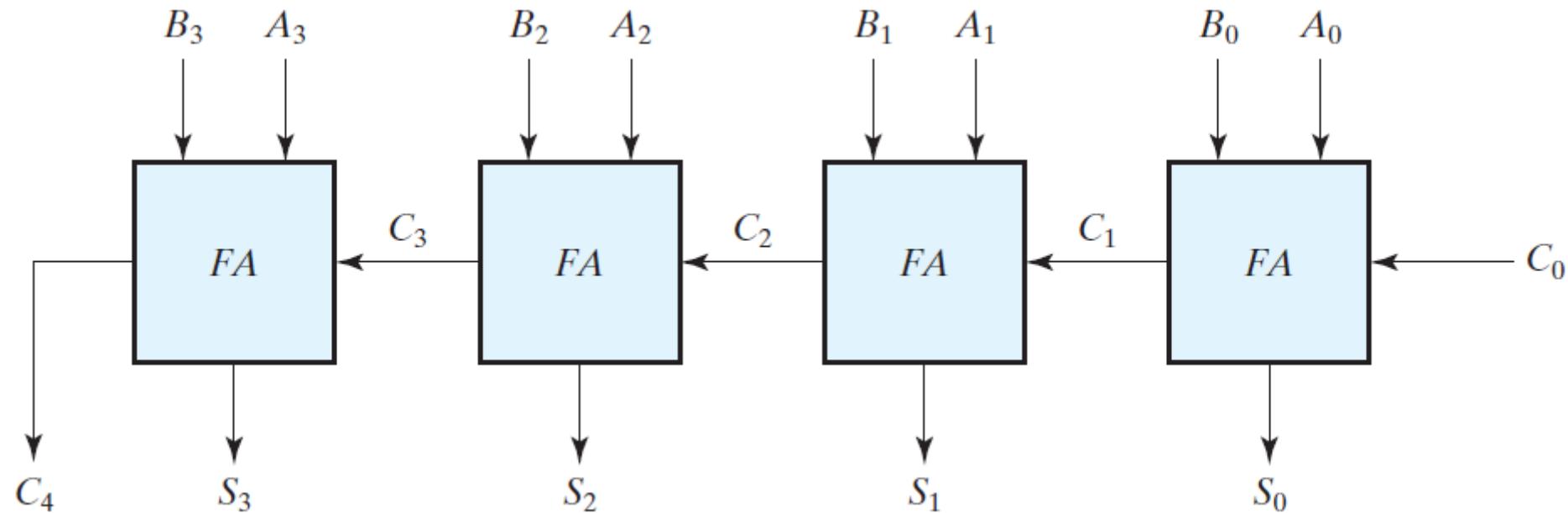


Carry propagation problem

- The number of gate levels for the carry propagation can be found from the circuit of the full adder
- The signals at P_i and G_i settle to their steady-state values after they propagate through their respective gates
- These two signals are common to all half adders and depend on only the input augend and addend bits
- The signal from the input carry C_i to the output carry C_{i+1} propagates through an AND gate and an OR gate, which constitute two gate levels
- If there are four full adders in the adder, the output carry C_4 would have $2 * 4 = 8$ gate levels from C_0 to C_4
- For an n -bit adder, there are $2n$ gate levels for the carry to propagate from input to output

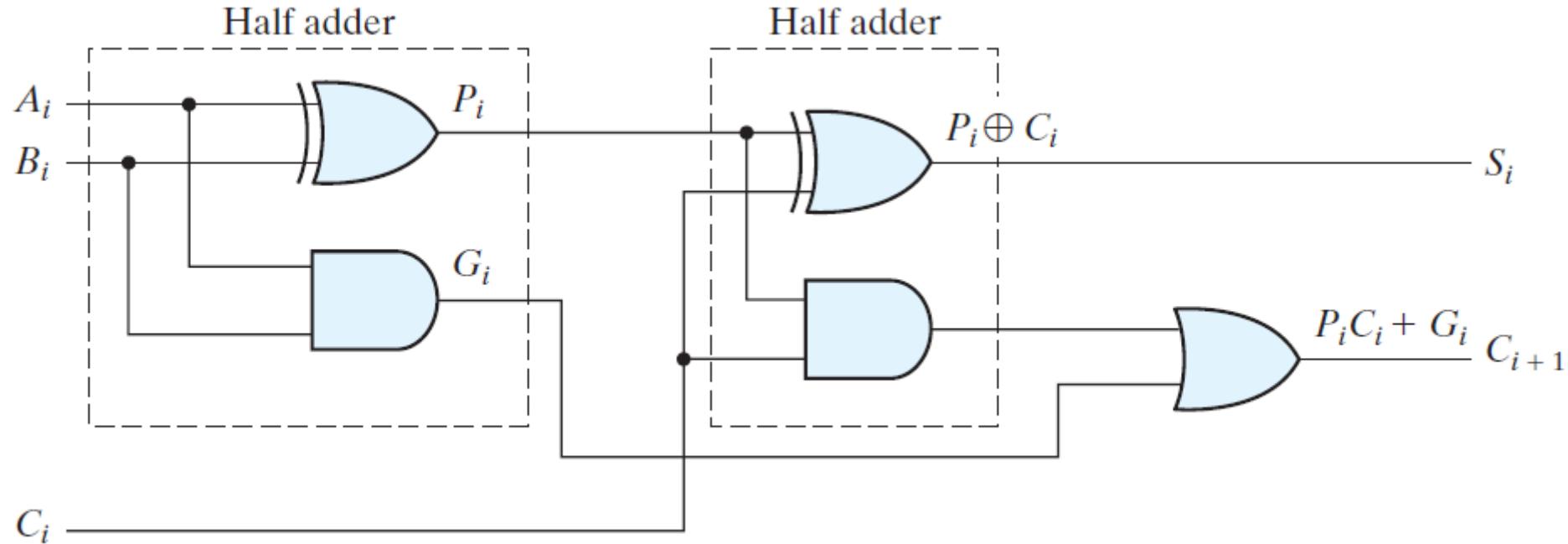

Carry propagation problem

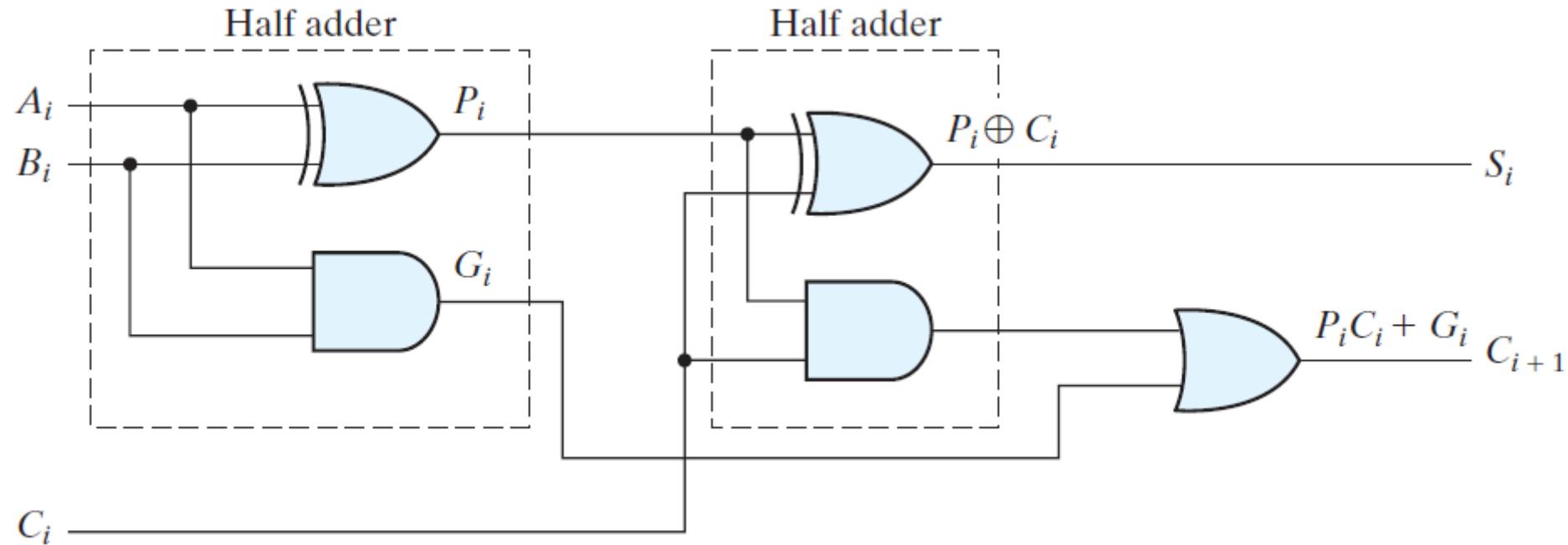- There are several techniques for reducing the carry propagation time in a parallel adder
- An obvious solution to this problem is to actually make the 2^n truth-table, K-map and get a two level implementation (either SoP or PoS)
- The most widely used technique employs the principle of *carry lookahead logic*




Carry propagation problem

- With the definition of P and G, we can write:

$$S_i = P_i + C_i \text{ and } C_{i+1} = G_i + P_i C_i$$

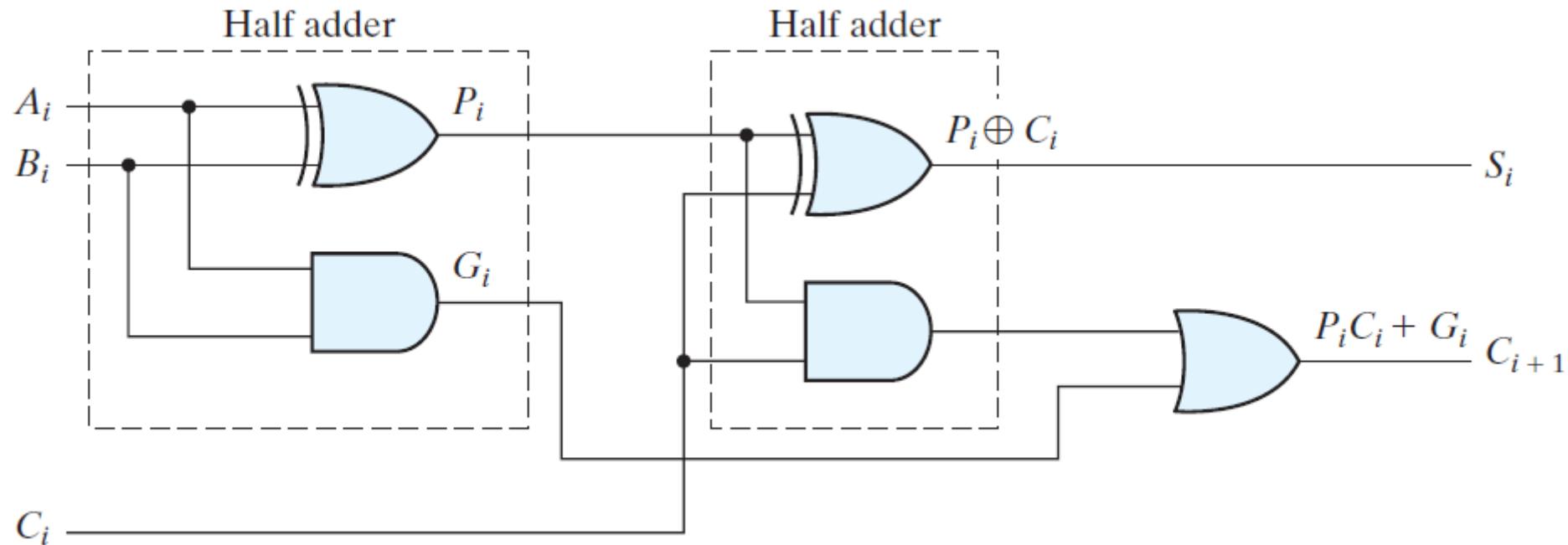- G_i is called a *carry generate*, and it produces a carry of 1 when both A_i and B_i are 1, regardless of the input carry C_i
- P_i is called a *carry propagate*, because it determines whether a carry into stage i will propagate into stage $i + 1$ (i.e., whether an assertion of C_i will propagate to an assertion of C_{i+1})



Carry propagation problem


- We now write the Boolean functions for the carry outputs of each stage and substitute the value of each C_i from the previous equations:

$$C_0 = \text{input carry}$$

$$C_1 = G_0 + P_0 C_0$$


$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$
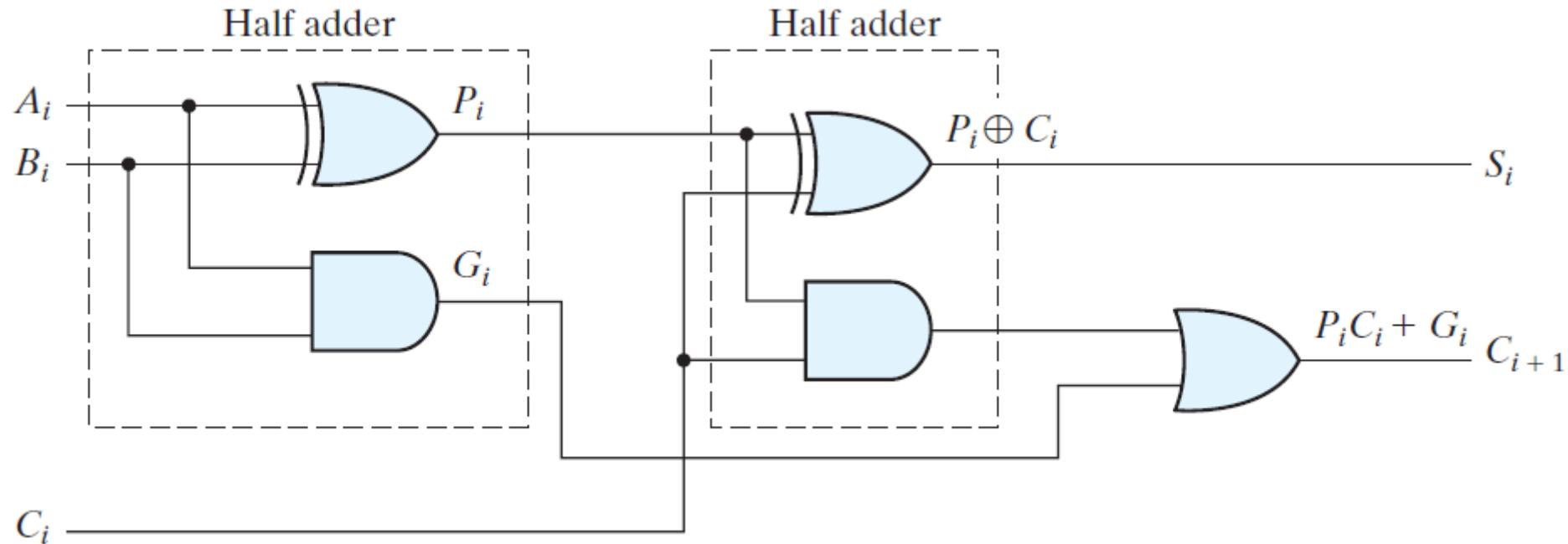
$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$




Carry propagation problem

- Since the Boolean function for each output carry is expressed in sum-of-products form only dependent on P and G , each function can be implemented with one level of AND gates followed by an OR gate (or by a two-level NAND)
- Note that this circuit can add in less time because C_3 does not have to wait for C_2 and C_1 to propagate; in fact, C_3 is propagated at the same time as C_1 and C_2
- This gain in speed of operation is achieved at the expense of additional complexity (hardware)

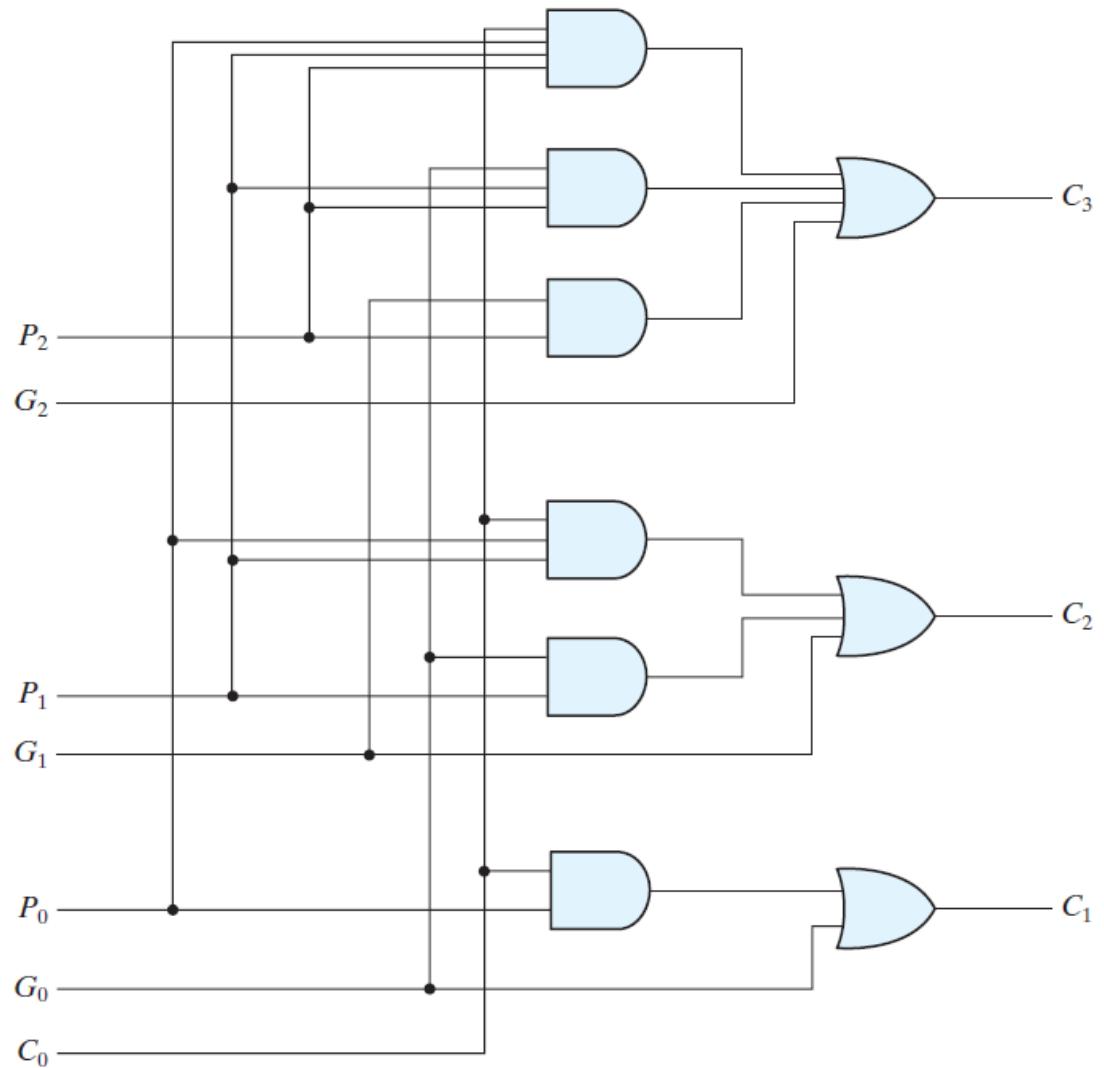

Carry propagation problem

- We can make the four bit adder as shown
- Each sum output requires two XOR gates
- The output of the first XOR gate generates the P_i variable, and the AND gate generates the G_i variable
- The carries are propagated through the carry lookahead generator and applied as inputs to the second XOR gate
- All output carries are generated after a delay through only two levels of gates
- Thus, outputs S_1 through S_3 have equal propagation delay times

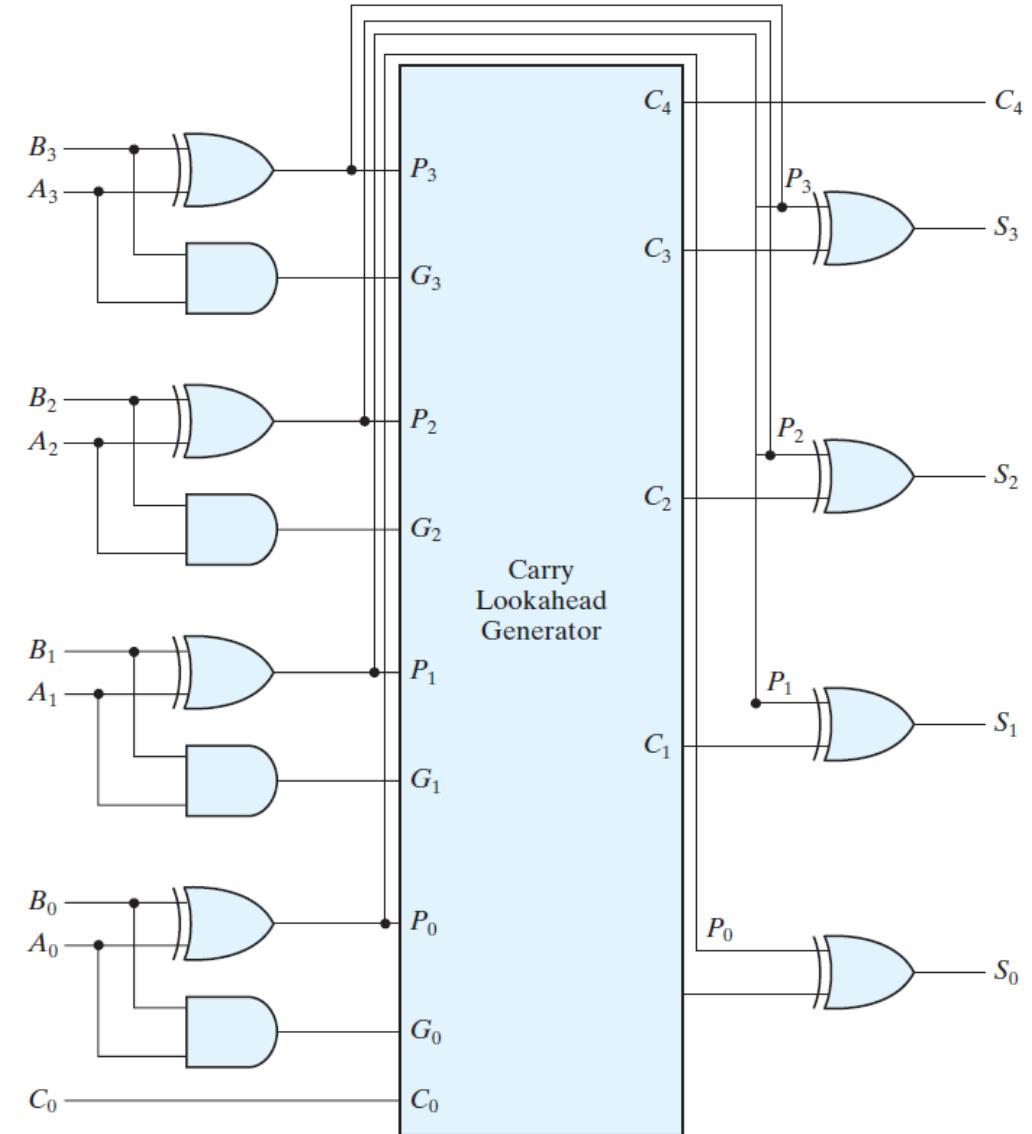




The Binary Subtractor

Binary subtractor

- The subtraction of unsigned binary numbers can be done most conveniently by means of complements
- Remember that the subtraction $A - B$ can be done by taking the 2's complement of B and **adding** it to A
- The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits
- The 1's complement can be implemented with inverters, and a 1 can be added to the sum through the input carry
- The circuit for subtracting $A - B$ consists of an adder with inverters placed between each data input B and the corresponding input of the full adder
- **The input carry C_0 must be equal to 1 when subtraction is performed**
- The operation thus performed becomes A , plus the 1's complement of B , plus 1. This is equal to A plus the 2's complement of B
- That gives $A - B$ if $A \geq B$ or the 2's complement of $B - A$ if $A < B$

Can we combine the binary adder & subtractor

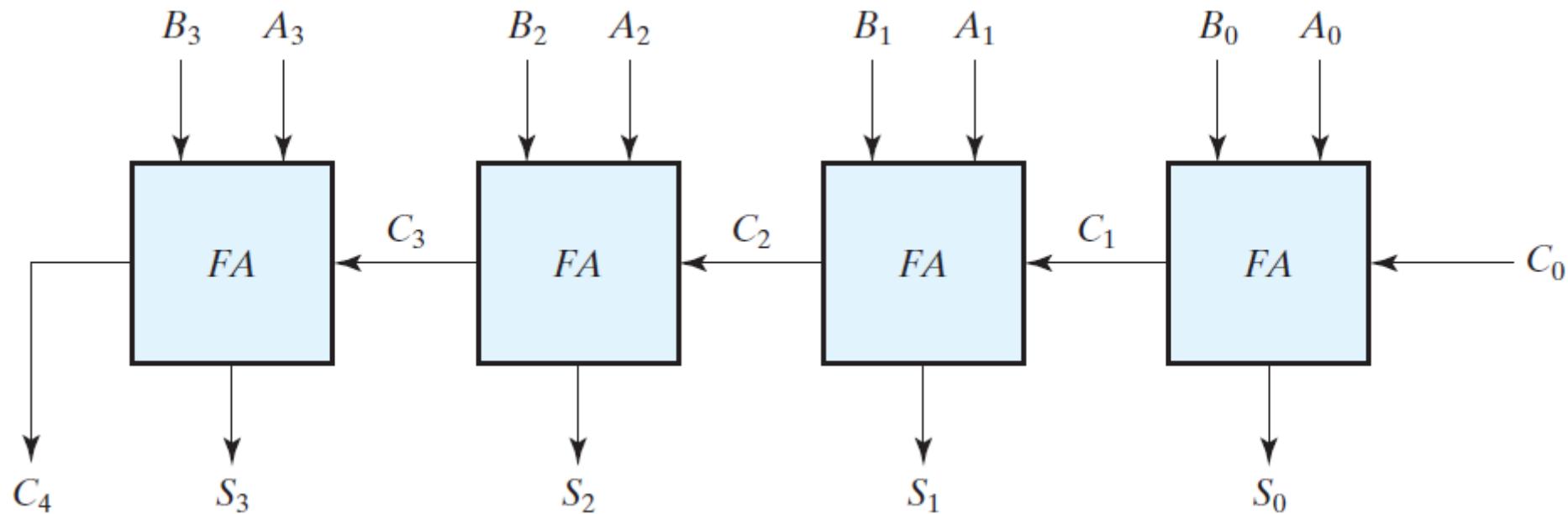
- Both use the 4-bit full adder. In one case, we use B and in another we use inverted B



Binary adder-subtractor

- Here is some magic: The addition and subtraction operations can be combined into one circuit
- The mode input M controls the operation
- When $M = 0$, the circuit is an adder, and when $M = 1$, the circuit becomes a subtractor
- When $M = 0$, the full adders receive the value of B , the input carry is 0, and the circuit performs $A + B$
- When $M = 1$, the full adders receive B' and $C_0 = 1$
- Thus, the B inputs are all complemented and a 1 is added through the input carry
- The circuit performs the operation A plus the 2's complement of B

Binary adder-subtractor

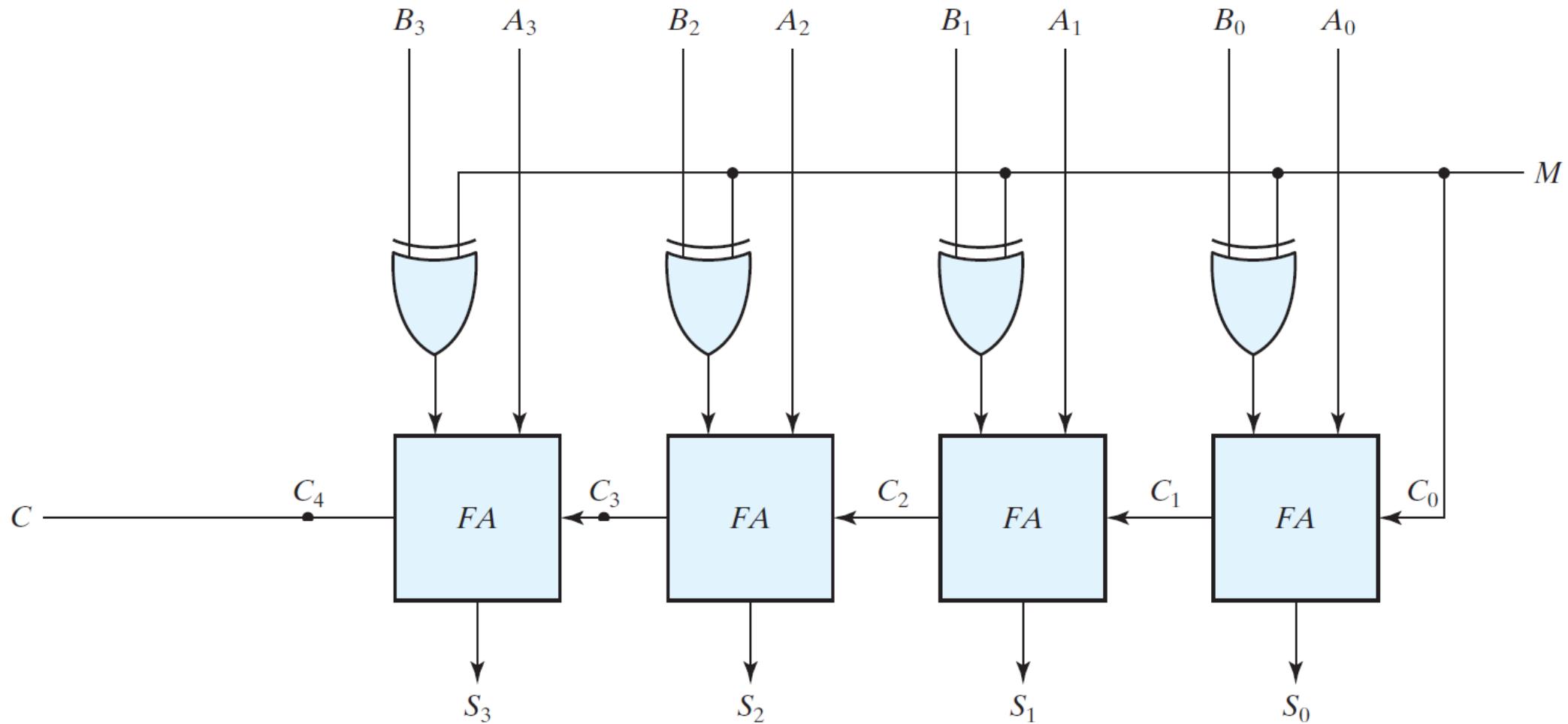



The BCD Idder

BCD adder

- Consider the arithmetic addition of two decimal digits in BCD, together with an input carry from a previous stage
- Since each input digit does not exceed 9, the output sum cannot be greater than $9 + 9 + 1 = 19$, the 1 in the sum being an input carry
- Suppose we apply two BCD digits to a four-bit binary adder
- The adder will form the sum in *binary* and produce a result that ranges from 0 through 19


K	Binary Sum				c	BCD Sum				Decimal
	z_8	z_4	z_2	z_1		s_8	s_4	s_2	s_1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

BCD adder

- In examining the contents of the table, it becomes apparent that when the binary sum is equal to or less than 1001, the corresponding BCD number is identical, and therefore no conversion is needed
- When the binary sum is greater than 1001, we obtain an invalid BCD representation
- The addition of binary 6 (0110) to the binary sum converts it to the correct BCD representation and also produces an output carry as required

K	Binary Sum				c	BCD Sum				Decimal
	z_8	z_4	z_2	z_1		s_8	s_4	s_2	s_1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

BCD adder - algorithm

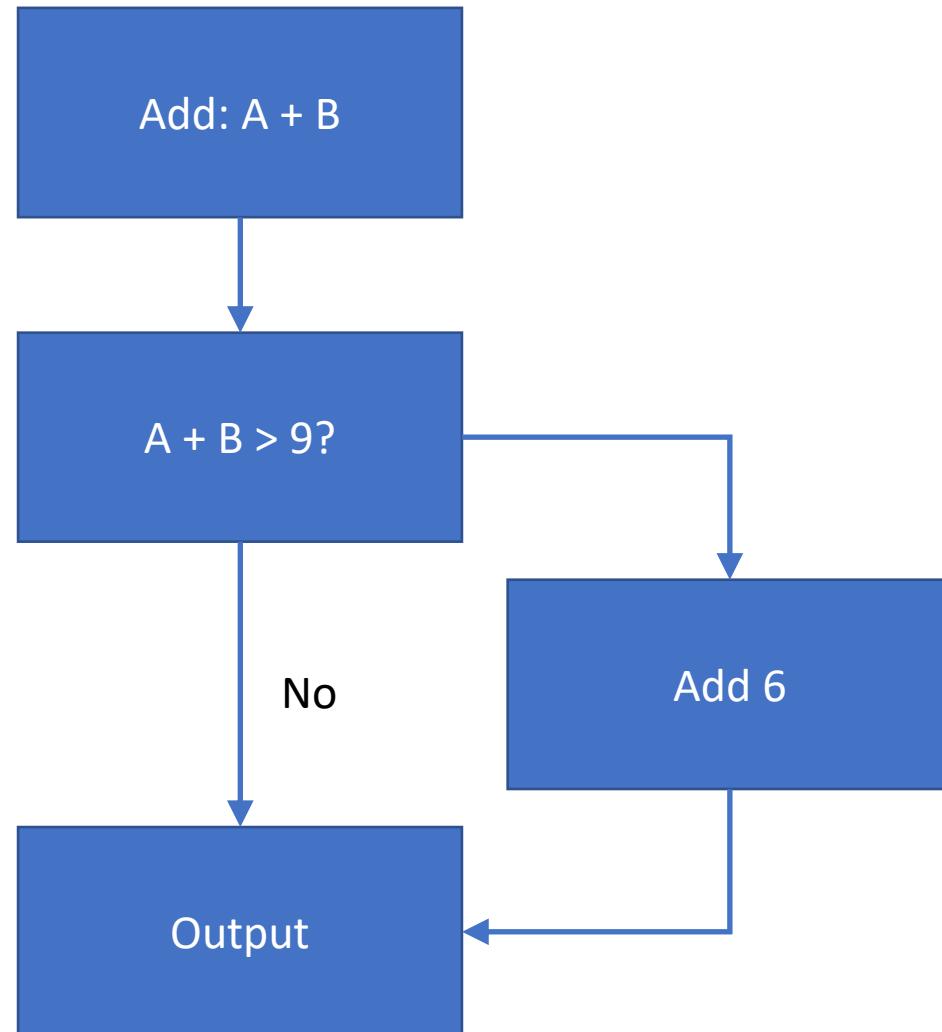

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


BCD adder

- The logic circuit that detects the necessary correction can be derived from the entries in the table
- It is obvious that a correction is needed when the binary sum has an output carry $K = 1$
- The other six combinations from 1010 through 1111 that need a correction have a 1 in position Z_8
- To distinguish them from binary 1000 and 1001, which also have a 1 in position Z_8 , we specify further that either Z_4 or Z_2 must have a 1
- Thus, the condition for a correction and an output carry can be expressed by the Boolean function: $Cor = K + Z_8Z_4 + Z_8Z_2$
- When $Cor = 1$, it is necessary to add 0110 to the binary sum and provide an output carry for the next stage

K	Binary Sum					BCD Sum				Decimal
	Z_8	Z_4	Z_2	Z_1	C	S_8	S_4	S_2	S_1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	1	0	1	19

BCD adder

- The logic circuit that detects the necessary correction can be derived from the entries in the table
- It is obvious that a correction is needed when the binary sum has an output carry $K = 1$
- The other six combinations from 1010 through 1111 that need a correction have a 1 in position Z_8
- To distinguish them from binary 1000 and 1001, which also have a 1 in position Z_8 , we specify further that either Z_4 or Z_2 must have a 1
- Thus, the condition for a correction and an output carry can be expressed by the Boolean function: $Cor = K + Z_8Z_4 + Z_8Z_2$
- When $Cor = 1$, it is necessary to add 0110 to the binary sum and provide an output carry for the next stage

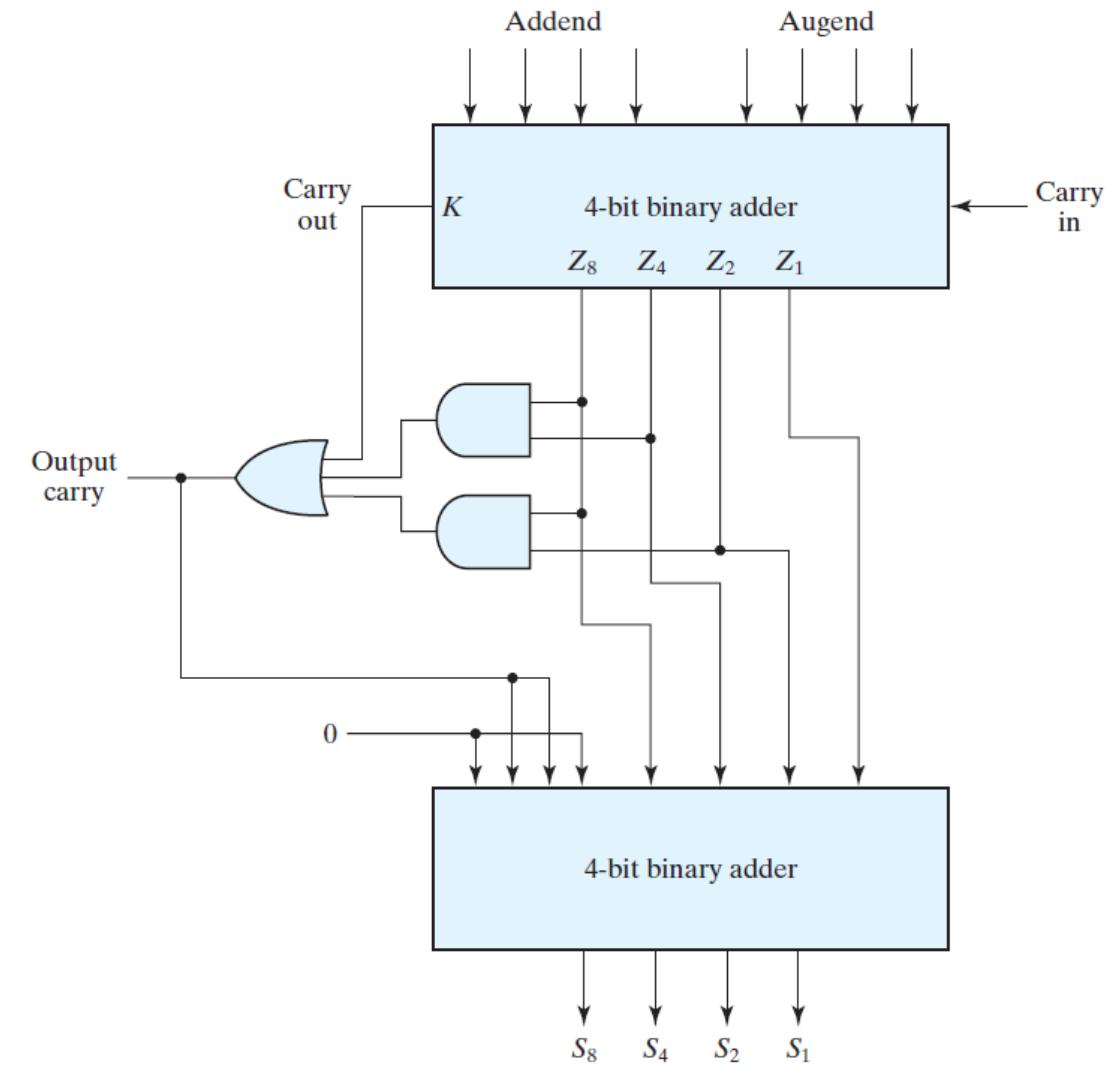

Lecture 15 – Sequential circuits

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 5



The Binary Multiplier


Binary multiplier

- Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers
- The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit
- Each such multiplication forms a partial product
- Successive partial products are shifted one position to the left
- The final product is obtained from the sum of the partial products
- Consider a 2-bit \times 2-bit multiplier.
Number of inputs/outputs?

$$\begin{array}{r} B_1 \quad B_0 \\ A_1 \quad A_0 \\ \hline A_0B_1 & A_0B_0 \\ \hline A_1B_1 & A_1B_0 \\ \hline C_3 & C_2 & C_1 & C_0 \end{array}$$

Binary multiplier

- The multiplicand bits are B_1 and B_0 , the multiplier bits are A_1 and A_0 , and the product is $C_3C_2C_1C_0$
- The first partial product is formed by multiplying B_1B_0 by A_0
- The multiplication of two bits such as A_0 and B_0 produces a 1 if both bits are 1; otherwise, it produces a 0
- This is identical to an AND operation
- Therefore, the partial products can be implemented with simple AND gates
- The two partial products are added with two half-adder (HA) circuits

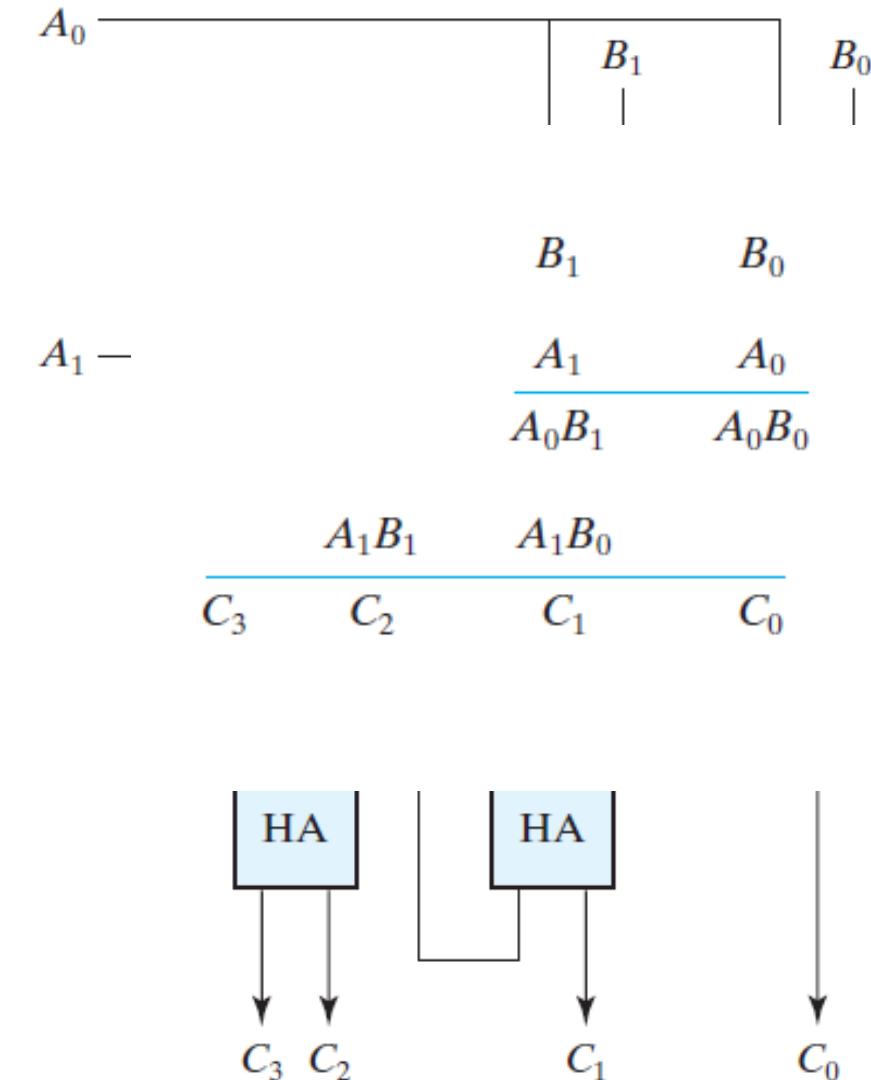


Binary multiplier

- A combinational circuit binary multiplier with more bits can be constructed in a similar fashion
- A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier
- The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product
- The last level produces the product
- For J multiplier bits and K multiplicand bits, we need $J * K$ AND gates and $(J - 1) K$ -bit adders to produce a product of $(J + K)$ bits
- Consider a multiplier circuit that multiplies a binary number represented by four bits by a number represented by three bits
- Let the multiplicand be represented by $B_3B_2B_1B_0$ and the multiplier by $A_2A_1A_0$

Binary multiplier

- A combinational circuit binary multiplier with more bits can be constructed in a similar fashion
- A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier
- The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product
- The last level produces the product
- For J multiplier bits and K multiplicand bits, we need $J * K$ AND gates and $(J - 1) K$ -bit adders to produce a product of $(J + K)$ bits
- Consider a multiplier circuit that multiplies a binary number represented by four bits by a number represented by three bits
- Let the multiplicand be represented by $B_3B_2B_1B_0$ and the multiplier by $A_2A_1A_0$

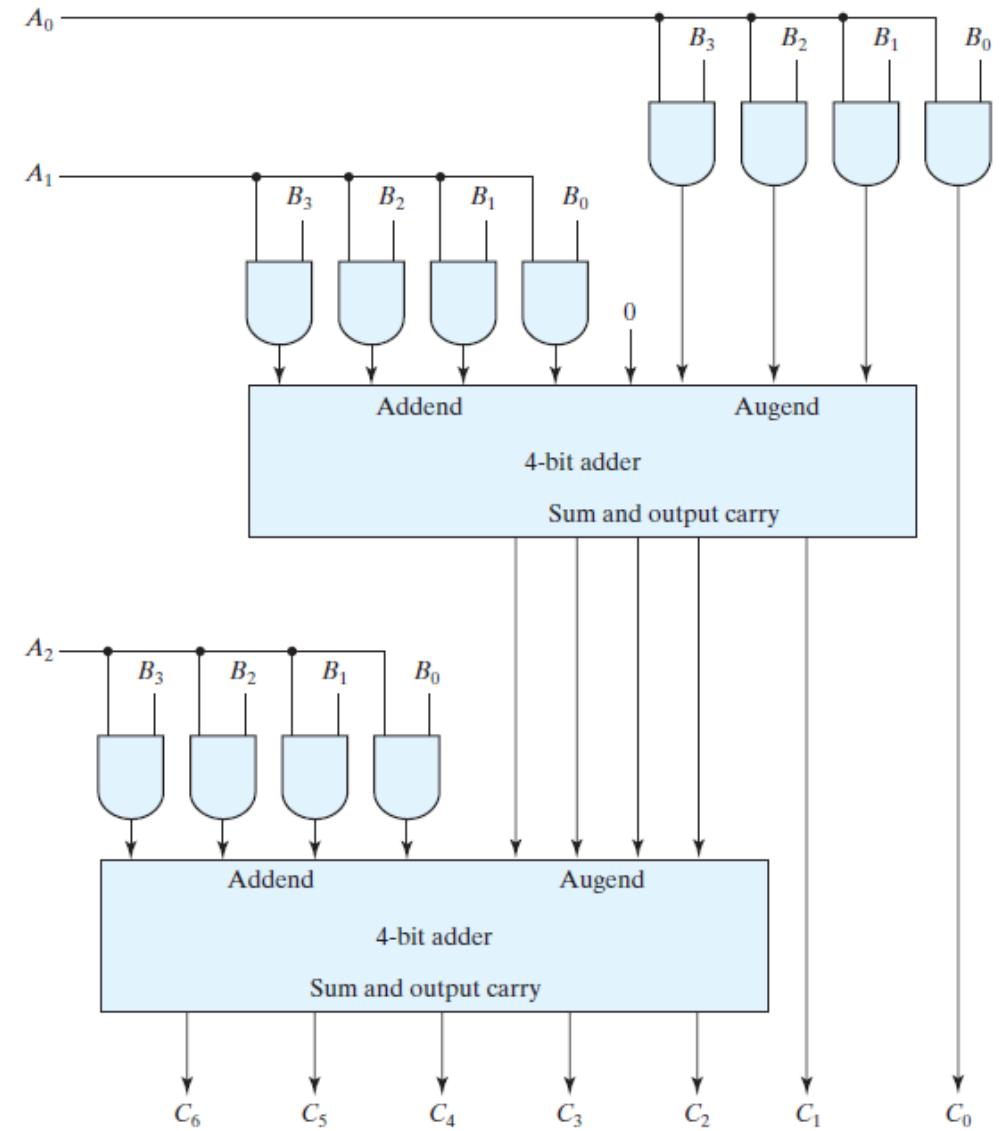



The Binary Comparator

Binary comparator

- The comparison of two numbers is an operation that determines whether one number is greater than, less than, or equal to the other number
- A *magnitude comparator* is a combinational circuit that compares two numbers A and B and determines their relative magnitudes
- The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$
- On the one hand, the circuit for comparing two n -bit numbers has 2^{2n} entries in the truth table and becomes too cumbersome, even with $n = 3$
- On the other hand, as one may suspect, a comparator circuit possesses a certain amount of regularity

Binary comparator

- Consider two numbers, A and B , with four digits each $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$
- The two numbers are equal if all pairs of significant digits are equal: $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$, **and** $A_0 = B_0$
- To check bit-wise equality, we can use the XNOR gate

$$x_i = A_i B_i + A'_i B'_i \text{ for } i = 0, 1, 2, 3$$

- For equality to exist, all x_i variables must be equal to 1, a condition that dictates an AND operation of all variables:

$$(A = B) = x_3 x_2 x_1 x_0$$

Binary comparator

- To determine whether A is greater or less than B , we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position
- If the two digits of a pair are equal, we compare the next lower significant pair of digits
- The comparison continues until a pair of unequal digits is reached
- If the corresponding digit of A is 1 and that of B is 0, we conclude that $A > B$.
If the corresponding digit of A is 0 and that of B is 1, we have $A < B$
- The comparison can be expressed logically by the two Boolean functions:

$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$
$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

Binary comparator

$$x_i = A_i B_i + A'_i B'_i \text{ for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$


$$(A > B)$$

$$= A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 \\ + x_3 x_2 x_1 A_0 B'_0$$

$$(A < B)$$

$$= A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 \\ + x_3 x_2 x_1 A'_0 B_0$$

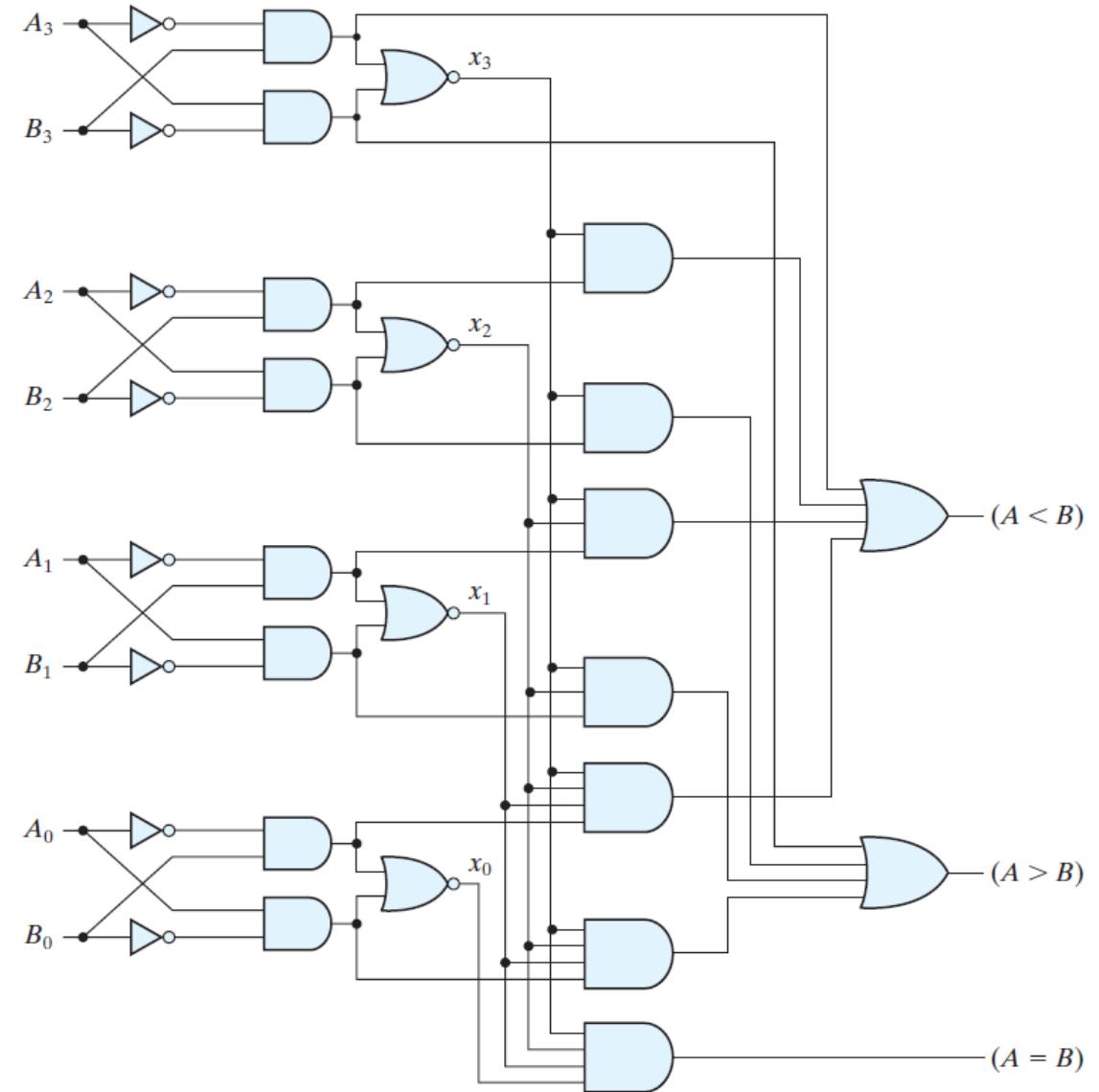Interesting: Can we prove that only one of $(A=B)$, $(A>B)$ and $(A<B)$ will be “1” at any given time?





Sequential circuits

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 5


Gate delays

- When we apply an input to a gate, the output does not change immediately – there is a delay between the input application and appearance of the correct output
- This delay is generally of the order of nanoseconds, but can add up as signal goes through multiple gates
- *While making a digital IC design, gate delay (and by extension timing) is the single biggest consideration of all time!*
- Other things to worry about are silicon real estate, power consumption, reliability, testability, etc.

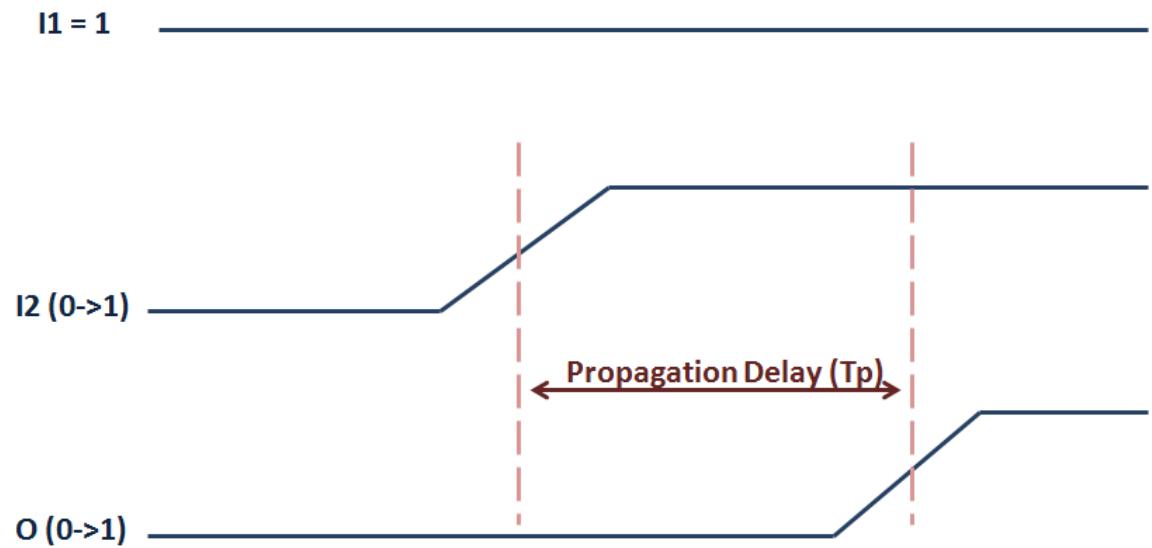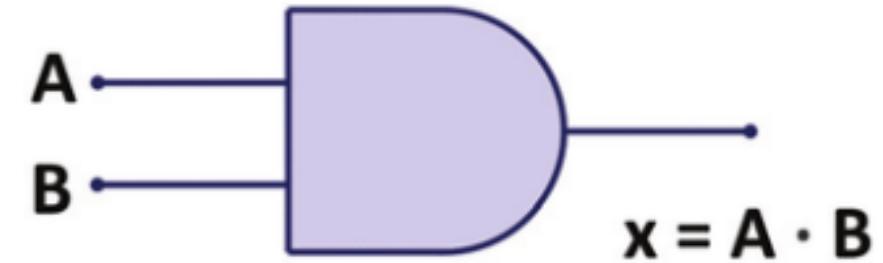


Glitches

- Improperly handled timing can lead to glitches and cause unexpected results
- This is particularly true for multi-level logic implementation wherein different literals are bypassing some levels
- Consider an AND gate connected to X and X'
- Such a connection will ALWAYS produce a glitch for X ($0 \rightarrow 1$)
- You can be sad about this glitch...
- Or you can call this circuit a “pulse generator”! ☺

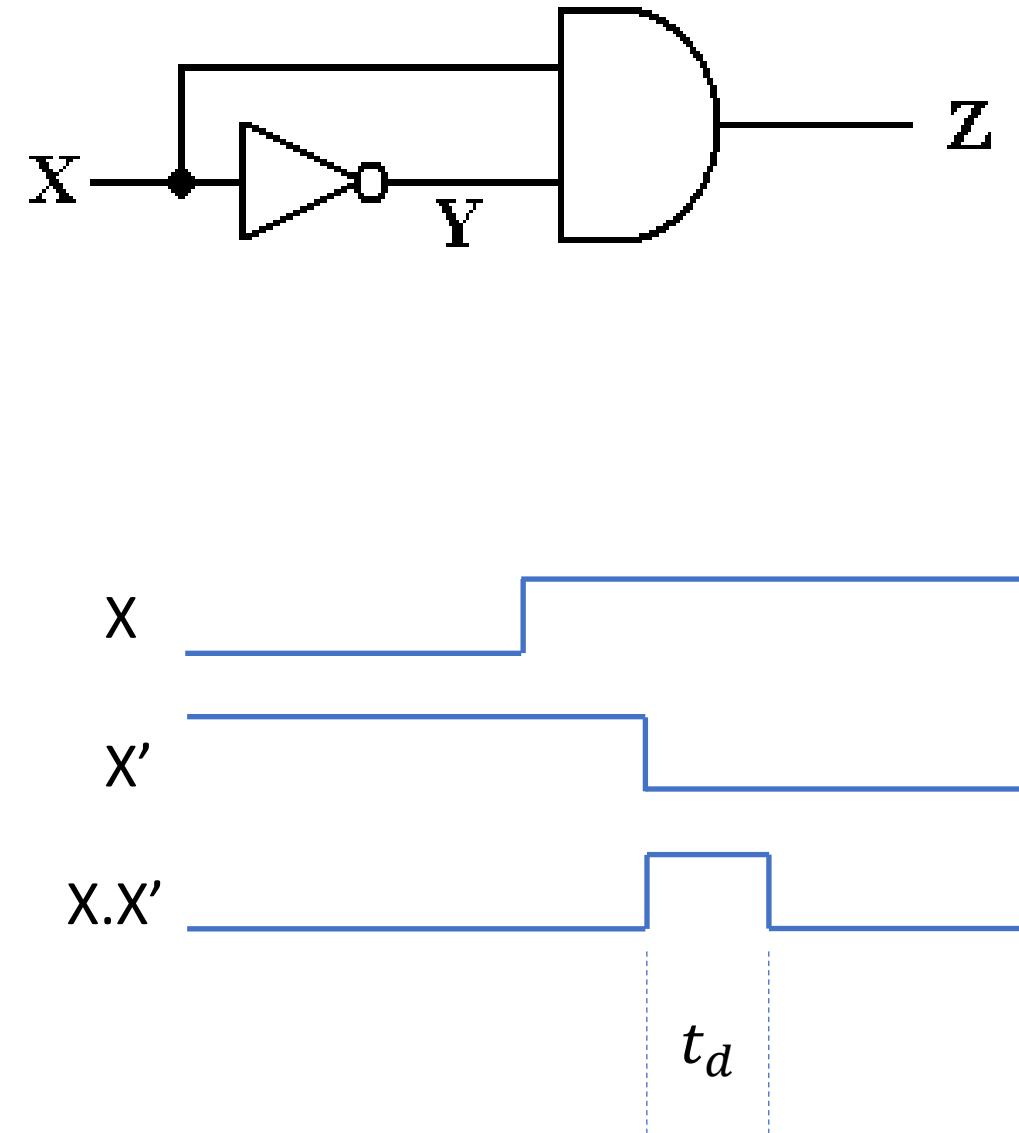

Ring oscillators

- Another clever use of gate delays in is in the construction of ring oscillators
- It is a series of odd number of NOT gates with the output connected back to the input gate of the first gate
- With this system, we can generate a continuous square wave at Q
- What is the frequency of the wave?
- In this case, it is $f = \frac{1}{T} = \frac{1}{3 \times 2t_d}$

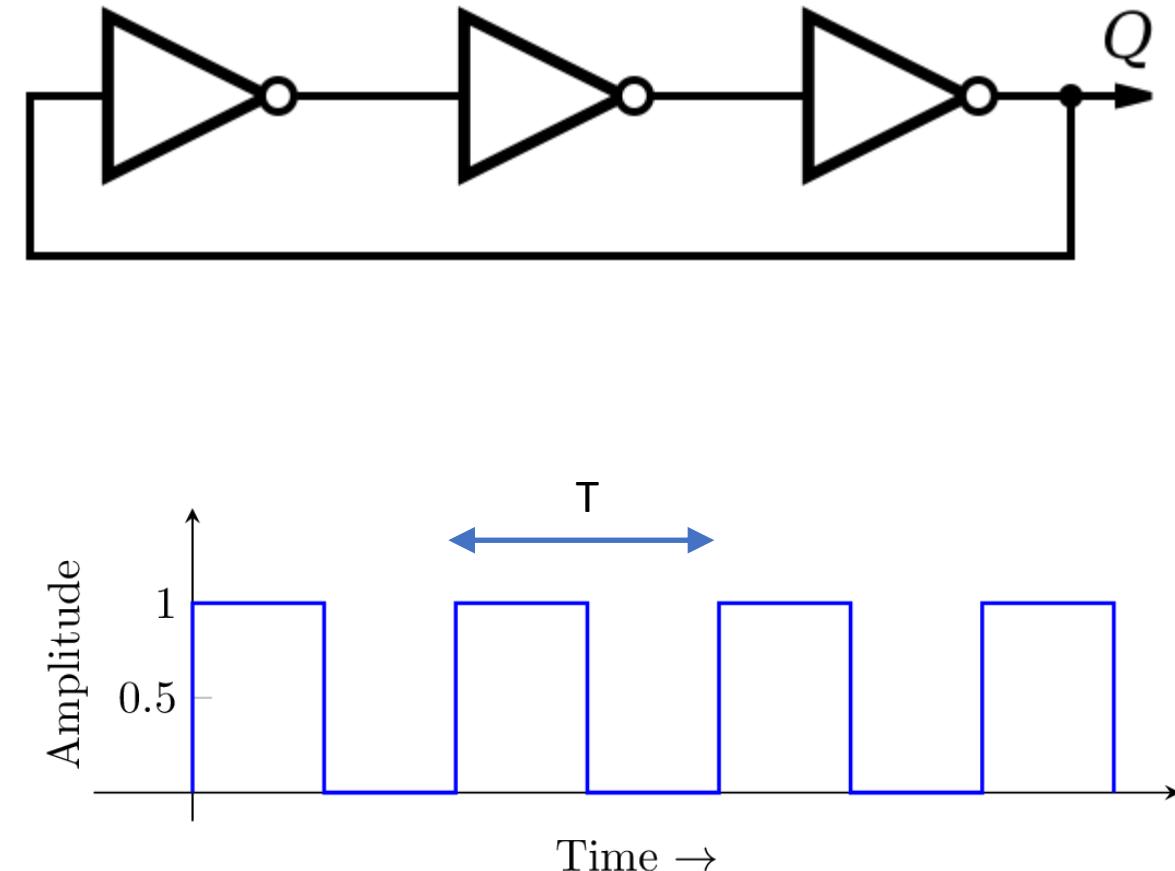

Lecture 16 – Sequential circuits 2

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST


Chapter 5

Sequential circuits

- The technology enabling and supporting modern digital devices is critically dependent on electronic components that can store information, i.e., have memory
- We will examine the operation and control of these devices and their use in circuits and enables you to better understand what is happening in these devices when you interact with them
- The digital circuits considered thus far have been combinational—their output depends only and immediately on their inputs—they have no memory, i.e., dependence on past values of their inputs
- Sequential circuits, however, act as storage elements and have memory, i.e., their output depends on past inputs as well

Sequential circuits

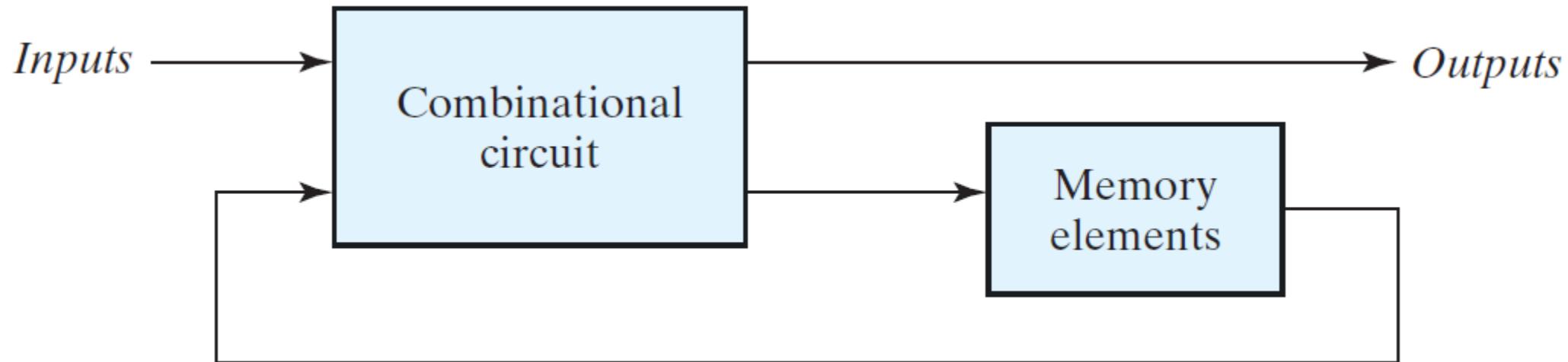- The main way sequential circuits remember things is through feedback paths and memory elements
- We know how combinational circuits are created
- The simplest storage elements (memory) used in sequential circuits are called *latches*




Latches

- A storage element in a digital circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit), until directed by an input signal to switch states
- Such a storage element is called a latch
- The major differences among various types of storage elements are in the number of inputs they possess and in the manner in which the inputs affect the binary state


SR Latch

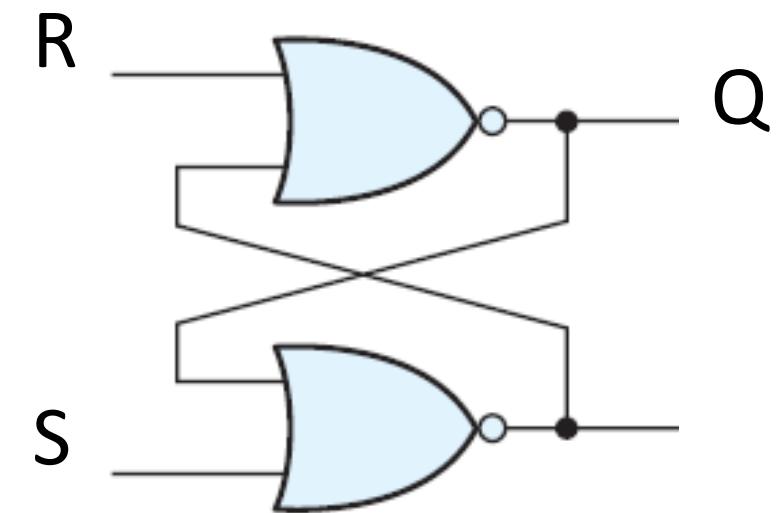- The *SR* latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates, and two inputs labeled *S* and *R*
- Let's analyze...




SR Latch

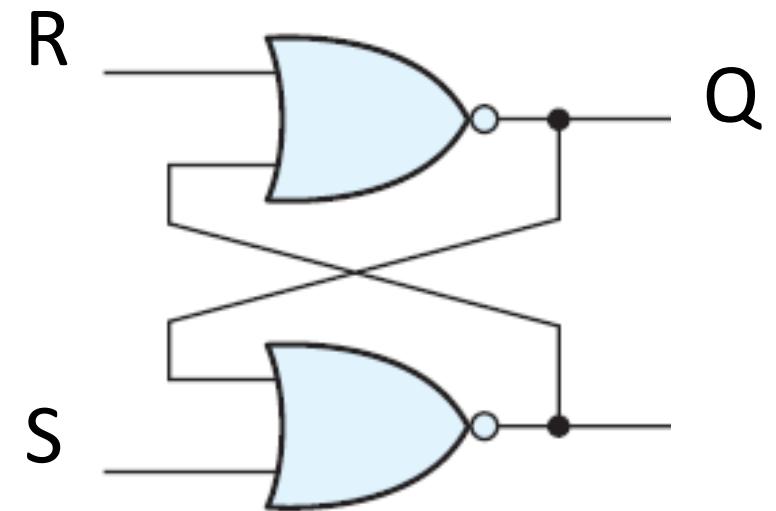- The latch has two stable states
- When output $Q = 1$ and $Q' = 0$, the latch is said to be in the *set state*
- When $Q = 0$ and $Q' = 1$, it is in the *reset state*
- We realize that the outputs Q and Q' are normally the complement of each other



SR Latch


- Setting and resetting can be done through the two inputs (SR)
- After setting or resetting, applying 00 at the input retains the previous state
- However, when both inputs are equal to 1 at the same time, a condition in which both outputs are equal to 0 (rather than be mutually complementary) occurs
- If both inputs are then switched to 0 simultaneously, the device will enter an unpredictable or undefined state or a metastable state

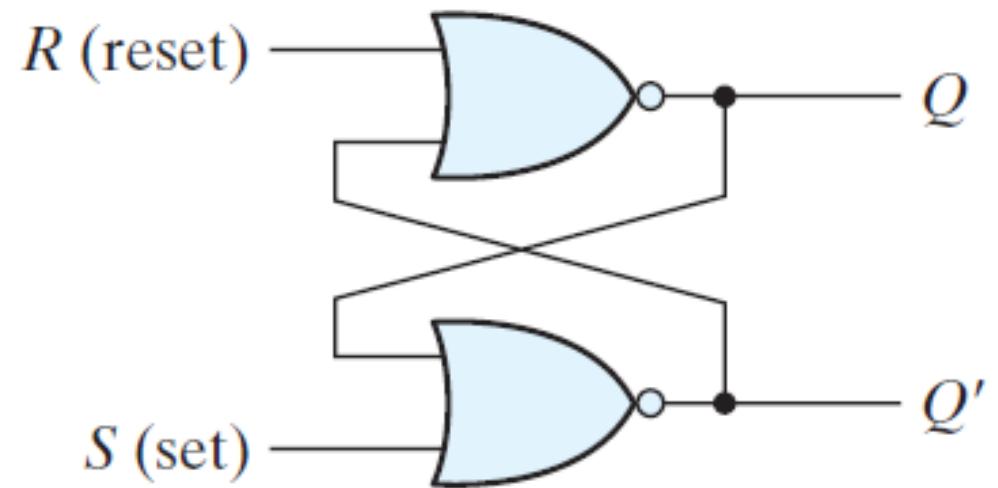

S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	(forbidden)

SR Latch – NAND implementation


- The SR latch with two cross-coupled NAND gates behaves in a similar way to NOR implementation
- It operates with both inputs normally at 1, unless the state of the latch has to be changed
- The application of 0 to the S input causes output Q to go to 1, putting the latch in the set state
- When the S input goes back to 1, the circuit remains in the set state
- The condition that is forbidden for the NAND latch is both inputs being equal to 0 at the same time, an input combination that should be avoided

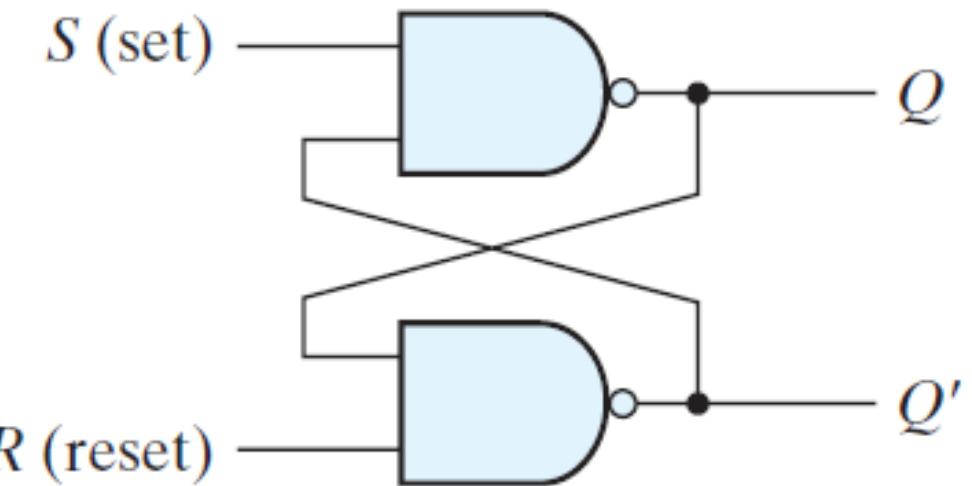

S	R	Q	Q'	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	(forbidden)

Latch with enable


- The operation of the basic SR latch can be modified by providing an additional input signal that determines (controls) *when* the state of the latch can be changed by determining whether S and R (or S and R) can affect the circuit
- It consists of the basic SR latch and two additional NAND gates
- The control input *En* acts as an *enable* signal for the other two inputs
- The outputs of the NAND gates stay at the logic-1 level as long as the enable signal remains at 0
- This is the quiescent condition for the SR latch

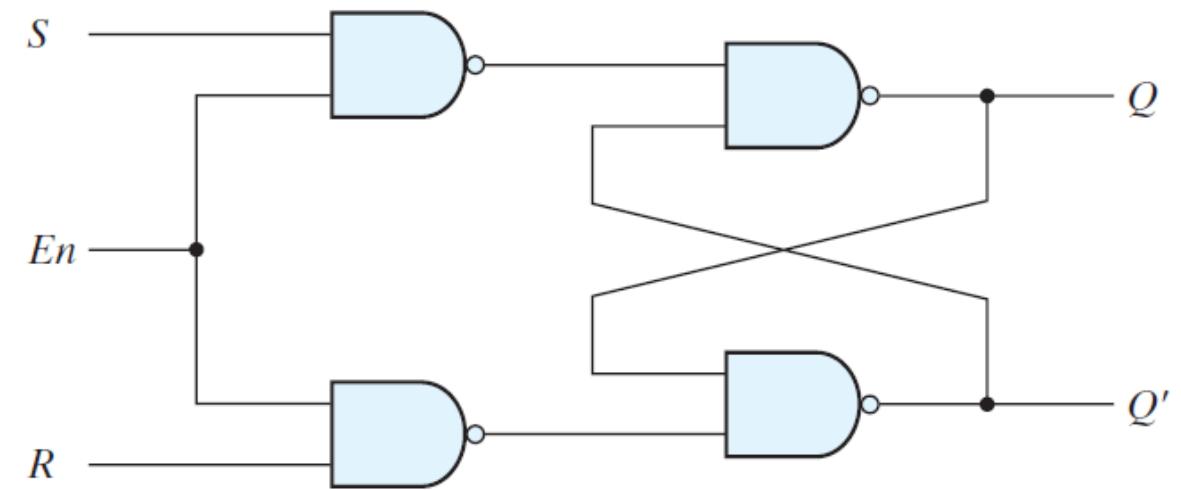

<i>En</i>	<i>S</i>	<i>R</i>	Next state of <i>Q</i>
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

Latch with enable


- When the enable input goes to 1, information from the S or R input is allowed to affect the latch
- The set state is reached with $S = 1$, $R = 0$, and $En = 1$ (active-high enabled) and reset is reached with $S = 0$, $R = 1$, and $En = 1$
- In either case, when En returns to 0, the circuit remains in its previous stable state
- Further, when $En = 1$ and both the S and R inputs are equal to 0, the state of the circuit does not change

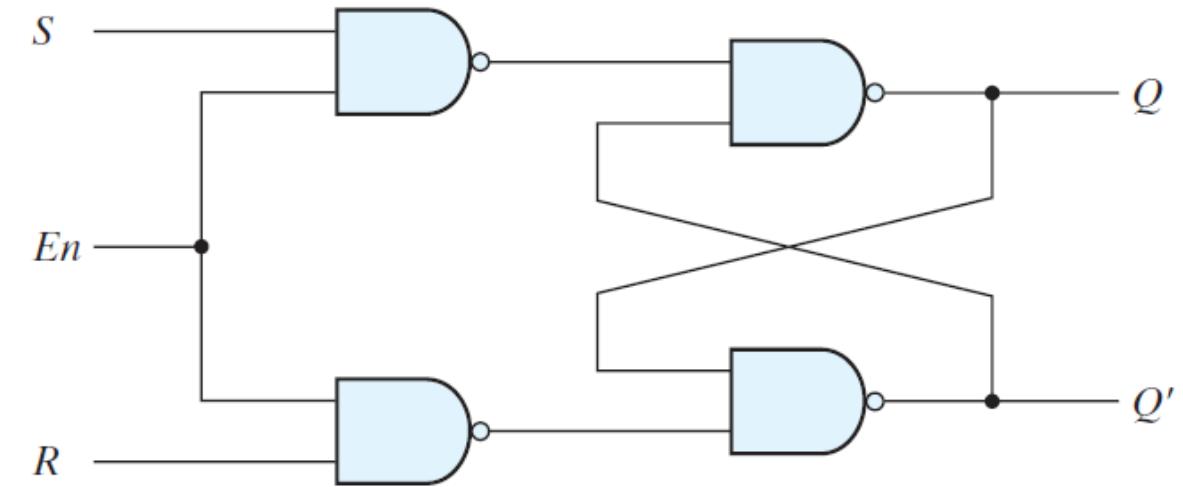

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

Latch with enable


- An indeterminate condition occurs when all three inputs are equal to 1
- This condition places 0's on both inputs of the basic *SR* latch, which puts it in the undefined state
- When the enable input goes back to 0, one cannot conclusively determine the next state, because it depends on whether the *S* or *R* input goes to 0 first
- This indeterminate condition makes this circuit difficult to manage, and it is seldom used in practice
- Nevertheless, the *SR* latch is an important circuit in conjunction with other modifications

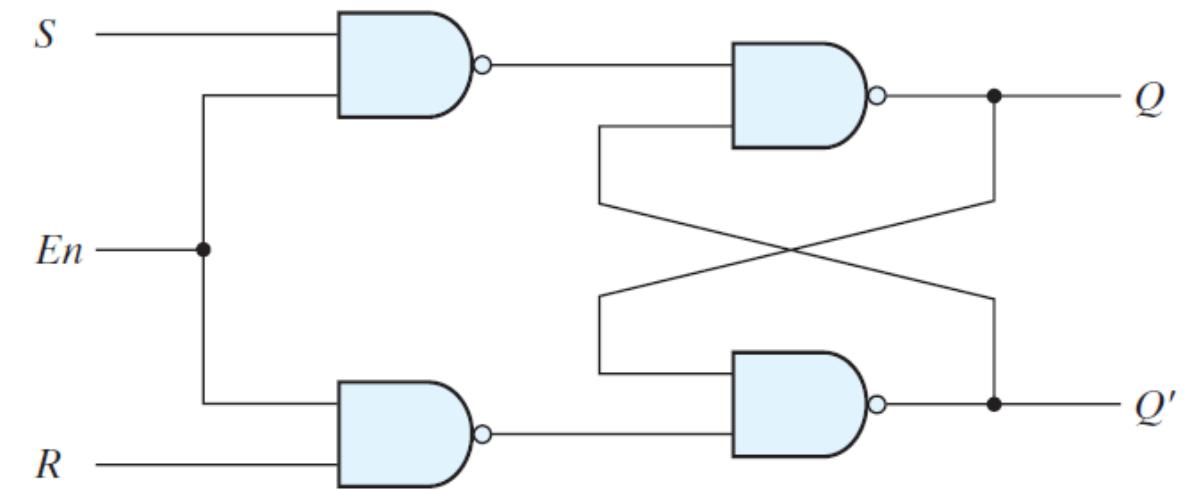

<i>En</i>	<i>S</i>	<i>R</i>	Next state of <i>Q</i>
0	X	X	No change
1	0	0	No change
1	0	1	<i>Q</i> = 0; reset state
1	1	0	<i>Q</i> = 1; set state
1	1	1	Indeterminate

D Latch


- One way to eliminate the undesirable condition of the indeterminate state in the SR latch is to ensure that inputs S and R are never equal to 1 at the same time
- This is done in the D latch
- The D input goes directly to the S input, and its complement is applied to the R input
- As long as the enable input is at 0, the cross-coupled SR latch has both inputs at the 1 level and the circuit cannot change state regardless of the value of D
- The D input is sampled when $En = 1$. If $D = 1$, the Q output goes to 1, placing the circuit in the set state
- If $D = 0$, output Q goes to 0, placing the circuit in the reset state

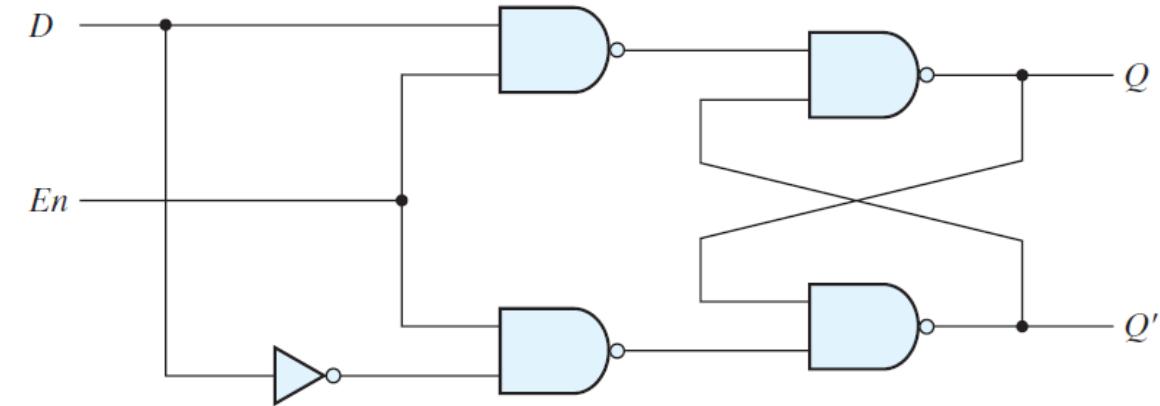

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

D Latch


- The D latch receives that designation from its ability to hold *data* in its internal storage
- It is suited for use as a temporary storage for binary information between a unit and its environment
- The binary information present at the data input of the D latch is transferred to the Q output when the enable input is asserted
- The output follows changes in the data input as long as the enable input is asserted
- This situation provides a path from input D to the output, and for this reason, the circuit is often called a *transparent* latch

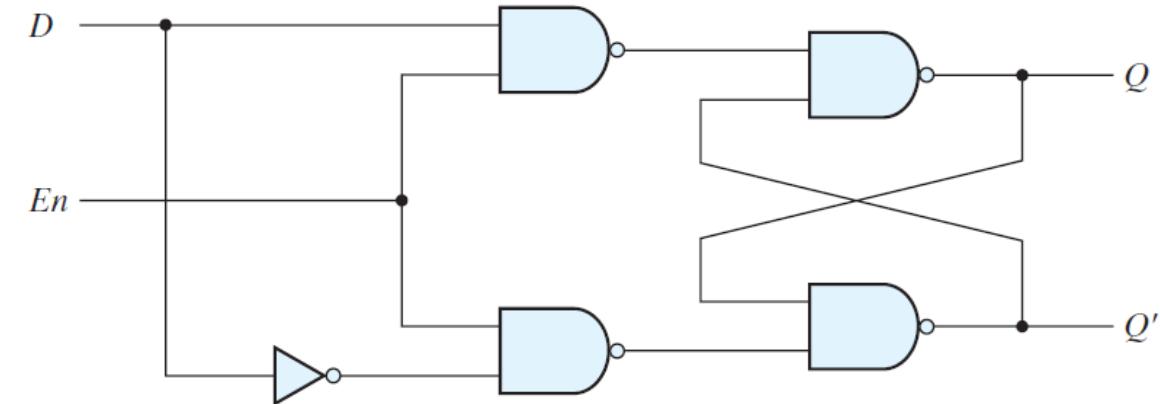

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

D Latch

- When the enable input signal is de-asserted, the binary information that was present at the data input at the time the transition occurred is retained (i.e., stored) at the Q output until the enable input is asserted again
- Note that an inverter could be placed at the enable input
- Then, depending on the physical circuit, the external enabling signal will be a value of 0 (active low) or 1 (active high)

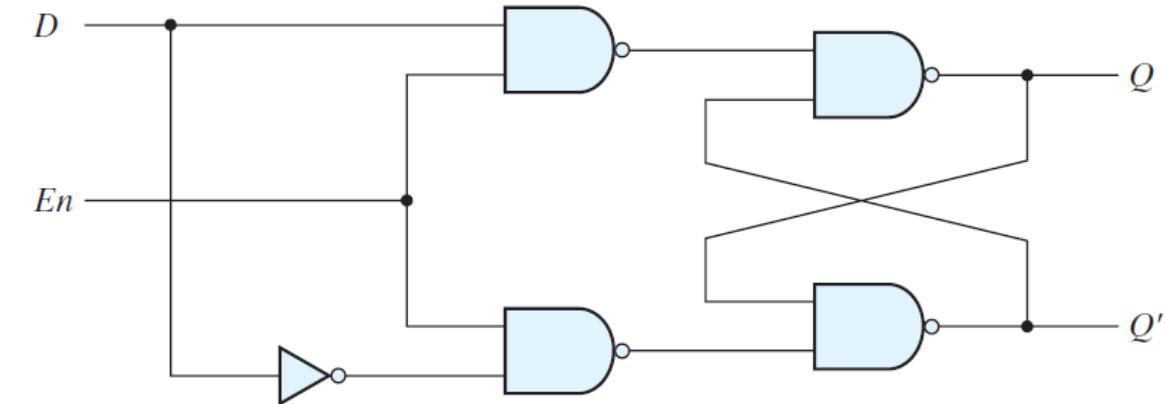

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

Lecture 17 – Sequential circuits 3

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 5

Problem with latches

- A sequential circuit has a feedback path from the outputs of the flip-flops to the input of the combinational circuit
- Consequently, the inputs of the latches are derived in part from the outputs of the same and other latches
- The state transitions of the latches start as soon as the enable/data pulse changes to the logic-1 level
- The new state of a latch appears at the output while the pulse is still active
- This output is connected to the inputs of the latches through the combinational circuit
- If the inputs applied to the latches change again while the enable pulse is still at the logic-1 level, the latches will respond to new values and a new output state may occur
- The result is an unpredictable situation, since the state of the latches may keep changing for as long as the enable pulse stays at the active level
- Because of this unreliable operation, the output of a latch cannot be applied directly or through combinational logic to the input of the same or another latch when all the latches are triggered by a enable signal
- <Cue: Hero's entry...>

Flip flops

- Enter: the Flip flop!




Flip flops

- Flip-flops are constructed in such a way as to make them operate properly when they are part of a sequential circuit that employs a common clock
- The problem with the latch is that it responds to a change in the *level* of a clock pulse
- A positive level response in the enable input allows changes in the output when the *D* input changes while the clock pulse stays at logic 1
- The key to the proper operation of a flip-flop is to trigger it only during a signal *transition*
- A clock pulse goes through two transitions: from 0 to 1 and the return from 1 to 0
- The positive transition (0->1) is defined as the positive edge and the negative transition (1->0) as the negative edge


Flip flops

- We can implement flip flops using two latches
- The first latch is called the master and the second the slave
- The circuit samples the D input and changes its output Q only at the negative edge of the synchronizing or controlling clock (designated as Clk)
- When the $Clk = 0$, the slave latch is enabled, and its output Q is equal to the master output Y
- When the input pulse changes, the data from the external D input are transferred to the master




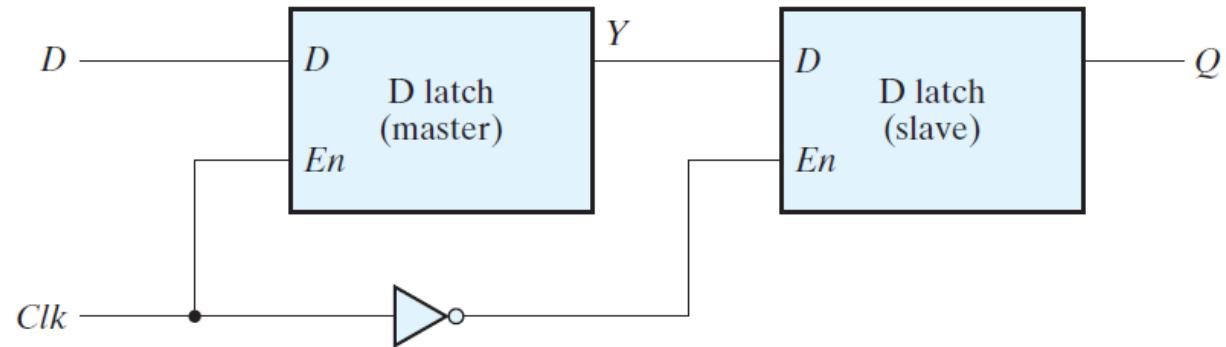


Flip flops


- The slave, however, is disabled as long as the clock remains at the 1 level, because its *enable* input is equal to 0
- Any change in the input changes the master output at Y , but cannot affect the slave output
- When the clock pulse returns to 0, the master is disabled and is isolated from the D input
- At the same time, the slave is enabled and the value of Y is transferred to the output of the flip-flop at Q
- Thus, *a change in the output of the flip-flop can be triggered only by and during the transition of the clock from 1 to 0 (-ve edge)*

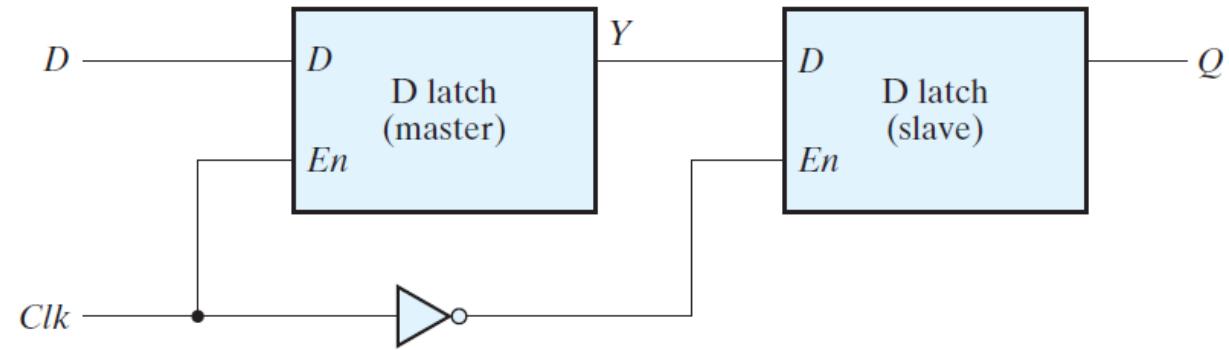

Graphical symbols

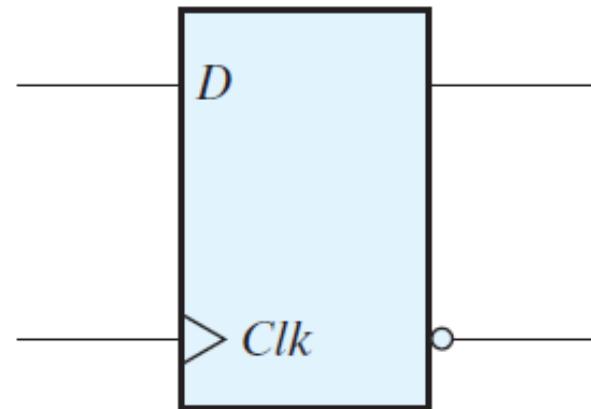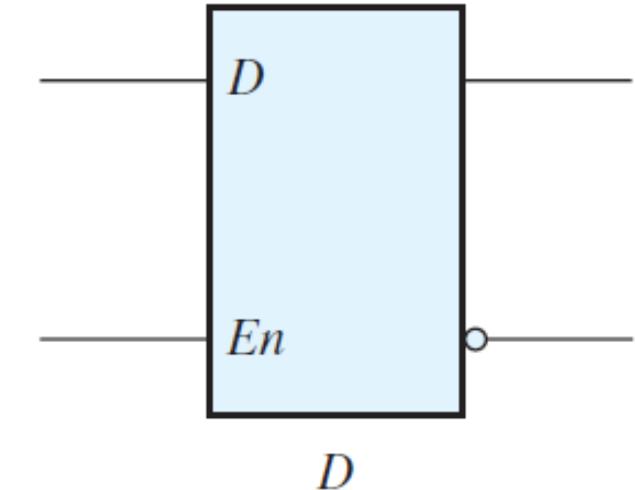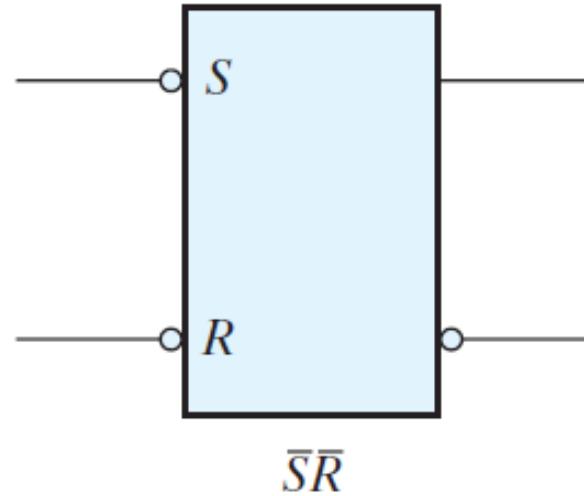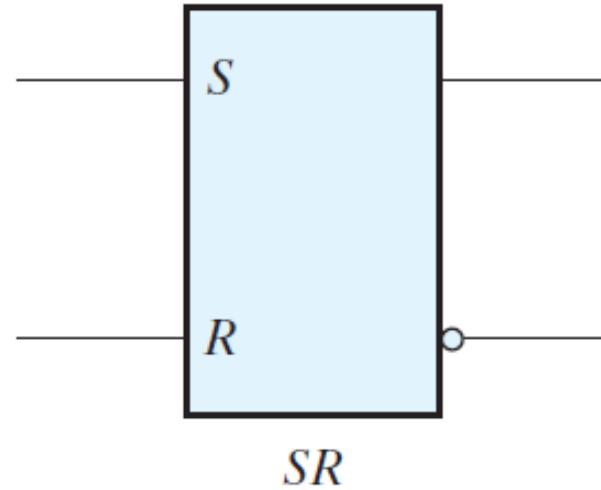

(a) Positive-edge

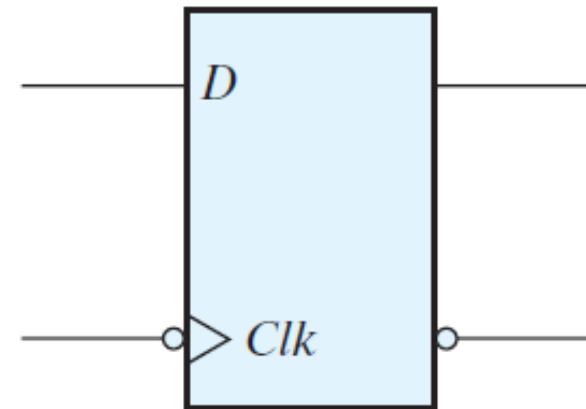

(a) Negative-edge

JK Flip Flop


- There are four operations we are looking to perform in a flip-flop: Set it to 1, reset it to 0, retain or complement its output
- With only a single input, the D flip-flop can set or reset the output, depending on the value of the D input immediately before the clock transition
- Synchronized by a clock signal, the JK flip-flop has two inputs and performs all four operations
- The J input sets the flip-flop to 1, the K input resets it to 0, and when both inputs are enabled, the output is complemented
- This can be obtained if the D input is:

$$D = JQ' + KQ$$

JK Flip Flop

$$D = JQ' + K'Q$$

- When $J = 1$ and $K = 0$, $D = Q' + Q = 1$, so the next clock edge sets the output to 1
- When $J = 0$ and $K = 1$, $D = 0$, so the next clock edge resets the output to 0
- When both $J = K = 1$ and $D = Q'$, the next clock edge complements the output
- When both $J = K = 0$ and $D = Q$, the clock edge leaves the output unchanged
- Because of their versatility, JK flip-flops are called *universal flip-flops*

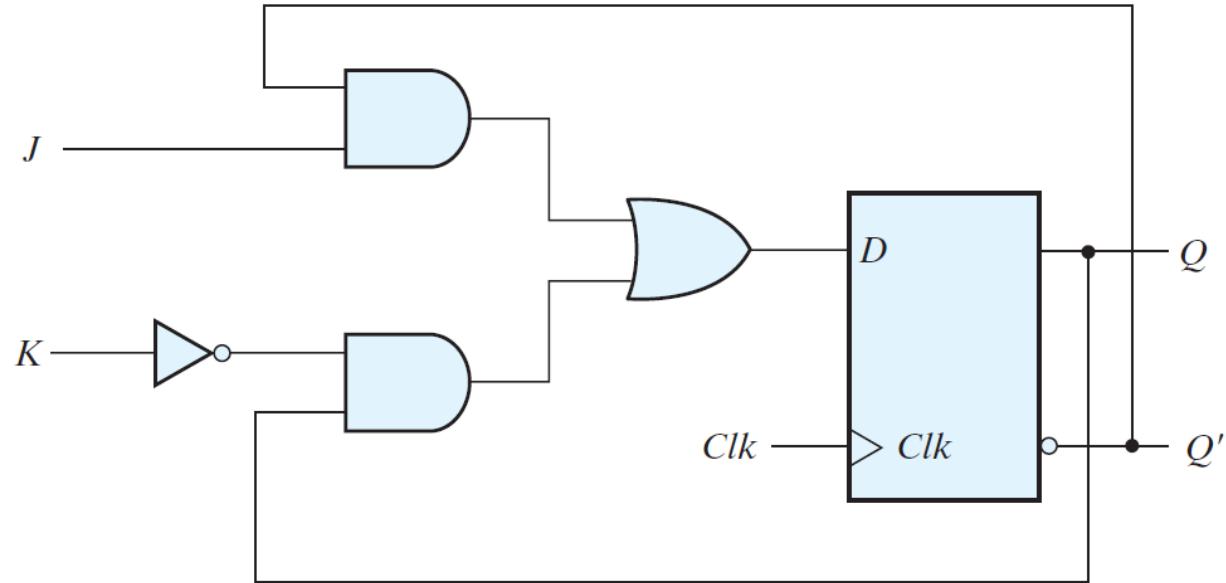

(a) Circuit diagram

JK Flip-Flop

<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement


Lecture 18 – Sequential circuits 4

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST


Chapter 5

D Flip Flop

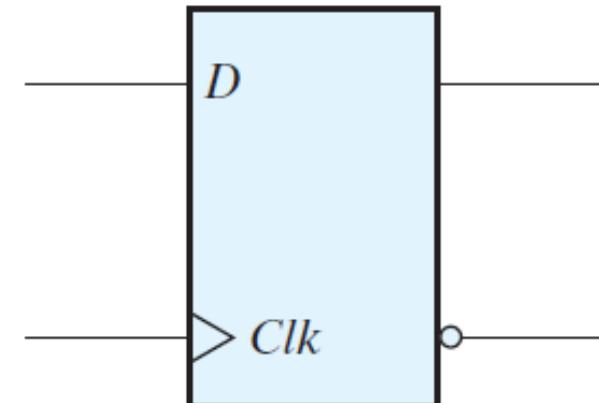- Transparent flip-flop
- The bit at D is transferred to Q at the edge of the clock
- The information is retained upto the next edge of the clock



(a) Positive-edge

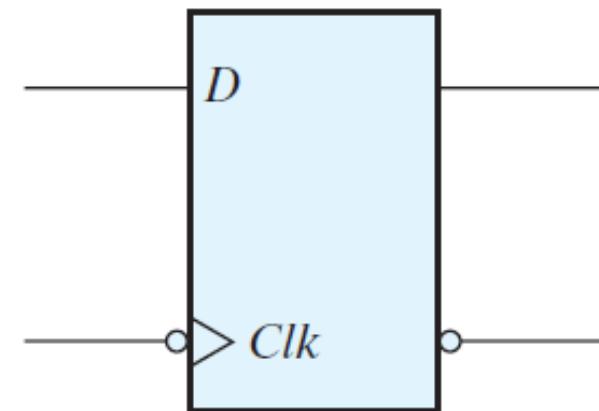


(a) Negative-edge

JK Flip Flop

$$D = JQ' + K'Q$$

- When $J = 1$ and $K = 0$, $D = Q' + Q = 1$, so the next clock edge sets the output to 1
- When $J = 0$ and $K = 1$, $D = 0$, so the next clock edge resets the output to 0
- When both $J = K = 1$ and $D = Q'$, the next clock edge complements the output
- When both $J = K = 0$ and $D = Q$, the clock edge leaves the output unchanged
- Because of their versatility, JK flip-flops are called *universal flip-flops*

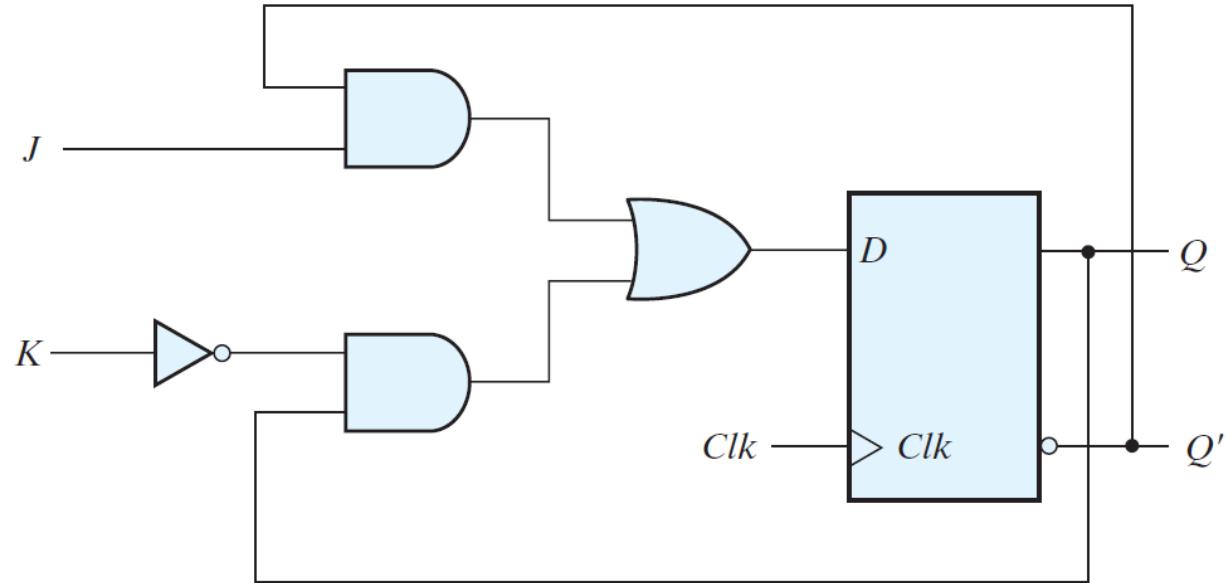


(a) Circuit diagram

JK Flip-Flop

J	K	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T Flip Flop

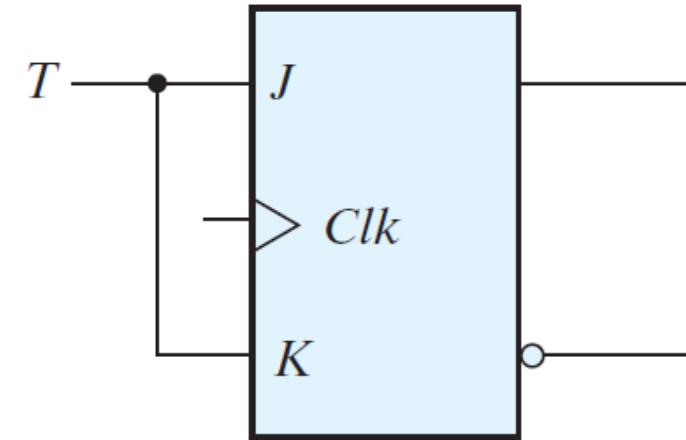- The T (toggle) flip-flop is a complementing flip-flop and can be obtained from a JK flip-flop when inputs J and K are tied together
- When $T = 0$ ($J = K = 0$), a clock edge does not change the output
- When $T = 1$ ($J = K = 1$), a clock edge complements the output
- The complementing flip-flop is useful for designing binary counters




(a) From JK flip-flop

T Flip-Flop		
T	Q(t + 1)	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

T Flip Flop

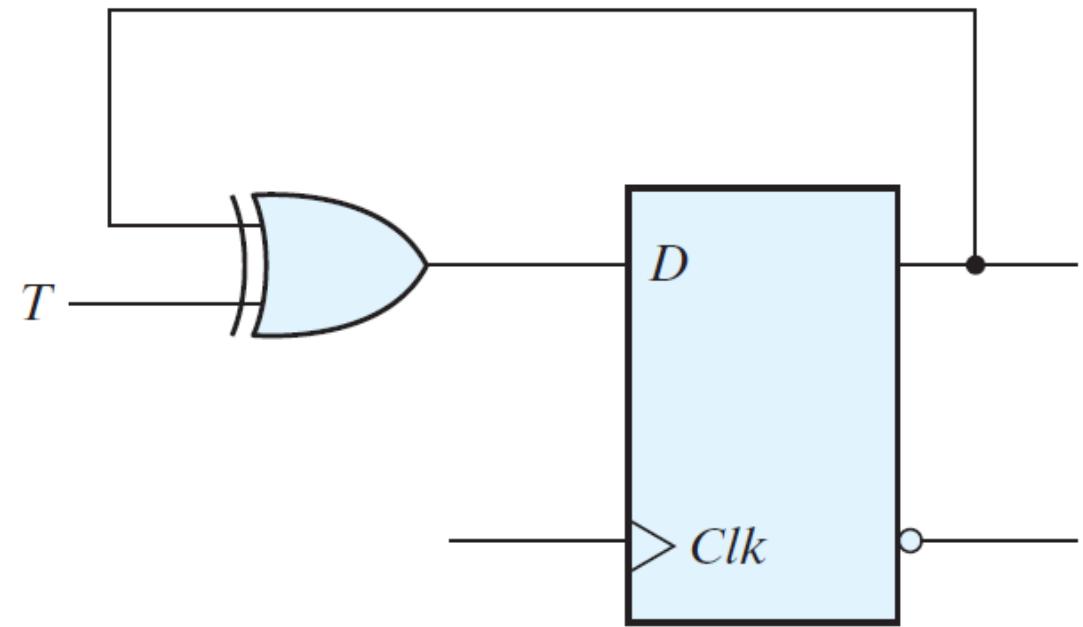- The T flip-flop can also be constructed using a D flip-flop
- The expression for the D input is:
$$D = T'Q + TQ'$$
- When $T = 0$, $D = Q$ and there is no change in the output
- When $T = 1$, $D = Q'$ and the output complements
- The graphic symbol for this flip-flop has a T symbol in the input




T Flip-Flop

T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Asynchronous inputs

- Some flip-flops have asynchronous inputs that are used to force the flip-flop to a particular state independently of the clock
- The input that sets the flip-flop to 1 is called *preset* or *direct set*
- The input that clears the flip-flop to 0 is called *clear* or *direct reset*
- When power is turned on in a digital system, the state of the flip-flops is unknown
- The direct inputs are useful for bringing all flip-flops in the system to a known starting state prior to the clocked operation.
- When the reset input is 0, it forces output Q' to stay at 1, which, in turn, clears output Q to 0, thus resetting the flip-flop

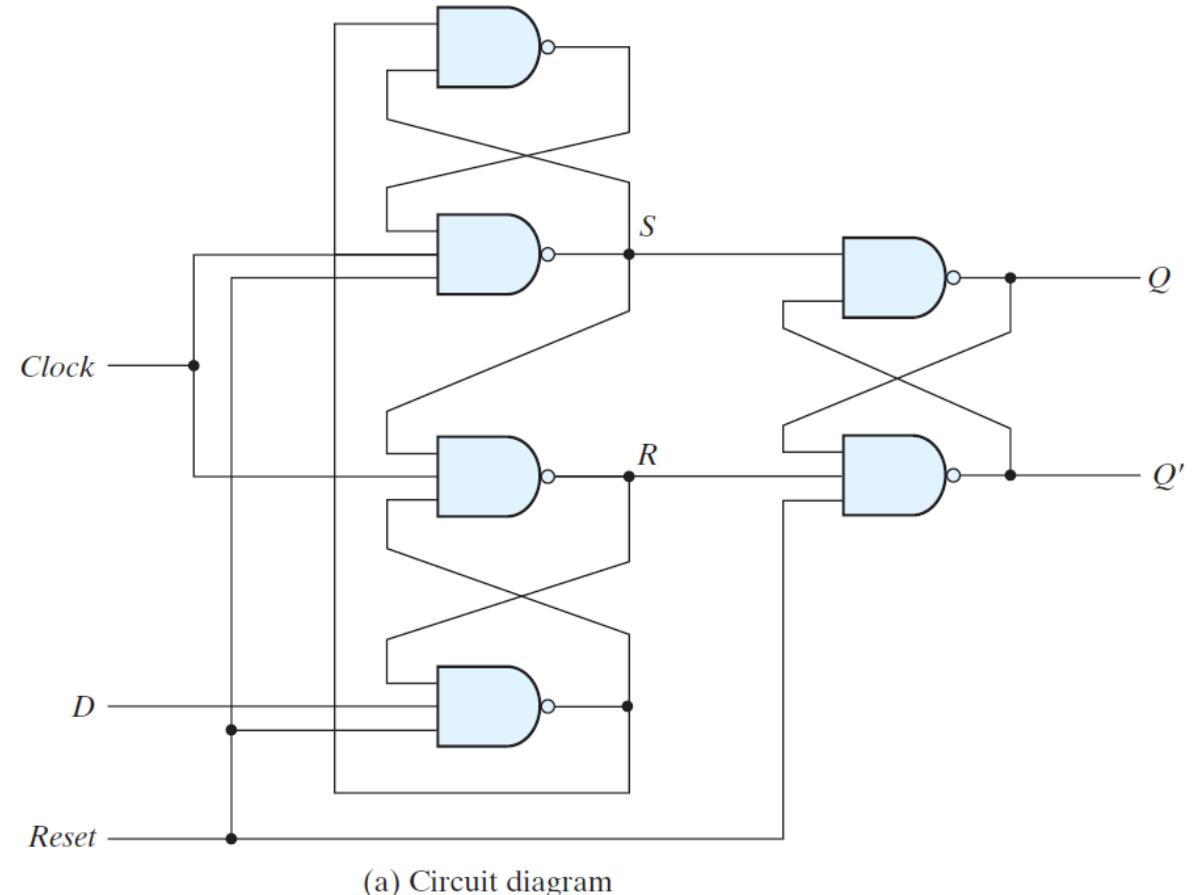

Analysis


- Analysis describes what a given circuit will do under certain operating conditions
- The behavior of a clocked sequential circuit is determined from the inputs, the outputs, and the state of its flip-flops
- The outputs and the next state are both a function of the inputs and the present state
- The analysis of a sequential circuit consists of obtaining a table or a diagram for the time sequence of inputs, outputs, and internal states
- It is also possible to write Boolean expressions that describe the behavior of the sequential circuit
- These expressions must include the necessary time sequence, either directly or indirectly

Analysis

- Consider this sequential circuit
- It consists of two D flip-flops A and B , an input x and an output y
- Since the D input of a flip-flop determines the value of the next state (i.e., the state reached after the clock transition), it is possible to write a set of state equations for the circuit as:

$$A(t + 1) = A(t)x(t) + B(t)x(t)$$


$$B(t + 1) = A'(t)x(t)$$

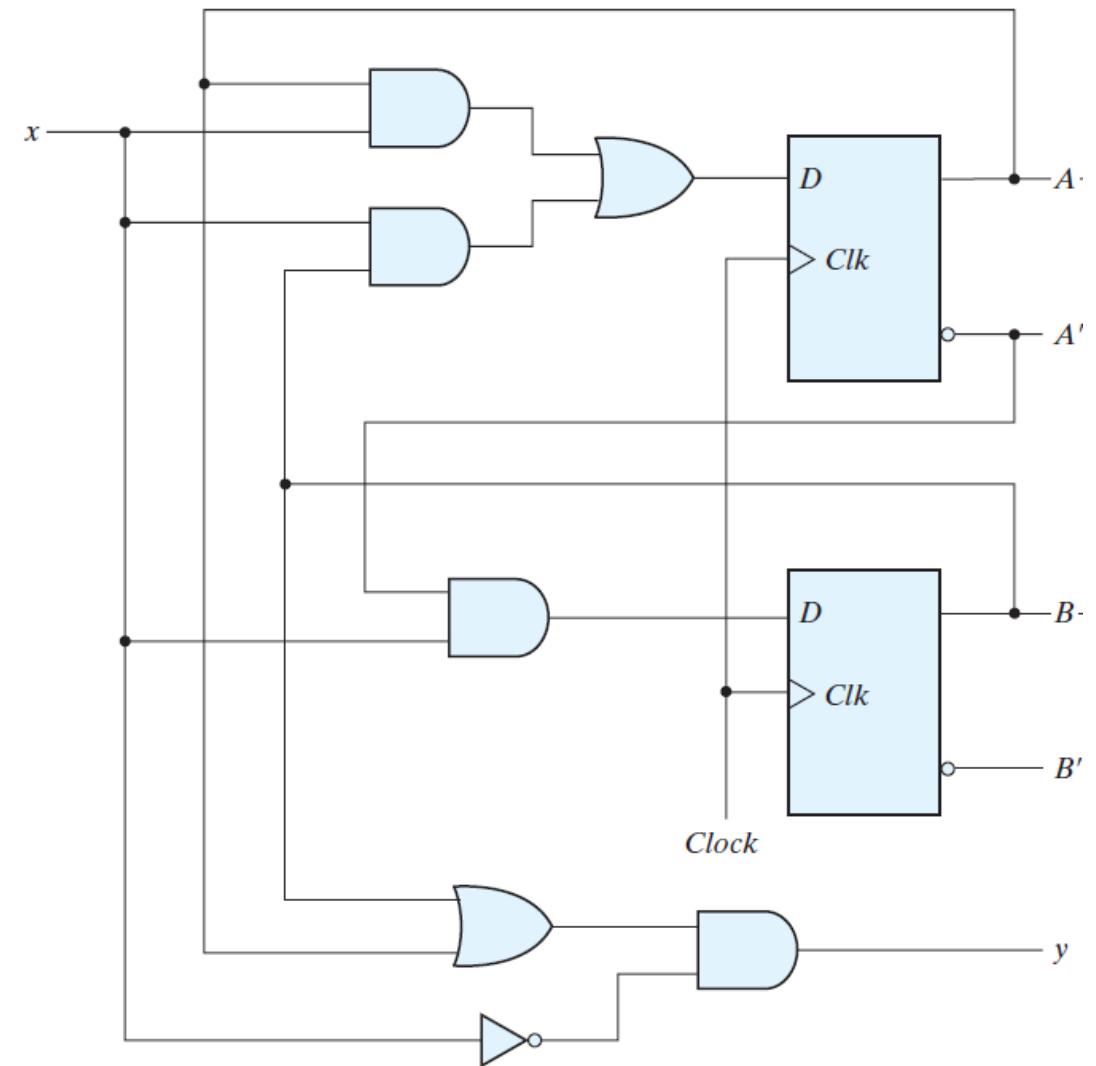

State equations

- A state equation is an algebraic expression that specifies the condition for a flip-flop state transition
 - The left side of the equation, with $(t + 1)$, denotes the next state of the flip-flop one clock edge later
 - The right side of the equation is a Boolean expression that specifies the present state and input conditions
 - Since all the variables in the Boolean expressions are a function of the present state, we can omit the designation (t) after each variable for convenience and can express the state equations in the more compact form
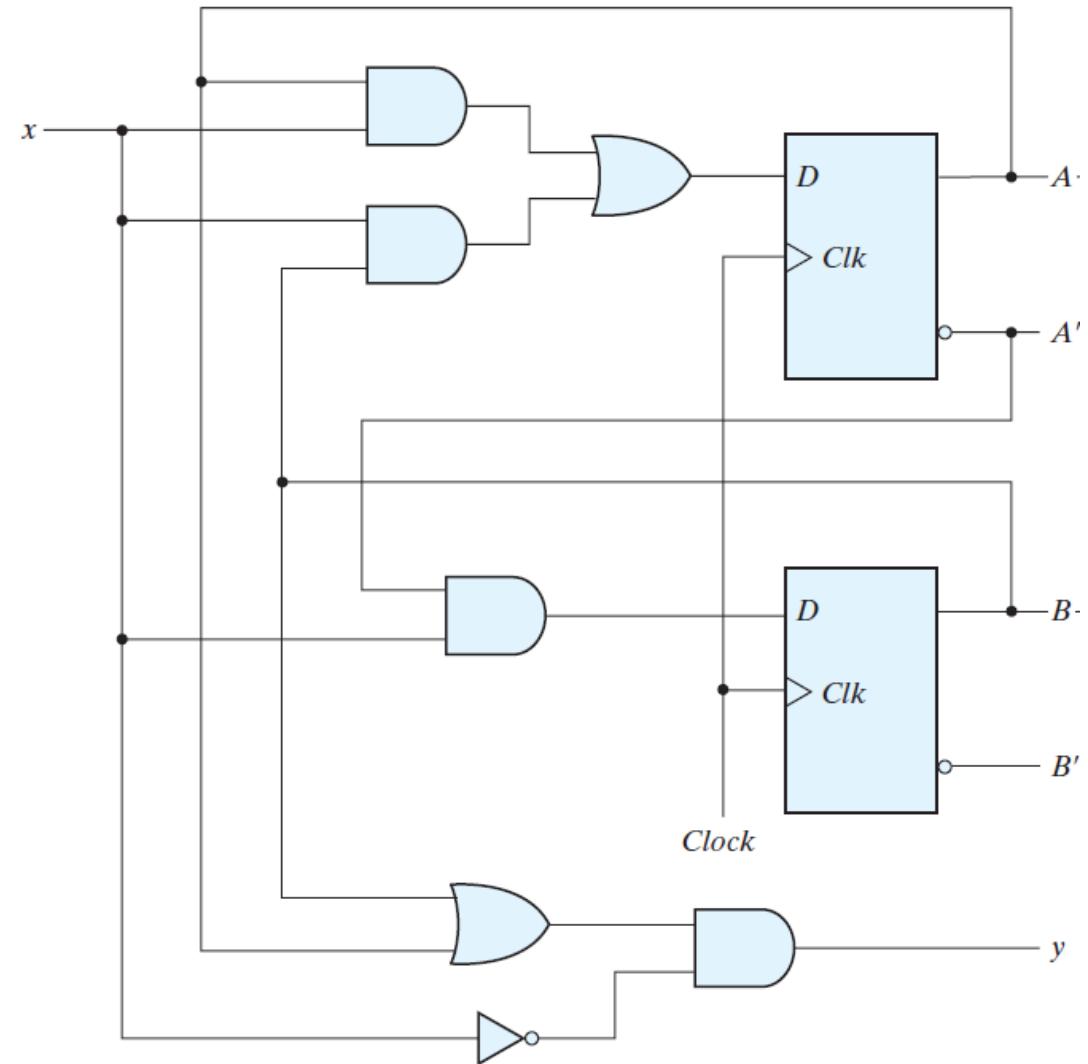
$$\begin{aligned} A(t+1) &= Ax + Bx \\ B(t+1) &= A'x \end{aligned}$$



State equations


- The Boolean expressions for the state equations can be derived directly from the gates that form the combinational circuit part of the sequential circuit, since the D values of the combinational circuit determine the next state

- Similarly, the present-state value of the output can be expressed algebraically as

$$y(t) = [A(t) + B(t)]x'(t)$$

- By removing the symbol (t) for the present state, we obtain the output Boolean equation:

$$y = (A + B)x'$$

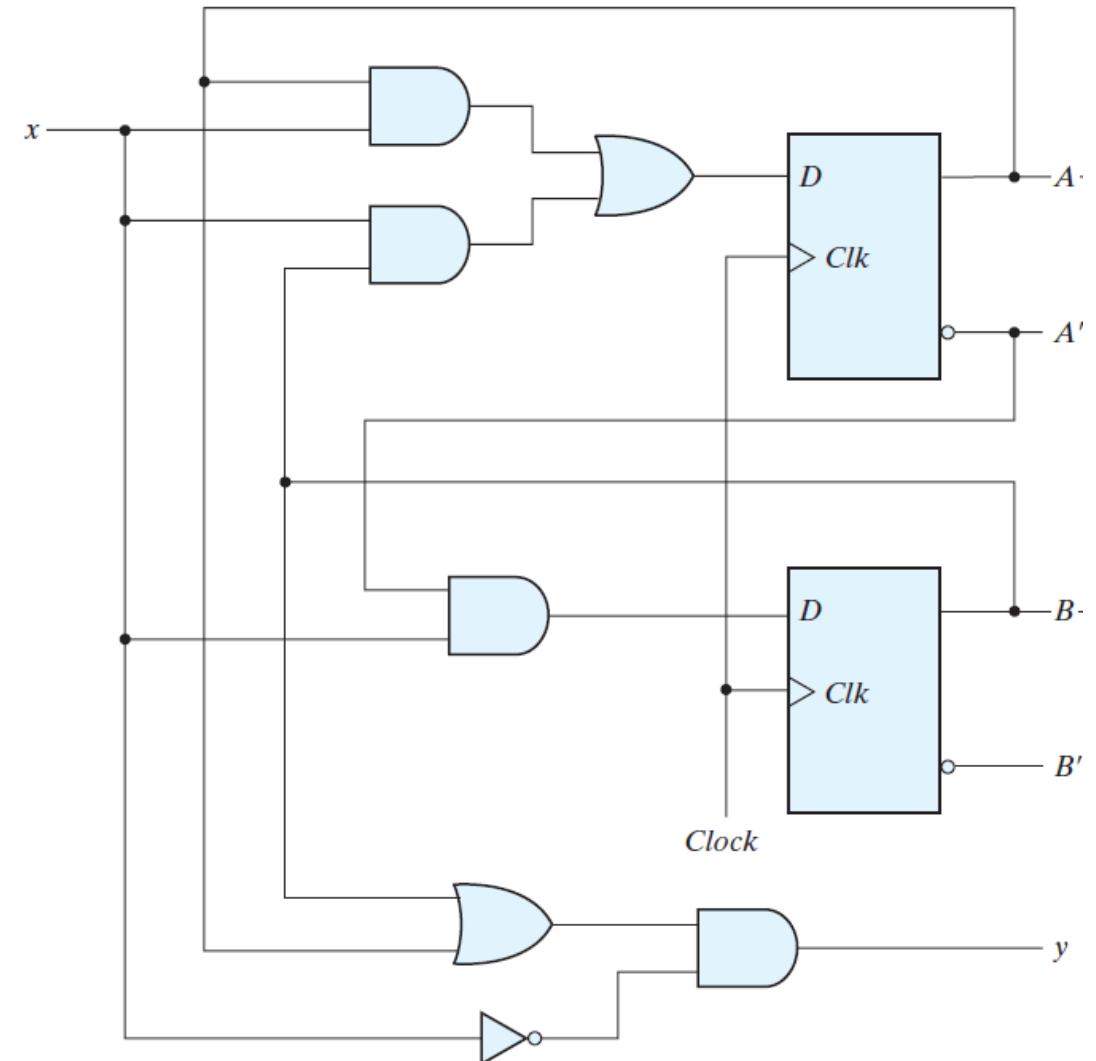

State tables

- Similar to truth tables, the derivation of a state table requires listing all possible binary combinations of present states and inputs
- In this case, we have eight binary combinations from 000 to 111
- The next-state values are then determined from the logic diagram or from the state equations
- The next state of flip-flops must satisfy the state equations:

$$A(t + 1) = Ax + Bx$$
$$B(t + 1) = A'x$$

Output is derived from:

$$y = (A + B)x'$$

Present State		Input
A	B	x
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

State tables

- In general, a sequential circuit with m flipflops and n inputs needs 2^{m+n} rows in the state table
- The binary numbers from 0 through $2^{m+n} - 1$ are listed under the present-state and input columns
- The next-state section has m columns, one for each flip-flop
- The binary values for the next state are derived directly from the state equations
- The output section has as many columns as there are output variables
- Its binary value is derived from the circuit or from the Boolean function in the same manner as in a truth table

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State tables

- It is sometimes convenient to express the state table in a slightly different form having only three sections: present state, next state, and output
- The input conditions are enumerated under the next-state and output sections

Present State	Next State				Output	
	x = 0		x = 1		x = 0	x = 1
A	B	A	B	y	y	
0	0	0	0	0	0	
0	1	0	0	1	0	
1	0	0	0	1	0	
1	1	0	0	1	0	

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	0	0

State diagram


- The information available in a state table can be represented graphically in the form of a state diagram
- In this type of diagram, a state is represented by a circle, and the (clock-triggered) transitions between states are indicated by directed lines connecting the circles
- The binary number inside each circle identifies the state of the flip-flops
- The directed lines are labeled with two binary numbers separated by a slash
- The input value during the present state is labeled first, and the number after the slash gives the output during the present state with the given input

Present State		Next State				Output	
		$x = 0$	$x = 1$	$x = 0$	$x = 1$		
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

State diagram

- For example, the directed line from state 00 to 01 is labeled 1/0, meaning that when the sequential circuit is in the present state 00 and the input is 1, the output is 0
- After the next clock cycle, the circuit goes to the next state, 01
- If the input changes to 0, then the output becomes 1, but if the input remains at 1, the output stays at 0
- This information is obtained from the state diagram along the two directed lines emanating from the circle with state 01
- A directed line connecting a circle with itself indicates that no change of state occurs

Present State		Next State				Output	
		$x = 0$	$x = 1$	$x = 0$	$x = 1$		
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

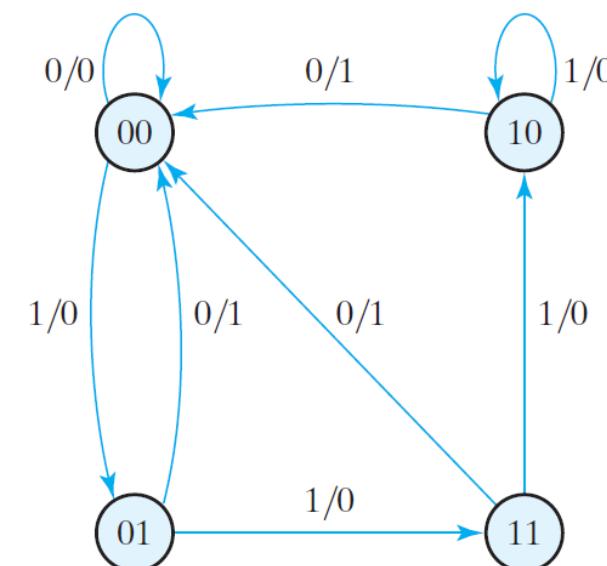

Lecture 19 – Sequential circuits 5

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 5

Design procedure

- The procedure for designing synchronous sequential circuits can be summarized by a list of recommended steps:
 1. Derive a state diagram for the circuit
 2. Assign binary values to the states
 3. Obtain the binary-coded state table
 4. Derive the simplified flip-flop input equations and output equations
 5. Draw the logic diagram

The sequence of three
detector

Sequence of three


- Suppose we wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*)
- We start with state S_0 , the reset state
- If the input is 0, the circuit stays in S_0 , but if the input is 1, it goes to state S_1 to indicate that a 1 was detected
- If the next input is 1, the change is to state S_2 to indicate the arrival of two consecutive 1's, but if the input is 0, the state goes back to S_0

Sequence of three

- The third consecutive 1 sends the circuit to state S_3
- If more 1's are detected, the circuit stays in S_3
- Thus, the circuit stays in S_3 as long as there are three or more consecutive 1's received
- The output is 1 when the circuit is in state S_3 and is 0 otherwise

Sequence of three

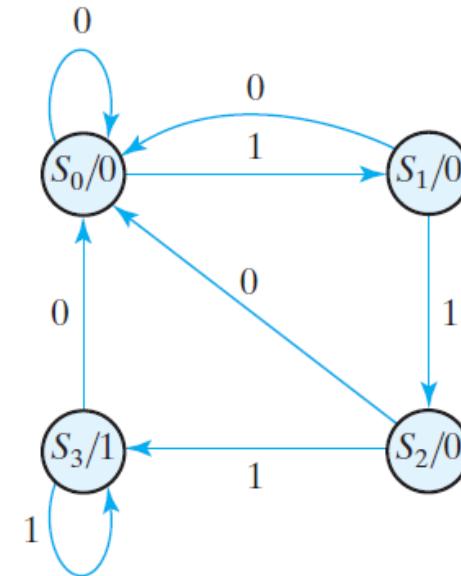- To design the circuit, we need to assign binary codes to the states and list the state table
- The table is derived from the state diagram with a sequential binary assignment
- We choose two D flip-flops to represent the four states, and we label their outputs A and B
- There is one input x and one output y



Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Sequence of three

- The flip-flop input equations can be obtained directly from the next-state columns of A and B and expressed in sum-of-minterms form as:

$$A(t + 1) = D_A(A, B, x) = \sum(3, 5, 7)$$

$$B(t + 1) = D_B(A, B, x) = \sum(1, 5, 7)$$


$$y(A, B, x) = \sum(6, 7)$$

- Using K-maps, we can find the expressions for D_A , D_B and y as:

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

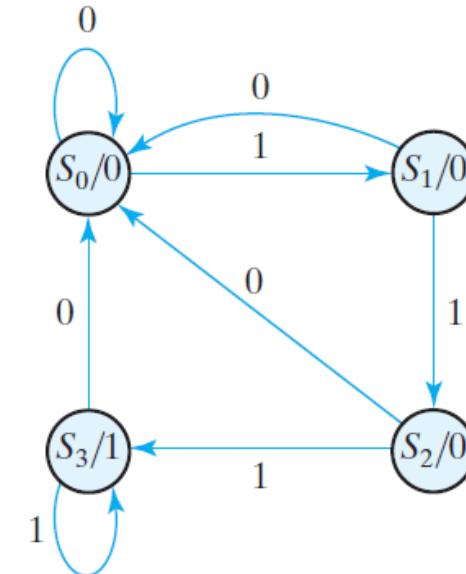

- The flip-flop input equations can be obtained directly from the next-state columns of A and B and expressed in sum-of-minterms form as:

$$A(t + 1) = D_A(A, B, x) = \sum(3, 5, 7)$$

$$B(t + 1) = D_B(A, B, x) = \sum(1, 5, 7)$$

$$y(A, B, x) = \sum(6, 7)$$


- Using K-maps, we can find the expressions for D_A , D_B and y as:

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

Sequence of three

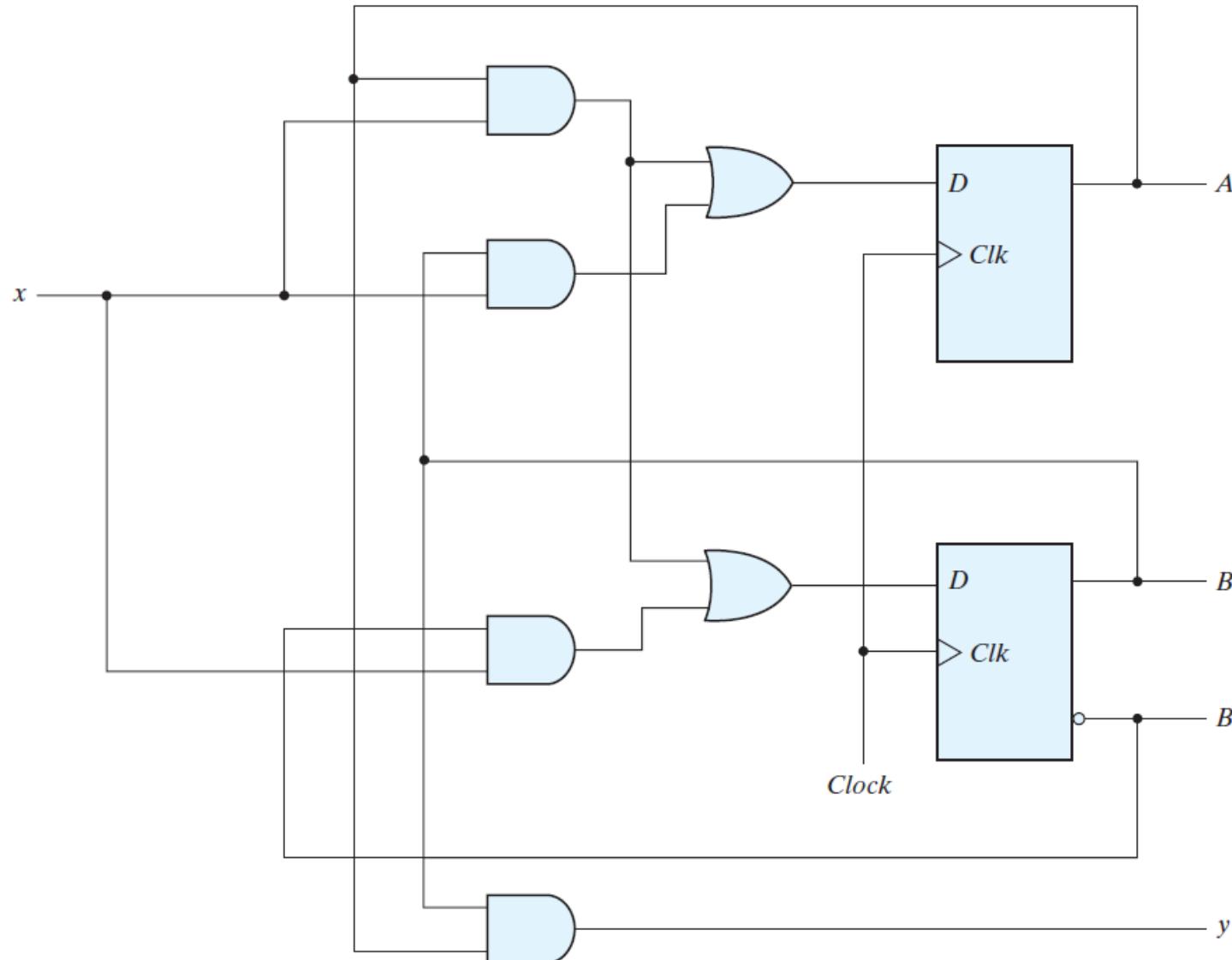


The vending machine

The vending machine


- Lets say we are asked to design a circuit for a vending machine that dispenses candy for Rs. 3
- The input consists of a coin slot that can accept Rs. 1 and Rs. 2 coins
- The deposit of these coins by the user is detected by a circuit that gives out two outputs x and y – when Rs. 1 is inserted, y goes to one, and when Rs. 2 is inserted, x goes to one, for one clock cycle. x and y are at zero by default
- Only one coin can be entered at once
- We need to design a circuit that takes x and y as inputs and outputs 1 if the sum is ≥ 3 , so that the machine can dispense the candy

The vending machine

- Lets say we are asked to design a circuit for a vending machine that dispenses candy for Rs. 3
- The input consists of a coin slot that can accept Rs. 1 and Rs. 2 coins
- The deposit of these coins by the user is detected by a circuit that gives out two outputs x and y – when Rs. 1 is inserted, y goes to one, and when Rs. 2 is inserted, x goes to one, for one clock cycle. x and y are at zero by default
- Only one coin can be entered at once
- We need to design a circuit that takes x and y as inputs and outputs 1 if the sum is ≥ 3 , so that the machine can dispense the candy

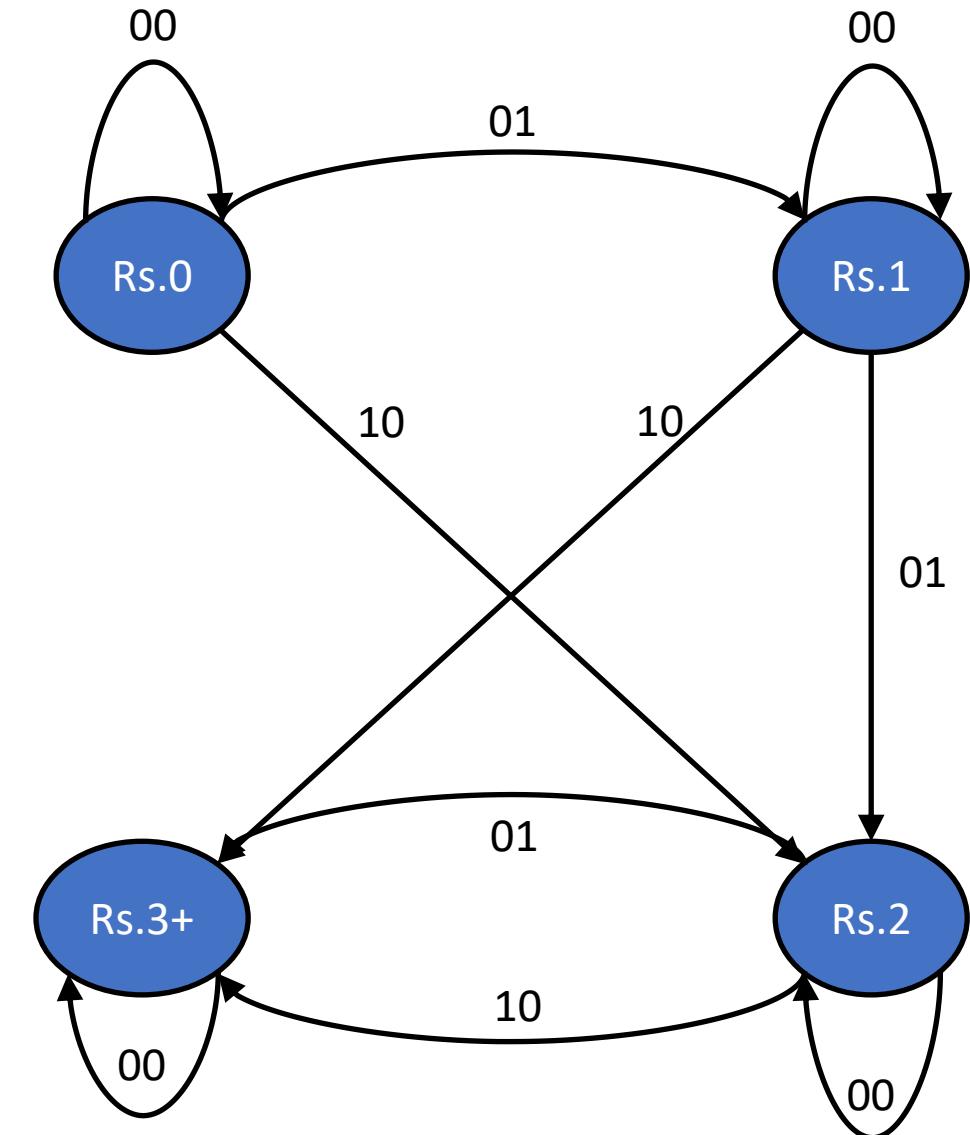


The vending machine

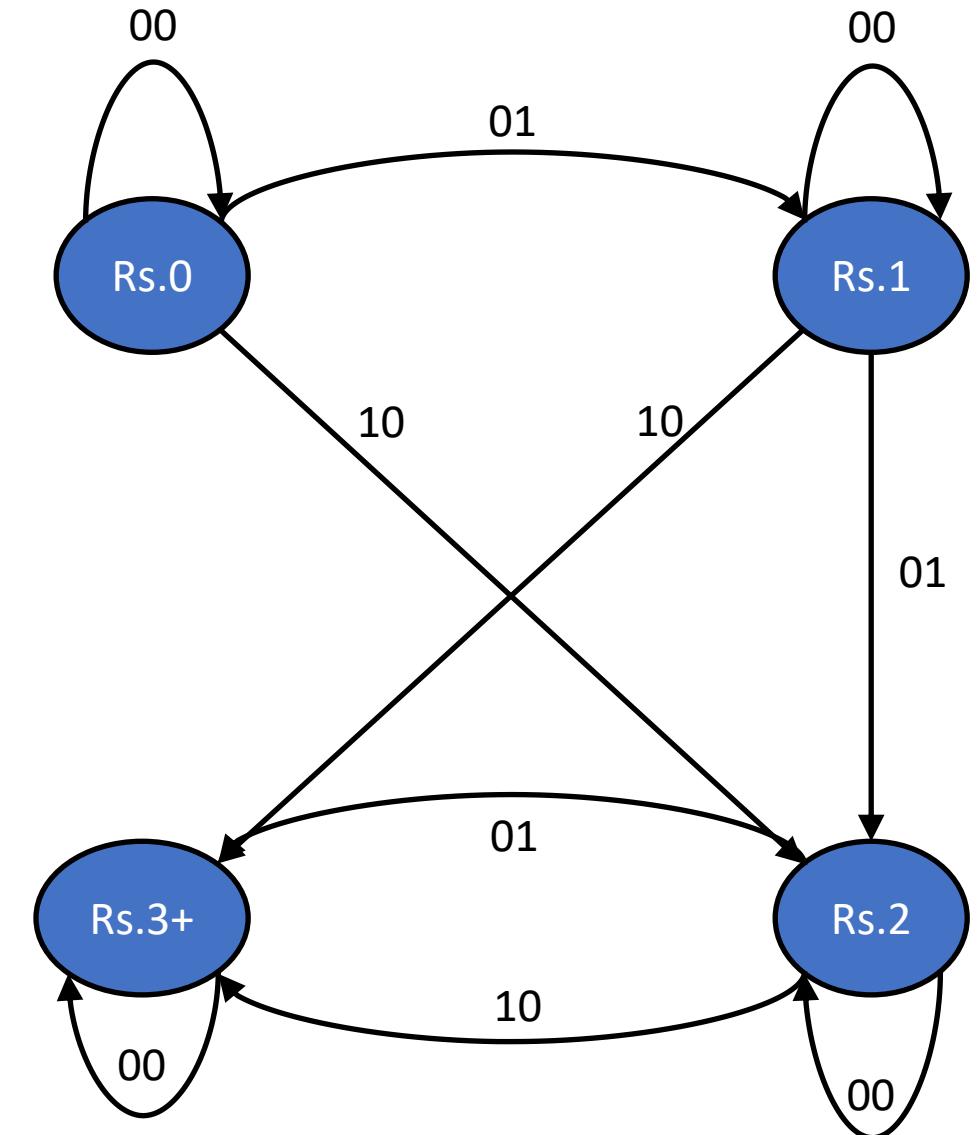

The vending machine

A	B	x	y	A(t+1)	B(t+1)	z
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	x	x	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
0	1	1	1	x	x	0
1	0	0	0	1	0	0
1	0	0	1	1	1	0
1	0	1	0	1	1	0
1	0	1	1	x	x	0
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	x	x	1

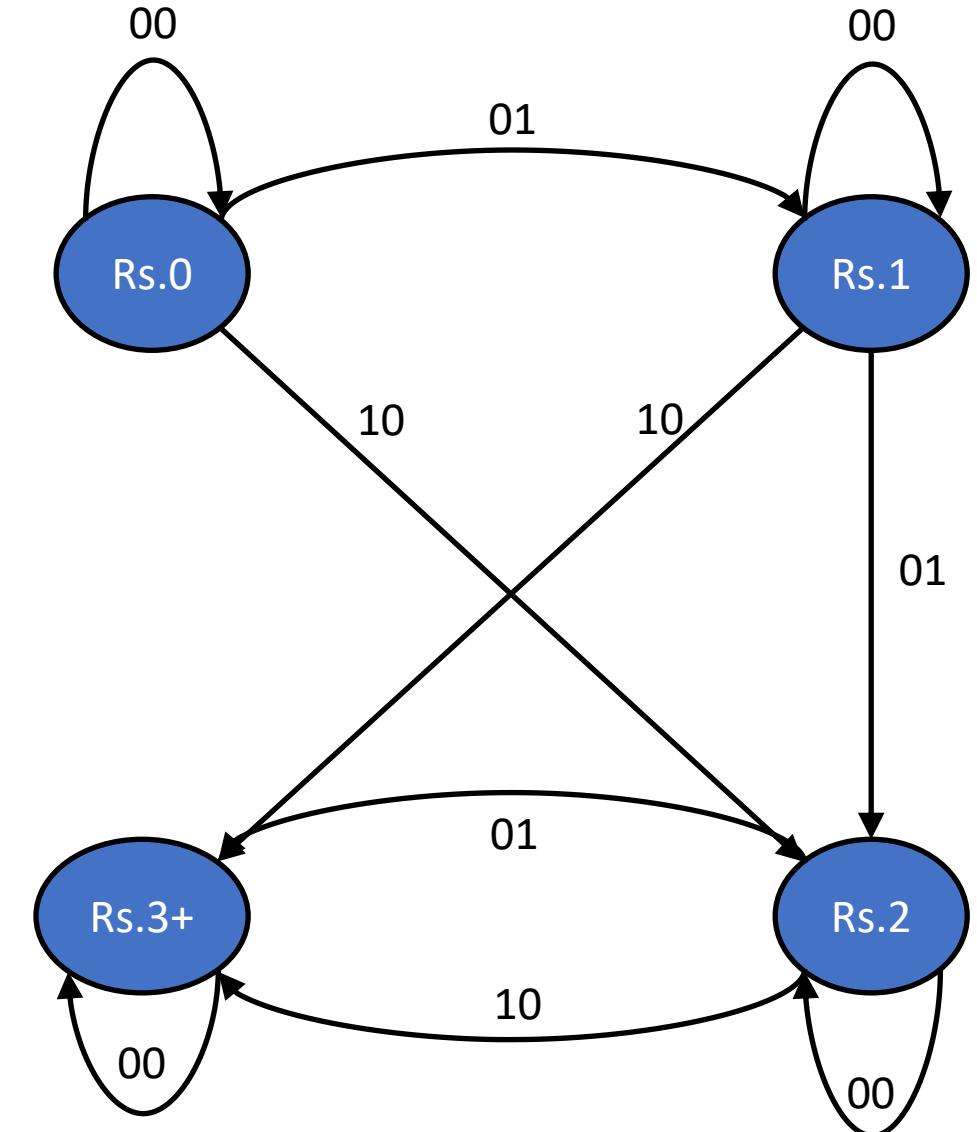

The vending machine

A(t+1)

AB \ xy


		x			
		00	01	11	10
AB		m_0	m_1	m_3	m_2
A	00	0	0	X	1
	01	0	1	X	1
	11	1	1	X	1
	10	1	1	X	1

y

B

$$A(t + 1) = A + x + By$$

The vending machine

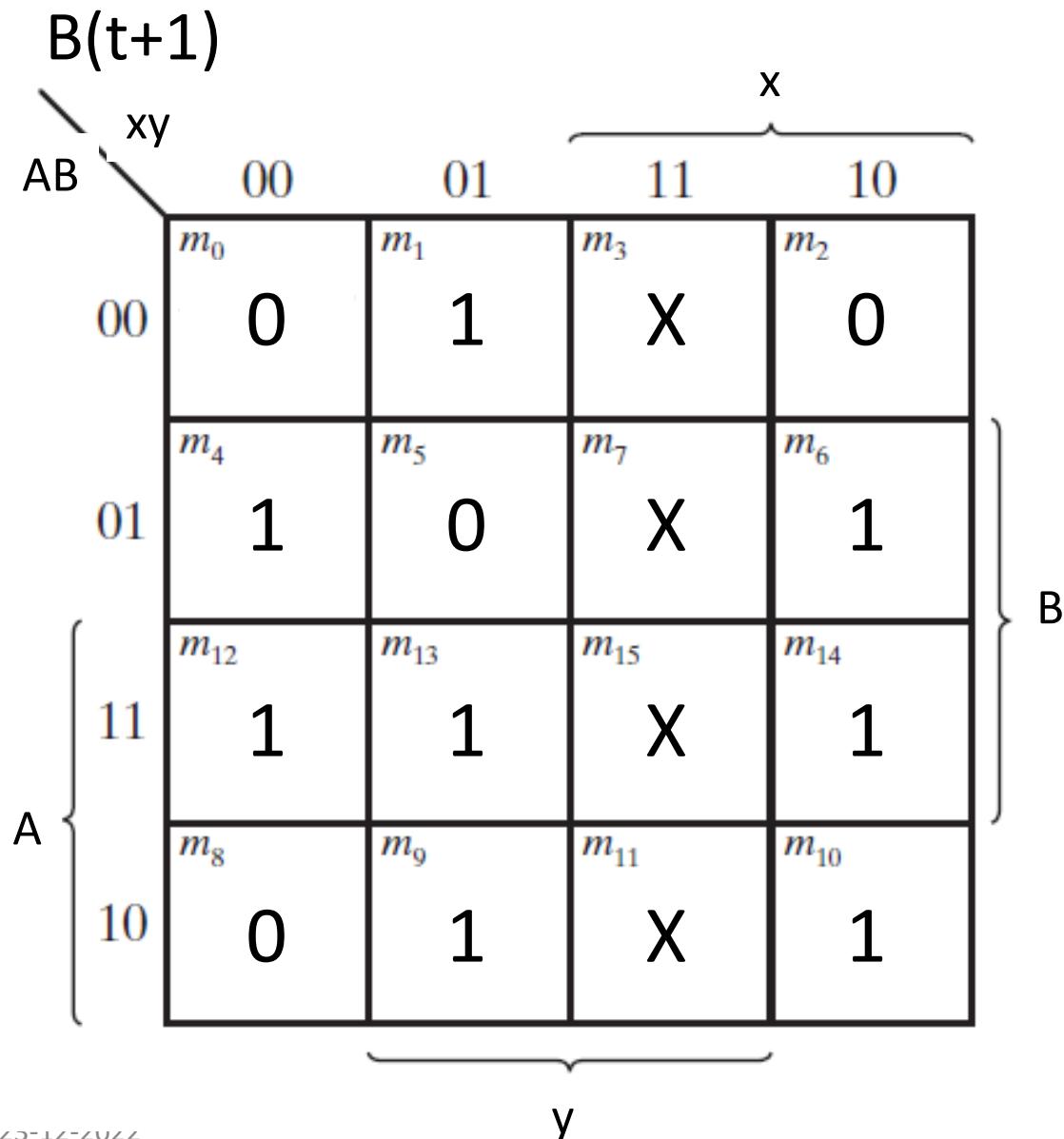

$$B(t + 1) = (B + y + Ax)(B' + y' + A)$$

Lecture 20 – Registers and Counters 1

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST


Chapter 6

Registers and counters

- A *register* is a group of flip-flops, each one of which shares a common clock and is capable of storing one bit of information
- An n -bit register consists of a group of n flip-flops capable of storing n bits of binary information
- A *counter* is essentially a register that goes through a predetermined sequence of binary states
- The counter circuit is designed in such a way as to produce the prescribed sequence of states
- Although counters are a special type of register, it is common to differentiate them by giving them a different name


Registers

- Consider a register constructed with four D -type flip-flops to form a four-bit data storage register
- The common clock input triggers all flip-flops on the positive edge of each pulse, and the binary data available at the four inputs are transferred into the register
- The value of (I_3, I_2, I_1, I_0) immediately before the clock edge determines the value of (A_3, A_2, A_1, A_0) after the clock edge

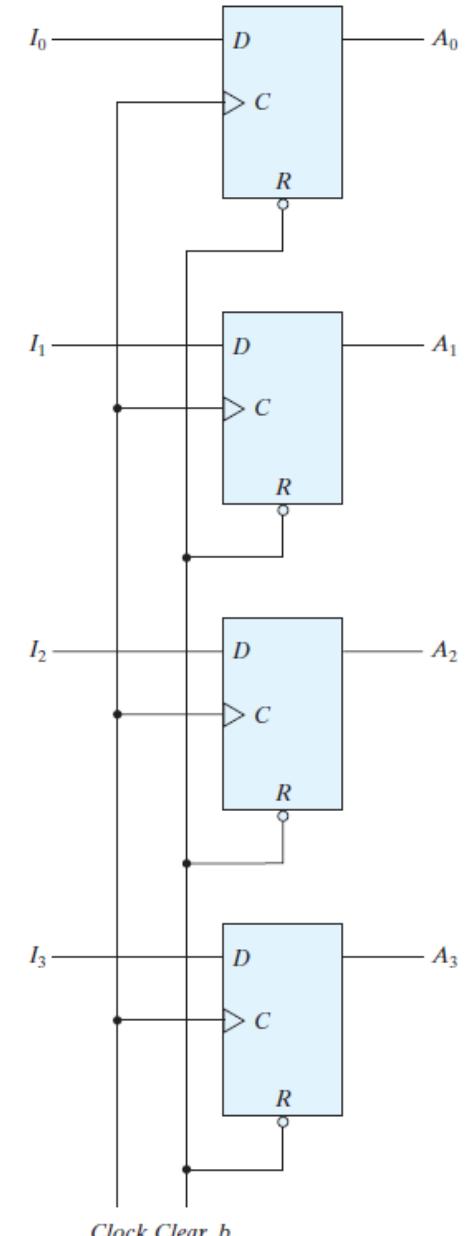

Registers

- The four outputs can be sampled at any time to obtain the binary information stored in the register
- The input *Clear_b* goes to the active-low *R* (reset) input of all four flip-flops
- When this input goes to 0, all flip-flops are reset asynchronously
- The *Clear_b* input is useful for clearing the register to all 0's prior to its clocked operation
- The *R* inputs must be maintained at logic 1 (i.e., de-asserted) during normal clocked operation

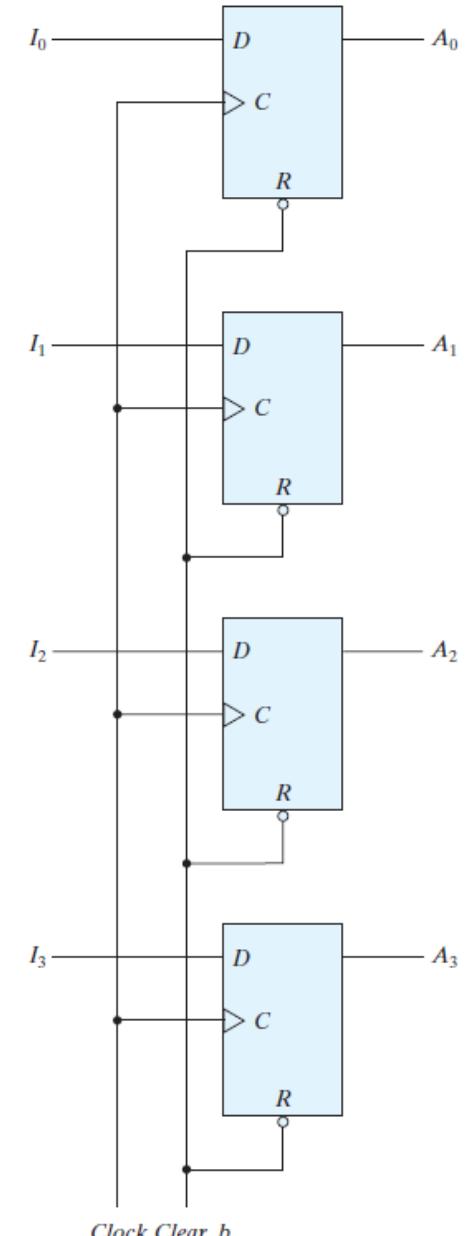

Registers with load input


- Synchronous digital systems have a master clock generator that supplies a continuous train of clock pulses
- The pulses are applied to all flip-flops and registers in the system
- The master clock acts like a drum that supplies a constant beat to all parts of the system (like the heart-beat of the processor)
- However, we might not be interested in changing data in the register every time, in some cases, we may want to keep the data unchanged
- A separate control signal must be used to decide which register operation will execute at each clock pulse
- The transfer of new information into a register is referred to as *loading* or *updating* the register

Registers with load input

- In this configuration, if the contents of the register must be left unchanged, the inputs must be held constant, or the clock must be inhibited from the circuit
- However, inserting gates into the clock path is ill advised because it means that logic is performed with clock pulses
- The insertion of logic gates produces uneven propagation delays between the master clock and the inputs of flip-flops
- To fully synchronize the system, we must ensure that all clock pulses arrive at the same time anywhere in the system, so that all flip-flops trigger simultaneously
- For this reason, it is advisable to control the operation of the register with the D inputs, rather than controlling the clock in the C inputs of the flip-flops
- This creates the effect of a gated clock, but without affecting the clock path of the circuit


Registers with load input

- A four-bit data-storage register with a load control input is as shown
- The additional gates implement a two-channel mux whose output drives the input to the register with either the data bus or the output of the register
- When the load input is 0, the data at the four external inputs are transferred into the register with the next positive edge of the clock
- When the load input is 1, the outputs of the flip-flops are connected to their respective inputs
- The feedback connection from output to input is necessary because a *D* flip-flop does not have a “no change” condition

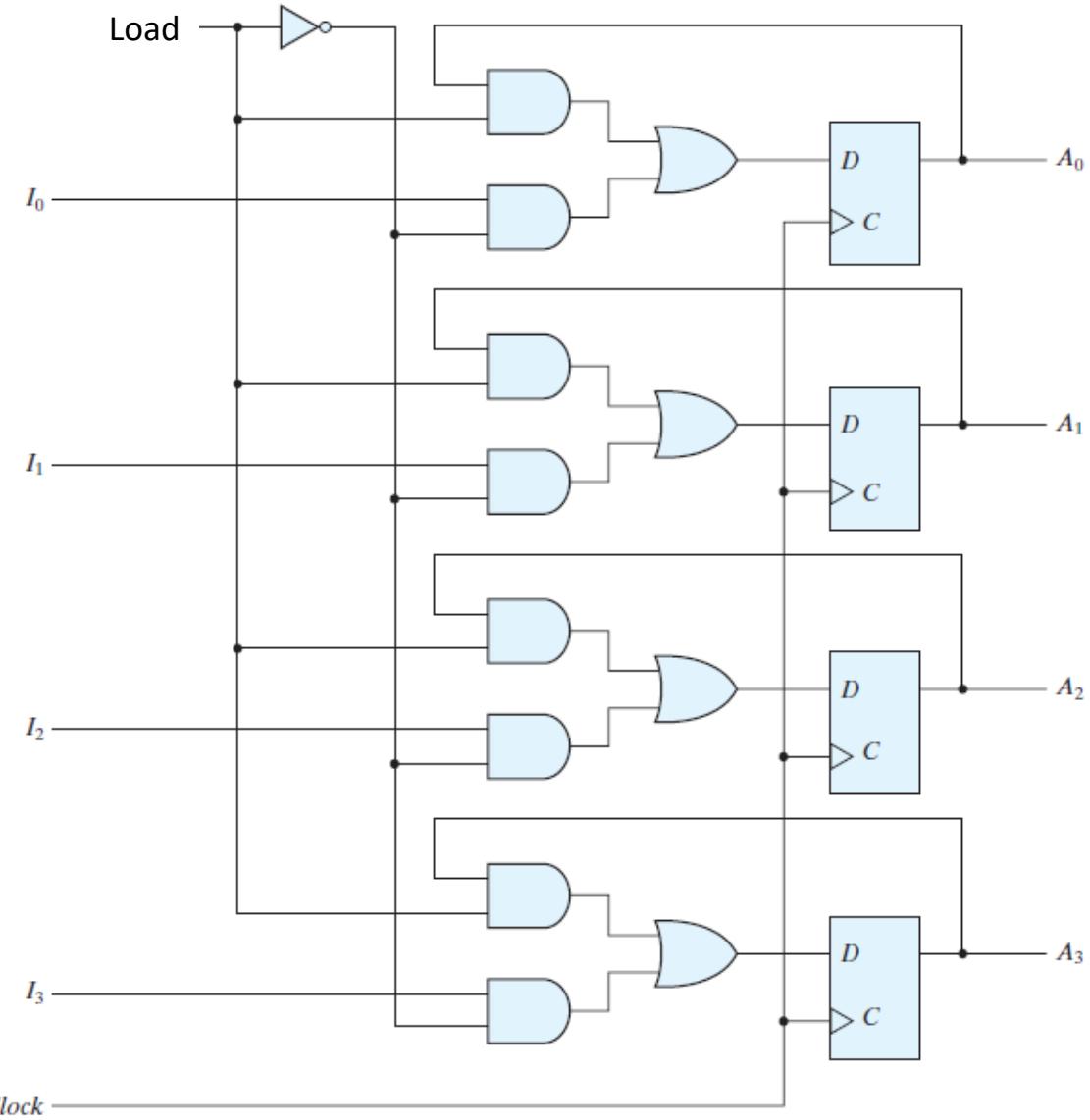


Shift register

- A register capable of shifting the binary information held in each cell to its neighboring cell, in a selected direction, is called a *shift register*
- The logical configuration of a shift register consists of a chain of flip-flops in cascade, with the output of one flip-flop connected to the input of the next flip-flop
- All flip-flops receive common clock pulses, which activate the shift of data from one stage to the next

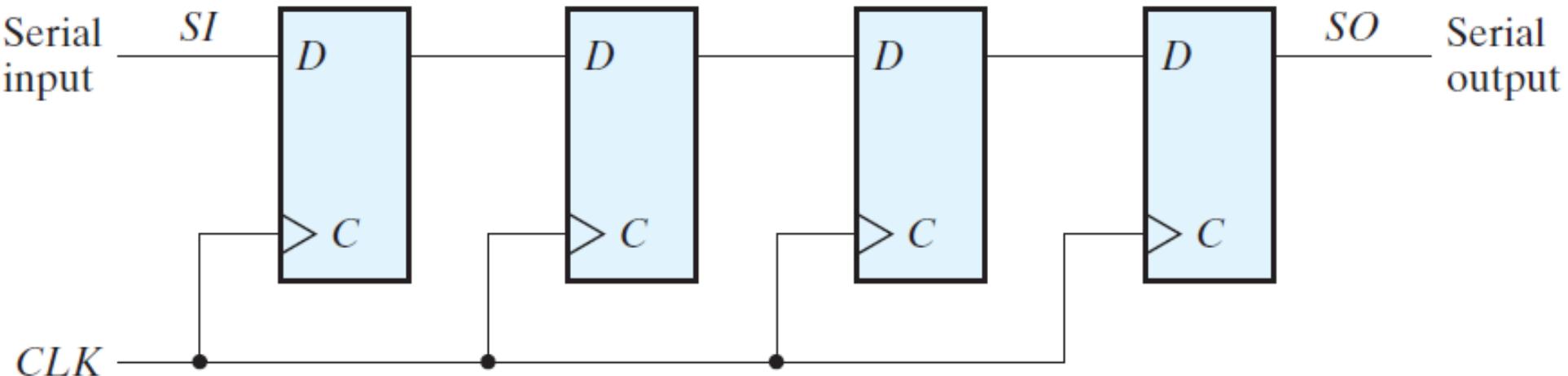


Shift register with load input

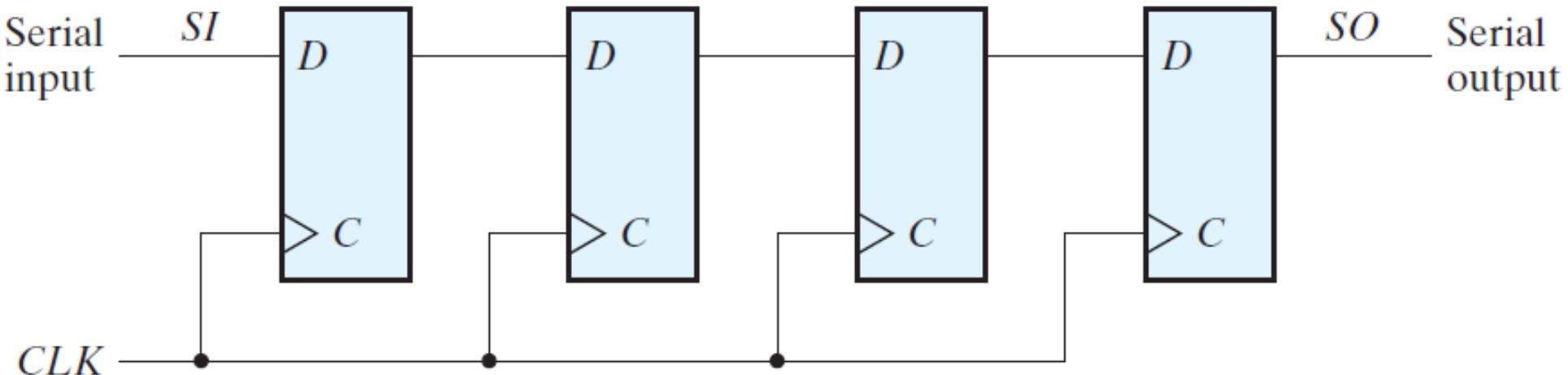- Sometimes it is necessary to control the shift so that it occurs only with certain pulses, but not with others
- Recirculate the output of each cell back through a two-channel mux whose output is connected to the input of the cell
- When the clock action is not suppressed, the other channel of the mux provides a datapath to the cell




Serial transfer

- The datapath of a digital system is said to operate in serial mode when information is transferred and manipulated one bit at a time
- Information is transferred one bit at a time by shifting the bits out of the source register and into the destination register
- This type of transfer is in contrast to parallel transfer, whereby all the bits of the register are transferred at the same time
- The serial transfer of information from register A to register B is done with shift registers, as shown
- The serial output (SO) of register A is connected to the serial input (SI) of register B

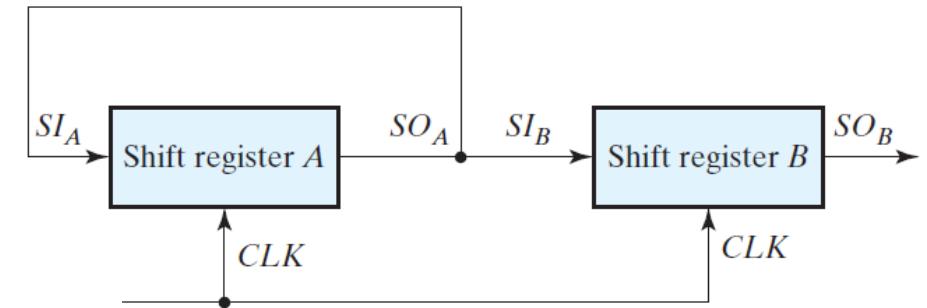


(a) Block diagram

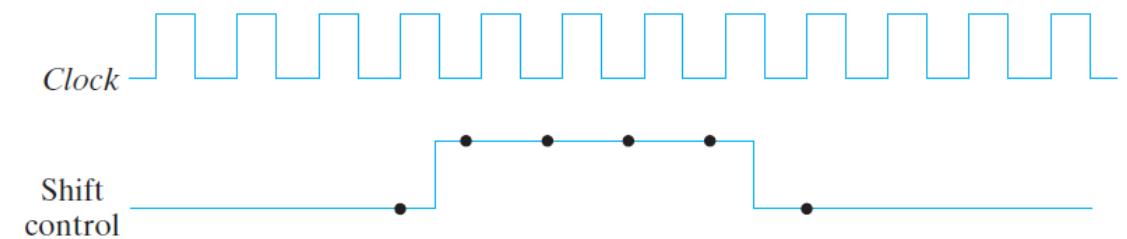


Serial transfer

- To prevent the loss of information stored in the source register, the information in register A is made to circulate by connecting the serial output to its serial input
- The initial content of register B is shifted out through its serial output and is lost unless it is transferred to a third shift register
- The shift control input determines when and how many times the registers are shifted
- For simplicity here, this is done with an AND gate that allows clock pulses to pass into the CLK terminals only when the shift control is active

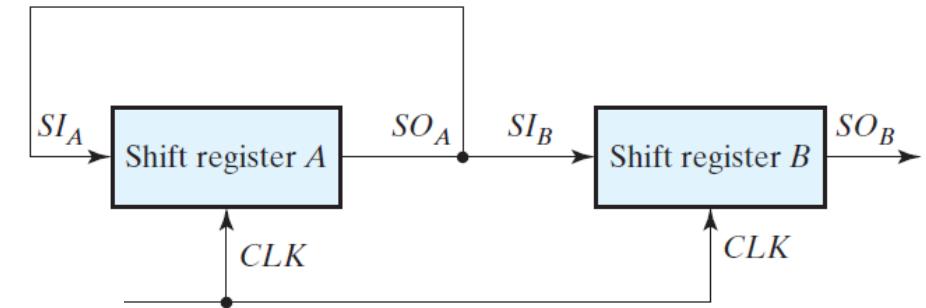


(a) Block diagram

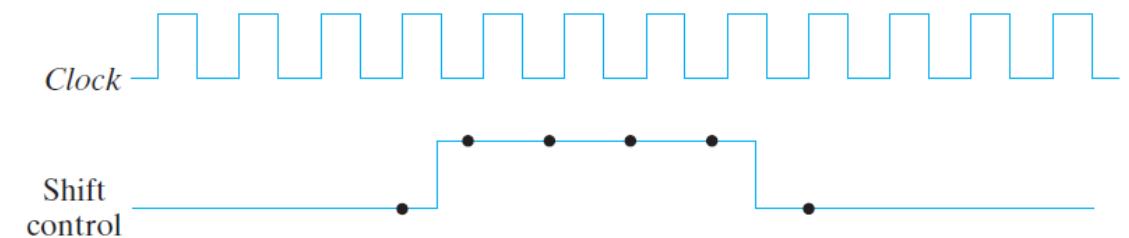

Serial transfer

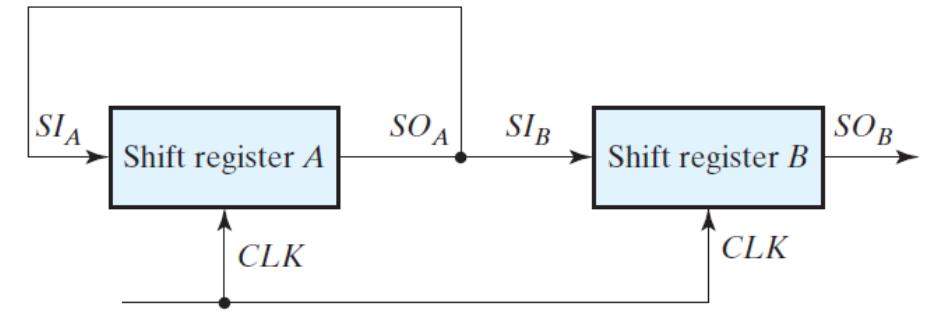
- Assume that the binary content of A before the shift is 1011 and that of B is 0010
- The serial transfer from A to B occurs in four steps
- With the first pulse, T_1 , the rightmost bit of A is shifted into the leftmost bit of B and is also circulated into the leftmost position of A
- At the same time, all bits of A and B are shifted one position to the right



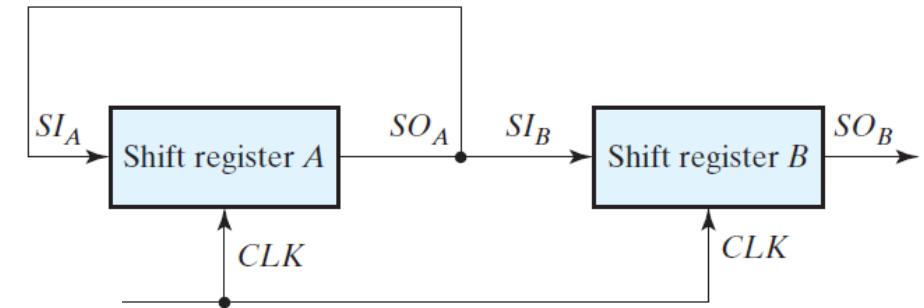(a) Block diagram

Serial transfer

- The previous serial output from B in the rightmost position is lost, and its value changes from 0 to 1
- The next three pulses perform identical operations, shifting the bits of A into B , one at a time
- After the fourth shift, the shift control goes to 0, and registers A and B both have the value 1011
- Thus, the contents of A are copied into B , so that the contents of A remain unchanged i.e., the contents of A are restored to their original value




(a) Block diagram

Timing Pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	0 0 1 0
After T_1	1 1 0 1	1 0 0 1
After T_2	1 1 1 0	1 1 0 0
After T_3	0 1 1 1	0 1 1 0
After T_4	1 0 1 1	1 0 1 1


Serial addition

- Can we design a serial addition circuit? The two binary numbers to be added serially are stored in two shift registers
- This is similar to the algorithm we use for adding manually
- Beginning with the least significant pair of bits, the circuit adds one pair at a time through a single full-adder (FA) circuit
- The carry out of the full adder is transferred to a D flip-flop, the output of which is then used as the carry input for the next pair of significant bits
- The sum bit from the S output of the full adder could be transferred into a third shift register
- By shifting the sum into A while the bits of A are shifted out, it is possible to use one register for storing both the augend and the sum bits
- The serial input of register B can be used to transfer a new binary number while the addend bits are shifted out during the addition

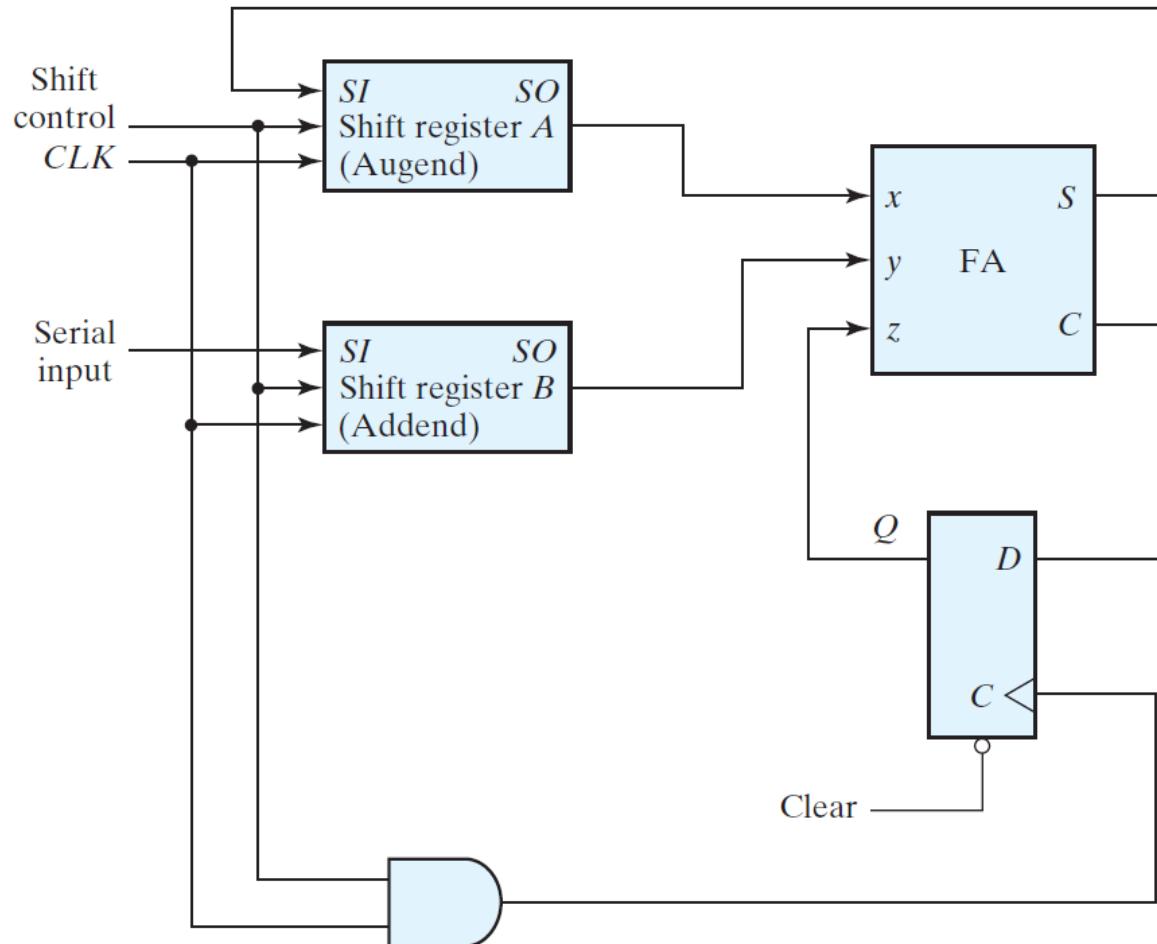

Serial addition

- Comparing the serial adder with the parallel adder (4-bit adder), we note several differences
- The parallel adder uses registers with a parallel load, whereas the serial adder uses shift registers
- The number of full-adder circuits in the parallel adder is equal to the number of bits in the binary numbers, whereas the serial adder requires only one full-adder circuit and a carry flip-flop
- Excluding the registers, the parallel adder is a combinational circuit, whereas the serial adder is a sequential circuit which consists of a full adder and a flip-flop that stores the output carry

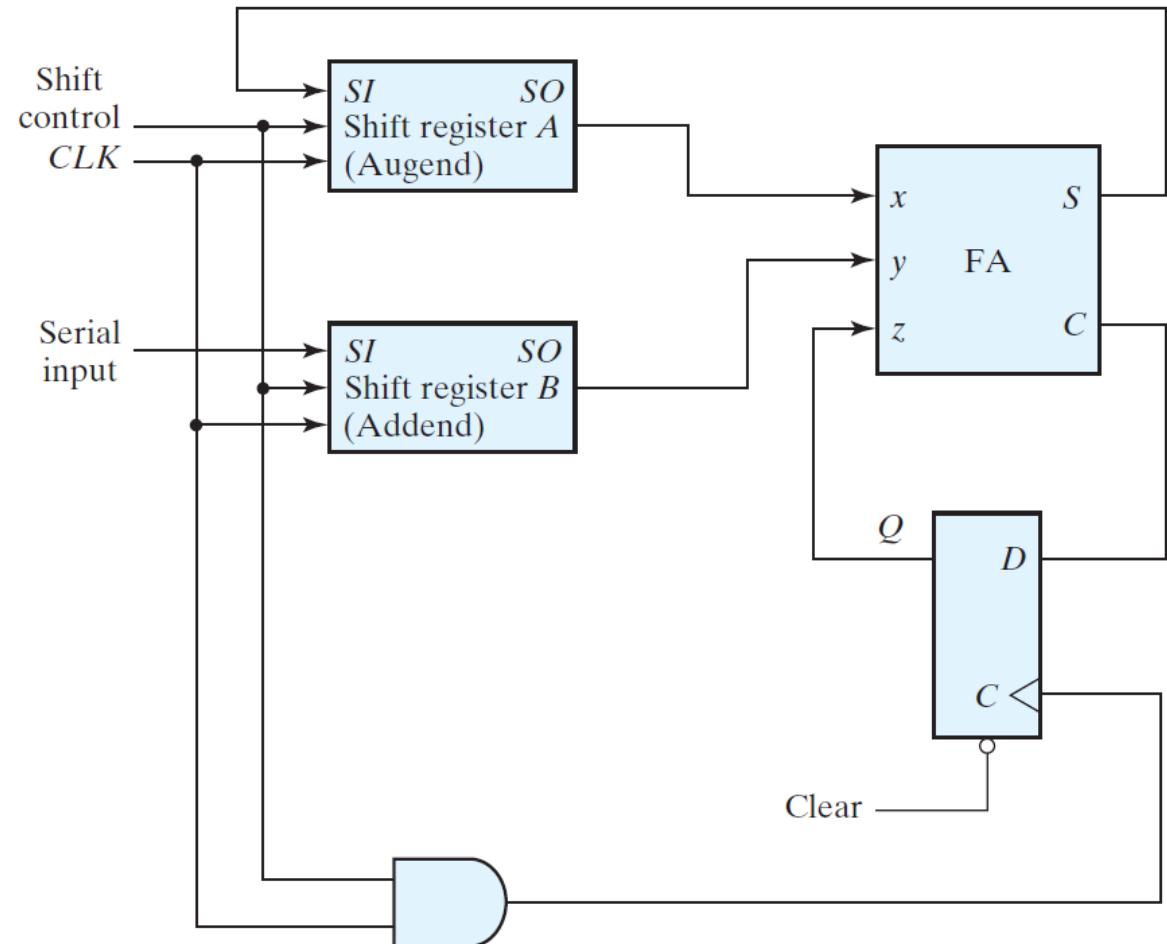

Lecture 21 – Registers and Counters 2

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 6


Universal register

- If the flip-flop outputs of a shift register are accessible, then information entered serially by shifting can be taken out in parallel from the outputs of the flip-flops
- If a parallel load capability is added to a shift register, then data entered in parallel can be taken out in serial fashion by shifting the data stored in the register
- Some shift registers provide the necessary input and output terminals for parallel transfer
- They may also have both shift-right and shift-left capabilities

Universal register

- The most general shift register has the following capabilities:
 1. A *clear* control to clear the register to 0
 2. A *clock* input to synchronize the operations
 3. A *shift-right* control to enable the shift-right operation and the *serial input* and *output* lines associated with the shift right
 4. A *shift-left* control to enable the shift-left operation and the *serial input* and *output* lines associated with the shift left
 5. A *parallel-load* control to enable a parallel transfer and the n input lines associated with the parallel transfer
 6. n parallel output lines
 7. A control state that leaves the information in the register unchanged in response to the clock

Universal register

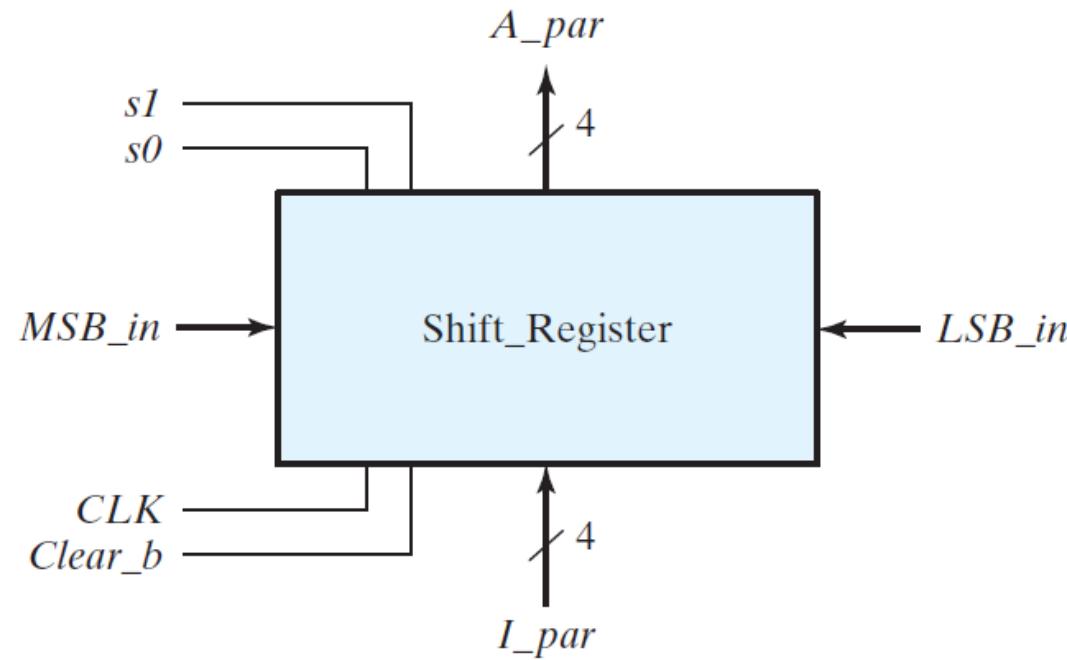


Mode Control

s_1	s_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


Universal register

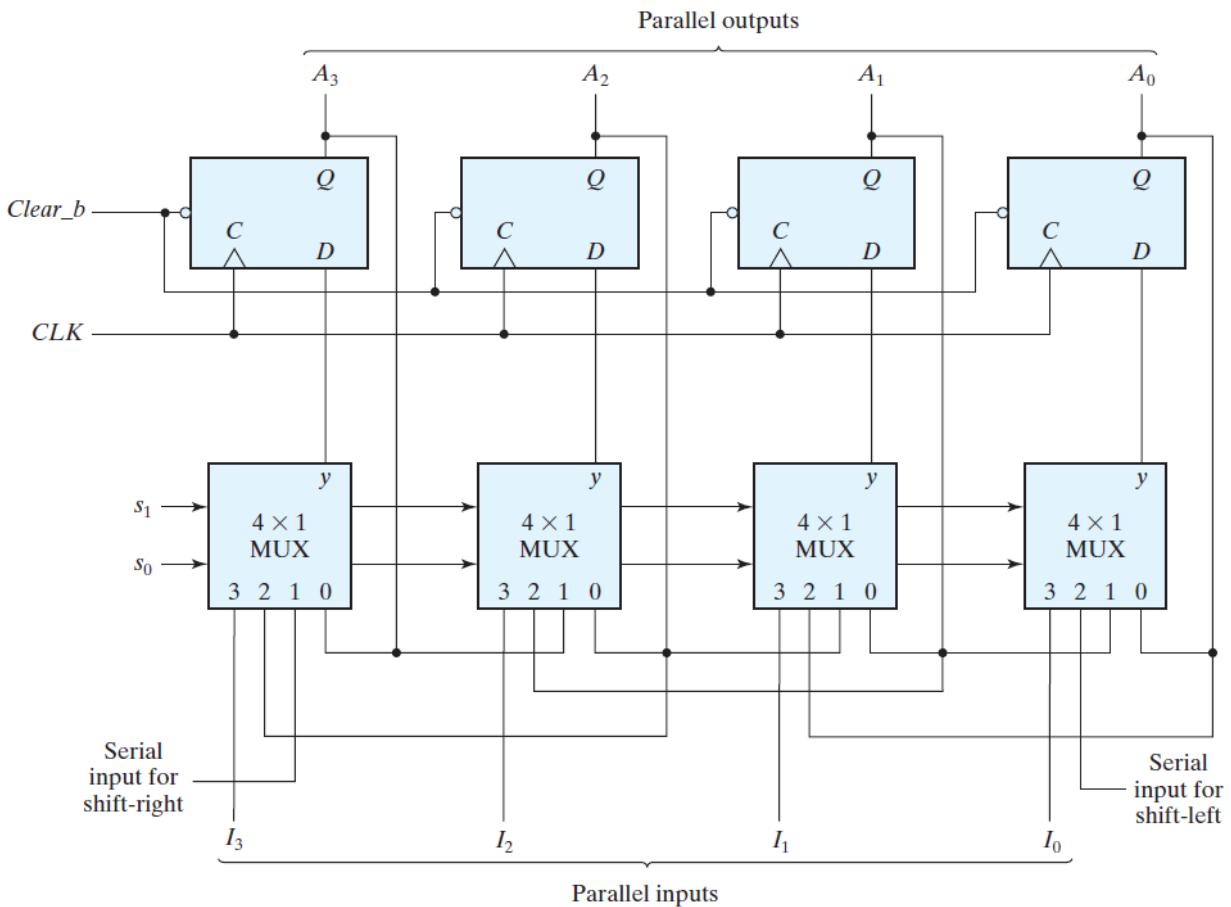- The circuit consists of four D flip-flops and four multiplexers
- The four multiplexers have two common selection inputs s_1 and s_0
- The selection inputs control the mode of operation of the register according to the function required
- The output of the MUXes are applied to the inputs of the FFs which controls the next state of the FF




Universal register

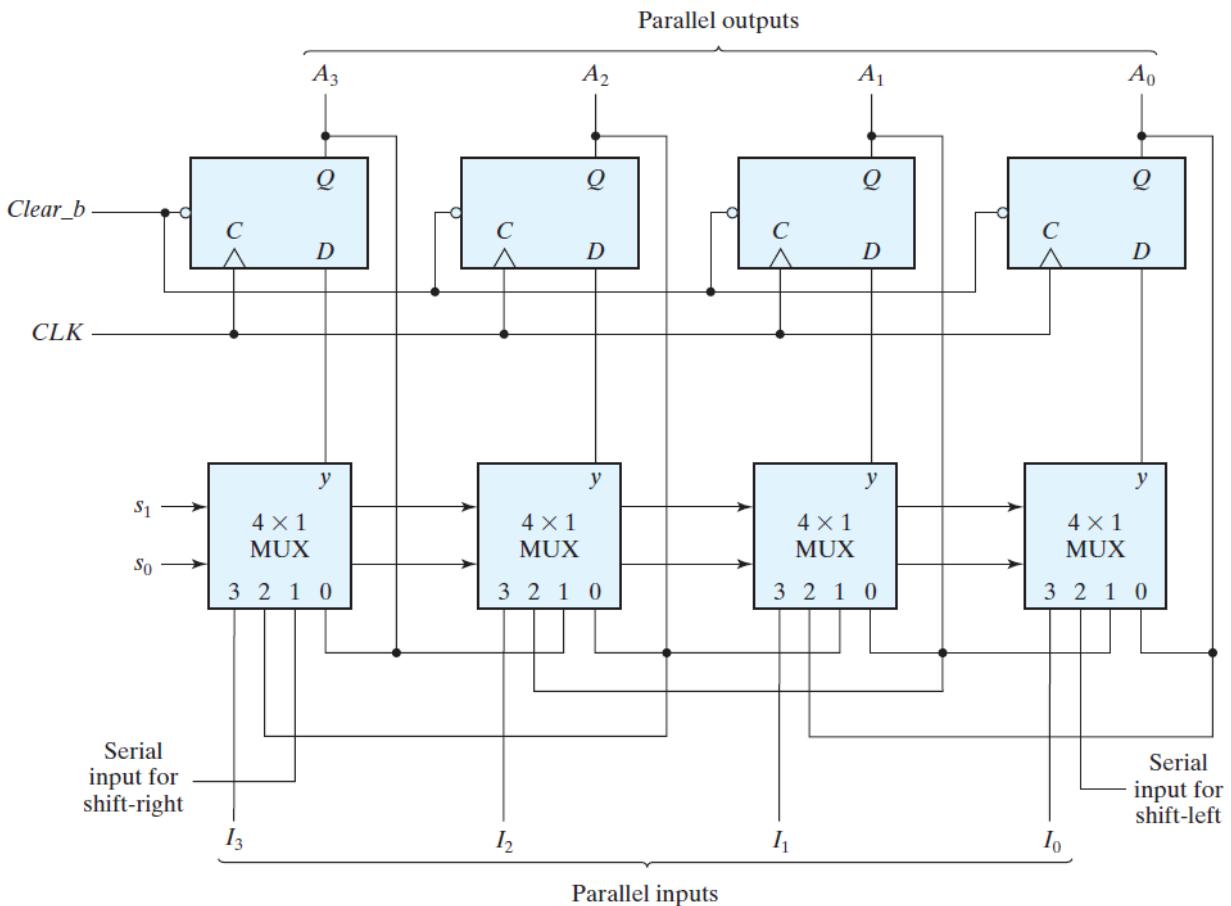- When $s_1s_0 = 00$, the present value of the register is applied to the D inputs of the flip-flops
- This condition forms a path from the output of each flip-flop into the input of the same flip-flop, so that the output recirculates to the input in this mode of operation
- The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs



Universal register

- When $s_1s_0 = 01$, terminal 1 of the multiplexer inputs has a path to the D inputs of the flip-flops
- This causes a shift-right operation, with the serial input transferred into flip-flop A_3
- When $s_1s_0 = 10$, a shift-left operation results, with the other serial input going into flip-flop A_0
- Finally, when $s_1s_0 = 11$, the binary information on the parallel input lines is transferred into the register simultaneously during the next clock edge

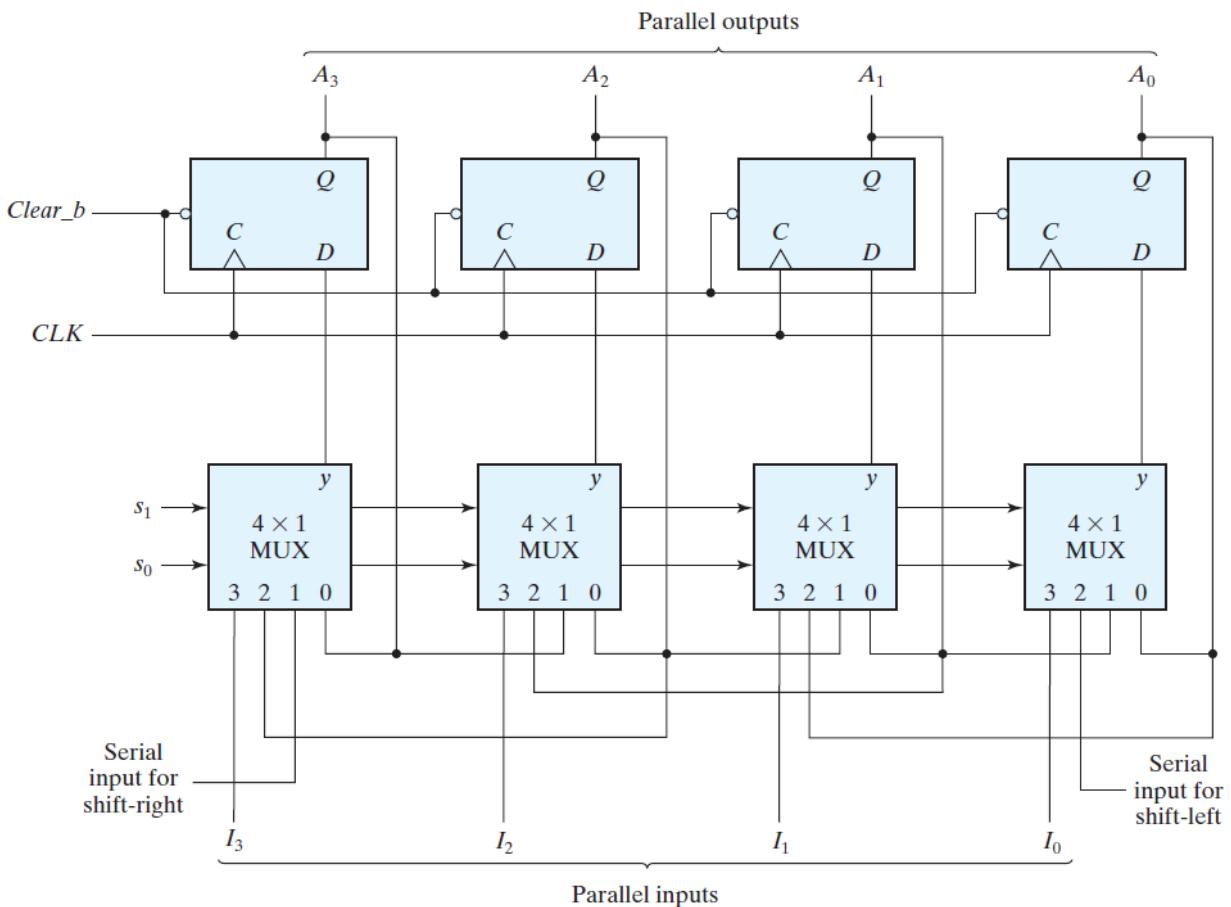


Counters

- A register that goes through a prescribed sequence of states upon the application of input pulses is called a *counter*
- The input pulses may be clock pulses, or they may originate from some external source and may occur at a fixed interval of time or at random
- The sequence of states may follow the binary number sequence or any other sequence of states
- Counters are available in two categories: ripple counters and synchronous counters
- In a ripple counter, a flip-flop output transition serves as a source for triggering other flip-flops
- In a synchronous counter, the C inputs of all flip-flops receive the common clock


Ripple counter - binary

- A binary ripple counter consists of a series connection of complementing flip-flops, with the output of each flip-flop connected to the C input of the next higher order flip-flop
- The flip-flop holding the least significant bit receives the incoming count pulses
- A complementing flip-flop can be obtained from a JK flip-flop with the J and K inputs tied together or from a T flip-flop
- A third possibility is to use a D flip-flop with the complement output connected to the D input
- In this way, the D input is always the complement of the present state, and the next clock pulse will cause the flip-flop to complement

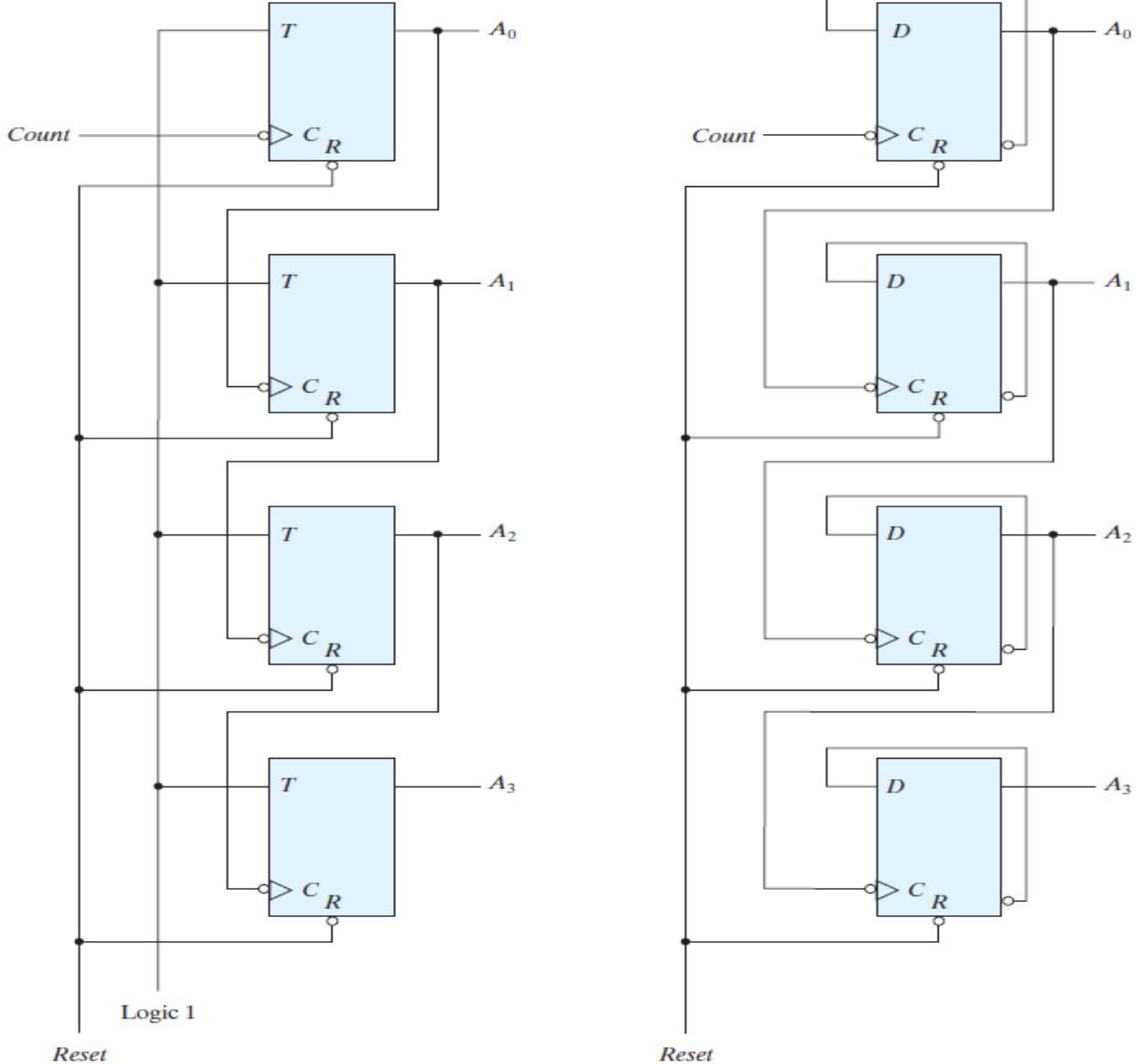


Ripple counter - binary

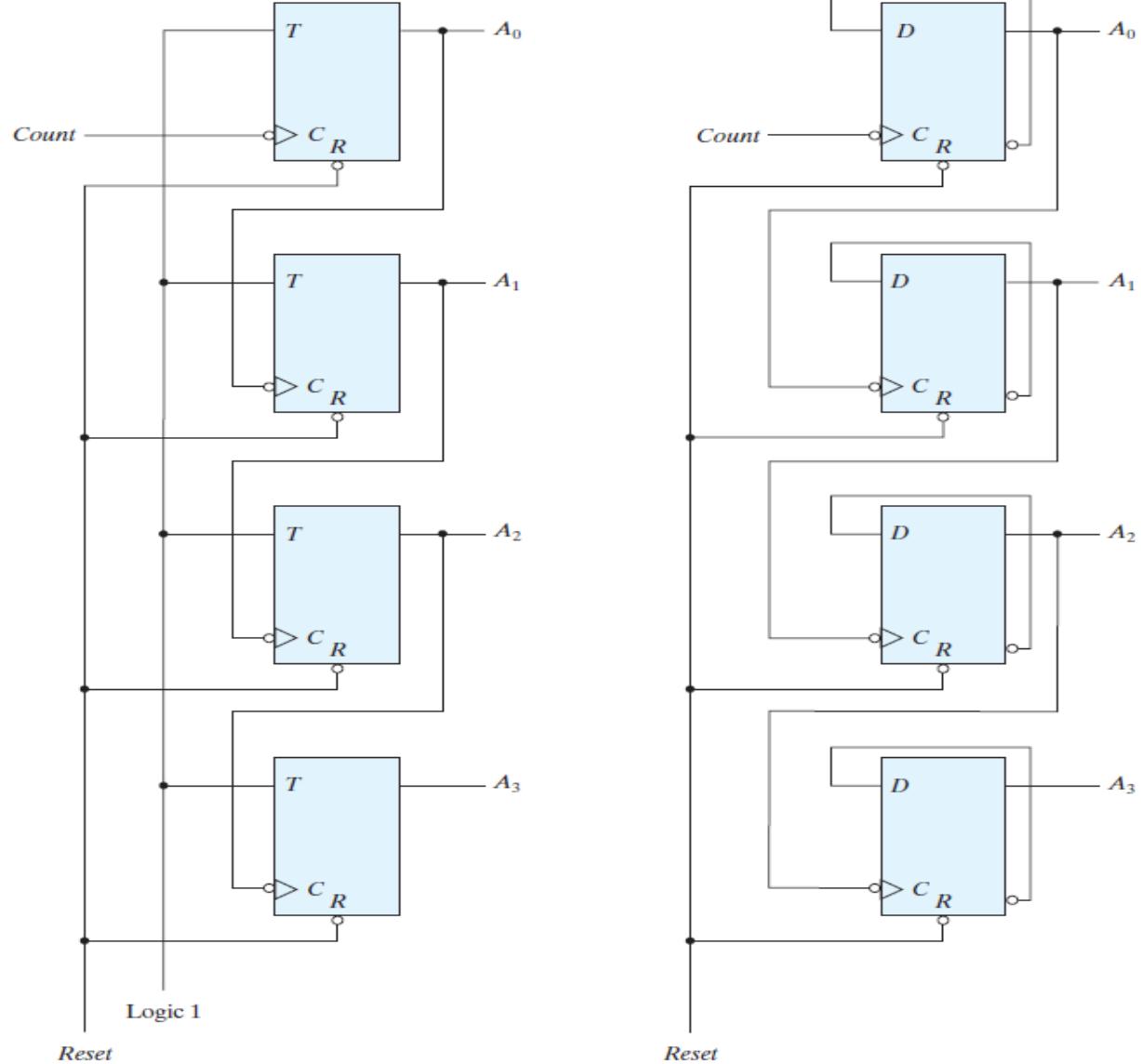- The count starts with binary 0 and increments by 1 with each count pulse input
- After the count of 15, the counter goes back to 0 to repeat the count
- The least significant bit, A_0 , is complemented with each count pulse input
- Every time that A_0 goes from 1 to 0, it complements A_1 and so on...




Ripple counter - binary

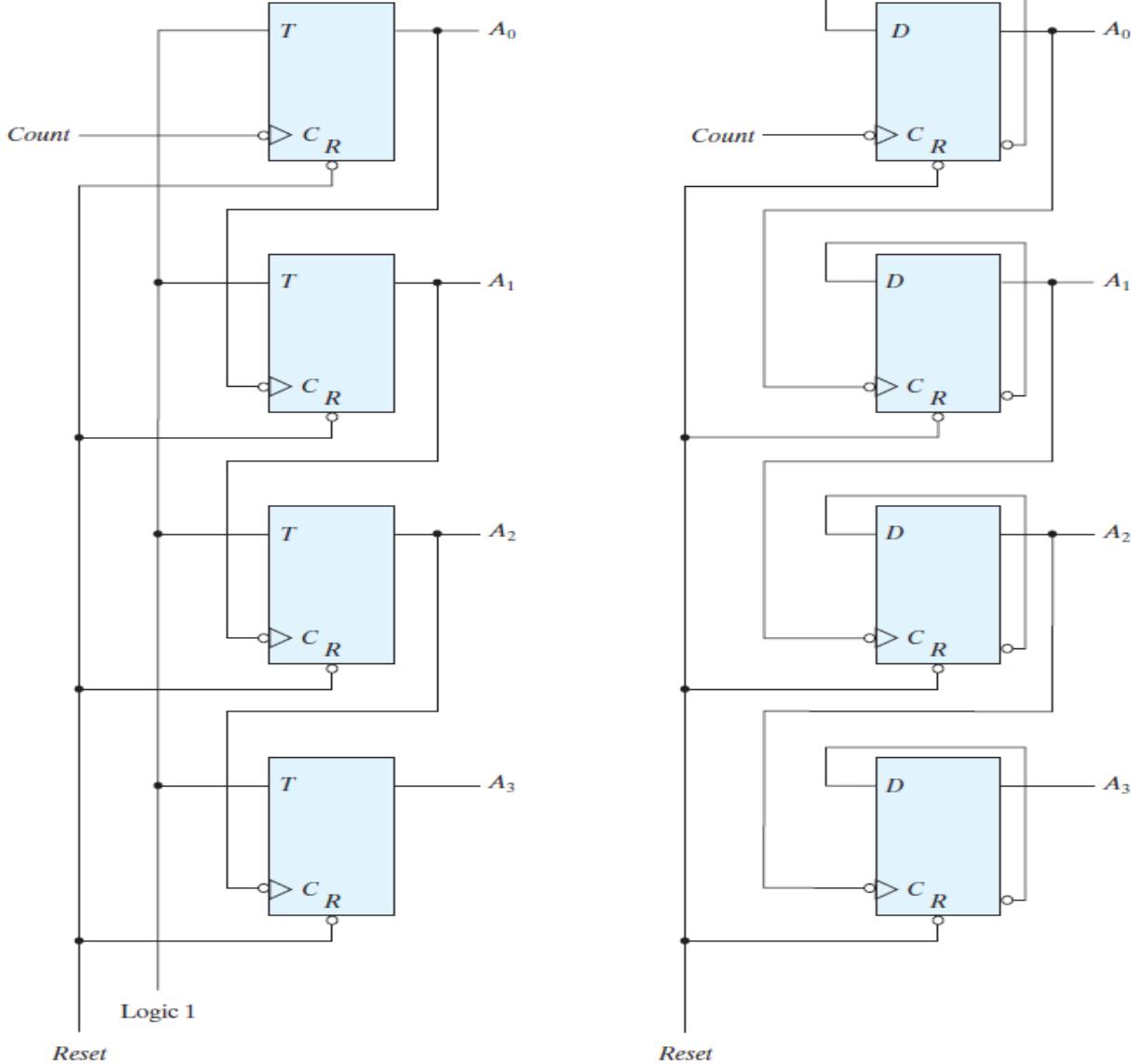- For example, consider the transition from count 0011 to 0100
- A_0 is complemented with the count pulse
- Since A_0 goes from 1 to 0, it triggers A_1 and complements it
- As a result, A_1 goes from 1 to 0, which in turn complements A_2 , changing it from 0 to 1
- A_2 does not trigger A_3 , because A_2 produces a positive transition, and the flip-flop responds only to negative transitions




Ripple counter - BCD

- A decimal counter follows a sequence of 10 states and returns to 0 after the count of 9
- Such a counter must have at least four flip-flops to represent each decimal digit, since a decimal digit is represented by a binary code with at least four bits
- The sequence of states in a decimal counter is dictated by the binary code used to represent a decimal digit
- A decimal counter is similar to a binary counter, except that the state after 1001 (the code for decimal digit 9) is 0000 (the code for decimal digit 0)

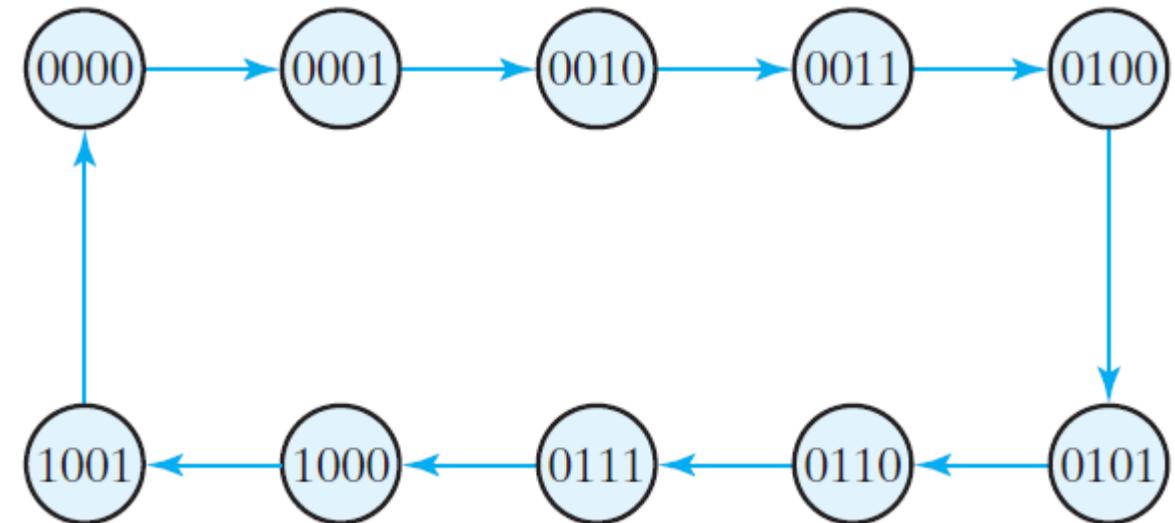


Ripple counter - BCD

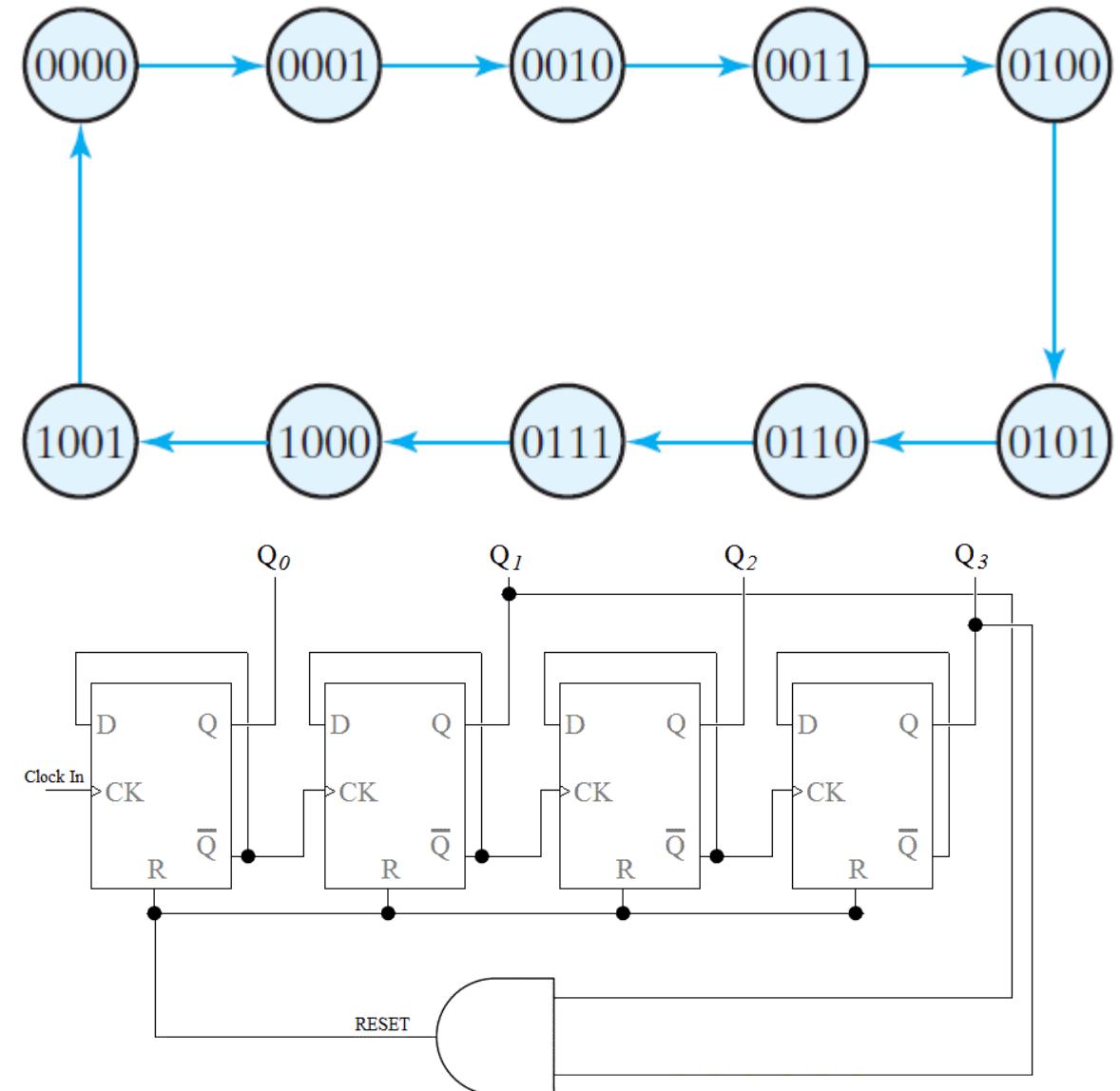- We can obtain a decade counter by clearing all the flip-flops as soon as the state 1010 is obtained
- This can be done with the asynchronous input of CLR
- The condition for 1010 is checked by ANDing Q_3 and Q_1
- This is a very commonly used counter for making clocks/timer circuits
- Can we make it stop at any other number?



Ripple counter - BCD

- A decade counter counts from 0 to 9
- To count in decimal from 0 to 99, we need a two-decade counter circuit
- To count from 0 to 999, we need a three-decade counter circuit
- Multiple decade counters can be constructed by connecting BCD counters in cascade, one for each decade
- The inputs to the second and third decades come from Q_8 of the previous decade
- When Q_8 in one decade goes from 1 to 0, it triggers the count for the next higher order decade while its own decade goes from 9 to 0

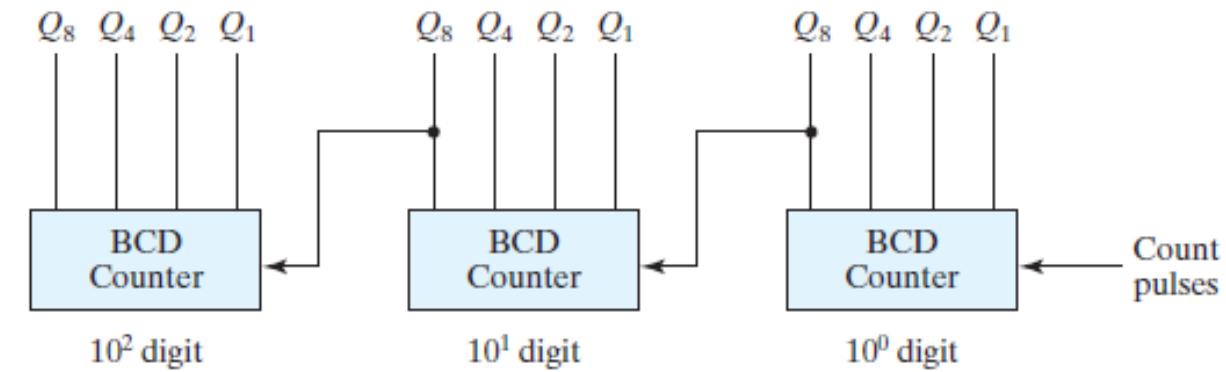

Lecture 22 – Registers and Counters 3

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 6

Synchronous counter - binary


- The key problem with ripple counters is that they do not update their states immediately after the arrival of the clock
- Synchronous counters are different from ripple counters in that clock pulses are applied to the inputs of all flip-flops
- A common clock triggers all flip-flops simultaneously, rather than one at a time in succession as in a ripple counter
- The decision whether a flip-flop is to be complemented is determined from the values of the data inputs, such as T or J and K at the time of the clock edge
- If $T = 0$ or $J = K = 0$, the flip-flop does not change state. If $T = 1$ or $J = K = 1$, the flip-flop complements

Synchronous counter - binary

- The design of a synchronous binary counter is very simple
- In a synchronous binary counter, the flip-flop in the least significant position is complemented with every pulse
- *A flip-flop in any other position is complemented when all the bits in the lower significant positions are equal to 1*
- For example, if the present state of a four-bit counter is $A_3A_2A_1A_0 = 0011$, the next count is 0100
 - A_0 is always complemented
 - A_1 is complemented because the present state of $A_0 = 1$
 - A_2 is complemented because the present state of $A_1A_0 = 11$
 - However, A_3 is not complemented, because the present state of $A_2A_1A_0 = 011$, which does not give an all-1's condition


Synchronous counter - binary

- Synchronous binary counters have a regular pattern and can be constructed with complementing flip-flops and gates
- The regular pattern can be seen from the four-bit counter
- The C inputs of all flip-flops are connected to a common clock
- The counter is enabled by *Count_enable*
- If the enable input is 0, all J and K inputs are equal to 0 and the clock does not change the state of the counter
- The first stage, A_0 , has its J and K equal to 1 if the counter is enabled
- The other J and K inputs are equal to 1 if all previous least significant stages are equal to 1 and the count is enabled

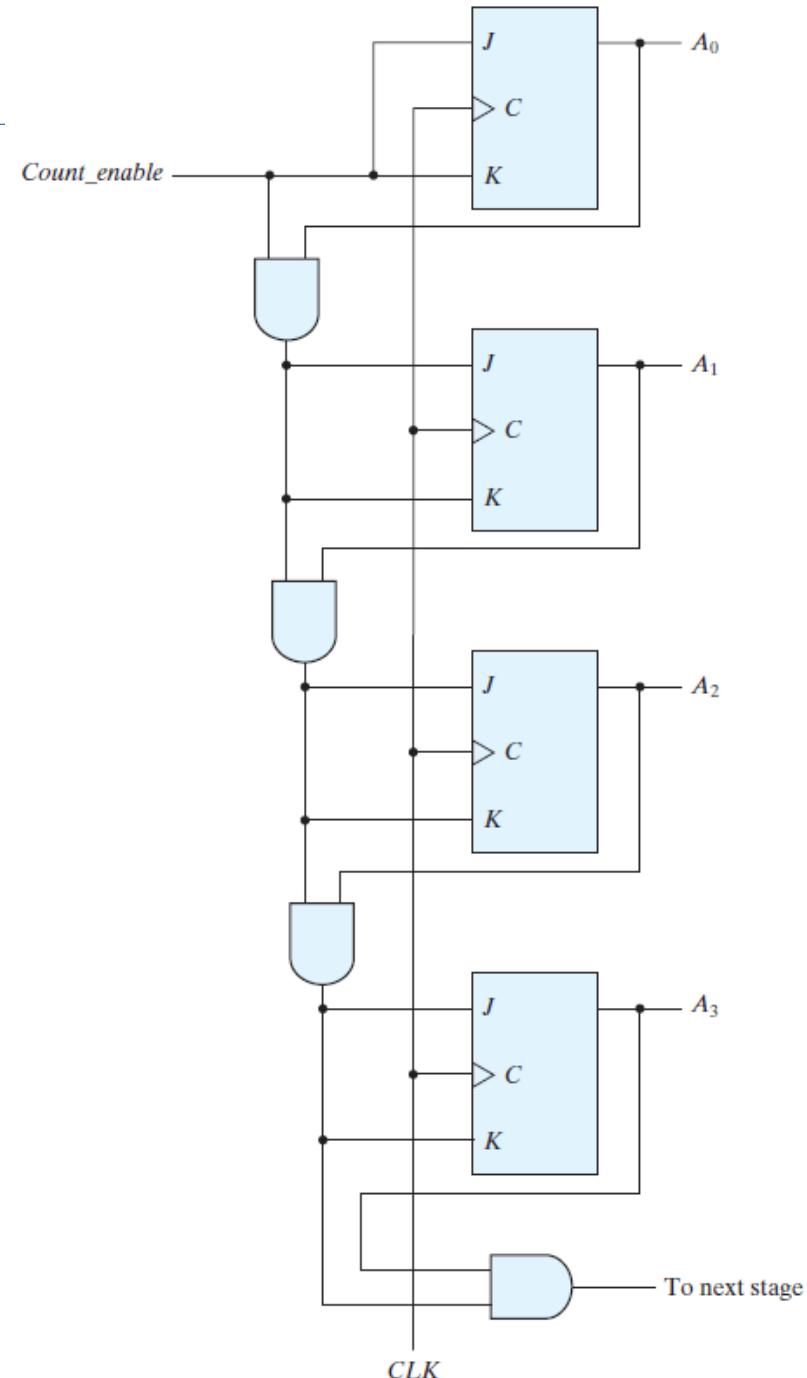

Synchronous counter - binary

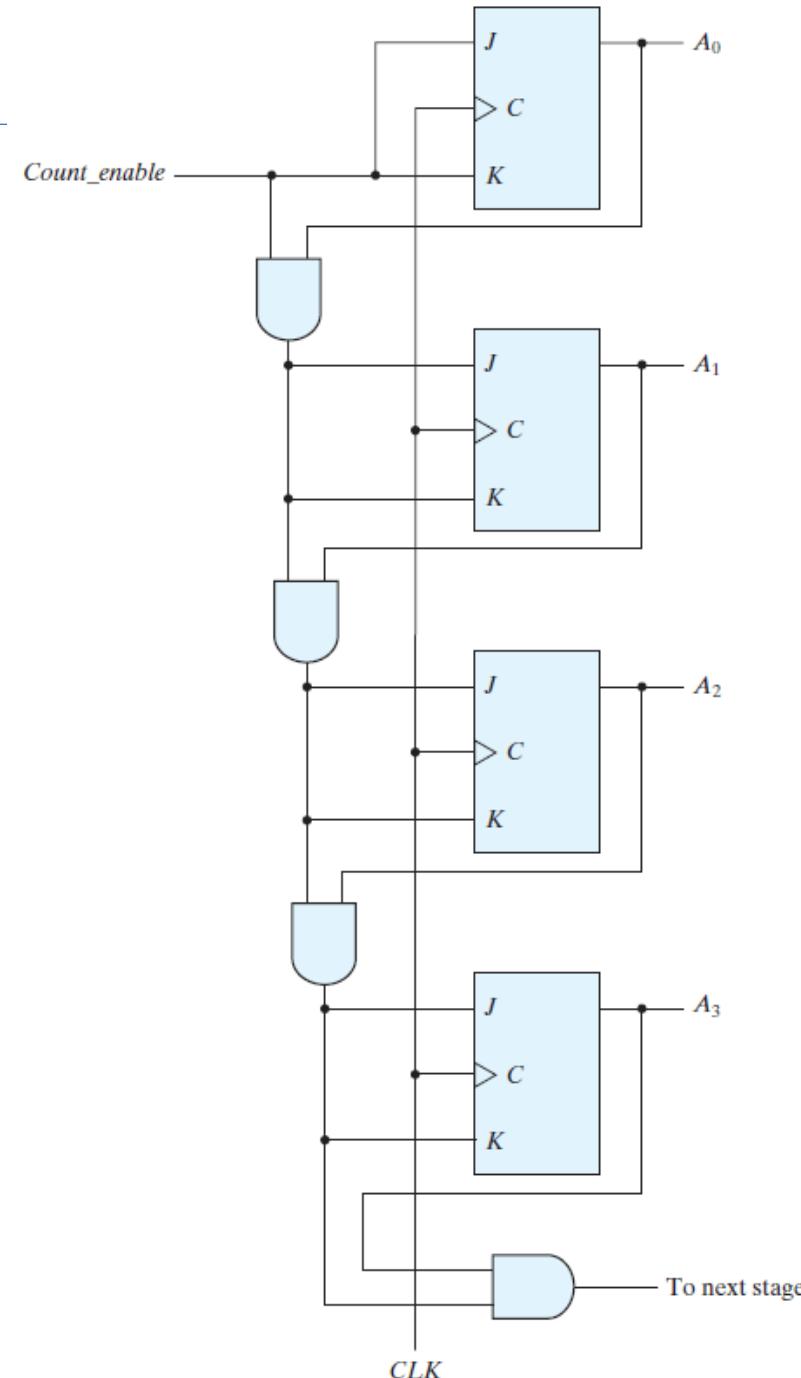- Note that the flip-flops trigger on the positive edge of the clock
- The polarity of the clock is not essential here, but it is with the ripple counter
- The synchronous counter can be triggered with either the positive or the negative clock edge
- The complementing flip-flops in a binary counter can be of either the *JK* type, the *T* type, or the *D* type with XOR gates



Synchronous counter – down counter


- A synchronous countdown binary counter goes through the binary states in reverse order, from 1111 down to 0000 and back to 1111 to repeat the count
- It is possible to design a countdown counter in the usual manner, but the result is predictable by inspection of the downward binary count
- The bit in the least significant position is complemented with each pulse
- *A bit in any other position is complemented if all lower significant bits are equal to 0*
- For example, the next state after the present state of 0100 is 0011
- The second significant bit is complemented because the first bit was 0
- The third significant bit is complemented because the first two bits were equal to 0
- But the fourth bit does not change, because not all lower significant bits are equal to 0
- A countdown binary counter can be constructed as a regular counter, except that the inputs to the AND gates must come from the complemented outputs, instead of the normal outputs, of the previous flip-flops

Synchronous counter – up/down counter

- Let us see if we can design a counter that counts up/down based on an input
- The counter should count up if $U=1$, $D=0$; down if $U=0$, $D=1$; no change if $U=D=0$; and up if $U=D=1$
- If we chose T flip-flops for this design, the inputs should be A if U is 1 (regardless of D), A' if $U'D$ is 1 and 0 if $U=D=0$
- We can cascade this logic to make the synchronous up/down counter

Synchronous counter – up/down counter

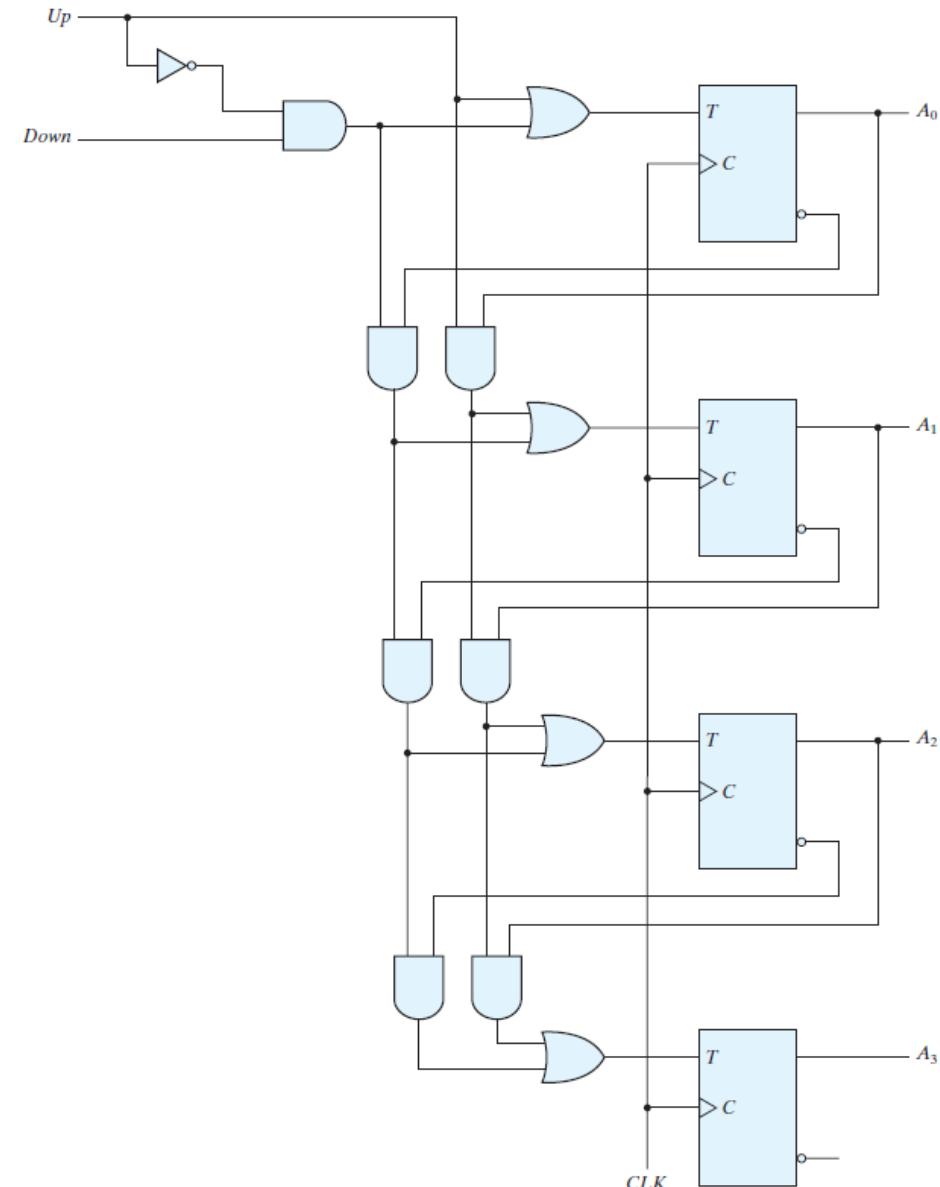- Let us see if we can design a counter that counts up/down based on an input
- The counter should count up if $U=1$, $D=0$; down if $U=0$, $D=1$; no change if $U=D=0$; and up if $U=D=1$
- If we chose T flip-flops for this design, the inputs should be A if U is 1 (regardless of D), A' if $U'D$ is 1 and 0 if $U=D=0$
- We can cascade this logic to make the synchronous up/down counter



Synchronous counter – BCD

- BCD counter counts in binary-coded decimal from 0000 to 1001 and back to 0000
- Because of the return to 0 after a count of 9, a BCD counter does not have a regular pattern, unlike a straight binary count
- The input conditions for the T flip-flops are obtained from the present- and next-state conditions
- Also shown in the table is an output y , which is equal to 1 when the present state is 1001
- In this way, y can enable the count of the next-higher significant decade while the same pulse switches the present decade from 1001 to 0000

Present State				Next State				Output
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y
0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	1	0
0	0	1	1	0	1	0	0	0
0	1	0	0	0	1	0	1	0
0	1	0	1	0	1	1	0	0
0	1	1	0	0	1	1	1	0
0	1	1	1	1	0	0	0	0
1	0	0	0	1	0	0	1	0
1	0	0	1	0	0	0	0	1

Synchronous counter – BCD

- The flip-flop input equations can be simplified by means of maps
- The unused states for minterms 10 to 15 are taken as don't-care terms
- The simplified functions are:

$$TQ_1 = 1$$

$$TQ_2 = Q'_8 Q_1$$

$$TQ_4 = Q_2 Q_1$$

$$TQ_8 = Q_8 Q_1 + Q_4 Q_2 Q_1$$


$$y = Q_8 Q_1$$

- The circuit can be made using these expressions

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	0
0	0	0	1	0	0	1	0	0	0	0	0	1
0	0	1	0	0	0	1	1	0	0	0	0	0
0	0	1	1	0	1	0	0	0	0	0	1	1
0	1	0	0	0	1	0	1	0	0	0	0	0
0	1	0	1	0	1	1	0	0	0	0	0	1
0	1	1	0	0	1	1	1	0	0	0	0	0
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	0
1	0	0	1	0	0	0	0	1	1	0	0	1


Synchronous counter – with parallel load

- Counters employed in digital systems quite often require a parallel-load capability for transferring an initial binary number into the counter prior to the count operation
- When equal to 1, the input load control disables the count operation and causes a transfer of data from the four data inputs into the four flip-flops
- If both control inputs are 0, clock pulses do not change the state of the counter

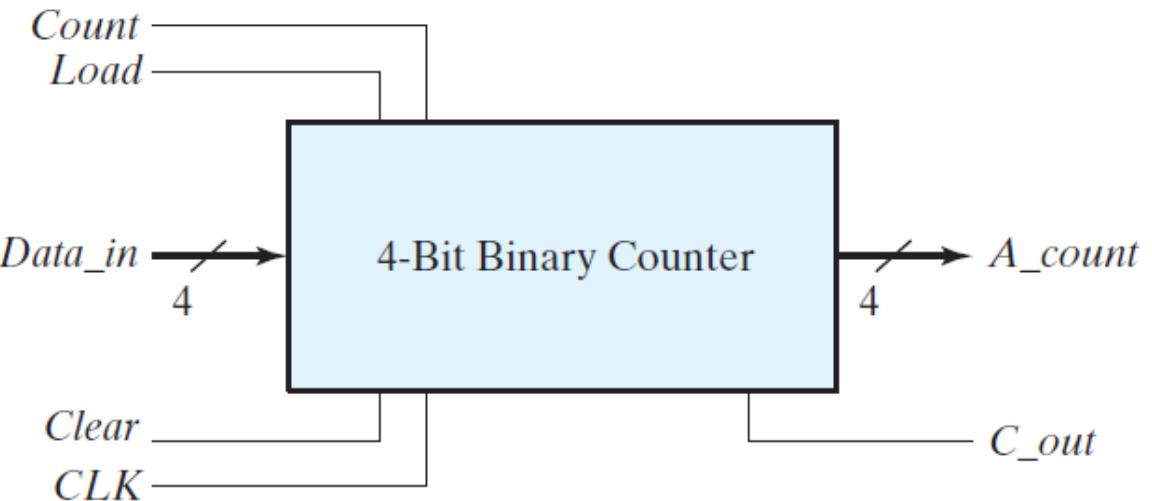


Synchronous counter – with parallel load

- The four control inputs— *Clear*, *CLK*, *Load*, and *Count* —determine the next state
- The *Clear* input is asynchronous and, when equal to 0, causes the counter to be cleared regardless of the presence of clock pulses or other inputs
- With the *Load* and *Count* inputs both at 0, the outputs do not change, even when clock pulses are applied
- A *Load* input of 1 causes a transfer from inputs $I_0 - I_3$ into the register during a positive edge of *CLK*
- The *Load* input must be 0 for the *Count* input to control the operation of the counter

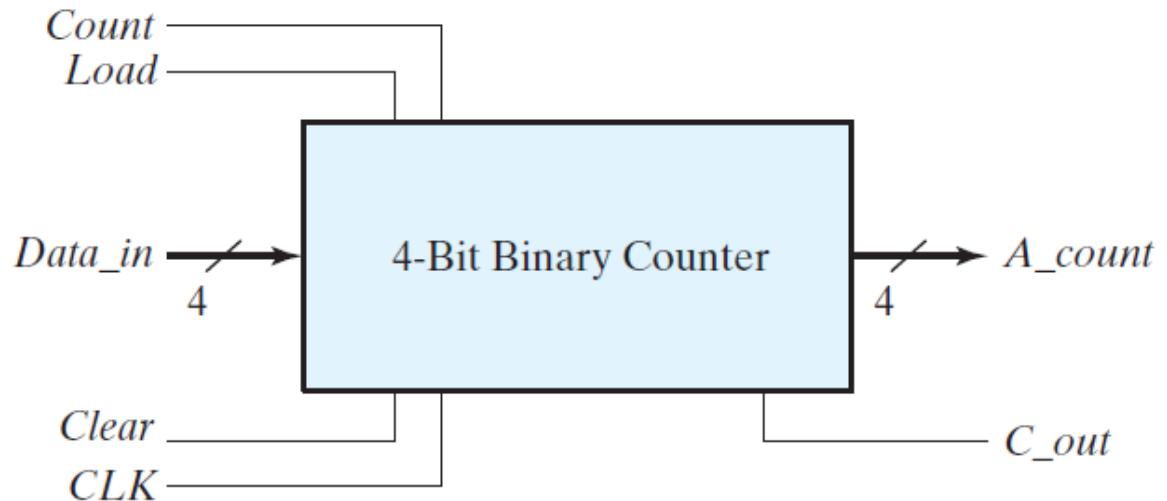

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

Synchronous counter – with parallel load

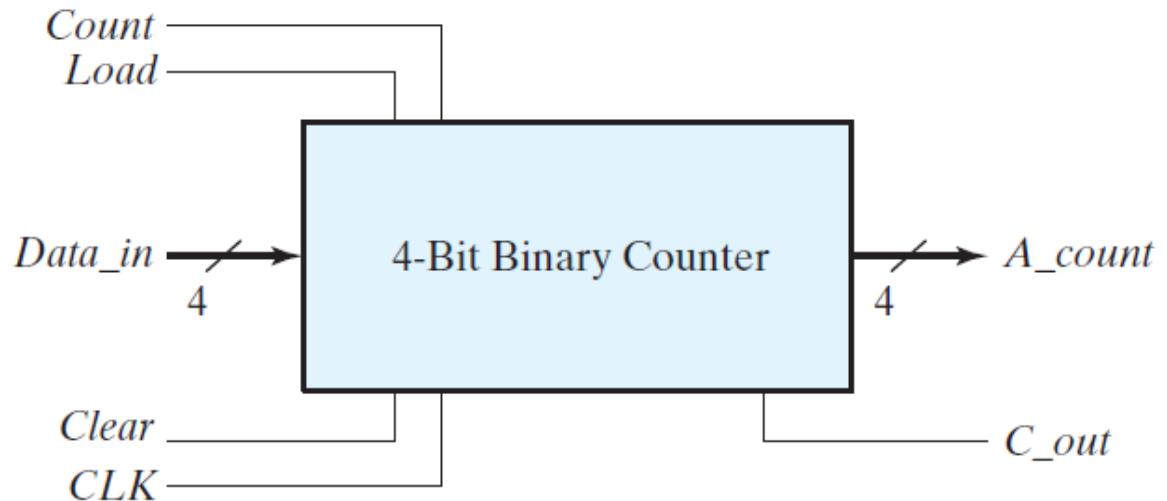

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change


Lecture 23 – Memory architecture 1

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 7

Synchronous counter – with parallel load

- The four control inputs— *Clear*, *CLK*, *Load*, and *Count* —determine the next state
- The *Clear* input is asynchronous and, when equal to 0, causes the counter to be cleared regardless of the presence of clock pulses or other inputs
- With the *Load* and *Count* inputs both at 0, the outputs do not change, even when clock pulses are applied
- A *Load* input of 1 causes a transfer from inputs $I_0 - I_3$ into the register during a positive edge of *CLK*
- The *Load* input must be 0 for the *Count* input to control the operation of the counter

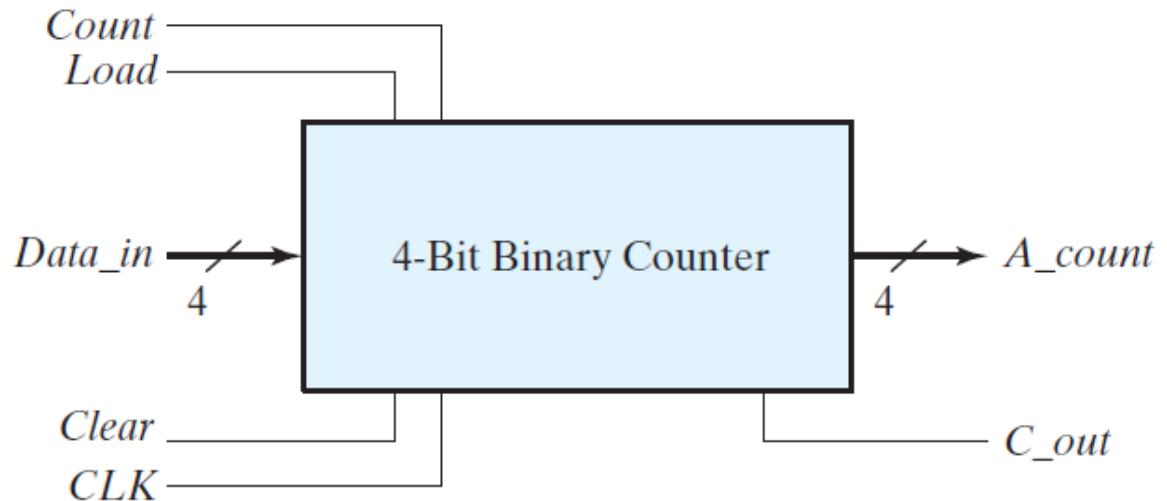


Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

Random Access Memory (RAM)

- A memory unit is a collection of storage cells, together with associated circuits needed to transfer information into and out of a device
- The architecture of memory is such that information can be selectively retrieved from any of its internal locations
- The time it takes to transfer information to or from any desired random location is always the same—hence the name *random-access memory*, abbreviated RAM
- In contrast, the time required to retrieve information that is stored on magnetic tape depends on the location of the data
- A memory unit stores binary information in groups of bits called *words*
- A word in memory is an entity of bits that move in and out of storage as a unit
- Most computer memories use words that are multiples of 8 bits in length
- The capacity of a memory unit is usually stated as the total number of bytes that the unit can store

Random Access Memory (RAM)

- Communication between memory and its environment is achieved through data input and output lines, address selection lines, and control lines that specify the direction of transfer
- The n data input lines provide the information to be stored in memory, and the n data output lines supply the information coming out of memory
- The k address lines specify the particular word chosen among the many available
- The two control inputs specify the direction of transfer desired: The *Write* input causes binary data to be transferred into the memory, and the *Read* input causes binary data to be transferred out of memory
- The address lines select one particular word

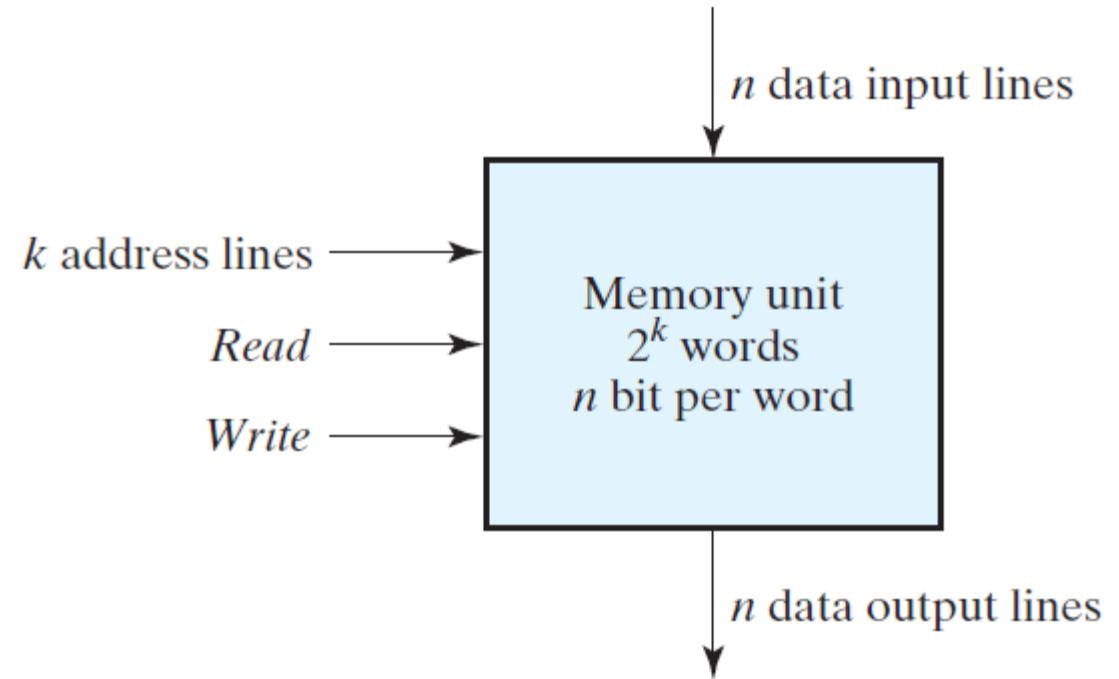


Random Access Memory (RAM)

- Consider, for example, a memory unit with a capacity of 1K words of 16 bits each
- Since $1K = 1,024 = 2^{10}$ and 16 bits constitute two bytes, we can say that the memory can accommodate $2,048 = 2Kb$
- The words are recognized by their decimal address from 0 to 1,023
- The equivalent binary address consists of 10 bits
- A word in memory is selected by its binary address
- When a word is read or written, the memory operates on all 16 bits as a single unit

Memory address	Binary	Decimal	Memory content
	0000000000	0	1011010101011101
	0000000001	1	1010101110001001
	0000000010	2	0000110101000110
		⋮	⋮
		⋮	⋮
	1111111101	1021	1001110100010100
	1111111110	1022	0000110100011110
	1111111111	1023	1101111000100101


Random Access Memory (RAM) – internal structure

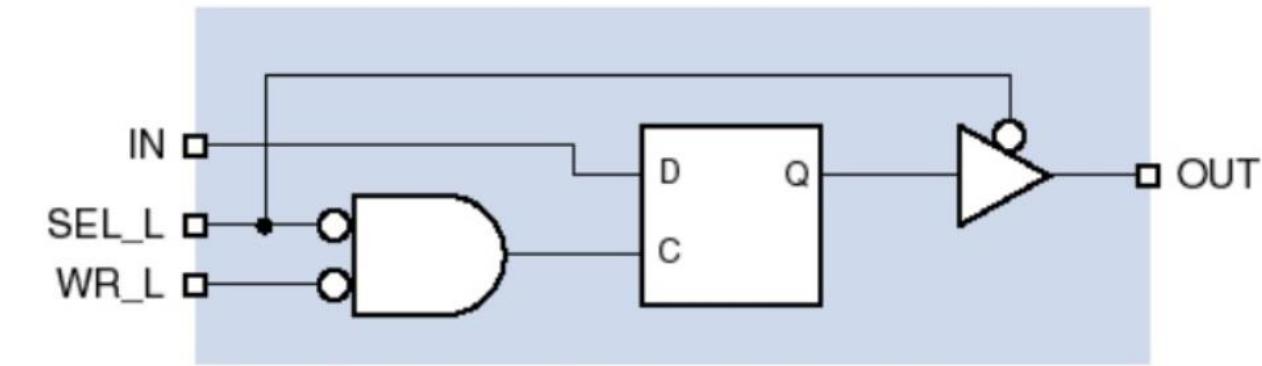- The internal construction of a RAM of m words and n bits per word consists of $m * n$ binary storage cells and associated decoding circuits for selecting individual words
- The binary storage cell (SR latch) is the basic building block of a memory unit
- The storage part of the cell is modeled by an SR latch with associated gates to form a D latch
- *Note that this is not a D flip-flop*




Write and Read operations

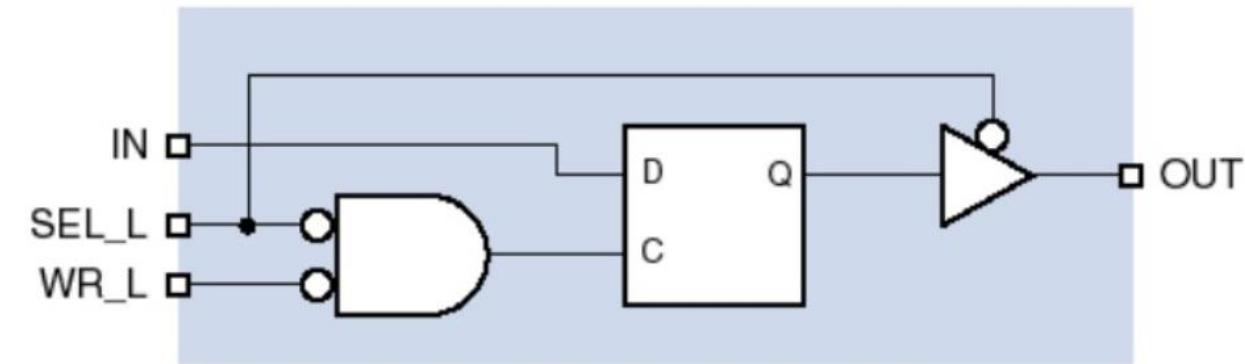- The two operations that RAM can perform are the write and read operations
- The write signal specifies a transfer-in operation and the read signal specifies a transfer-out operation
- On accepting one of these control signals, the internal circuits inside the memory provide the desired operation



Write and Read operations

- The steps that must be taken for the purpose of transferring a new word to be stored into memory are as follows:
 1. Apply the binary address of the desired word to the address lines.
 2. Activate the *write* input.
 3. Apply the data bits that must be stored in memory to the data input lines.
- The memory unit will then take the bits from the input data lines and store them in the word specified by the address lines

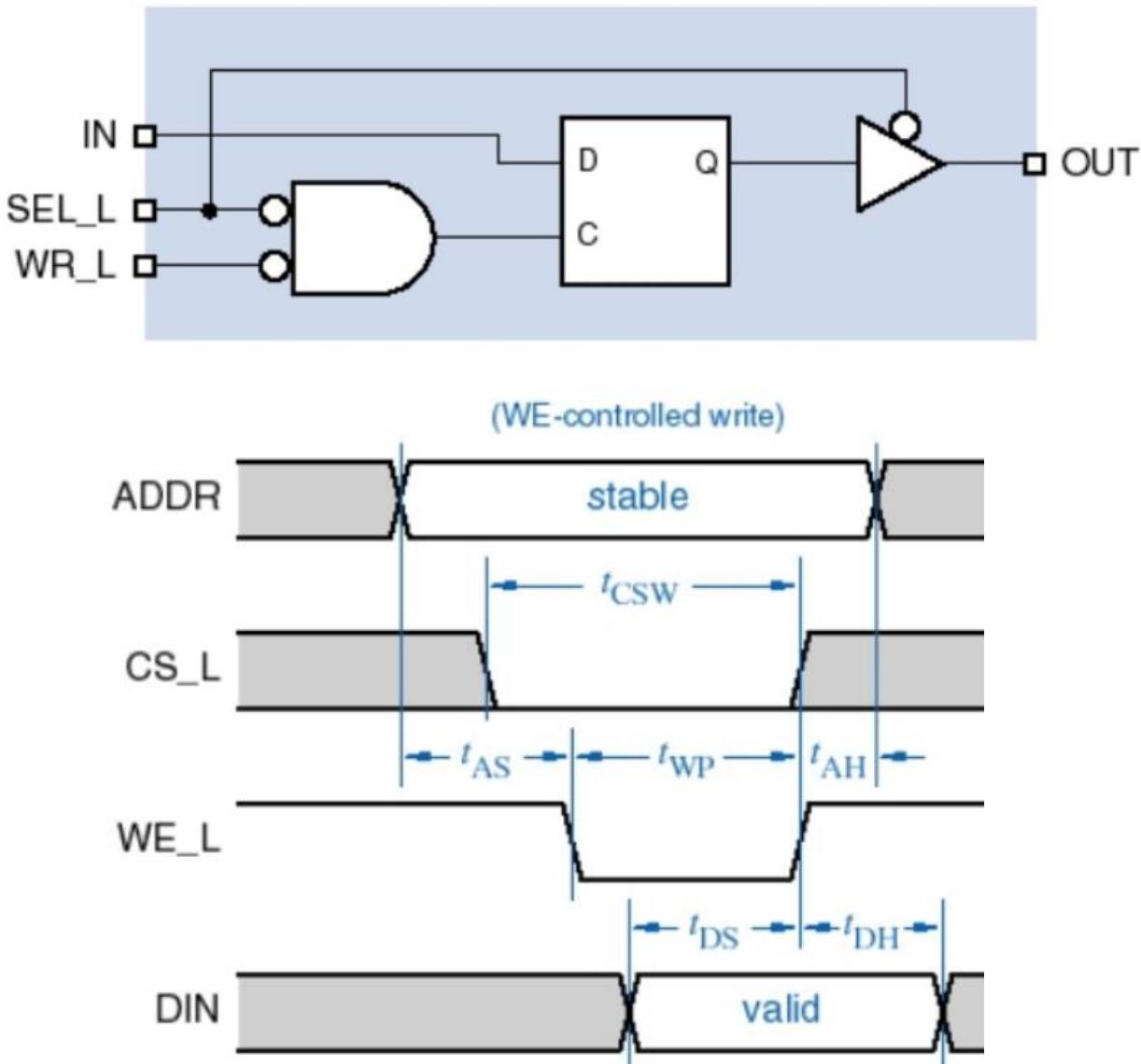


Write and Read operations


- The steps that must be taken for the purpose of transferring a stored word out of memory are as follows:

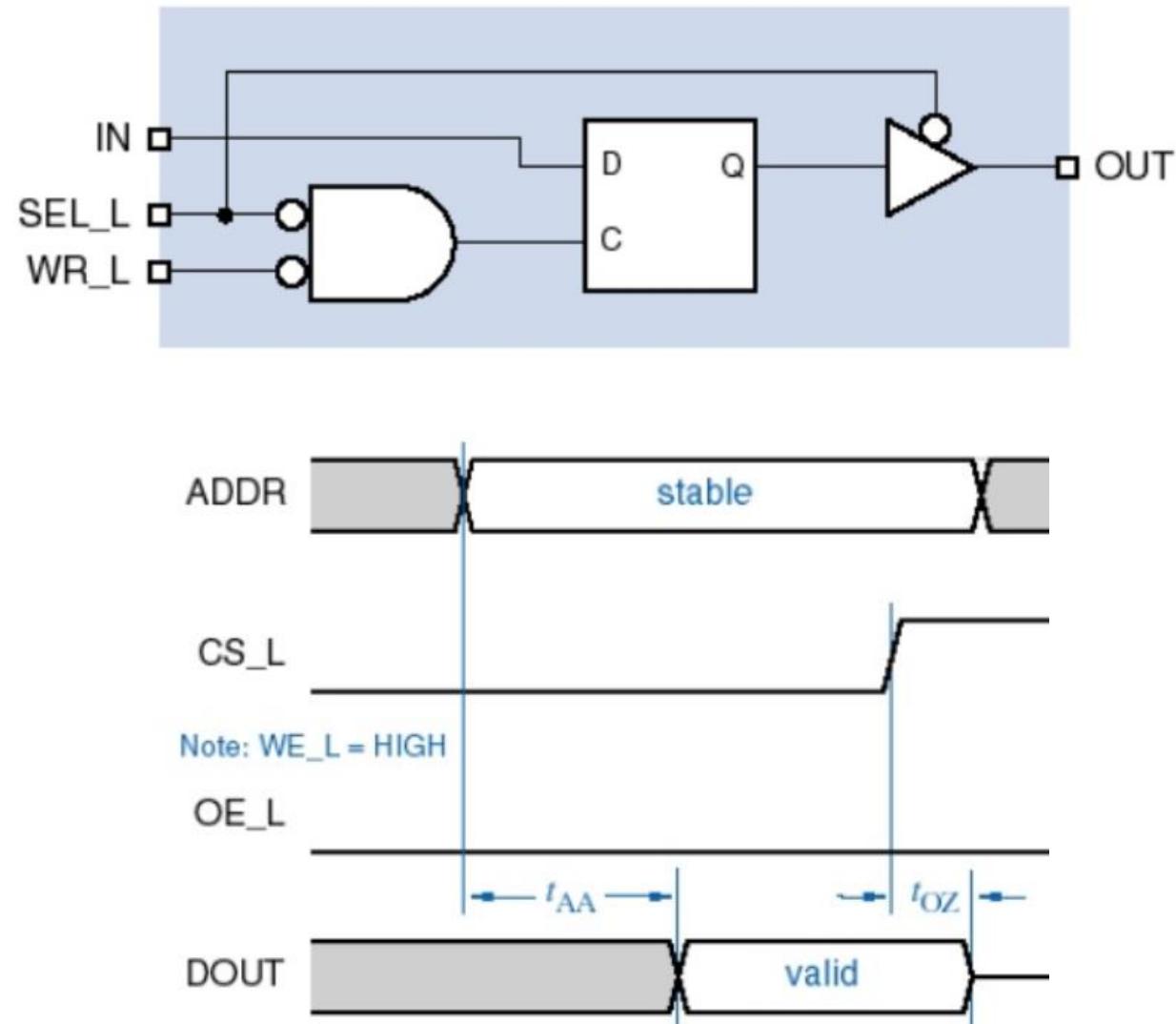1. Apply the binary address of the desired word to the address lines


- The data shows up on the output lines after a certain delay from the application of the stable address (selecting the word)



Memory design

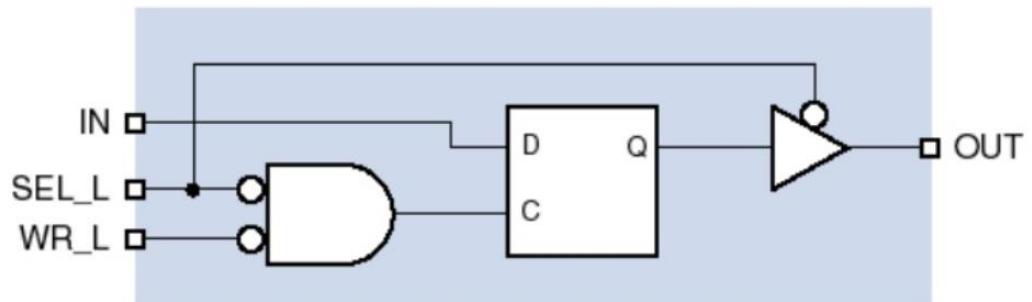

02-01-2023

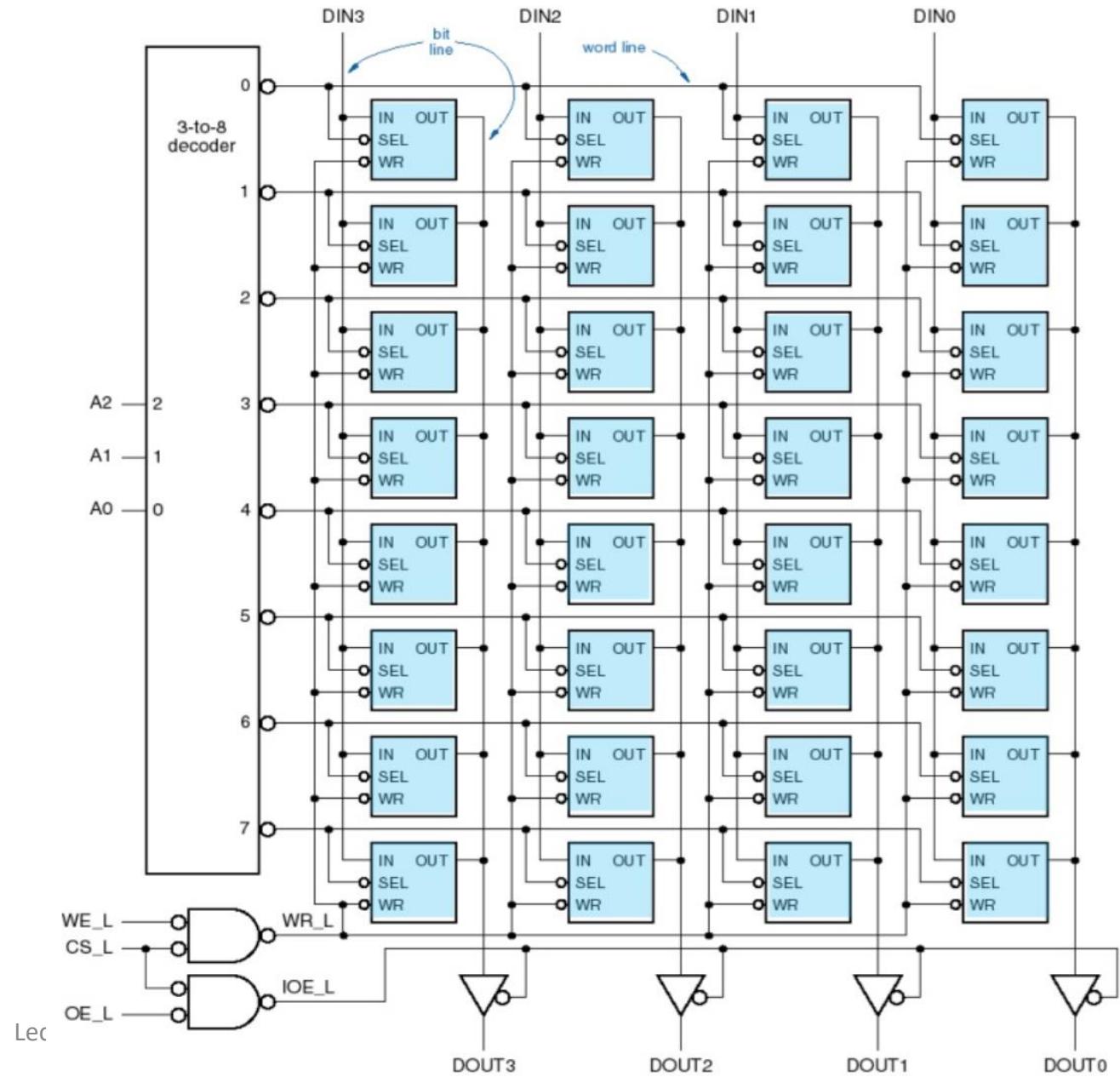


Lecture 24 – Memory architecture 2

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST


Chapter 7

Memory design

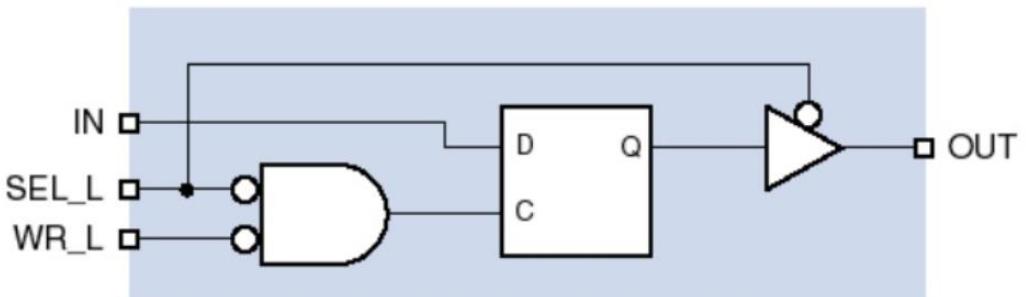- The design of a memory will consist of a decoder circuit to select a particular “word line” based on the address
- The write enable, chip select and other inputs are common to all the latches
- The “bit line” determines what the bit at a particular position in the word will be




04-01-2023

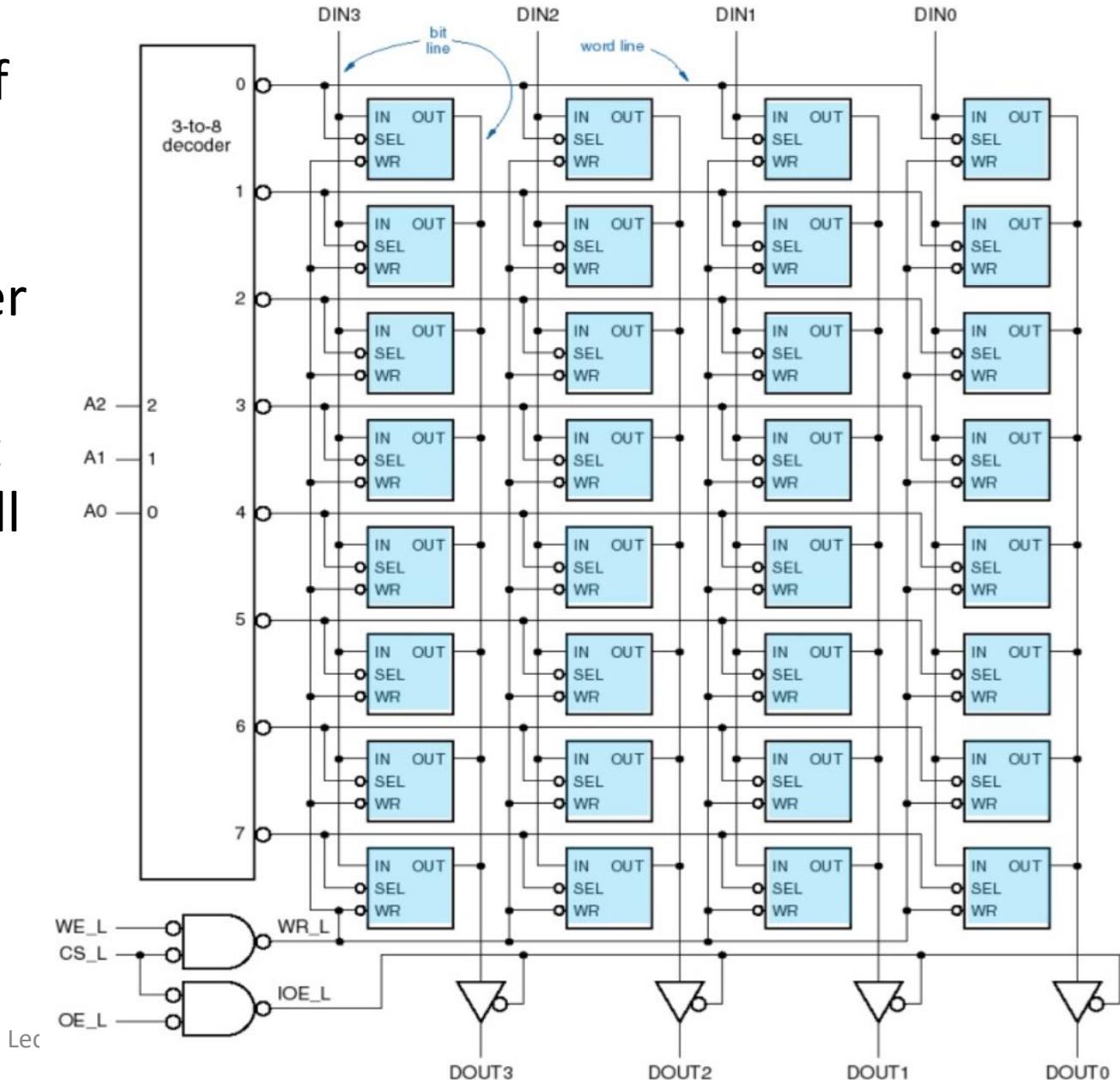

Lec


Memory design

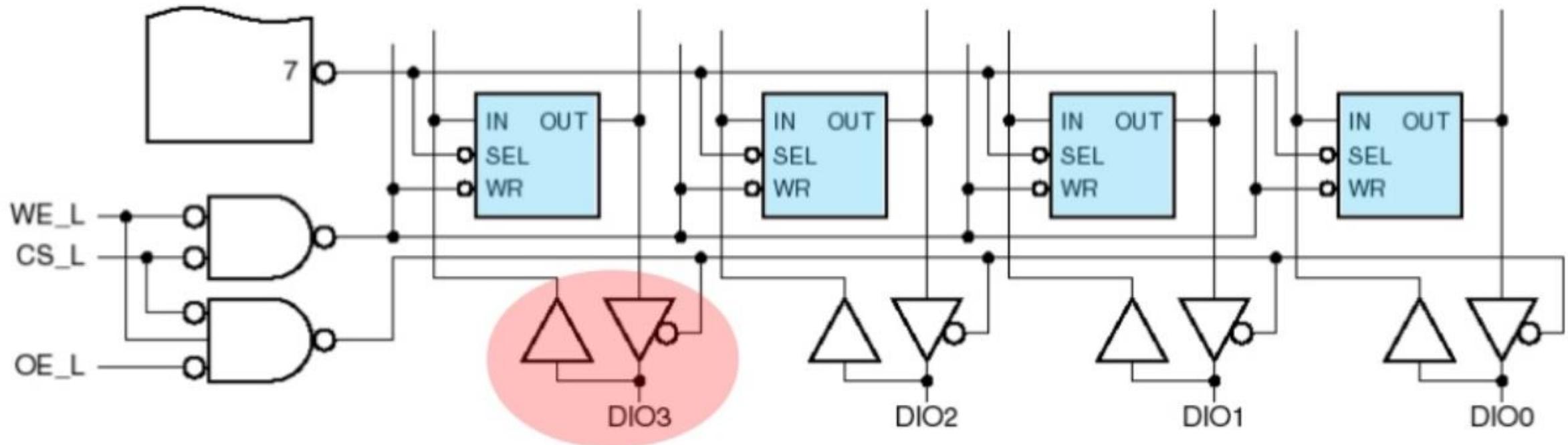- We can modify the output such that we have the same lines for both input and output case
- This is very common both inside the processor (internal buses) and outside the processor (such as digital IO or GPIO)



Synchronous RAMs

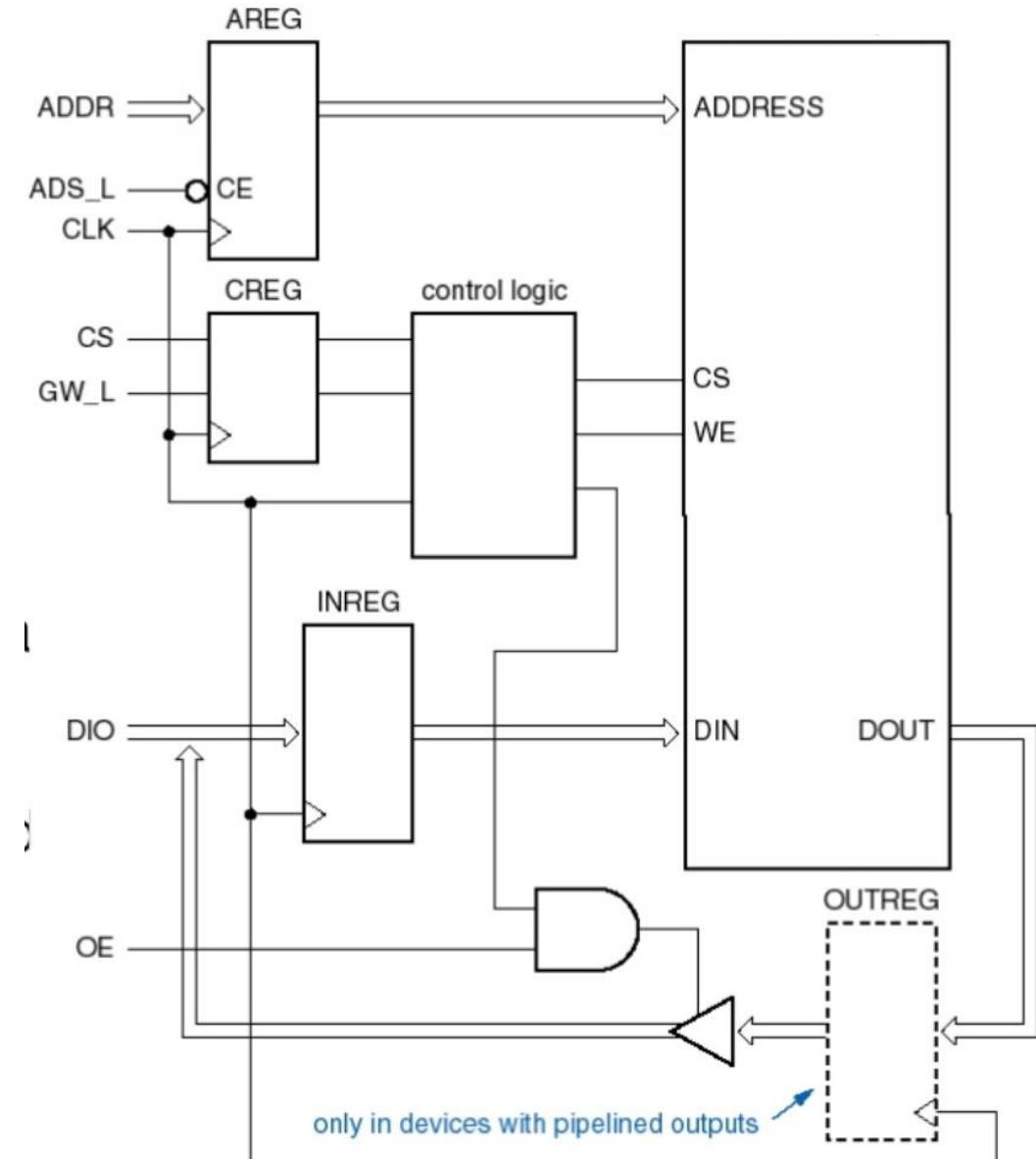- We can modify the input output behaviour of the SRAM array to make it synchronous
- We can easily do it using registers for address (AREG), control inputs (CREG), inputs (INREG) and outputs (OUTREG)
- We can make the output synchronous or flow through
- They are all controlled using a common clock
- An asynchronous SRAM array is used to store the data




Coincident decoding

- A decoder with k inputs and 2^k outputs requires 2^k AND gates with k inputs per gate
- The total number of gates and the number of inputs per gate can be reduced by employing two decoders in a two-dimensional selection scheme
- The basic idea in two-dimensional decoding is to arrange the memory cells in an array that is close as possible to square
- In this configuration, two $k/2$ -input decoders are used instead of one k -input decoder
- One decoder performs the row selection and the other the column selection in a two-dimensional matrix configuration


Coincident decoding

- For example, instead of using a single $10 \times 1,024$ decoder, we use two 5×32 decoders
- With the single decoder, we would need 1,024 AND gates with 10 inputs in each
- In the two-decoder case, we need 64 AND gates with 5 inputs in each
- The five most significant bits of the address go to input X and the five least significant bits go to input Y
- Each word within the memory array is selected by the coincidence of one X line and one Y line
- Thus, each word in memory is selected by the coincidence between 1 of 32 rows and 1 of 32 columns, for a total of 1,024 words

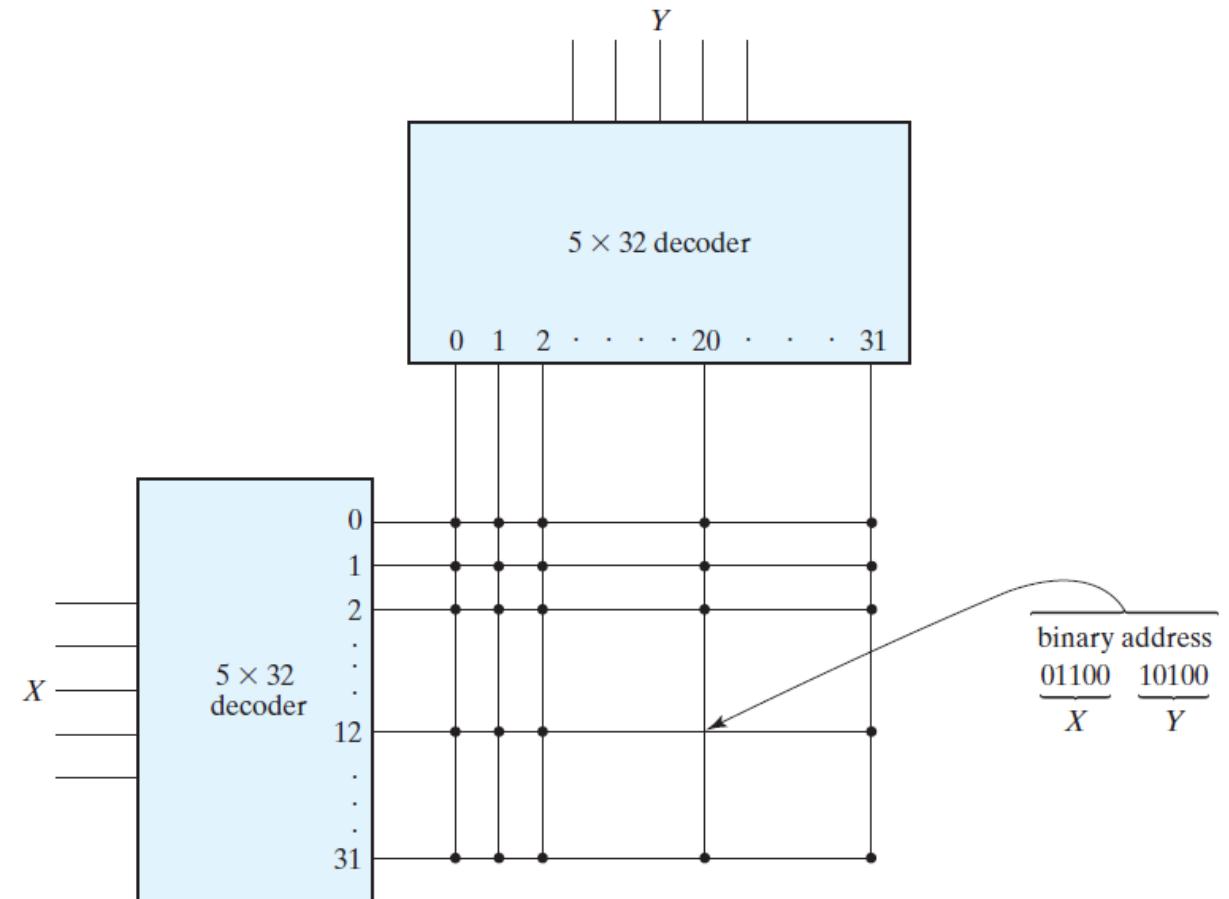


Coincident decoding

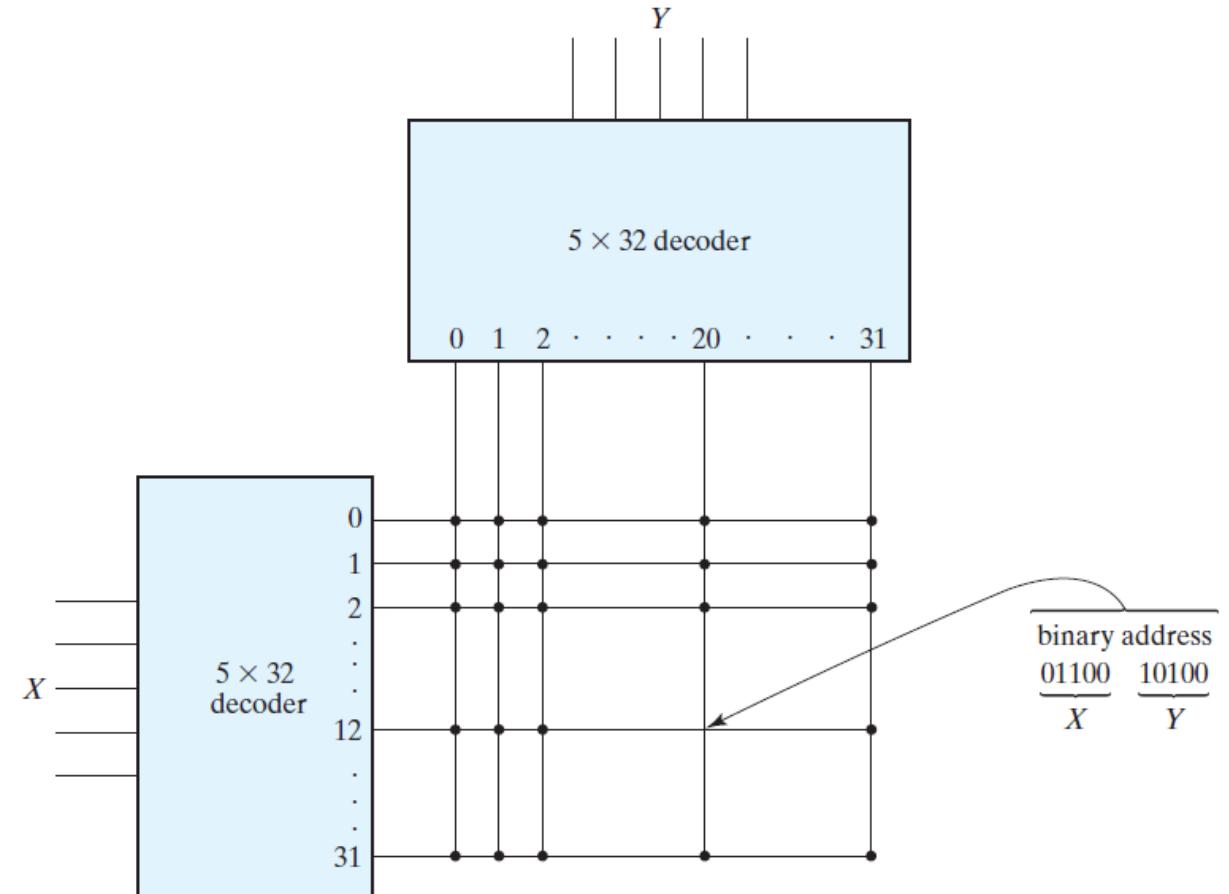- As an example, consider the word whose address is 404. The 10-bit binary equivalent of 404 is 01100 10100. This makes $X = 01100$ (binary 12) and $Y = 10100$ (binary 20)
- The n -bit word that is selected lies in the X decoder output number 12 and the Y decoder output number 20
- All the bits of the word are selected for reading or writing




Address multiplexing

- To reduce the number of pins in the IC package, designers utilize address multiplexing whereby one set of address input pins accommodates the address components
- In a two-dimensional array, the address is applied in two parts at different times, with the row address first and the column address second
- Since the same set of pins is used for both parts of the address, the size of the package is decreased significantly

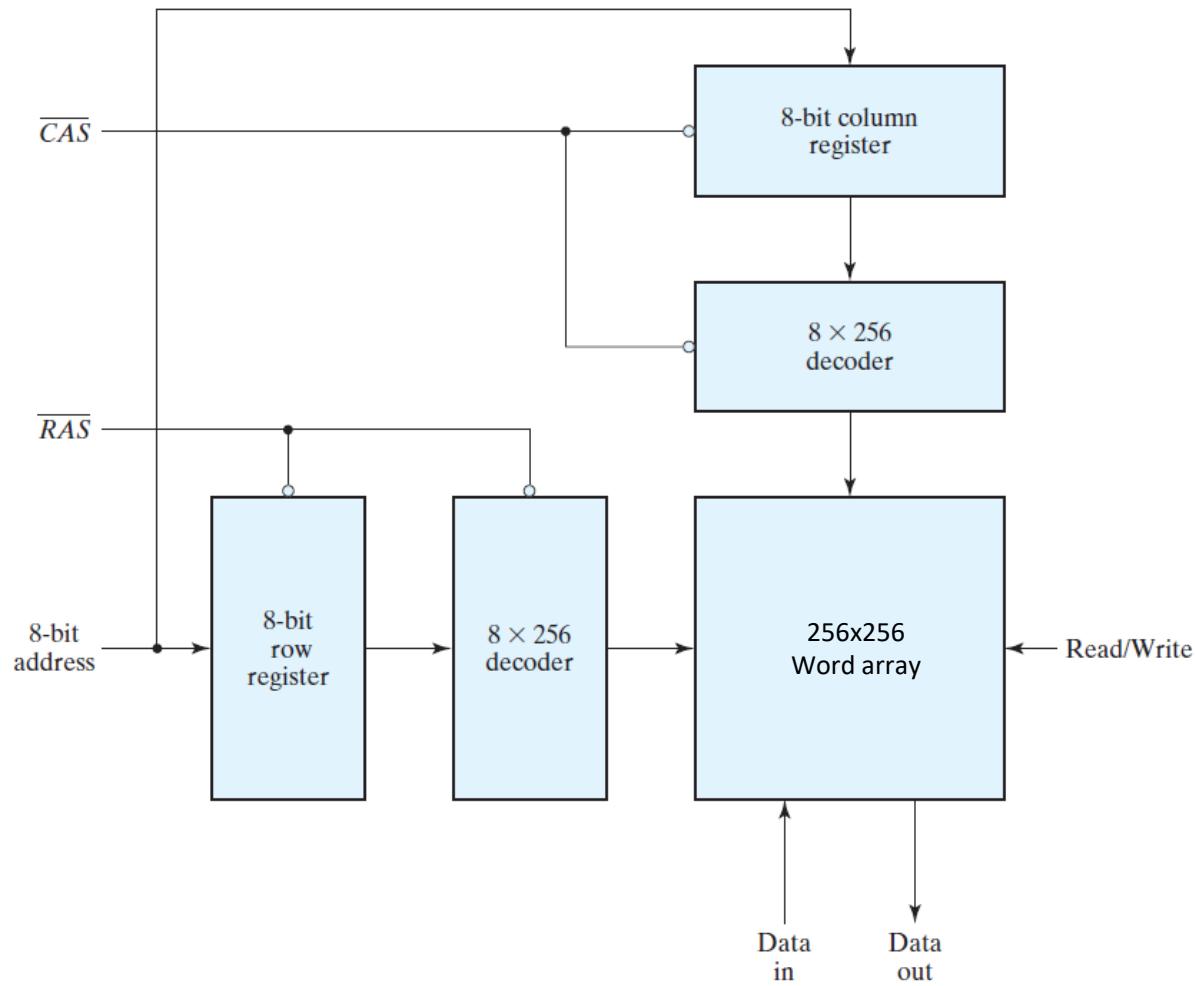


Address multiplexing

- We will use a 64K-word memory to illustrate the address-multiplexing idea
- The memory consists of a two-dimensional array of cells arranged into 256 rows by 256 columns, for a total of $2^8 * 2^8 = 2^{16} = 64K$ words
- There is a single data input line, a single data output line, and a read/write control, as well as an eight-bit address input and two address *strokes*, the latter included for enabling the row and column address into their respective registers
- The row address strobe (RAS) enables the eight-bit row register, and the column address strobe (CAS) enables the eight-bit column register

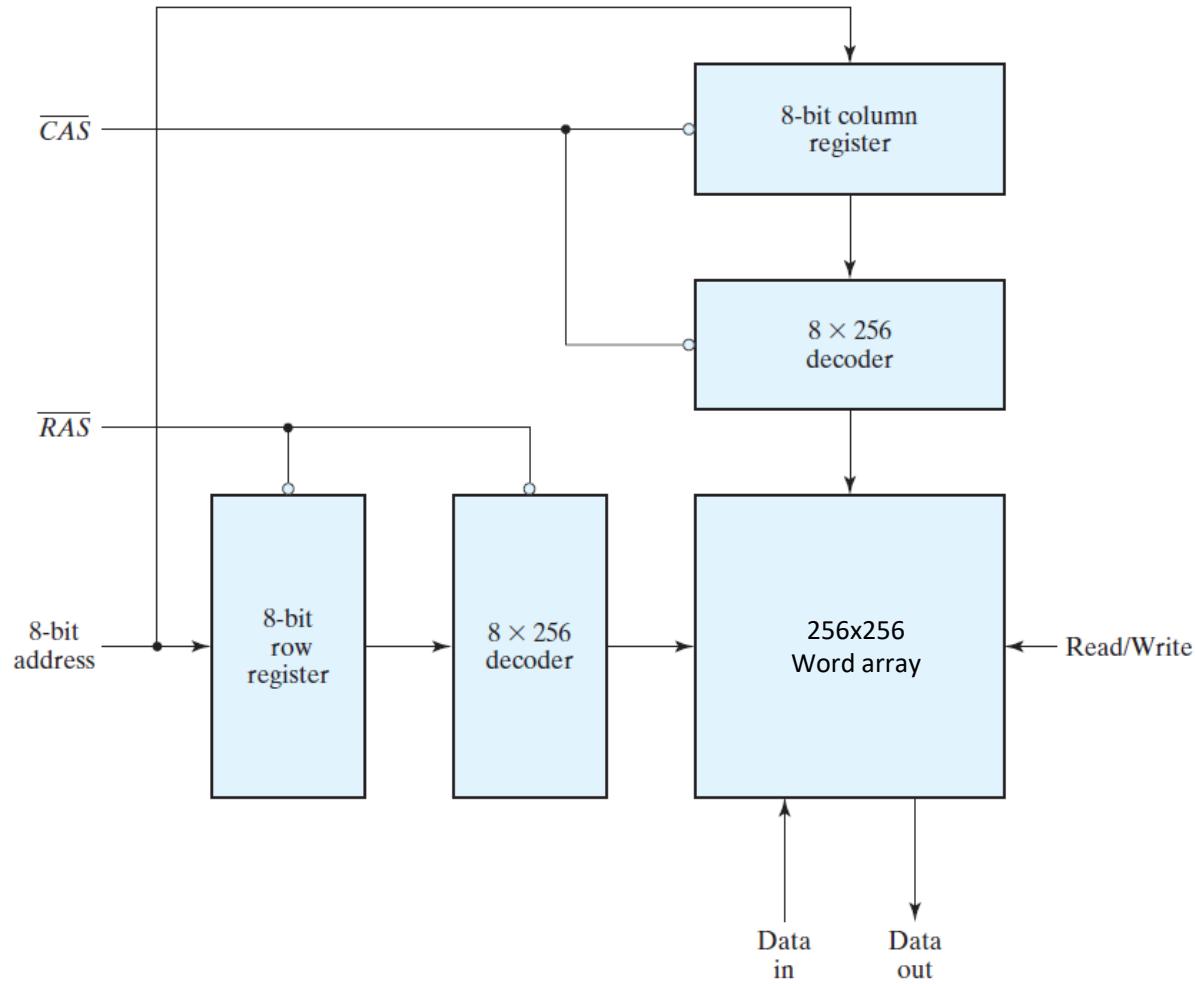


Address multiplexing

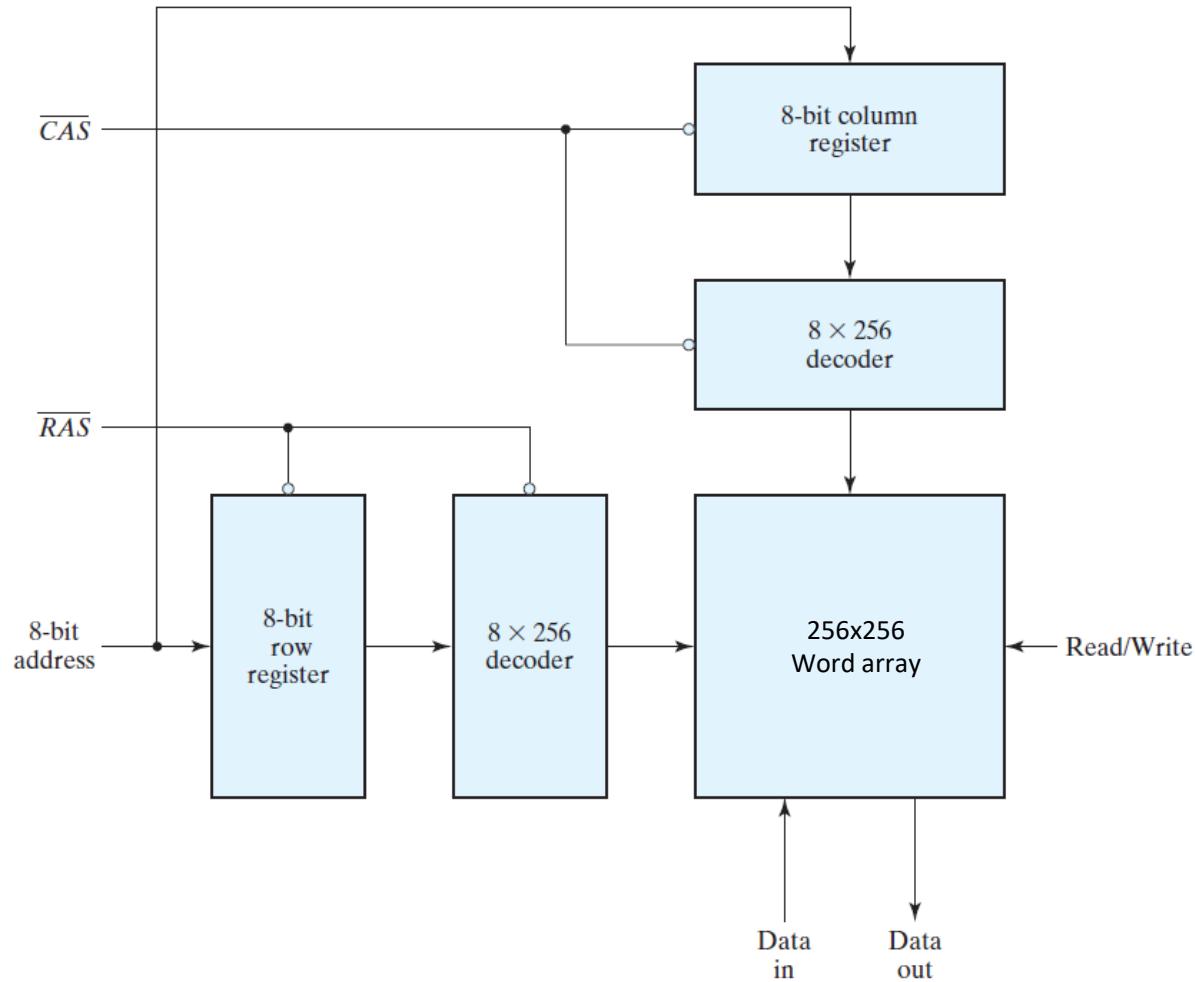- The 8-bit row address is applied to the address inputs and RAS is activated
- This loads the row address into the row address register
- RAS also enables the row decoder so that it can decode the row address and select one row of the array



Address multiplexing

- The 8-bit column address is again applied to the address inputs, and CAS activated
- This transfers the column address into the column register and enables the column decoder
- Now the two parts of the address are in their respective registers, the decoders have decoded them to select the one cell corresponding to the row and column address, and a read or write operation can be performed on that cell
- CAS must go back to the logic 1 level before initiating another memory operation

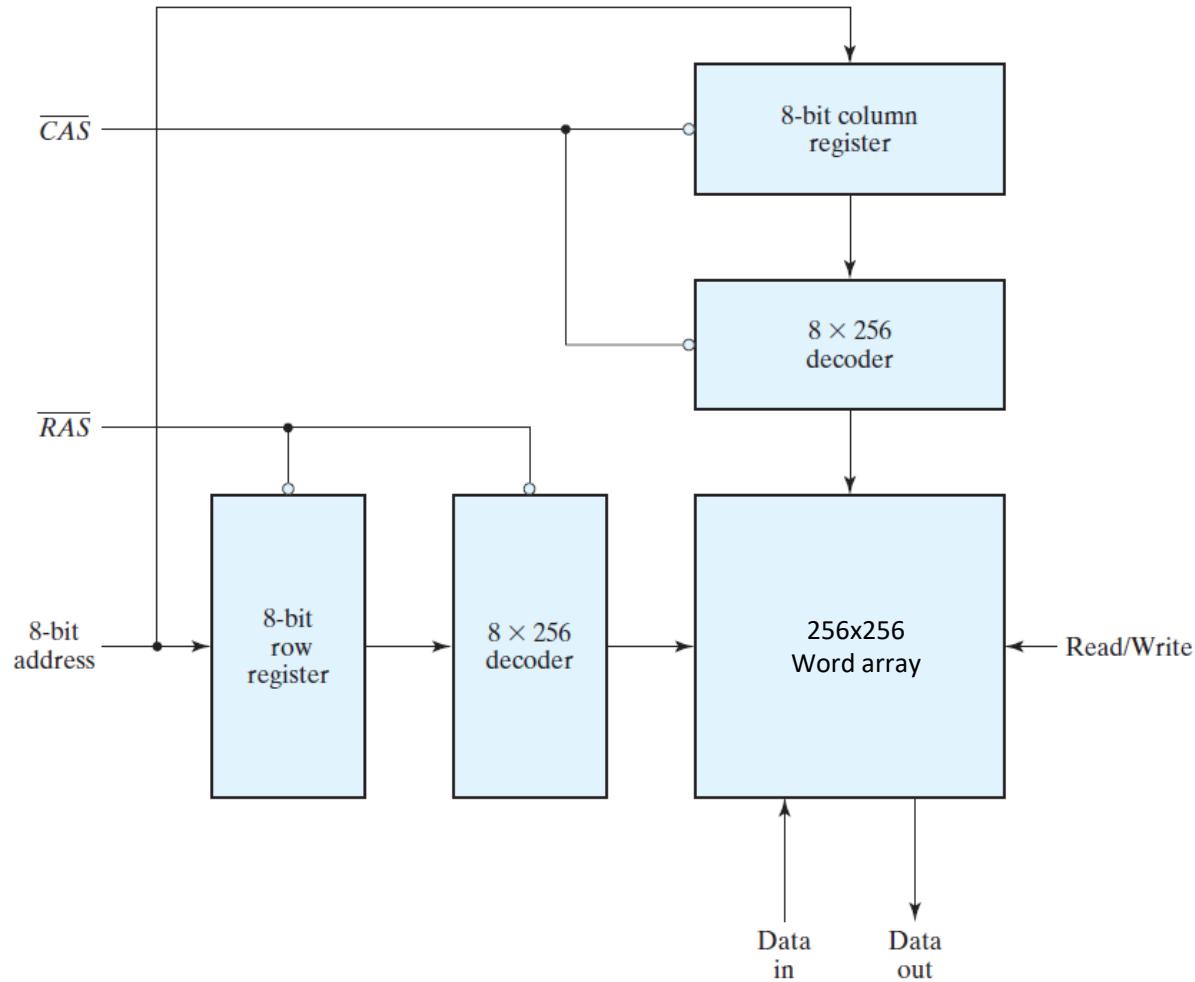

Lecture 25 – Memory architecture 3

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Chapter 7

Error detection and correction

- The dynamic physical interaction of the electrical signals affecting the data path of a memory unit may cause occasional errors in storing and retrieving the binary information
- The reliability of a memory unit may be improved by employing error-detecting and error-correcting codes
- The most common error detection scheme is the parity bit

The parity bit

- A parity bit is generated and stored along with the data word in memory
- The parity of the word is checked after reading it from memory
- The data word is accepted if the parity of the bits read out is correct
- If the parity checked results in an inversion, an error is detected
- However, it cannot be corrected
- Error correction requires more complex mechanisms such as the Hamming code

The Hamming code

- The poison and the rats!
- You are throwing a party in an hour. You have 1000 wine bottles, and you come to know that one of them contains poison! You decide to use some rats to find out which bottle is poised. The rats will die one hour after consuming the poisoned wine. The rats can consume any amount of wine. What is the minimum number of rats needed?

The Hamming code

- One of the most common error-correcting codes used in RAMs was devised by R. W. Hamming
- In the Hamming code, k parity bits are added to an n -bit data word, forming a new word of $n + k$ bits
- The bit positions are numbered in sequence from 1 to $n + k$
- Those positions numbered as a power of 2 are reserved for the parity bits
- The code can be used with words of any length
- Consider, for example, the 8-bit data word 11000100
- We include 4 parity bits with the 8-bit word and make a 12 bit word

While storing:												
Bit position:	1	2	3	4	5	6	7	8	9	10	11	12
	P_1	P_2	1	P_4	1	0	0	P_8	0	1	0	0

$$\begin{aligned}P_1 &= \text{XOR of bits } (3, 5, 7, 9, 11) = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0 \\P_2 &= \text{XOR of bits } (3, 6, 7, 10, 11) = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0 \\P_4 &= \text{XOR of bits } (5, 6, 7, 12) = 1 \oplus 0 \oplus 0 \oplus 0 = 1 \\P_8 &= \text{XOR of bits } (9, 10, 11, 12) = 0 \oplus 1 \oplus 0 \oplus 0 = 1\end{aligned}$$

While reading:												
Bit position:	0	0	1	1	1	0	0	1	0	1	0	0
	1	2	3	4	5	6	7	8	9	10	11	12

$$\begin{aligned}C_1 &= \text{XOR of bits } (1, 3, 5, 7, 9, 11) \\C_2 &= \text{XOR of bits } (2, 3, 6, 7, 10, 11) \\C_4 &= \text{XOR of bits } (4, 5, 6, 7, 12) \\C_8 &= \text{XOR of bits } (8, 9, 10, 11, 12)\end{aligned}$$

The Hamming code

- A 0 check bit designates even parity over the checked bits and a 1 designates odd parity
- Since the bits were stored with even parity, the result, $C = C_8C_4C_2C_1 = 0000$, indicates that no error has occurred
- **Here is some magic:** However, if $C \neq 0$, then the 4-bit binary number formed by the check bits gives the position of the erroneous bit!
- How? Check out the poison and rat puzzle

While storing:

Bit position:	1	2	3	4	5	6	7	8	9	10	11	12
	P_1	P_2	1	P_4	1	0	0	P_8	0	1	0	0

$$P_1 = \text{XOR of bits } (3, 5, 7, 9, 11) = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$P_2 = \text{XOR of bits } (3, 6, 7, 10, 11) = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$P_4 = \text{XOR of bits } (5, 6, 7, 12) = 1 \oplus 0 \oplus 0 \oplus 0 = 1$$

$$P_8 = \text{XOR of bits } (9, 10, 11, 12) = 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

While reading:

Bit position:	0	1	2	3	4	5	6	7	8	9	10	11	12
	1	0	0	1	1	0	0	1	0	1	0	0	0

$$C_1 = \text{XOR of bits } (1, 3, 5, 7, 9, 11)$$

$$C_2 = \text{XOR of bits } (2, 3, 6, 7, 10, 11)$$

$$C_4 = \text{XOR of bits } (4, 5, 6, 7, 12)$$

$$C_8 = \text{XOR of bits } (8, 9, 10, 11, 12)$$

Single correct, double detect

- The Hamming code can detect and correct only a single error
- By adding another parity bit to the coded word, the Hamming code can be used to correct a single error and detect double errors
- If we include this additional parity bit, then the previous 12-bit coded word becomes $001110010100P_{13}$, where P_{13} is evaluated from the exclusive-OR of the other 12 bits
- This produces the 13-bit word 0011100101001 (even parity)
- When the 13-bit word is read from memory, the check bits are evaluated, as is the parity P over the entire 13 bits
- The following four cases can arise:
 1. If $C = 0$ and $P = 0$, no error occurred
 2. If $C \neq 0$ and $P = 1$, a single error occurred that can be corrected
 3. If $C \neq 0$ and $P = 0$, a double error occurred, but that cannot be corrected
 4. If $C = 0$ and $P = 1$, an error occurred in the P_{13} bit!


Lecture 26 – Processor design: The Beginning

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST


The universal register

- A universal register is a very useful entity in processor design
- It can store value as well as have some basic arithmetic functions such as increment/decrement etc.
- The register has two input/output lines (sometimes coupled into one IO bus)
- Input lines IN are logically connected internally to the inputs of the n flip-flops inside the register
- Output lines OUT are the lines that hold the value stored in the register when the register is accessed for read. The OUT lines are tristate-capable so that they can be connected to a common data bus

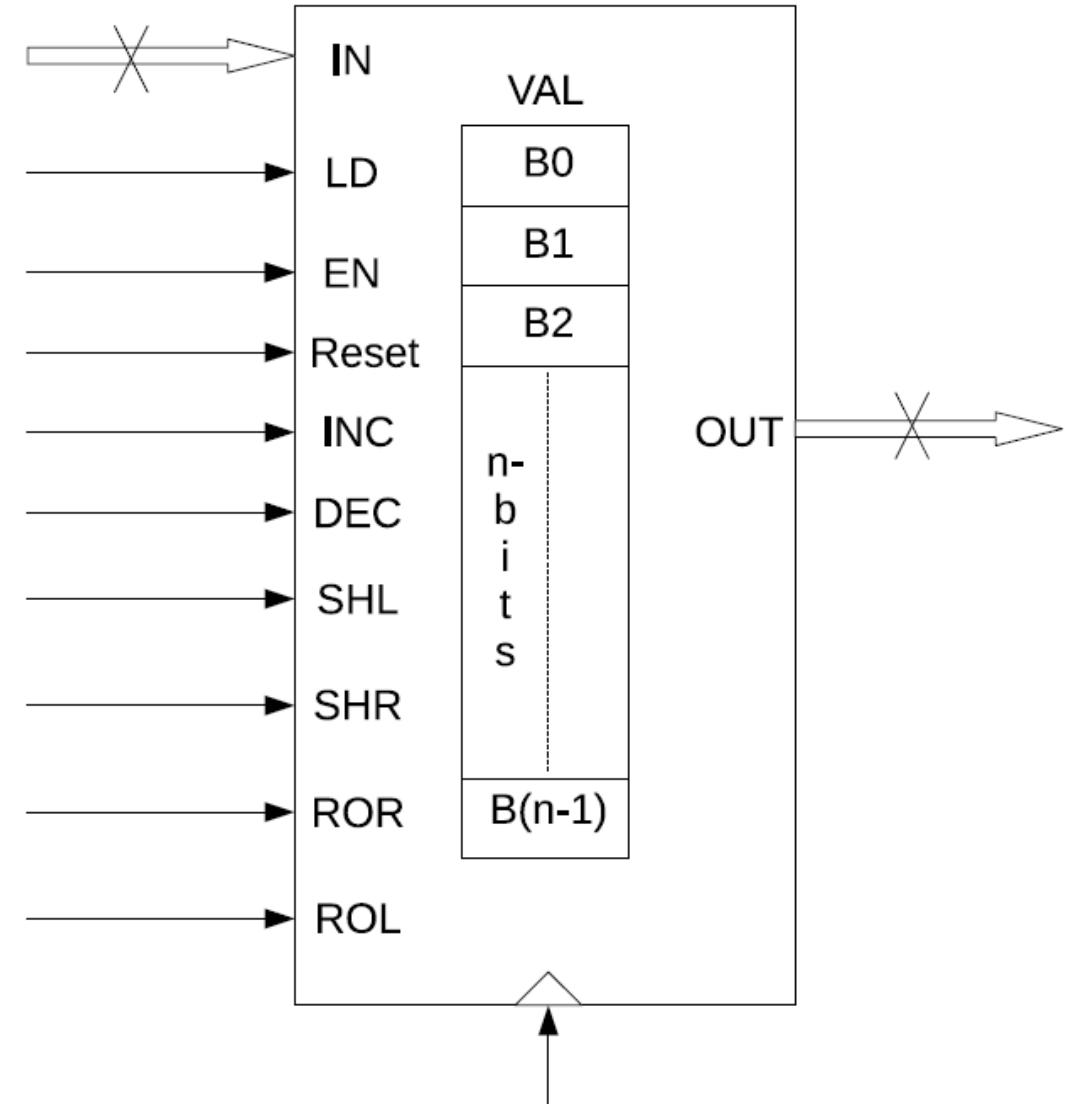


The universal register

- The control bits are as follows:
 - The input EN controls the high-impedance state of the output lines OUT. When EN is 0, the OUT lines will be in the high-impedance state. When EN is 1, the OUT lines will be driven to the electric levels corresponding to the value stored in the register
 - The input LD loads the register from the input, which changes the value stored in it. When LD is 1, the value indicated by the electric levels of the IN lines will replace the previous value stored in the register
 - The input RESET controls resetting of the register. When RESET is 1, a 0 value will be written to all bits stored in the register. We will assume a synchronous reset.

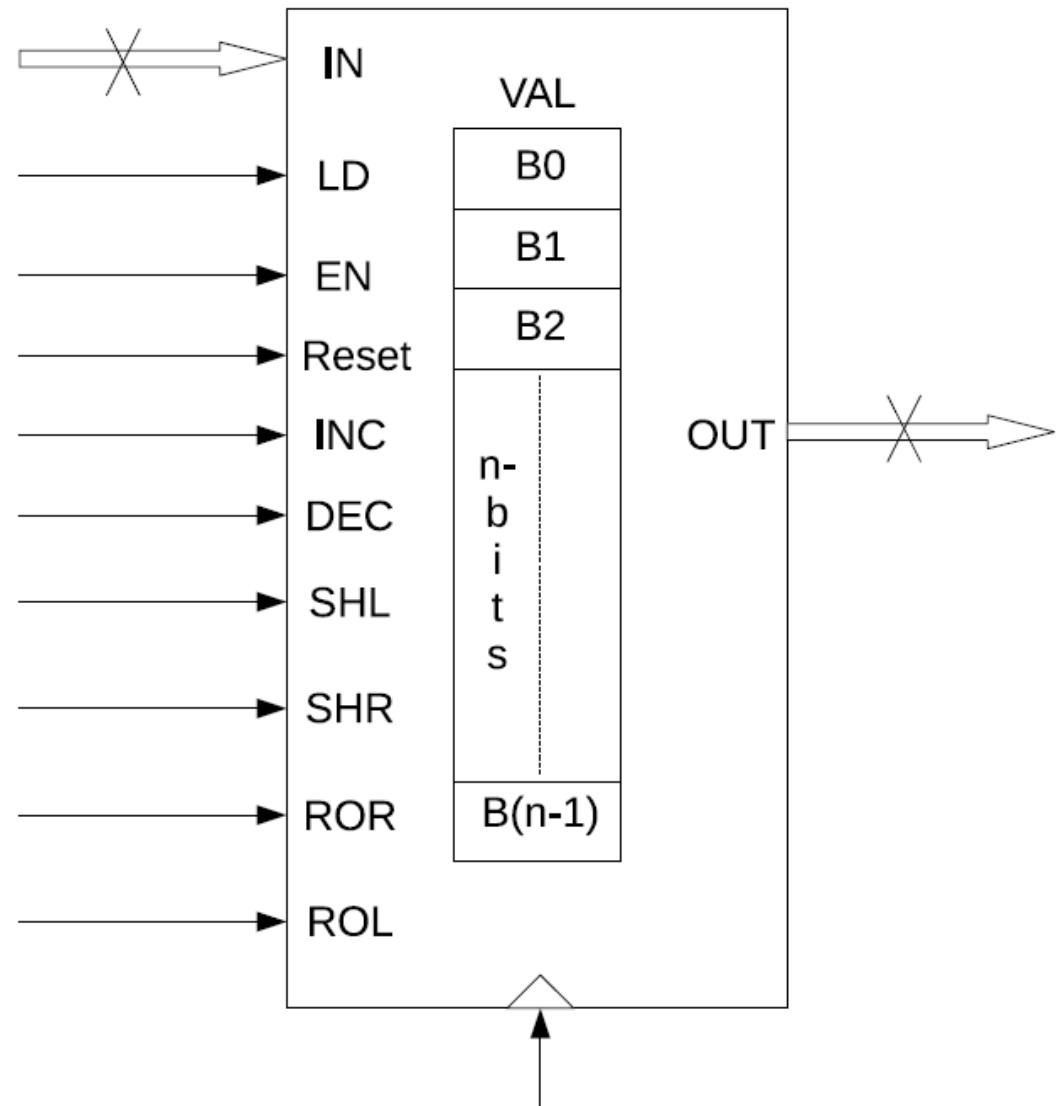


The universal register

- The control bits are as follows:
 - Inputs INC and DEC control the incrementing or decrementing the value stored in the register, interpreted as a number.
 - Inputs ROL, ROR control the left or right rotation of the register contents. This is shifting such that the last bit is feedback to the first bit
 - Inputs SHL, SHR control the left or right shift of the register contents. We assume a 0 will fill the void during the shift

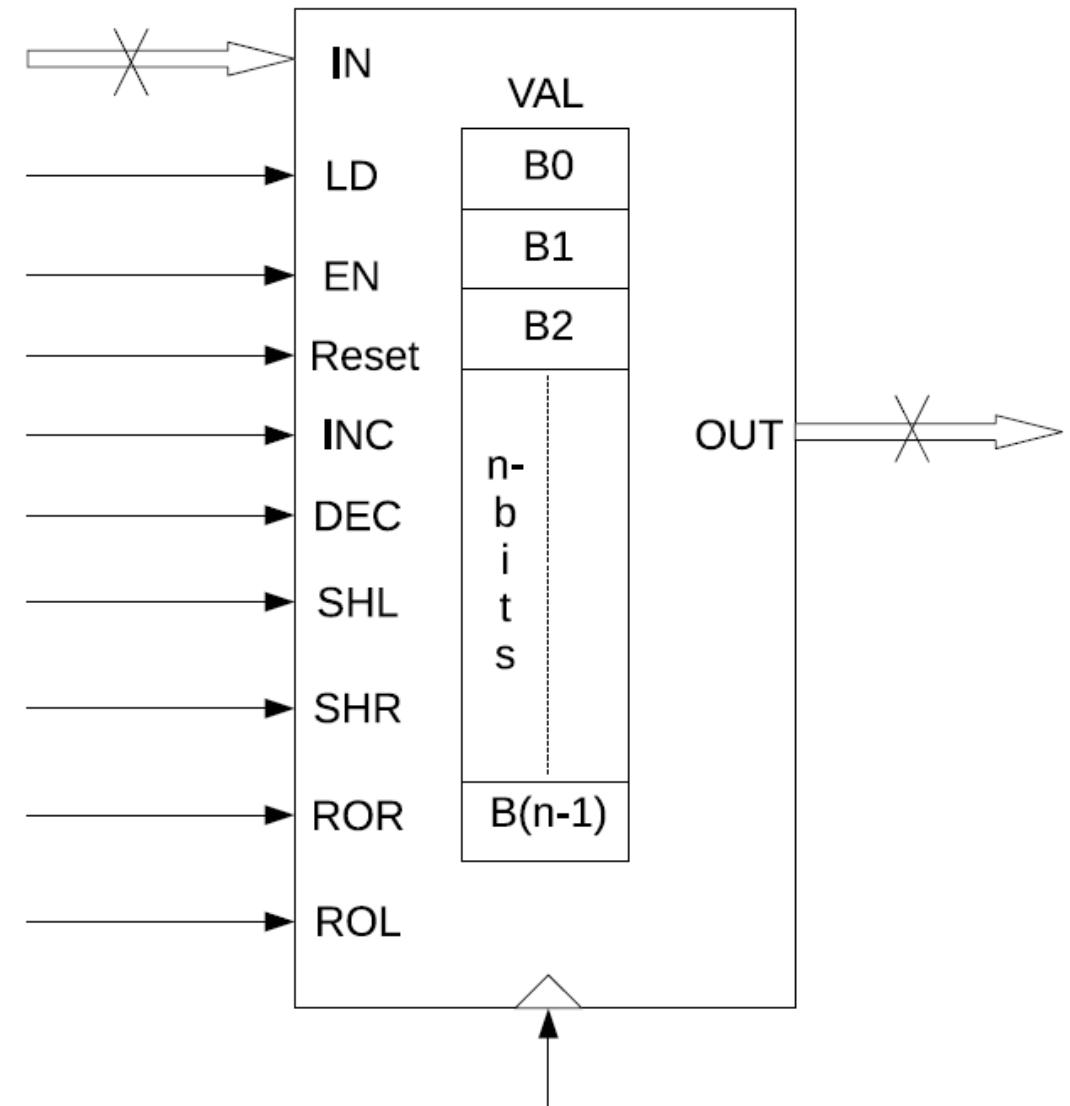


The universal register

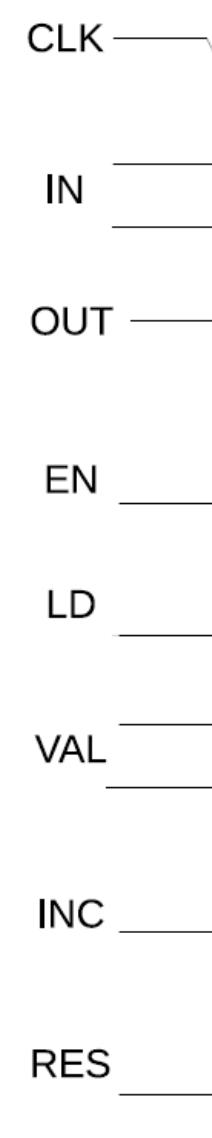- The timing diagram depends on how we design the register
- In this case, we have designed such that all instructions (actions) happen to the stored value at the negative edge of the clock
- While the EN puts the data on the output bus at the positive edge of the clock
- This makes the setup/hold more complex but can be time saving



Creating a common bus

- Using tristate buffers, we can connect multiple input/outputs of multiple registers on the same bus
- Consider registers A and B
- The enable, load, and increment control signals of register A are respectively E_A , L_A , and I_A and for register B are labelled E_B , L_B , and I_B
- Let us say we need to transfer from A to B
- We enable E_A and L_B and in one clock cycle, the contents get transferred

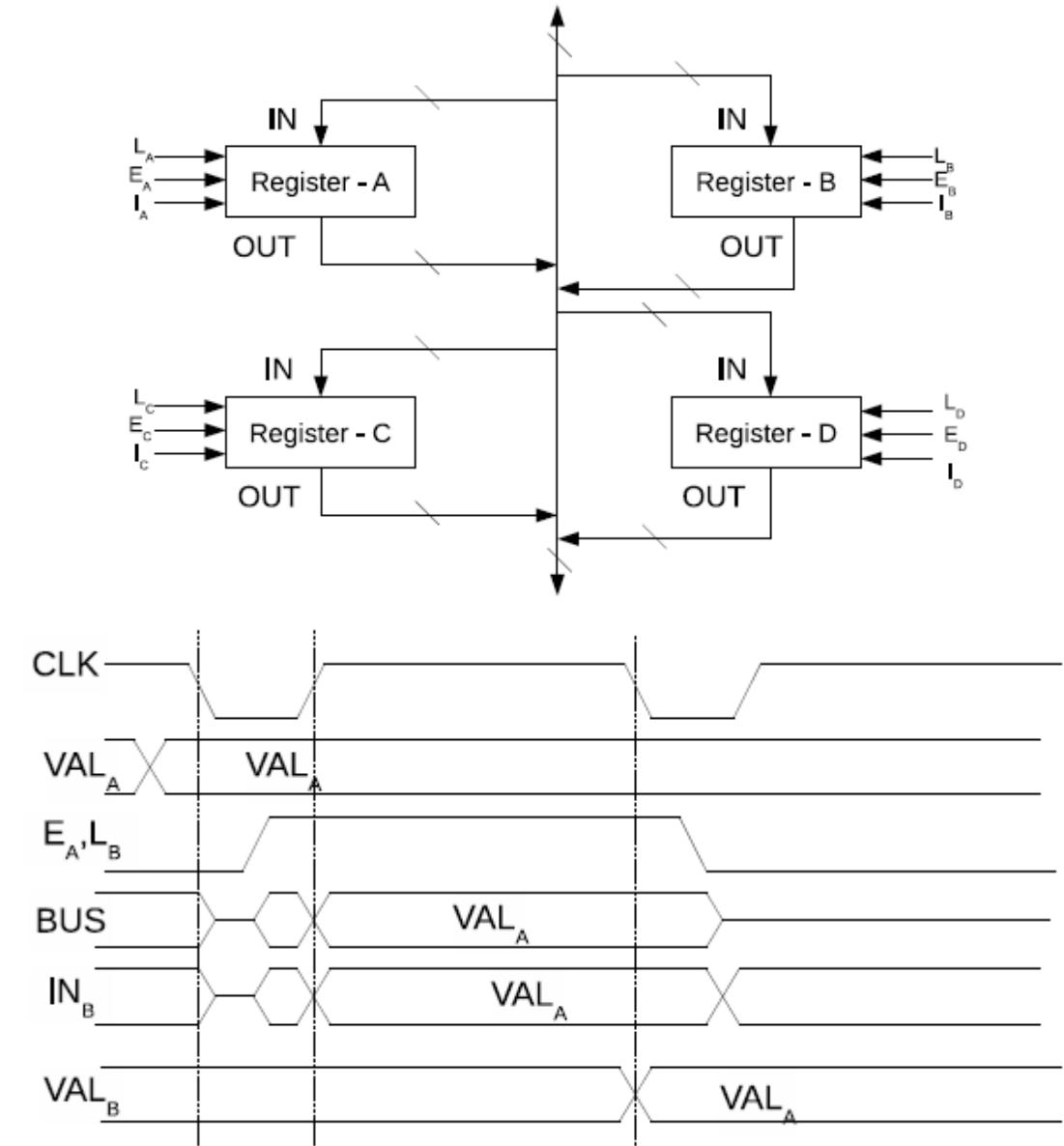



Creating a common bus

- In effect, we have moved the data to register B from register A, like a assignment instruction!

$A = B;$


MOV B A

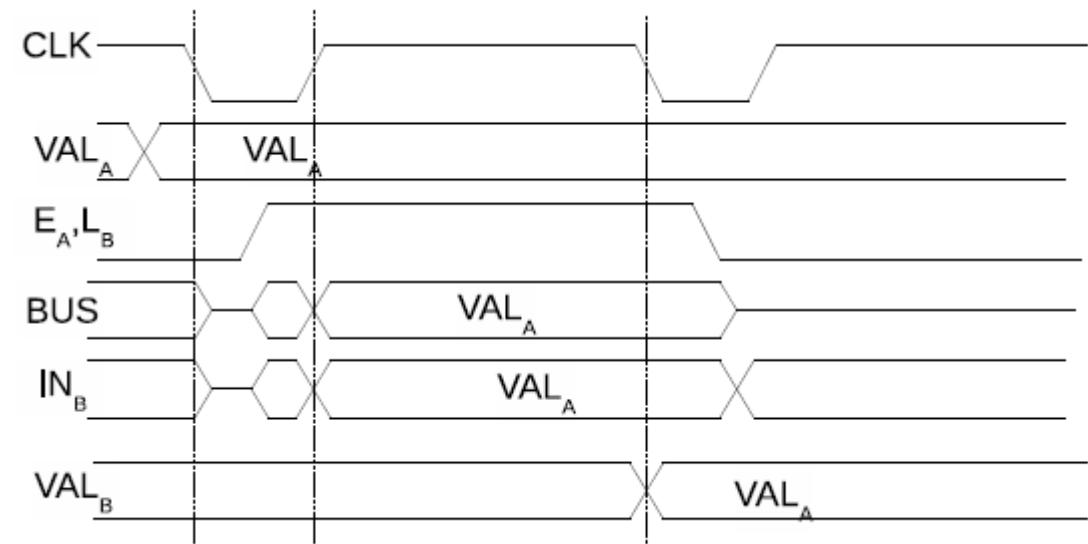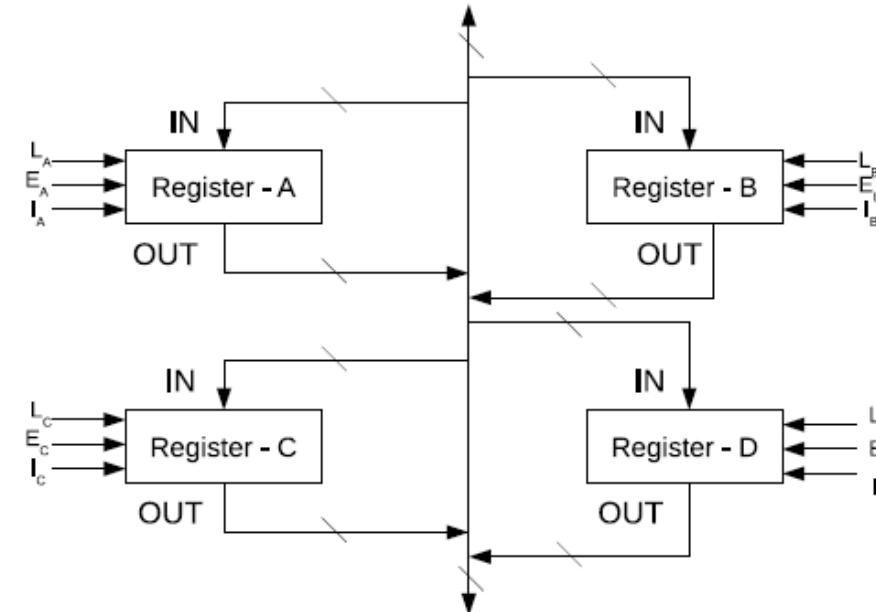- At the level of the hardware, activating 2 signals simultaneously was all that was done
- The rest happened due to the bus connection, the clock, and the design of the register
- What if we activate L_B, E_D, L_C, L_A together?
- What if we activate E_B, L_A, I_B



ALU design

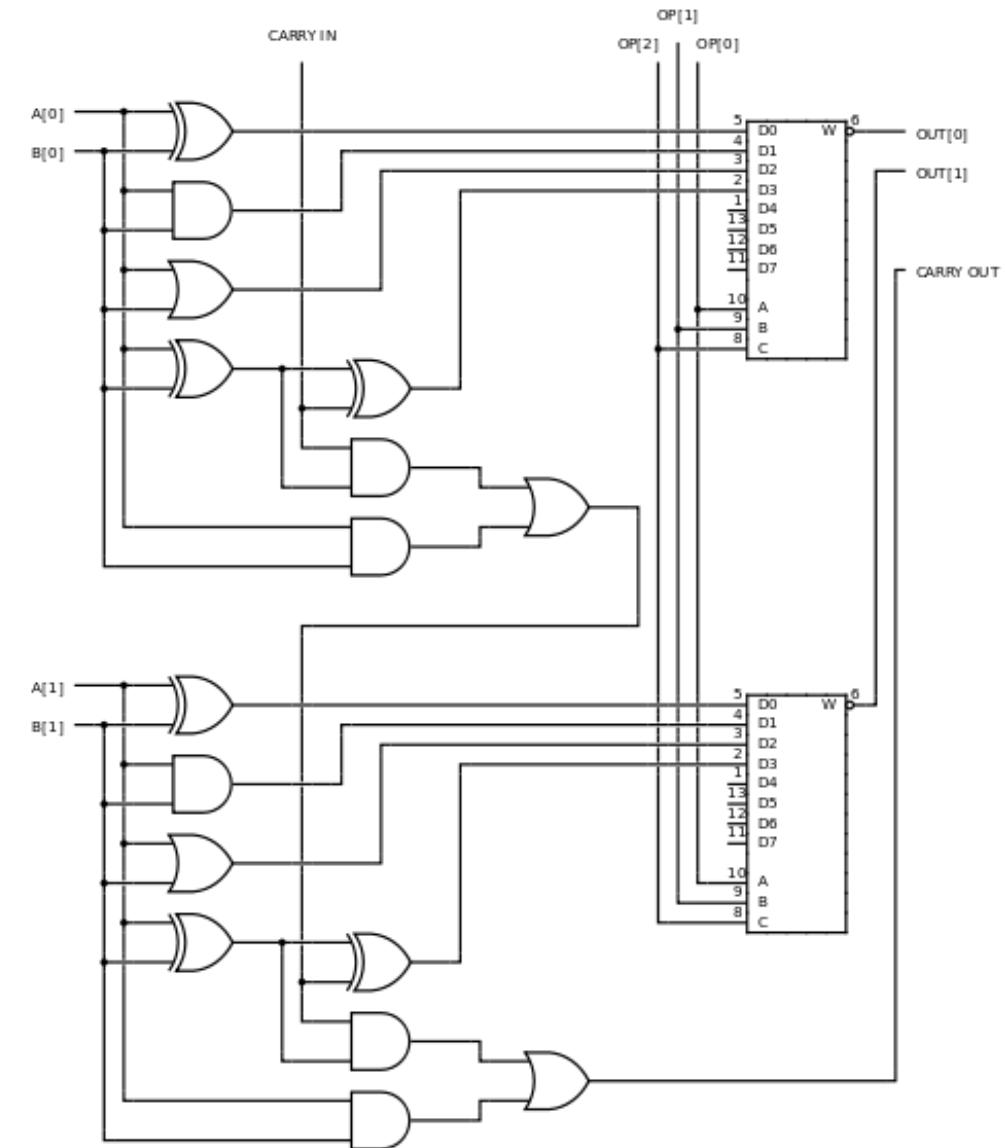
- Enter, The ALU!
- We generally consider an ALU as a “simple” combinational circuit capable of performing several basic functions on a set of two binary numbers – add, sub, multiply, increment, AND, OR, XOR, and many other operations based on a select input
- This is generally implemented using a combination of MUXes within the ALU



ALU design


- Internal architecture of ALU IC 74181

Selection				Active-low inputs & outputs	
S3	S2	S1	S0	Logic (M = 1)	Arithmetic (M = 0) (Cn = 0)
0	0	0	0	\bar{A}	$A \text{ minus } 1$
0	0	0	1	$\bar{A}\bar{B}$	$AB \text{ minus } 1$
0	0	1	0	$\bar{A} + B$	$A\bar{B} \text{ minus } 1$
0	0	1	1	Logical 1	-1
0	1	0	0	$\bar{A} + B$	$A \text{ plus } (A + \bar{B})$
0	1	0	1	\bar{B}	$AB \text{ plus } (A + \bar{B})$
0	1	1	0	$\bar{A} \oplus B$	$A \text{ minus } B \text{ minus } 1$
0	1	1	1	$A + \bar{B}$	$A + \bar{B}$
1	0	0	0	$\bar{A}\bar{B}$	$A \text{ plus } (A + B)$
1	0	0	1	$A \oplus B$	$A \text{ plus } B$
1	0	1	0	B	$A\bar{B}(A + B)$
1	0	1	1	$A + B$	$A + B$
1	1	0	0	Logical 0	$A \text{ plus } A$
1	1	0	1	$A\bar{B}$	$AB \text{ plus } A$
1	1	1	0	AB	$A\bar{B} \text{ plus } A$
1	1	1	1	A	A

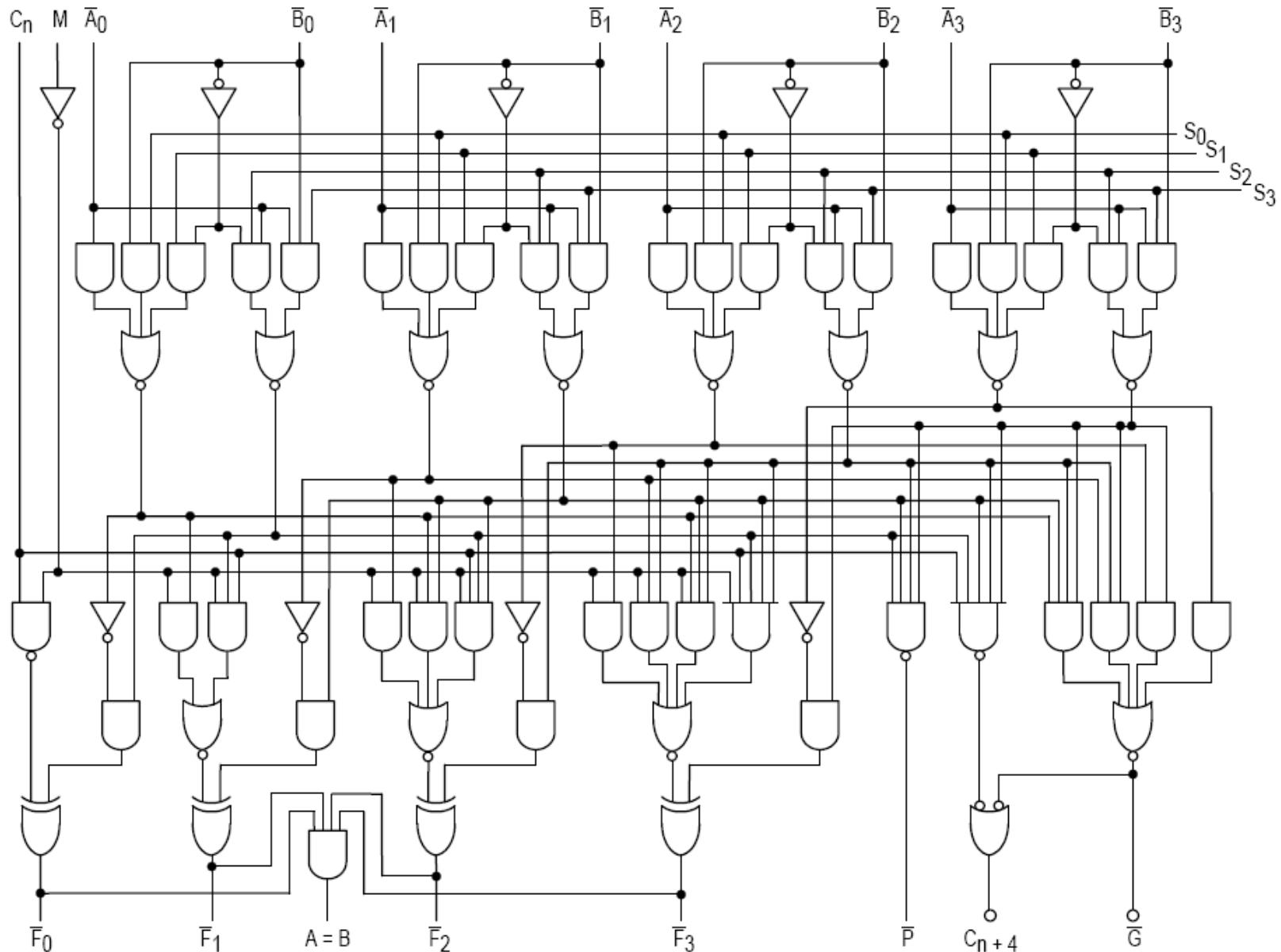


ALU on a bus

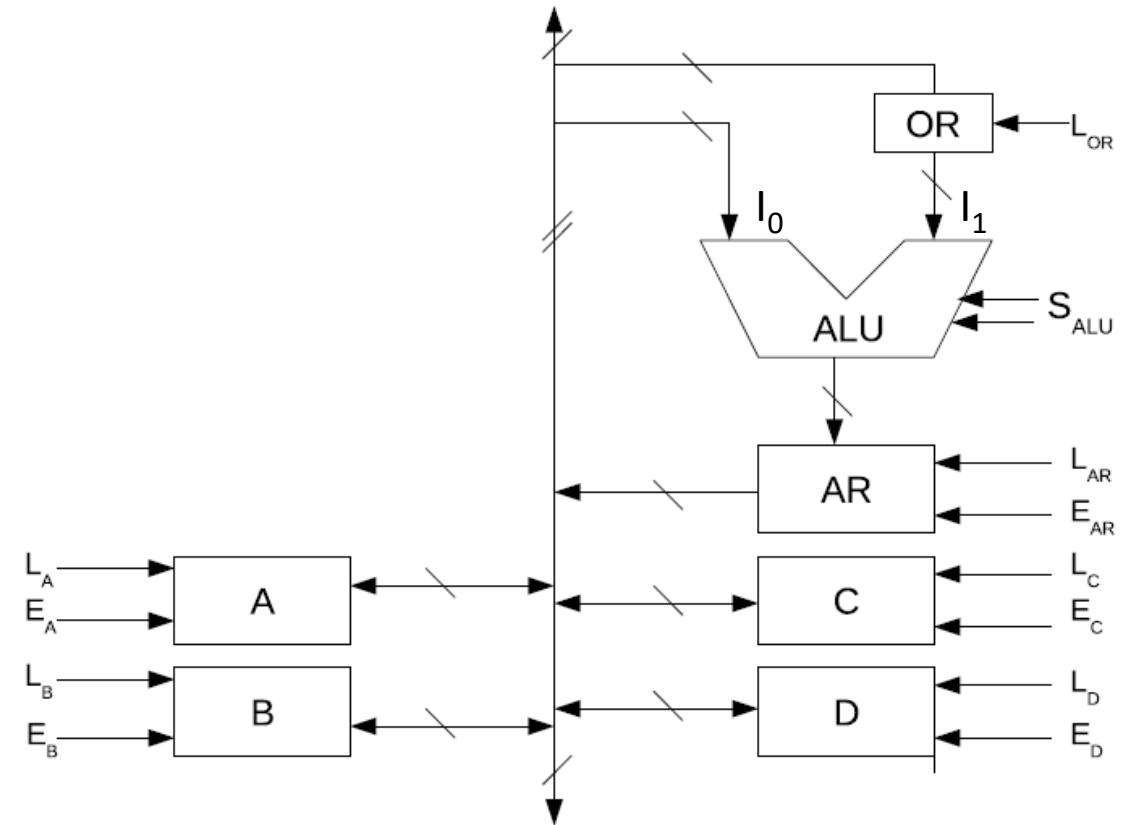- Consider the configuration which has a few registers and an ALU
- Assume all the registers are made using the multipurpose registers
- The ALU is a combinational circuit with 2 inputs and two lines to select the function to be performed
- The two select lines can be in one of 4 combinations
- We refer to them symbolically as ADD, SUB, AND, PASS0



ALU on a bus

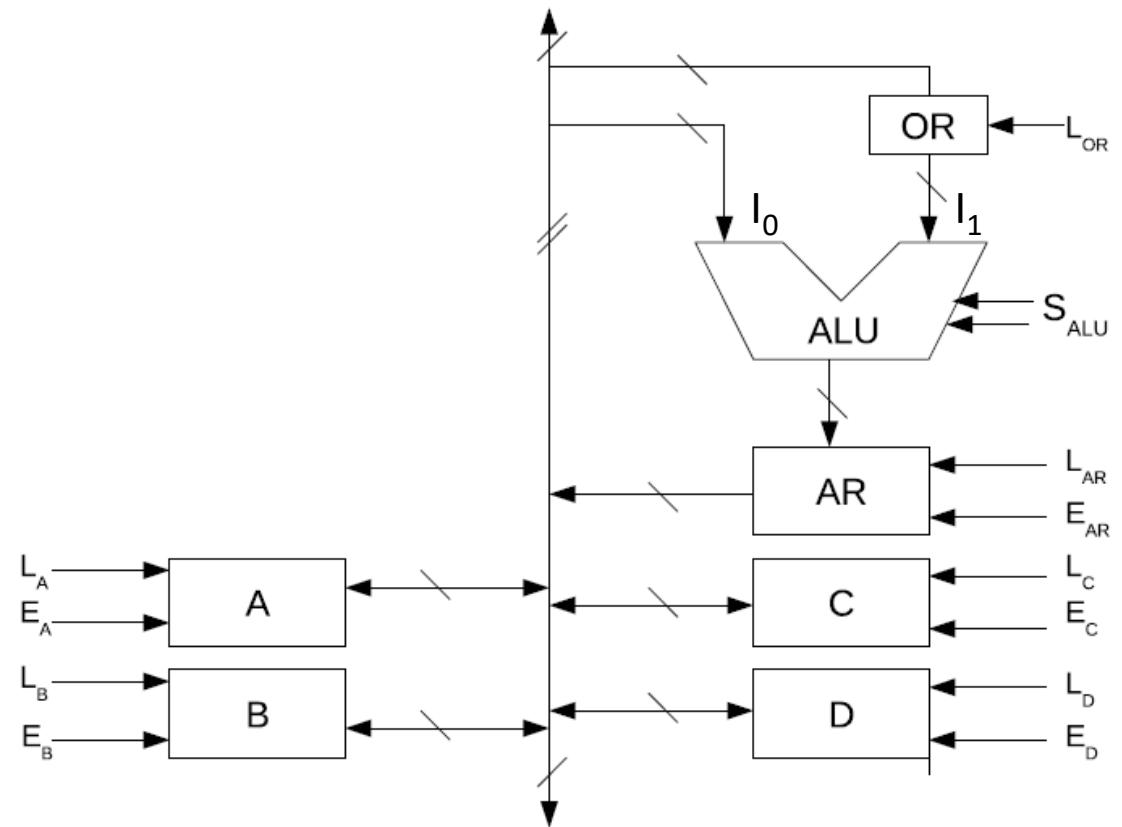
- The ALU has its left input connected to the bus and the right input to a register called OR or operand register, whose inputs are connected to the bus
 - The output of the ALU is connected to the input of a register called AR or accumulator register, whose output is connected to the bus
 - Every register has all the control signals of our generic multipurpose register



ALU on a bus

- What will happen if we activate the following controls: $E_{OR}, E_A, L_{AR}, S_{ALU_{ADD}}$
- Two enables are simultaneously active
- Does it cause conflict at the bus?
- No, since the output of OR is not connected to the bus, there will be no conflict
- The last term above indicates that the select lines of the ALU are set to the combination ADD
- The ALU performs addition of its inputs, which are the contents of OR register and register A
- The sum is written to AR register


$$AR \leftarrow A + OR$$

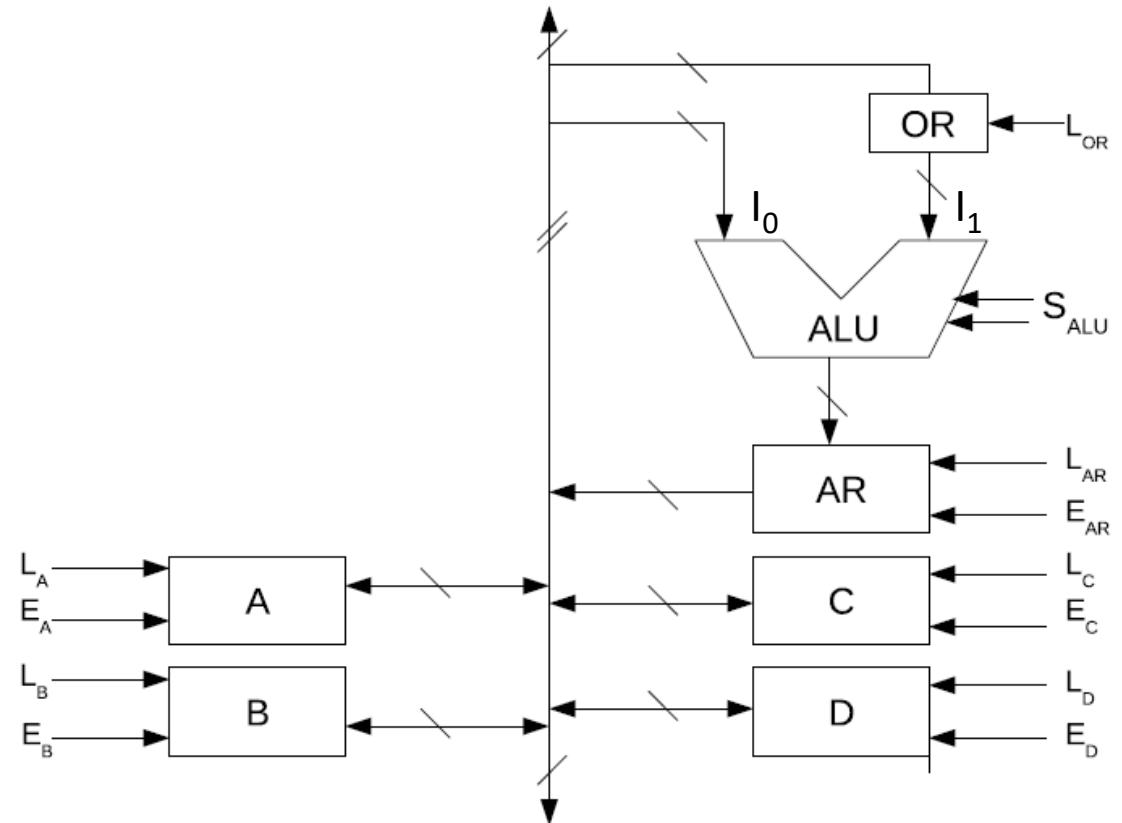

ALU on a bus

- Consider this multiclock instruction:
 - Ck 10: E_A, L_{OR}
 - Ck 11: $E_B, E_{OR}, L_{AR}, SALU_{SUB}$
 - Ck 12: E_{AR}, L_C
- What does the 3 clock cycle combination achieve?
- The contents of A are copied to OR in cycle 10
- The contents of OR are subtracted from the contents of B and the result is loaded to AR in cycle 11
- The contents of AR are copied to register C in cycle 12

$$C \leftarrow B - A$$

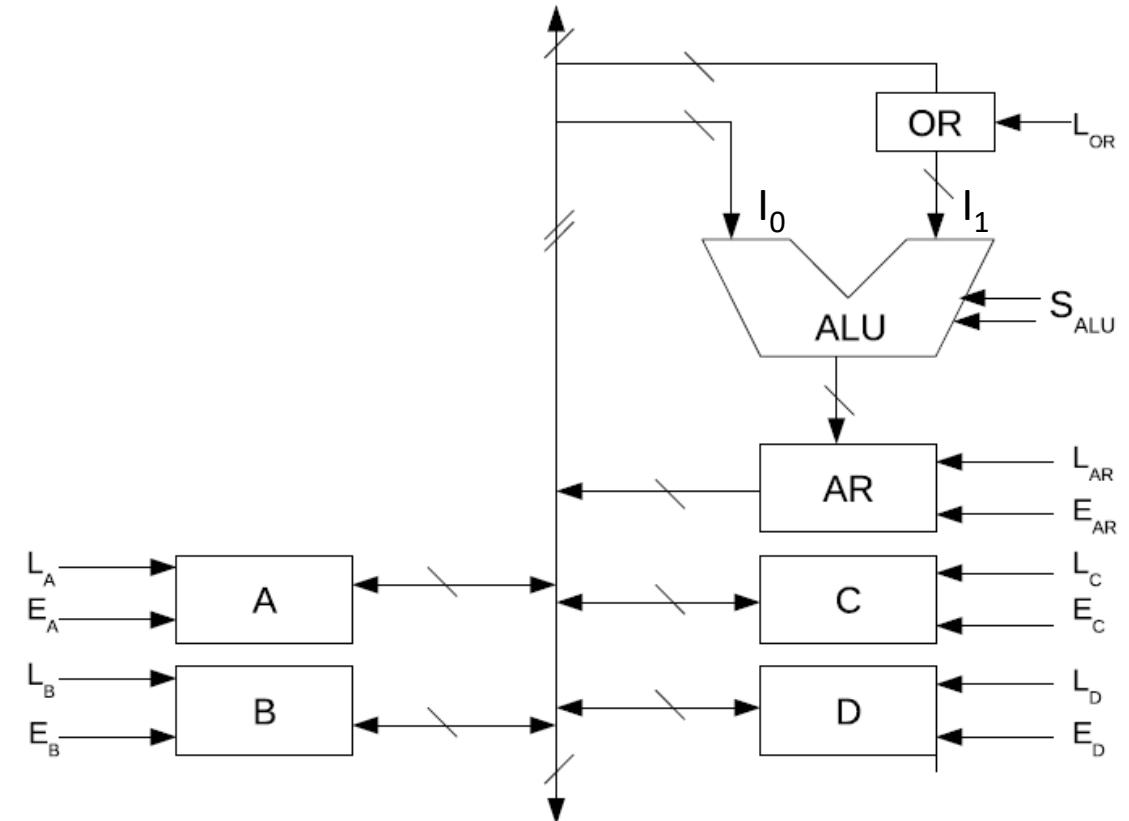

ALU on a bus


- It is easy to see how addition, subtraction and logical AND with any combination of 2 registers as input and any register as output can be implemented using a very similar 3-cycle sequence of combinations of signals
- Let us see if we can write control signals for this instruction:

$$D \leftarrow C \text{ AND } D$$

Ck 1: E_C, L_{OR}


Ck 2: $E_D, E_{OR}, L_{AR}, S_{ALU_{AND}}$

Ck 3: E_{AR}, L_D

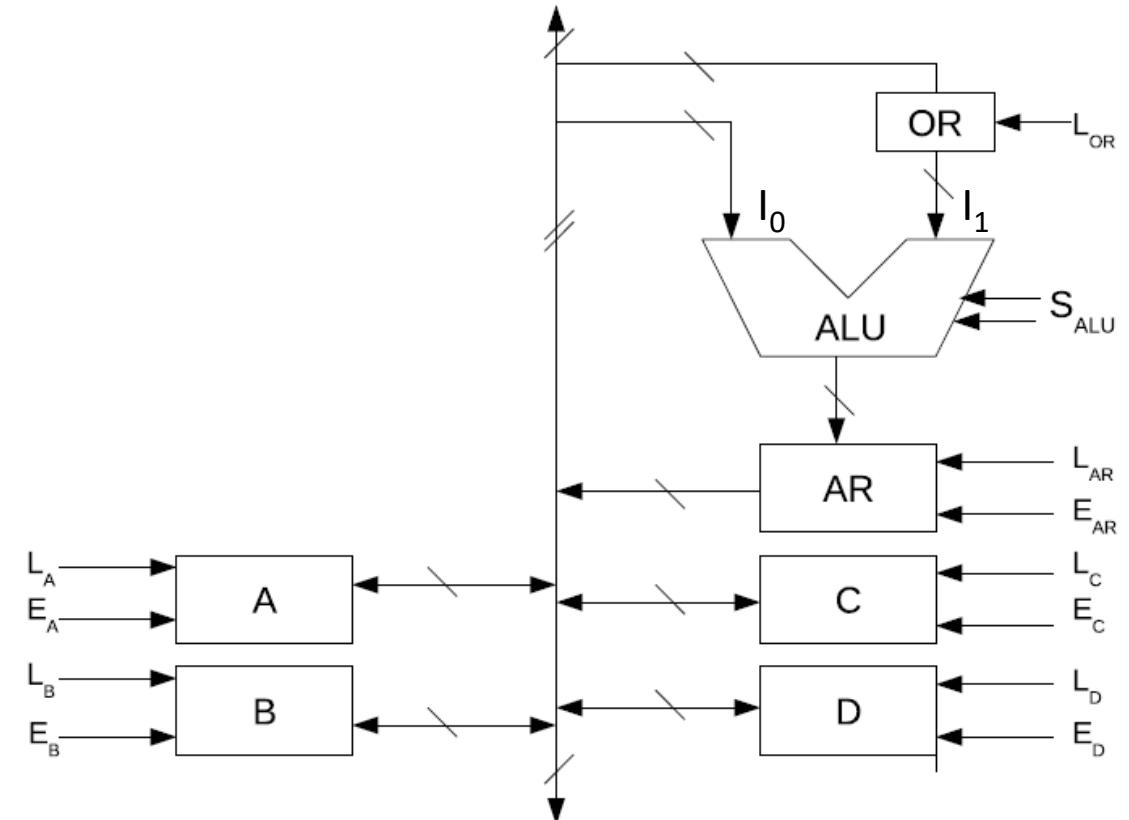


ALU on a bus

- It is clear that we can make the hardware perform several steps by carefully selecting the control signals to different units that are active in each clock cycle
- We can also get larger “operations” implemented using multiclock sequences of such combinations
- Each such clock cycle is typically referred to as a microcycle, which is the basic time unit in which something happens within the processor

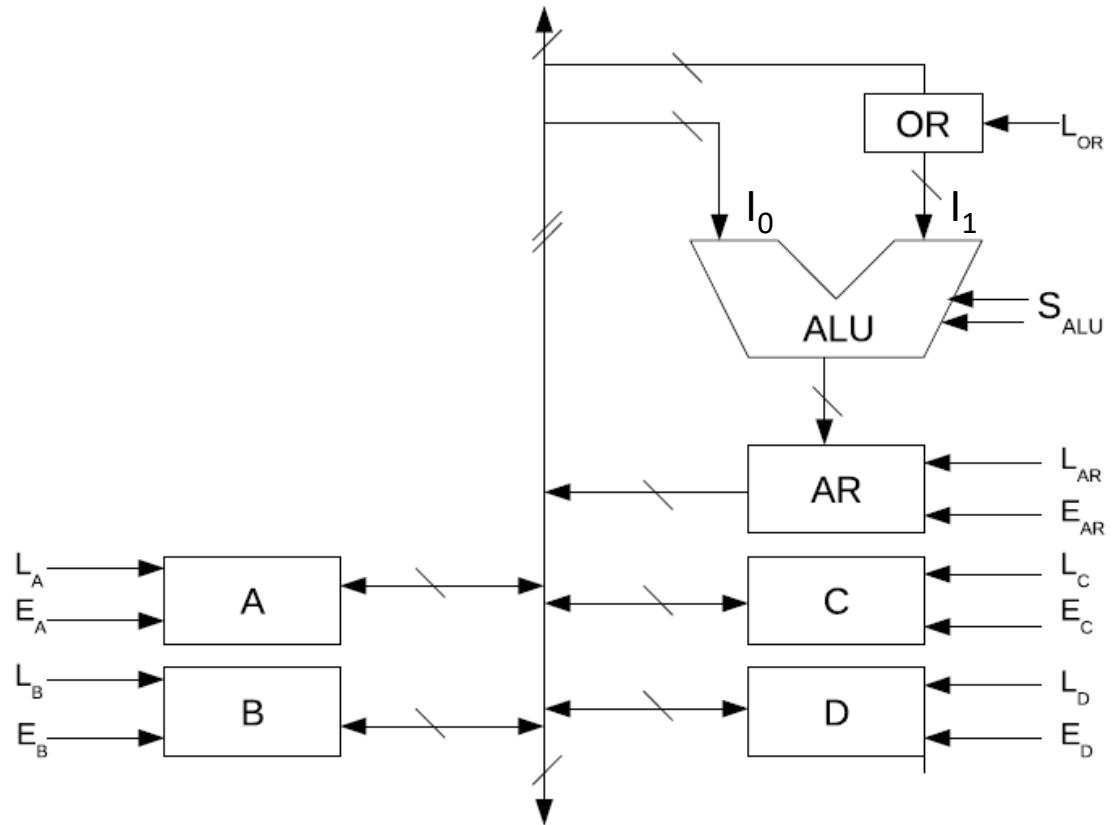

Enhanced singlebus architecture

- We can consolidate the registers into a register array or a register file
- These are numbered R_0 through R_{11}
- The register file has a single enable input E_{RG} and a single load L_{RG} and 4 select lines S_{RG}
- The select lines identify which register of the file is being operated on, with enable or load controlling the action performed on it
- The new design of the register array needs only 6 control signals – 4 for select and 2 for enable/load – as opposed to 22 that would be needed were each register to have its individual enable and load signals
- Some generality is, however, lost as only one register can be selected for writing

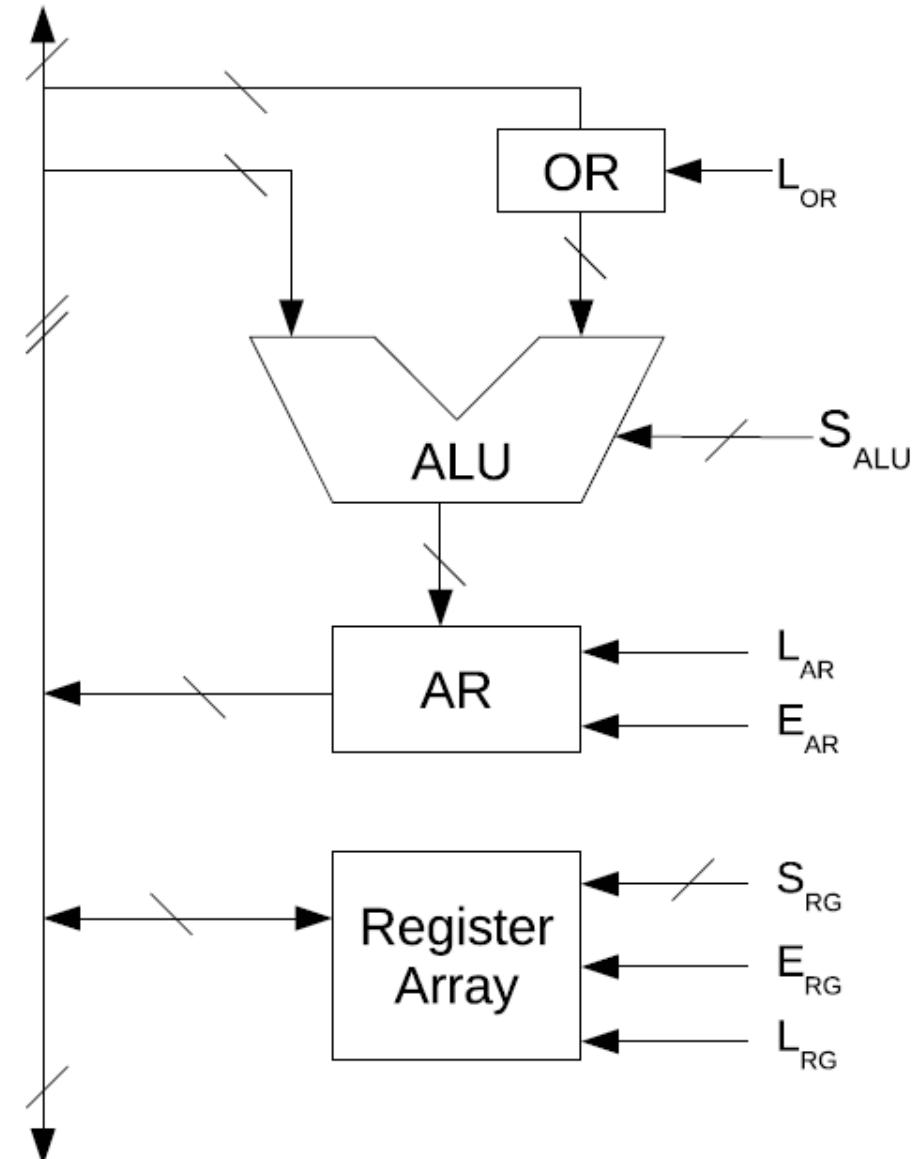


Lecture 27 – Processor design: The Age of ALU

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST


Enhanced singlebus architecture

- We also decide to make the registers also simpler devices as they need to do only parallel load and read
- Reset, increment, shift, etc., are not possible on them
- These registers are temporary store of information
- We also have an enhanced ALU in place, with 3 select lines and supporting 8 operations: zero, add, subtract, logical AND, OR, XOR, and pass left. The ALU takes the left operand from the bus and the right one from OR

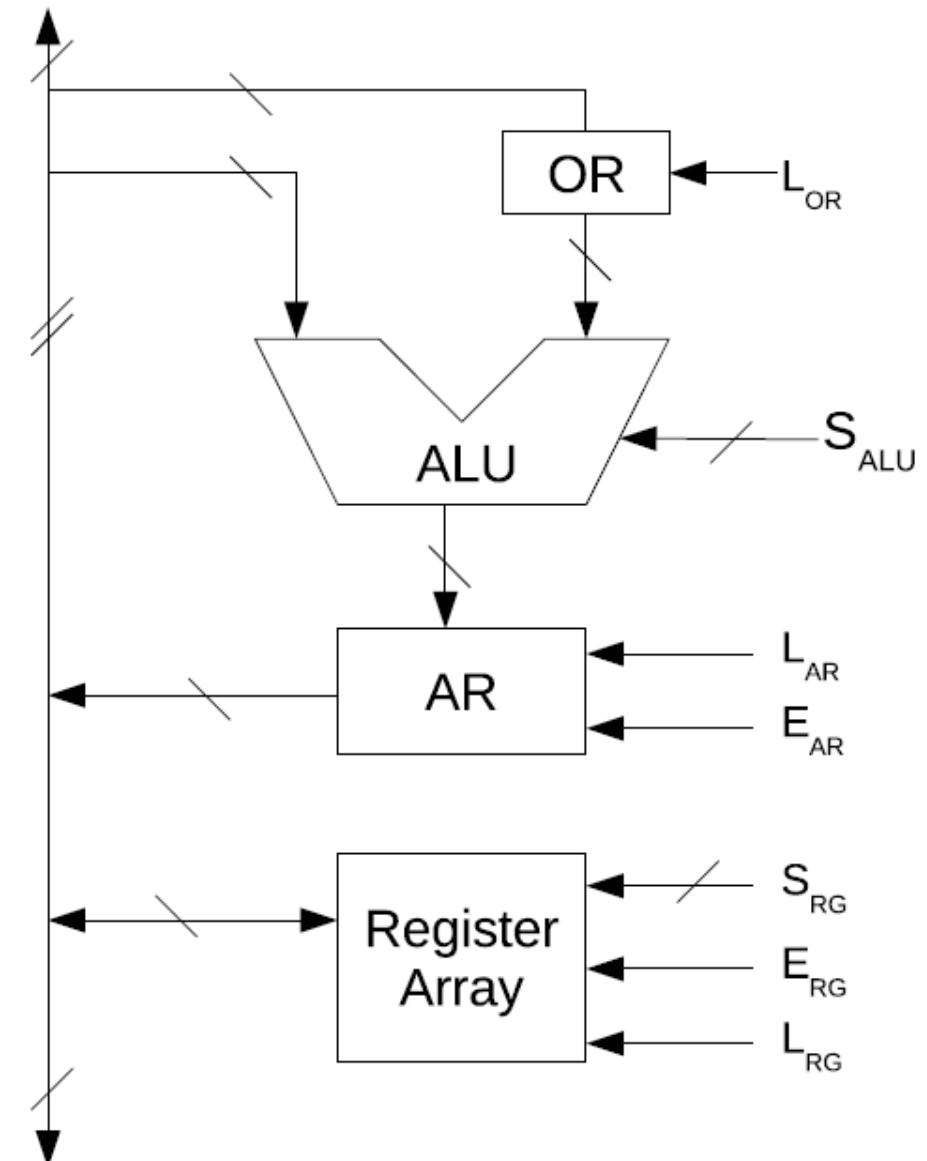


Enhanced singlebus architecture

- ADD R1: ($AR = AR + R1$)
 - Ck 0: $E_{RG}, L_{OR}, S_{RG} \leftarrow 1$
 - Ck 1: $E_{AR}, L_{AR}, SALU \leftarrow ADD$
- SUB R7: ($AR = AR - R7$)
 - Ck 0: $E_{RG}, L_{OR}, S_{RG} \leftarrow 7$
 - Ck 1: $E_{AR}, L_{AR}, SALU \leftarrow SUB$
- XOR R11: ($AR = AR \text{ XOR } R11$)
 - Ck 0: $E_{RG}, L_{OR}, S_{RG} \leftarrow 11$
 - Ck 1: $E_{AR}, L_{AR}, SALU \leftarrow XOR$
- OR R0: ($AR = AR \text{ OR } R0$)
 - Ck 0: $E_{RG}, L_{OR}, SRG \leftarrow 0$
 - Ck 1: $E_{AR}, L_{AR}, SALU \leftarrow OR$

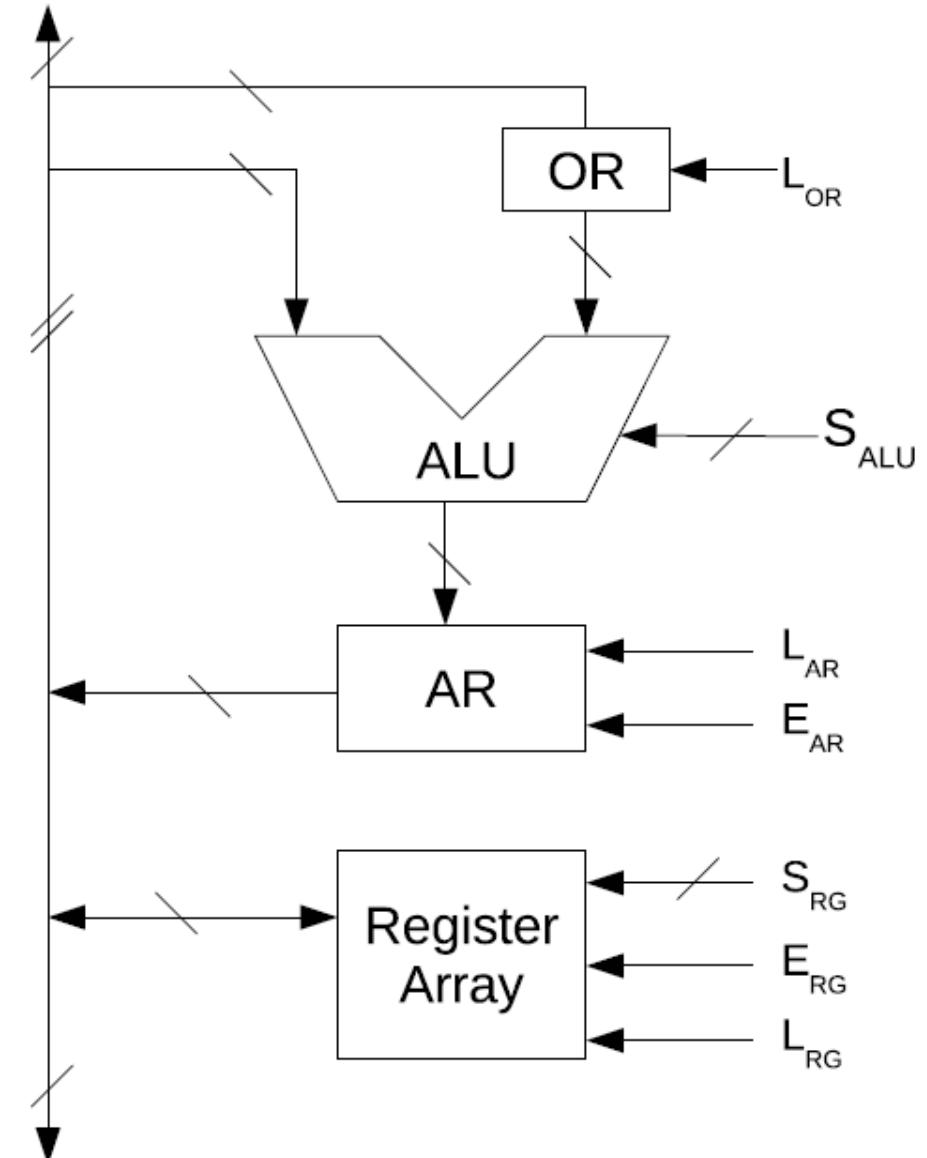


Enhanced singlebus architecture

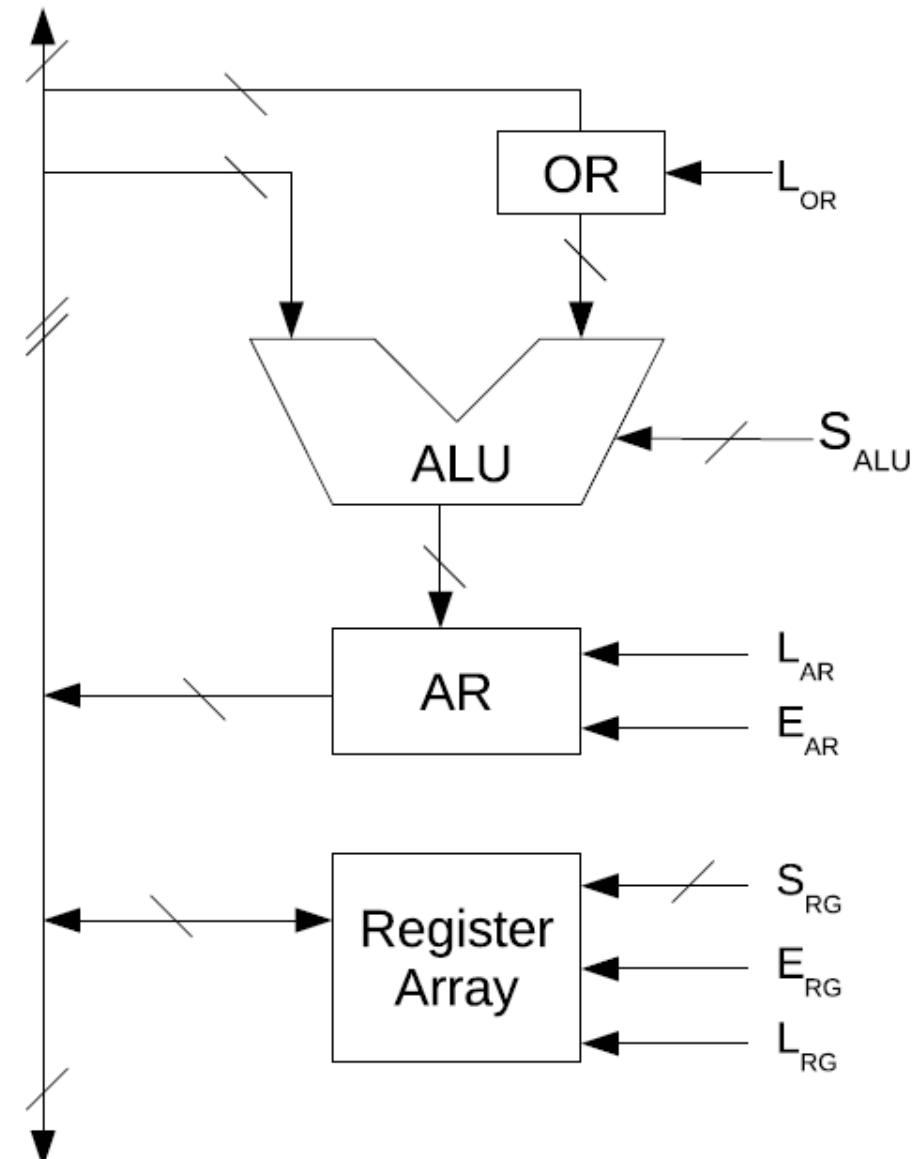- We also need a way to load values from register to AR and to save results from AR to a different register
- We call these load and store respectively
- MOVS R4 and MOVD R9 can be implemented as follows:
- MOVS R4:
 - Ck0: $E_{RG}, L_{AR}, S_{RG} \leftarrow 4, SALU \leftarrow PASS0$
- MOVD R9:
 - Ck0: $E_{AR}, L_{RG}, S_{RG} \leftarrow 9$




Instructions

- A digital processor can handle only binary strings at the very lowest level
- Thus, all instructions to be carried out by a digital processor needs to be coded or represented as binary strings
- Different basic instructions have to be coded as unambiguous binary strings
- The hardware is capable of looking at a string, decoding it, and carrying out the corresponding instruction
- A sequence of such strings forms a program

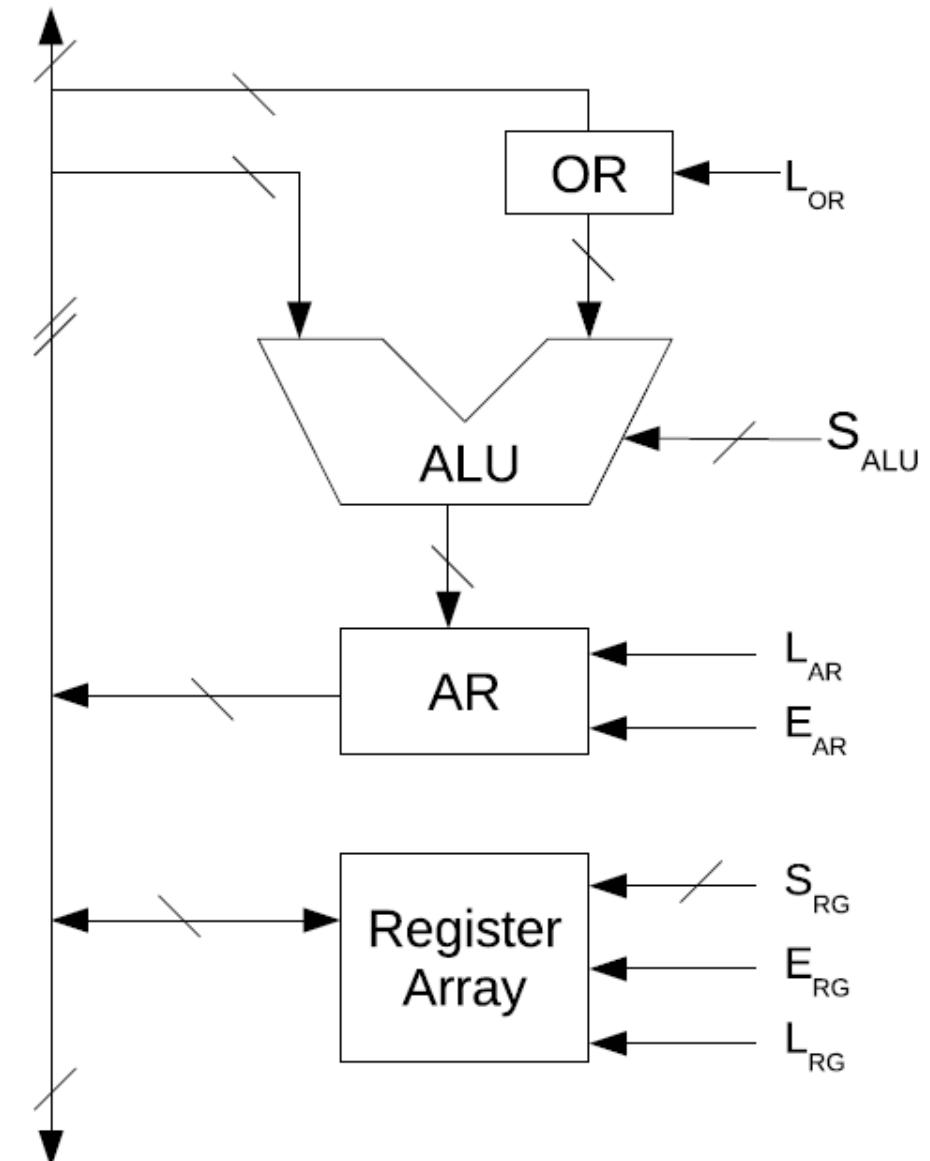


Instructions

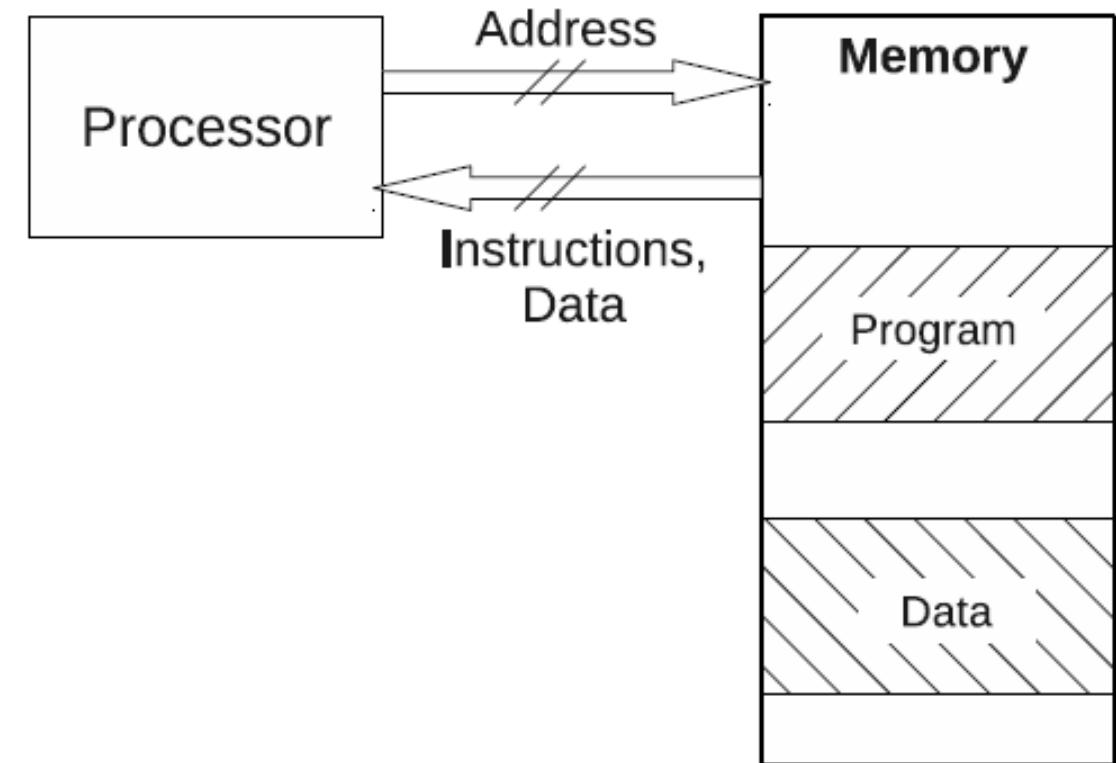- Both the data to be processed and the program are stored in the same memory
- Instructions that make up the program are stored sequentially in memory
- Each instruction is a binary string that encodes the operations to be performed without ambiguity
- The processor fetches the instructions one by one from the memory and executes it or carries out the corresponding actions



Instructions

- Meaningful work gets done as a side-effect of executing these instructions, as the instructions can read data stored in memory, perform arithmetic, logic, and other operations on the data, and store the results back into the memory
- In fact, the processor is engaged in a perpetual loop of fetch and execute, with the “real work” done as the side effect of executing the instructions
- Special instructions can also control the input and output from the processor, but we will not consider those for the simple processor

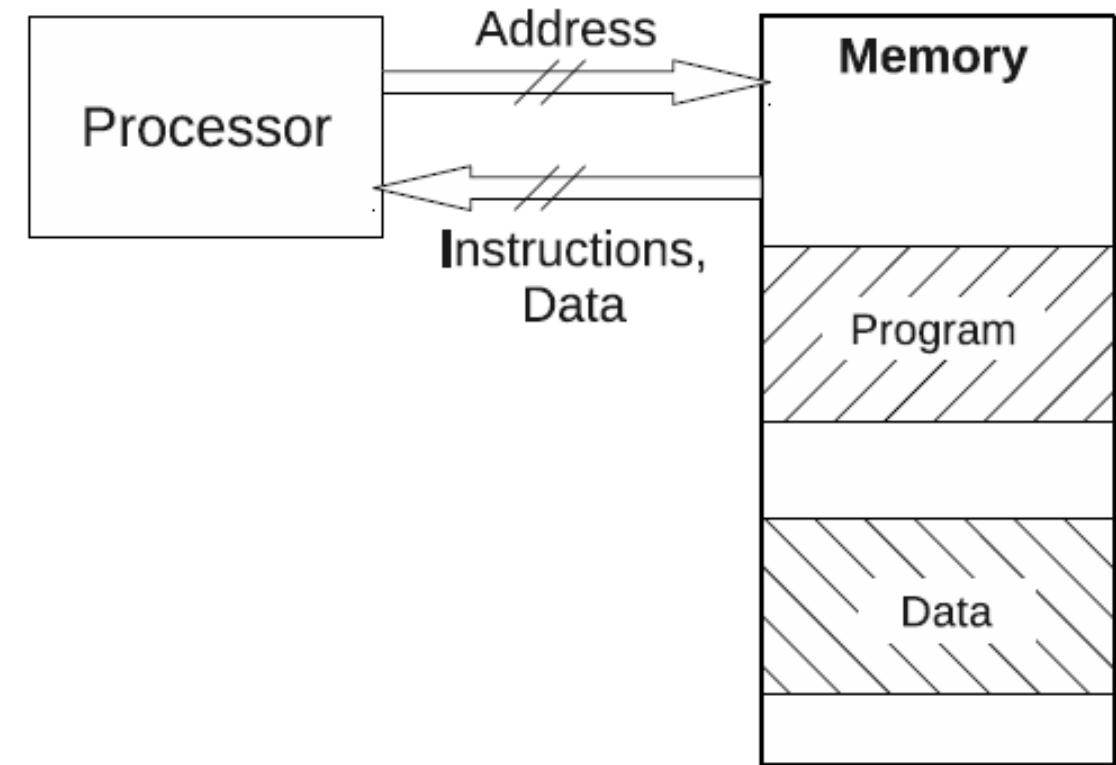


Lecture 28 – Processor design: Homecoming

Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST


Machine language

- The binary coded instructions are referred to as machine instructions, following the machine language
- This is really no “language” but an encoding scheme that makes unique decoding of the instructions possible
- Encoded instructions are called machine code or opcode for operation code
- These are understood by the processor naturally
- Importantly, that is the only “language” understood by the processor as it cannot understand high level language (like C++/Python)

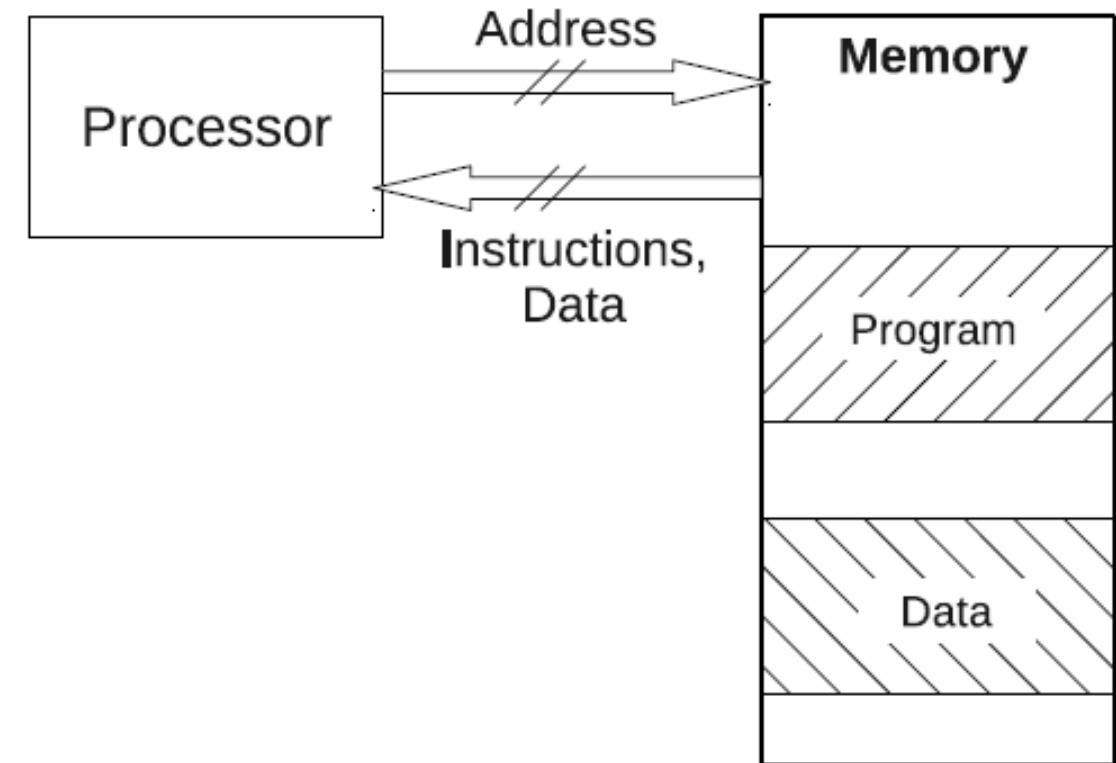

Assembly language

- Machine instructions are meant only for the processor; they require tremendous effort to interpret by us
- A mapping of the machine instructions for easier grasp by humans is used widely by processors
- This representation is essentially a one-to-one mapping from machine instructions, using mnemonics or nearly comprehensible short words and symbolic representation of internal resources like the registers
- Such a representation of the basic instructions is called the assembly language

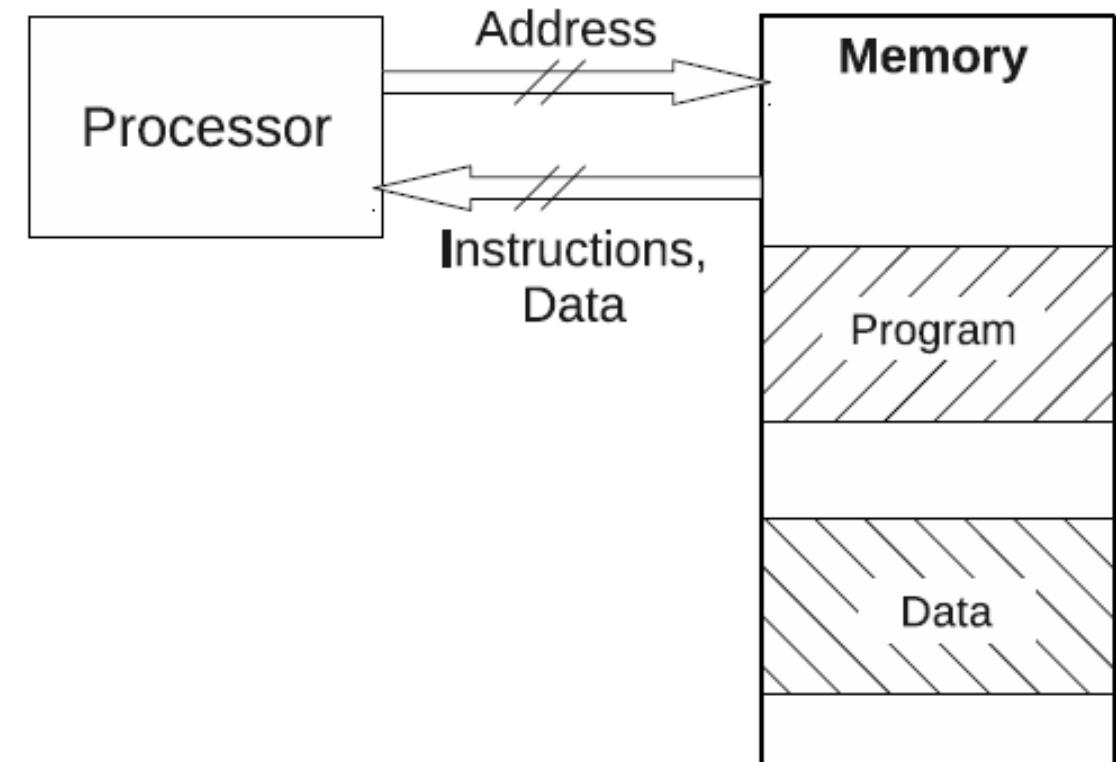

The instruction set – ALU

- Let us assume the word length of our processor is 8 bits
- Thus, all entities we will handle are 8-bits wide, which includes the coded instructions as well as data elements
- Our instruction set will have the arithmetic and logic instructions, namely, add, subtract, and, or, and xor
- We can come up with an arbitrary assembly to machine code mapping as shown in the table

Assembly Instruction	Machine Code	Action
add <R>	10-1F	$[AR] \leftarrow [AR] + [<R>]$
sub <R>	20-2F	$[AR] \leftarrow [AR] - [<R>]$
xor <R>	30-3F	$[AR] \leftarrow [AR] \oplus [<R>]$
and <R>	40-4F	$[AR] \leftarrow [AR] \wedge [<R>]$
or <R>	50-5F	$[AR] \leftarrow [AR] \vee [<R>]$
cmp <R>	60-6F	$[AR] = [<R>]$

The instruction set – ALU

- The $\langle R \rangle$ in the first column of the table is a parameter that can be replaced by one of R0 to R11, with the corresponding number appearing in the lower significant half of the machine code, given in the second column
- Thus, ADD R1 will be coded as 0x11, XOR R8 as 0x38, and OR R11 as 0x5B
- Any opcode in that range can be unambiguously understood too
- Thus, 0x27 stands for SUB R7, 0x42 for AND R2, etc.

Assembly Instruction	Machine Code	Action
add $\langle R \rangle$	10-1F	$[AR] \leftarrow [AR] + [\langle R \rangle]$
sub $\langle R \rangle$	20-2F	$[AR] \leftarrow [AR] - [\langle R \rangle]$
xor $\langle R \rangle$	30-3F	$[AR] \leftarrow [AR] \oplus [\langle R \rangle]$
and $\langle R \rangle$	40-4F	$[AR] \leftarrow [AR] \wedge [\langle R \rangle]$
or $\langle R \rangle$	50-5F	$[AR] \leftarrow [AR] \vee [\langle R \rangle]$
cmp $\langle R \rangle$	60-6F	$[AR] - [\langle R \rangle]$

The instruction set – ALU

- The last instruction performs a comparison of the register and AR without changing the value of the accumulator
- This may seem pointless as the results are not used
- However, the arithmetic and logic operations have other side-effects based (flags) on the results of the operation
- This could include overflow, carry generation, value being negative, etc. These find use in controlling loops in conjunction with conditional branching instructions we will encounter later

Assembly Instruction	Machine Code	Action
add <R>	10-1F	$[AR] \leftarrow [AR] + [<R>]$
sub <R>	20-2F	$[AR] \leftarrow [AR] - [<R>]$
xor <R>	30-3F	$[AR] \leftarrow [AR] \oplus [<R>]$
and <R>	40-4F	$[AR] \leftarrow [AR] \wedge [<R>]$
or <R>	50-5F	$[AR] \leftarrow [AR] \vee [<R>]$
cmp <R>	60-6F	$[AR] - [<R>]$

The instruction set – ALU

- We should have another variation of the above arithmetic and logic instructions in which the actual operand is specified in the instruction itself as a constant
- Such instructions are frequently needed to initialize variables to a constant, such as the loop counter to 0
- Such instructions are set to provide their arguments in the immediate mode
- Here is the problem – all our registers are 8 bits, so these constants should be 8 bits
- We assume the operand is stored in the word that immediately follows the machine code that indicates such an operation

Assembly Instruction	Machine Code	Action
adi xx	01	$[AR] \leftarrow [AR] + xx$
sbi xx	02	$[AR] \leftarrow [AR] - xx$
xri xx	03	$[AR] \leftarrow [AR] \oplus xx$
ani xx	04	$[AR] \leftarrow [AR] \wedge xx$
ori xx	05	$[AR] \leftarrow [AR] \vee xx$
cmi xx	06	$[AR] \leftarrow xx$

The instruction set – data movement

- We need instructions to move data from and to the accumulator to get our work done
- We have seen the instructions to move contents of AR from or to a register
- We also need instructions to move from AR to and from the memory, which lies outside the processor
- Registers are not sufficient to hold all our data, such as the array of marks obtained by all students
- These are kept in the memory and is brought in and out of the processor as needed
- The *movs* instruction moves a register to the accumulator and the *movd* instruction moves the accumulator to a register
- The register number involved is embedded into the opcode as a parameter as before
- An additional instruction *movi* is provided to move an immediate constant directly to a register

The instruction set – data movement

- The *load* and *stor* instructions involve a register and a memory location
- Memory resides outside of the processor
- To access the memory, one needs to give it an address to indicate which of its words is to be accessed
- The contents of the corresponding memory word will be given to the processor on a read
- The processor has to supply the contents to be written memory for a write
- The number of bits of address determines the maximum capacity of memory that can be used
- We assume that the memory address is represented using one word of 8 bits in our processor
- Thus, the maximum memory capacity is $2^8 = 256$ words in our simple processor

The instruction set – data movement

- The *load* and *stor* instructions use the contents of AR as the address
- The word read from the memory is stored into the register specified in the instruction for the *load* instruction
- The value to be written is available in such a register for the *stor* instruction

Assembly Instruction	Machine Code	Action
movs <R>	70-7F	[AR] \leftarrow [<R>]
movd <R>	80-8F	[<R>] \leftarrow [AR]
movi <R> xx	90-9F	[<R>] \leftarrow xx
stor <R>	A0-AF	[[AR]] \leftarrow [<R>]
load <R>	B0-BF	[<R>] \leftarrow [[AR]]

Lecture 28 – Processor design: Infinity War

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST

The fetch-execute cycle


- We will look at the process of instruction fetching and execution
- The processor works autonomously as a continuous fetch-and-execute engine, with no other input than an external clock
- Since instructions as in the machine code are stored in memory, they have to be brought to the processor one by one and executed
- The instruction at address $(i + 1)$ has to be fetched and executed after instruction i , since the instructions of a program are stored consecutively in the memory
- The processor has to do all these by itself

The fetch-execute cycle

- Processors have a special register inside them that manages the process of instruction fetch by keeping track of the address of the next instruction to be fetched at all times
- This register is called the program counter or the PC
- The processing of an instruction begins with fetching its opcode from the memory word whose address is in the PC
- The contents of the PC are incremented while this happens to hold the address of the next instruction in the sequential order
- The opcode is brought to the processor and appropriate action is performed in the execution phase
- Once this is completed, the next instruction is processed by fetching it from the memory using PC as the address
- This goes on for ever inside the processor until a special STOP instruction is encountered
- Executing this instruction stops all activities of the processor


The fetch-execute cycle

- So how do we start the process?
- It is clear that once one instruction is done with, the next one is taken up by incrementing the PC
- Thus, once the execution of a program starts, everything goes on as the program indicates
- So how to start a program?
- A program can be started by loading the address of its first instruction into the PC
- However, how does the very first program start when the computer's power is turned on?

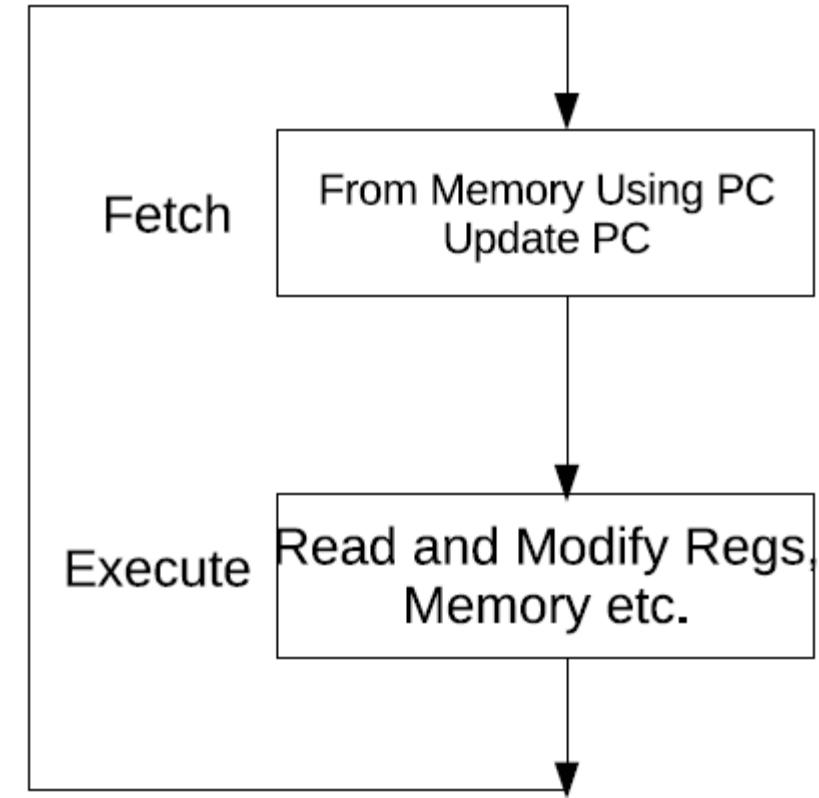


The fetch-execute cycle

- The processor hardware has a special feature to load a value of 0 to the PC when power is turned on or when the reset button of the computer is pressed (*literally “resets” the “PC”*)
- Thus, the very first program that gets control is the one that is saved at memory address 0
- Computer manufacturers place a special program at address 0 that has the BIOS program, which knows how to load the operating system from the boot record and proceed accordingly
- Any corruption in the BIOS can be very detrimental to booting the computer

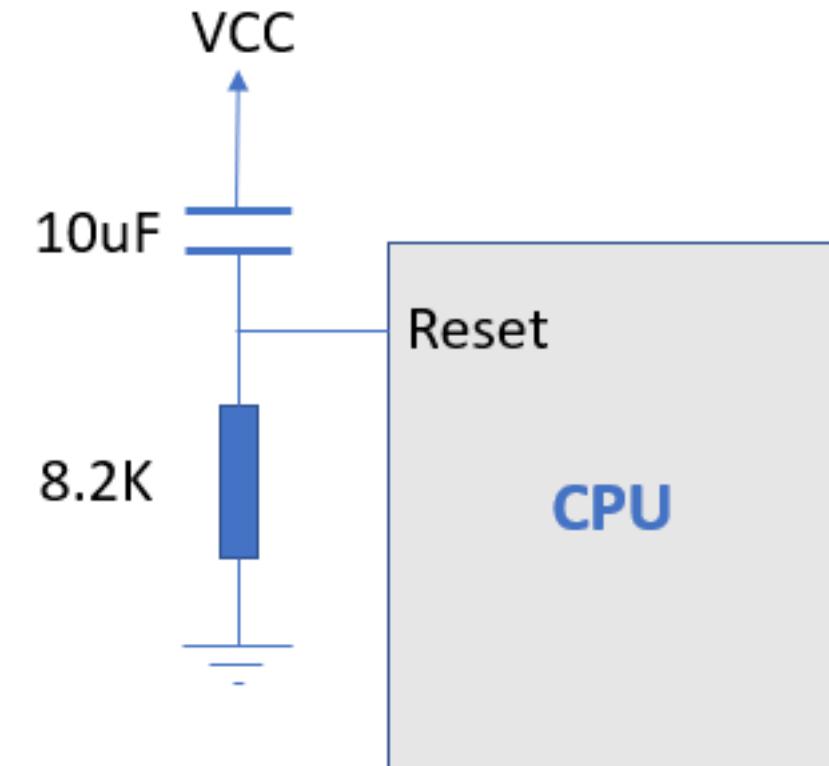


Memory access

- How does the simple processor access the memory?
- We will use a memory interface that supplies the address to the memory along with the signals to indicate if a read or a write is desired
- Data should be presented separately for writes; data supplied by the memory should be used inside the processor for reads
- We assume an external memory interface consisting of address lines, data lines, and two control lines
- The data lines are connected directly to the data lines of the bus, as if the memory is a large register array, but outside of the processor

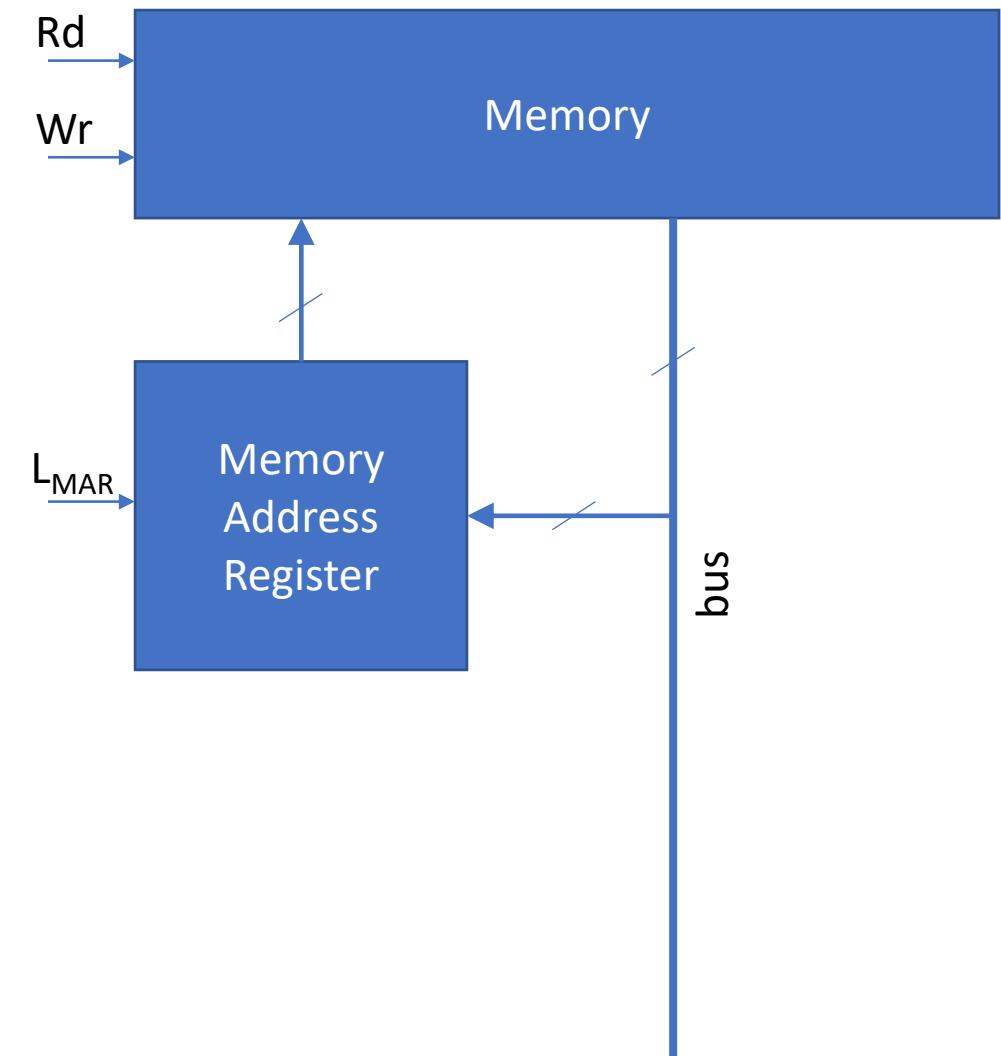


Memory access

- The address has to be supplied separately, prior to the read or write operation
- We assign a memory address register (MAR) to hold the address
- The MAR is connected to the bus like other registers and can be written to from the bus
- There is usually no need to enable the MAR to the internal bus
- It can be assumed to be enabled always to the external memory interface
- Two control lines RD and WR are sent to the memory to indicate memory read and write respectively

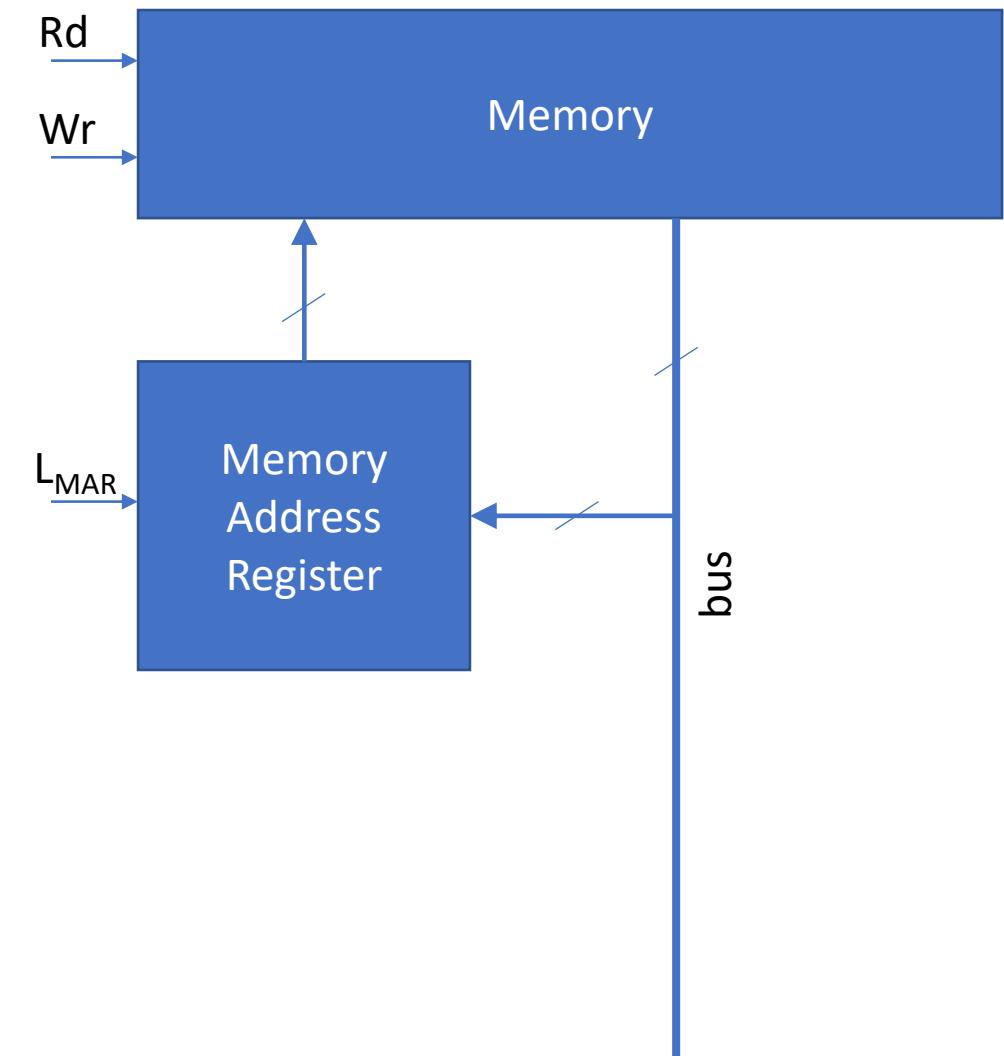

Enhanced enhanced single bus architecture

- With this information, the enhanced single bus architecture is modified to include additional components
- The memory address register to store the next memory address to be accessed
- The program counter to store the current address of the instruction being performed

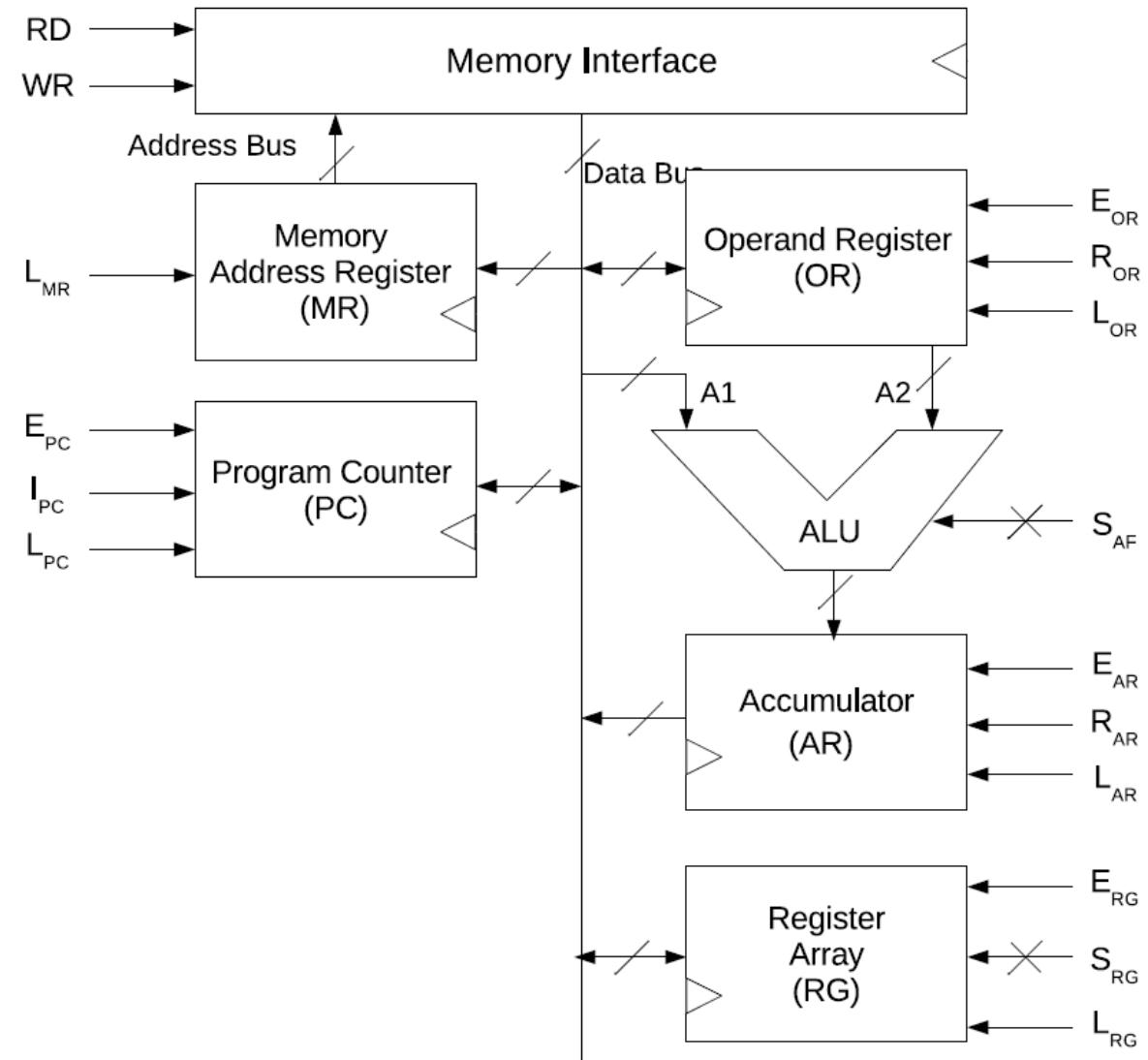

Lecture 29 – Processor design: Guardians of the Instructions


Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST

Implementing instructions – ALU


- Consider the simple instruction:
ADD <R>
- This instruction can be executed in two clock cycles:
 - We need to enable RG and load the OR with the value [<R>] using the select lines for RG
 - Enable AR, load the instruction for ADD in the ALU select lines, activate load AR

add <R>	Ck 3. E _{RG} , L _{OR} Ck 4: E _{AR} , L _{AR} , End	S _{RG} ← <R> S _{ALU} ← ADD
---------	--	---

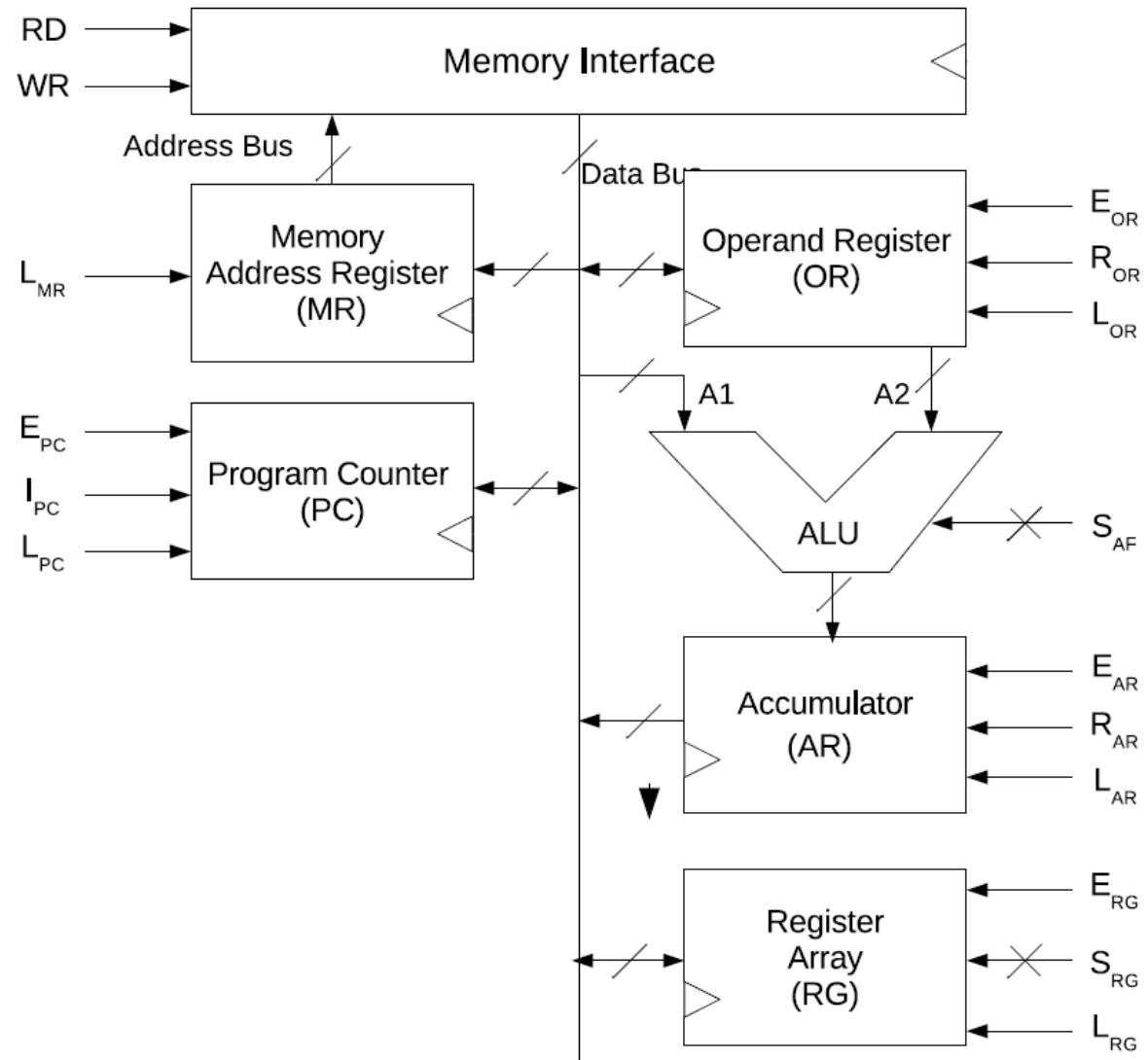


Implementing instructions – ALU

CLK
 E_{RG}, L_{OR}
 S_{RG}

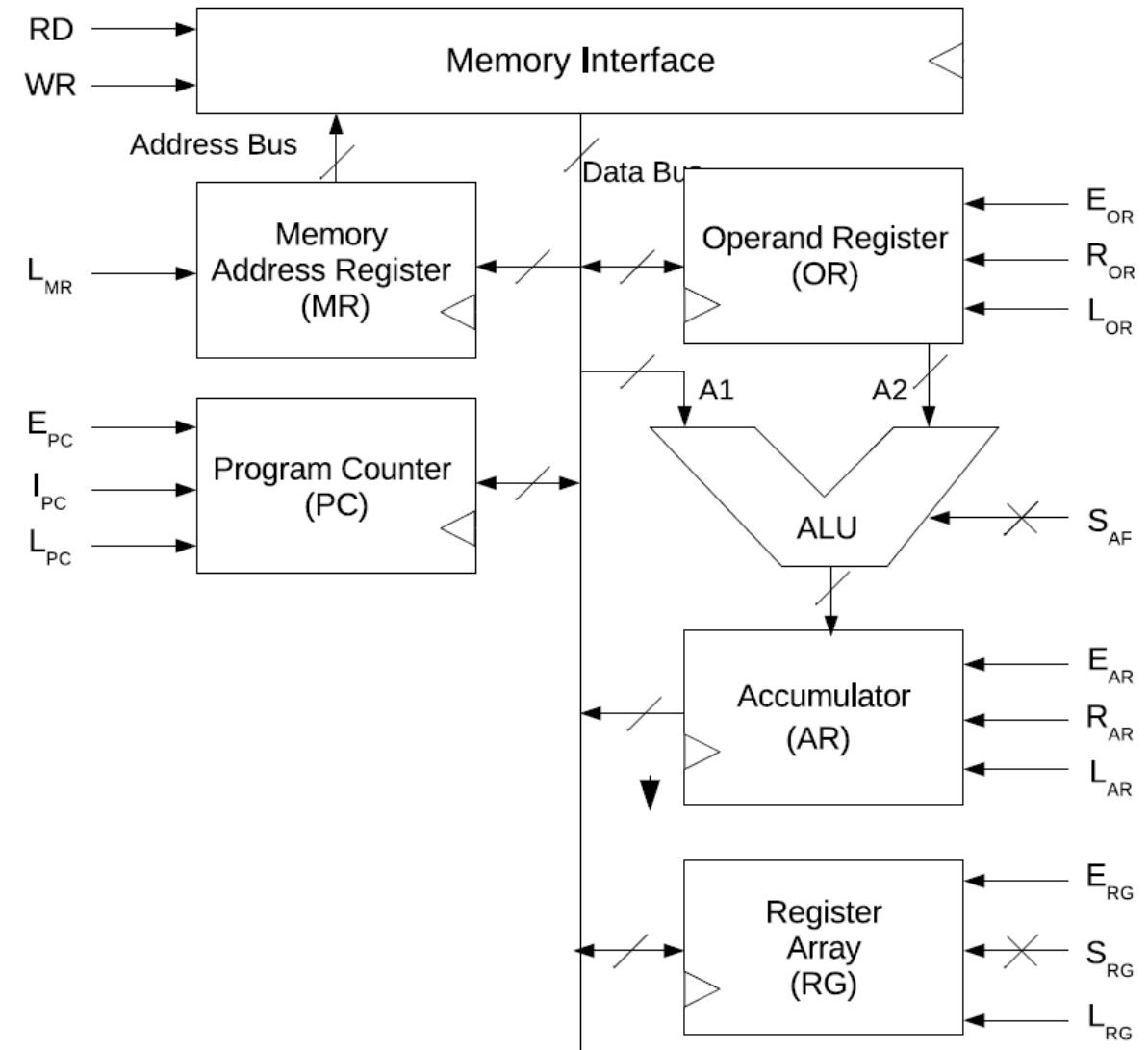

Implementing instructions – ALU

Instruction	Control Signals	Select Signals
add <R>	Ck 3: E _{RG} , L _{OR} Ck 4: E _{AR} , L _{AR} , End	S _{RG} ← <R> S _{ALU} ← ADD
sub <R>	Ck 3: E _{RG} , L _{OR} Ck 4: E _{AR} , L _{AR} , End	S _{RG} ← <R> S _{ALU} ← SUB
xor <R>	Ck 3: E _{RG} , L _{OR} Ck 4: E _{AR} , L _{AR} , End	S _{RG} ← <R> S _{ALU} ← XOR
and <R>	Ck 3: E _{RG} , L _{OR} Ck 4: E _{AR} , L _{AR} , End	S _{RG} ← <R> S _{ALU} ← AND
or <R>	Ck 3: E _{RG} , L _{OR} Ck 4: E _{AR} , L _{AR} , End	S _{RG} ← <R> S _{ALU} ← OR
cmp <R>	Ck 3: E _{RG} , L _{OR} Ck 4: E _{AR} , End	S _{RG} ← <R> S _{ALU} ← CMP
nop	Ck 3: End	-

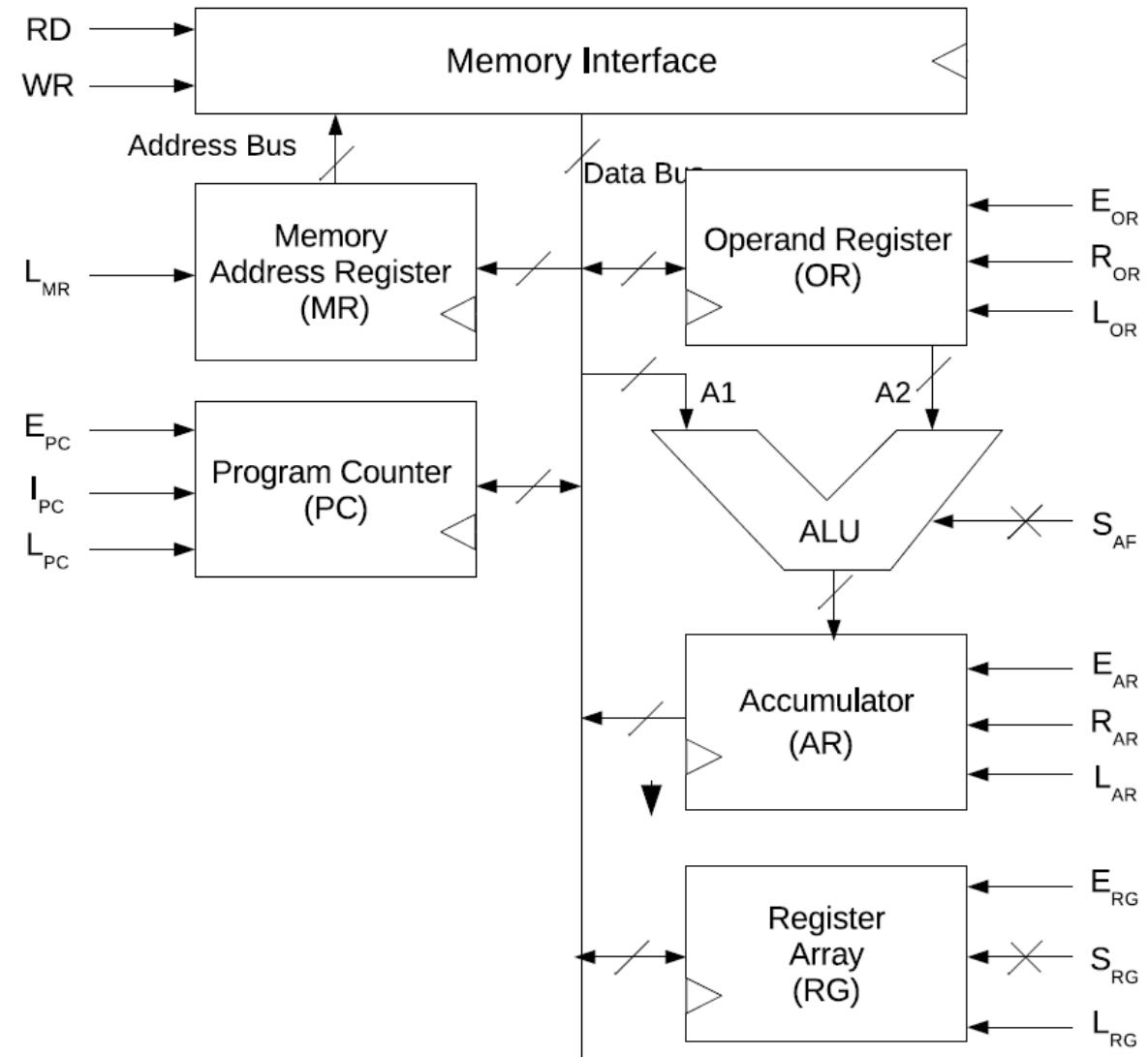


Implementing instructions

- A clock cycle in which one basic operation is performed is called a microcycle
- The combination of control signals that are active (or at level 1) in a microcycle determines what operation is performed in that cycle
- The operation performed in a microcycle is often referred to as a *microinstruction*
- The execution of each machine instruction (such as ADD <R>) needs one or more microcycles
- Faster instructions take fewer microcycles and vice versa
- The number of microcycles needed for different machine instructions depends on the processor architecture – some processors are “hardwired” to perform certain instructions very rapidly


Implementing instructions – data movement

- Moving from AR to a register is achieved using the *movd* instruction
- It is quite straightforward to implement, enable AR and load RG, and needs only one cycle to execute
- To load form register to ALU: we load the register value to the bus by setting S_{RG} and choosing the pass option of the ALU
- The register contents are available at the input of AR in the same clock cycle
- If L_{AR} is also active in that clock, the data will go from the register to ALU input through the bus, pass through the ALU to AR and be stored into it all in *one clock cycle!*

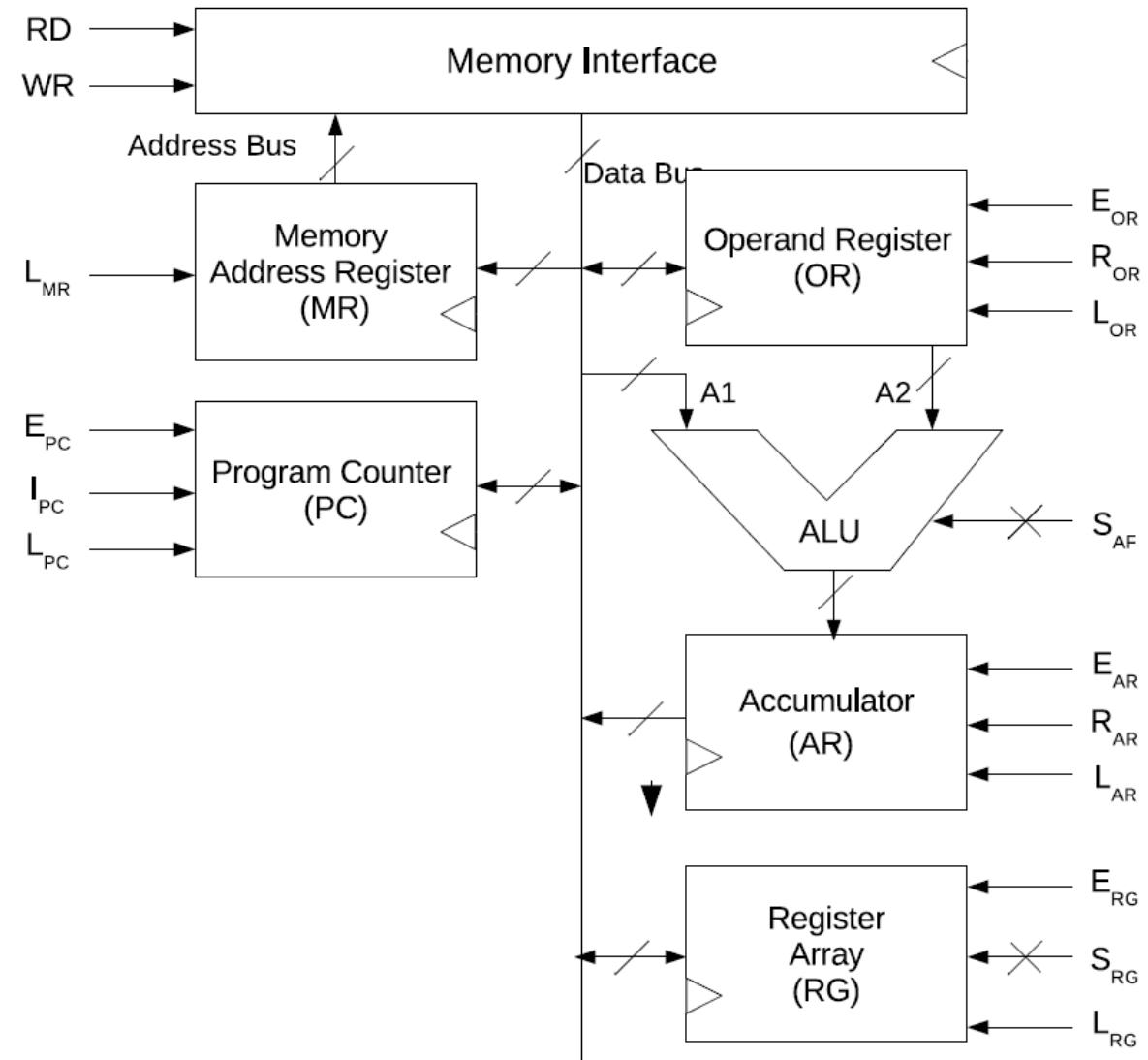


Implementing instructions – data movement

- Now, we look at the two data movement instructions, namely, *load* and *stor*
- The load instruction reads a value from the memory to a register
- The address of the memory location is given in AR
- The memory sits outside of the processor and is accessed by giving it an address through the MAR register and a command through the RD and WR lines, as is appropriate
- The first microcycle of execution moves the address from AR to MAR for both instructions
- This is done using the E_{AR} and L_{MR} signals

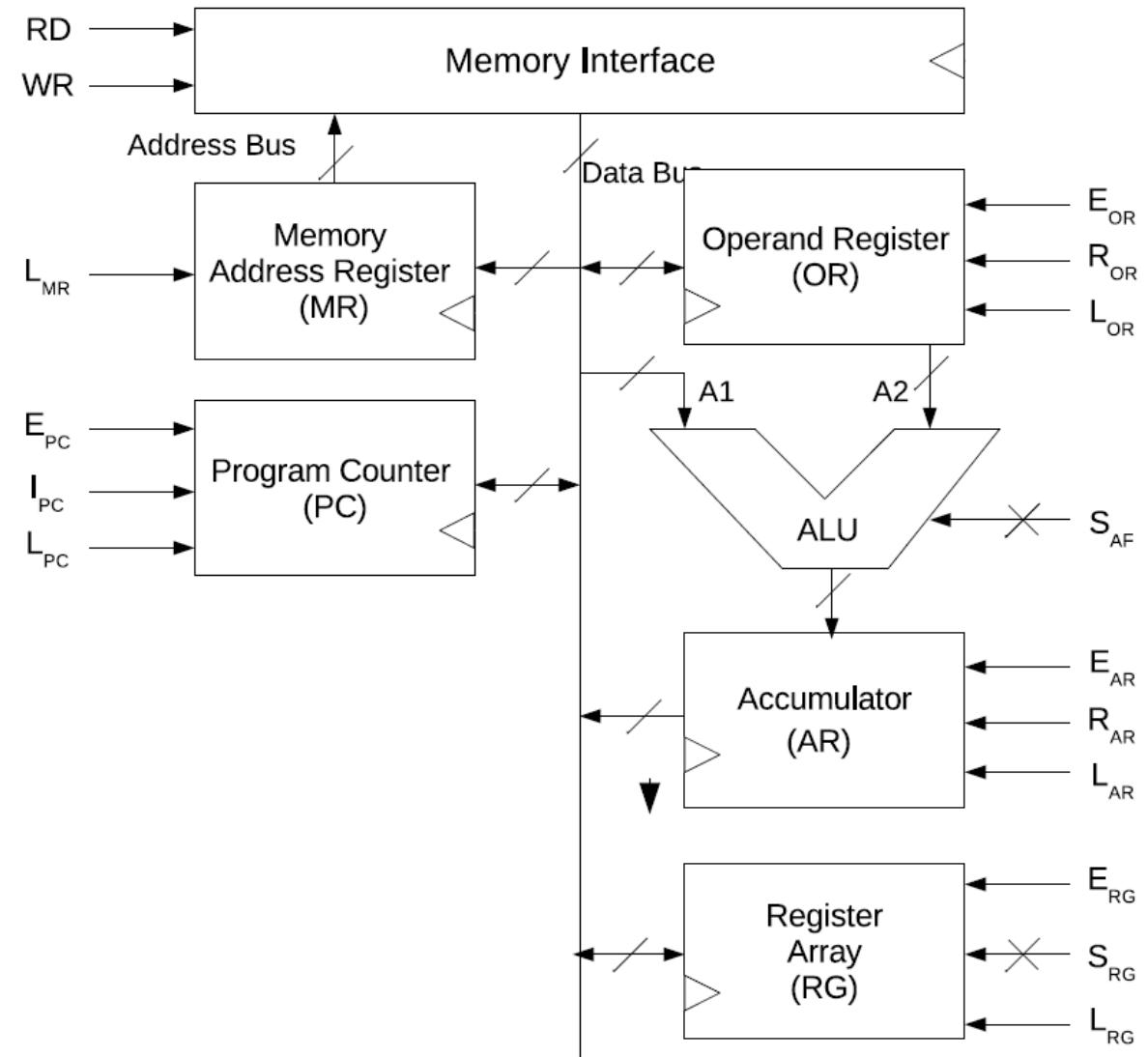


Implementing instructions – data movement

- In case of *load*, the next microcycle asks the memory to read the location using RD and L_{RG} is activated
- In case of *stor*, the next microcycle activates WR and E_{RG}
- In case of *load*, we assume the value will be available on the data bus before the end of the clock cycle
- Thus, the memory is treated like an external register file, whose address (or select) is given through MAR
- However, in practice, the memory is significantly slower than the registers and the read cannot complete in the same clock cycle
- We will ignore that aspect as we are designing a very simple processor
- Thus, the data movement instructions only take 2 clock cycles for their execution on our architecture

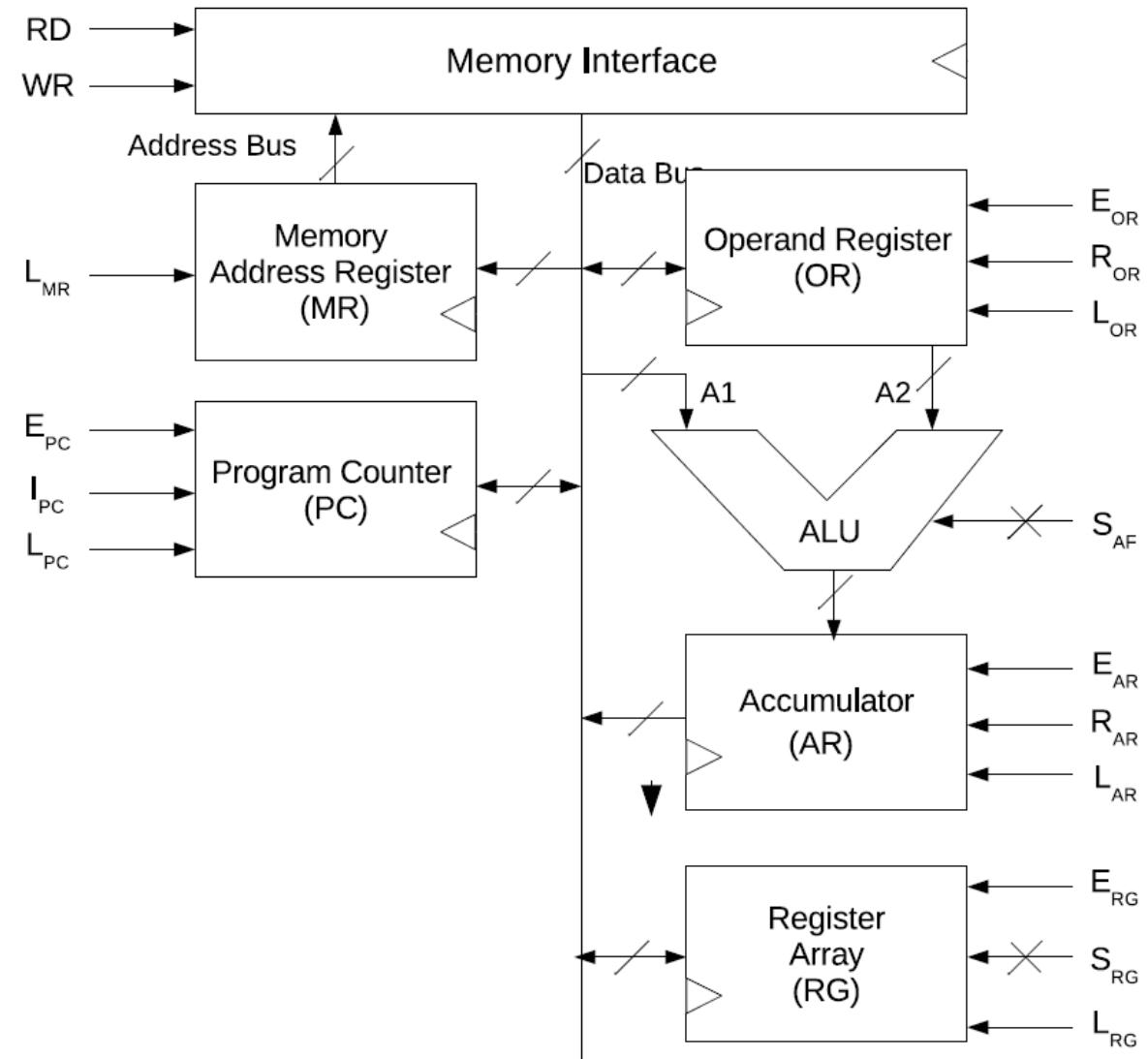


Implementing instructions – data movement

- The third data movement operation uses an immediate argument
- This is very similar to *load* except for the specification of the source memory address
- The source value is stored immediately along with the instruction
- As we have seen before, the immediate argument xx is stored in a memory location with address $(addr + 1)$ if the opcode for *movi* is stored in a memory location with address $addr$
- Moreover, we assume that as the opcode for *movi* is fetched from $addr$, the PC value is incremented by 1 to point to the next instruction

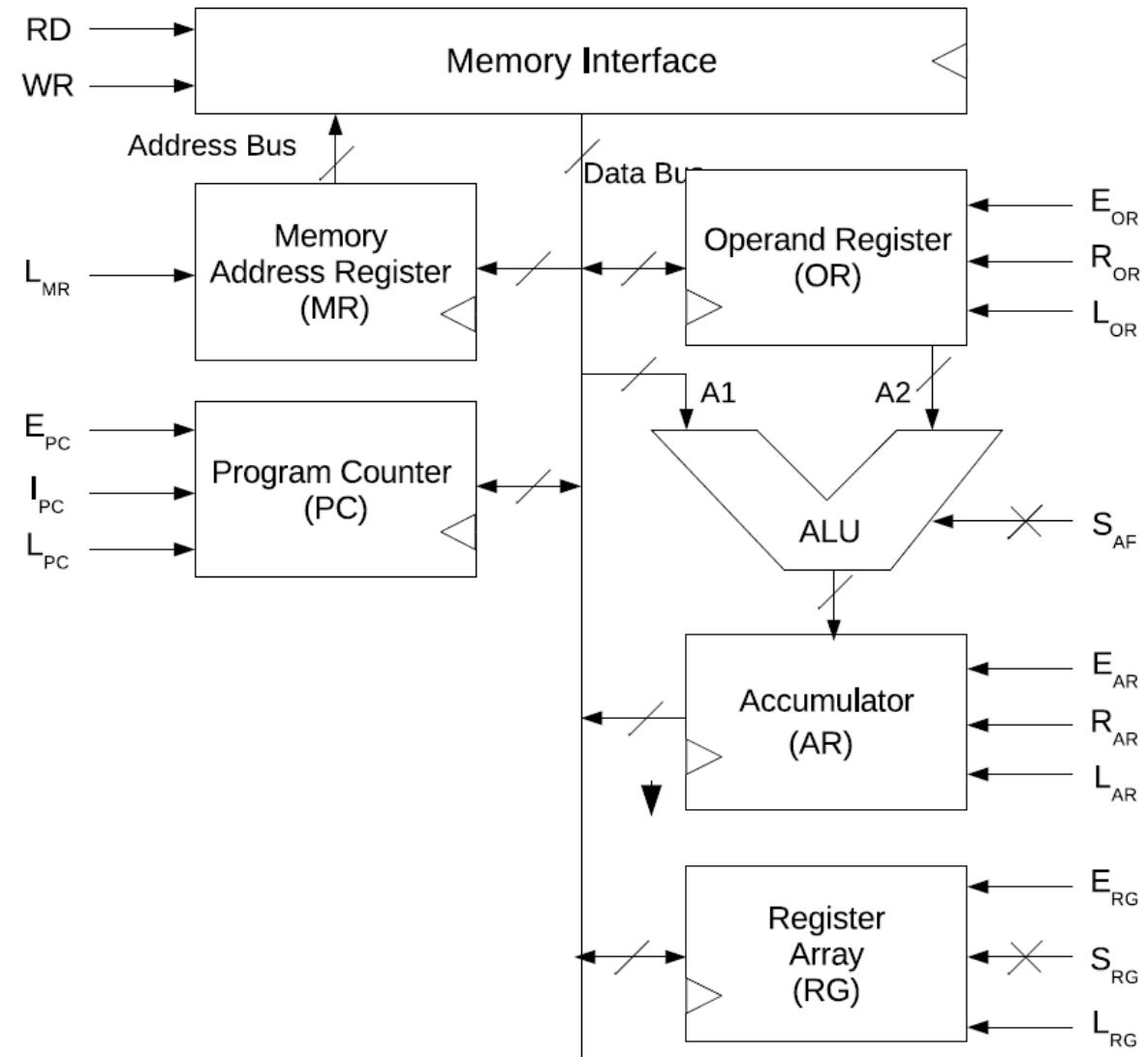

Implementing instructions – data movement

- Thus, when the execution of *movi* starts, the PC is pointing to the word following the opcode
- This word holds the immediate operand xx
- Thus, the situation is similar to *load*, except for the PC supplying the address of the operand instead of AR
- Thus, the execution of *movi* proceeds very similarly: E_{PC} , L_{MR}
- However, the PC needs to point to the next real opcode at the end of executing *movi*
- We achieve this by incrementing PC while it is loaded onto MAR, by enabling the I_{PC} control signal
- Thus, the microcycle activates: E_{PC} , L_{MR} , I_{PC}
- Then the memory can be read as before

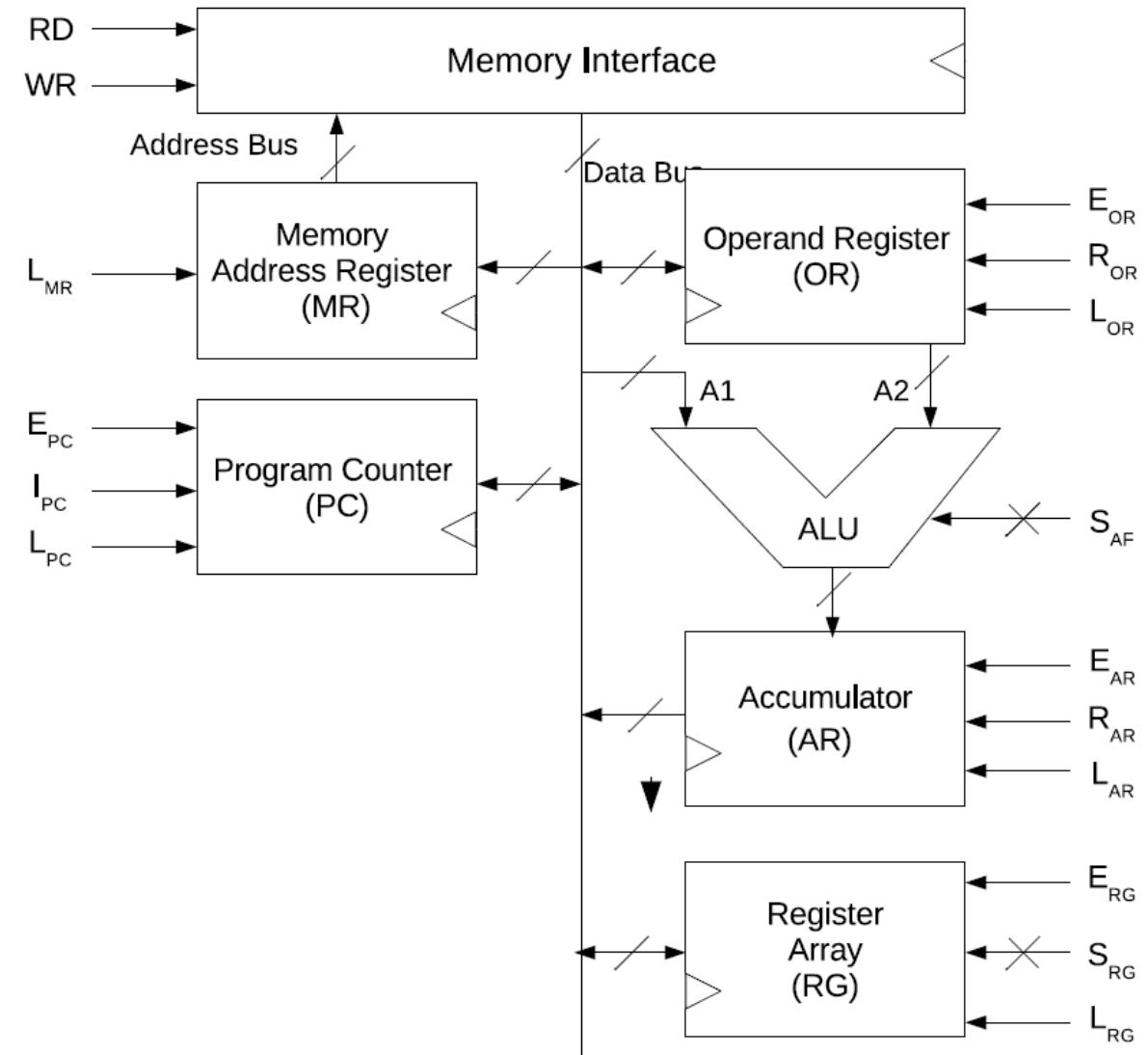


Lecture 29 – Processor design: Guardians of the Instructions

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST


Implementing instructions – ALU immediate

- The only difference between an instruction that uses a register argument and one that uses an immediate argument is the source of the argument
- Earlier, we loaded the source from the selected register in one clock to OR through the bus
- In immediate case, we have to get it from the memory, and we know that the PC holds the operand's address when execution starts
- All arithmetic and logic instructions can be implemented keeping this in mind
- Note that these instructions require 3 clock cycles each for their execution

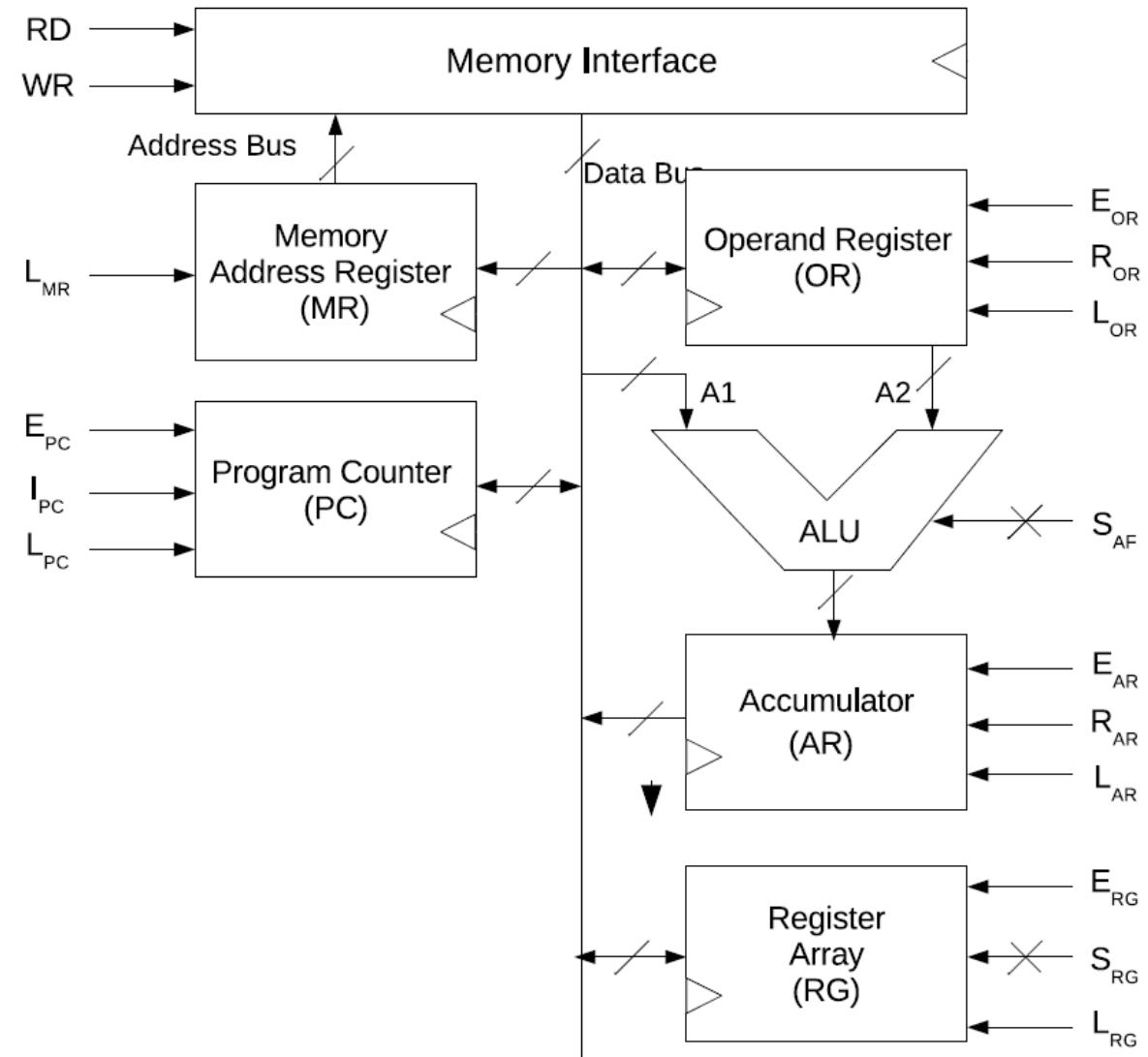

Implementing instructions

Instruction	Control Signals	Select Signals
movs <R>	Ck 3: E _{RG} , L _{AR} , End	S _{RG} ← <R>, S _{ALU} ← PASS0
movd <R>	Ck 3: E _{AR} , L _{RG} , End	S _{RG} ← <R>
load <R>	Ck 3: E _{AR} , L _{MR} Ck 4: RD, L _{RG} , End	- S _{RG} ← <R>
stor <R>	Ck 3: E _{AR} , L _{MR} Ck 4: E _{RG} , WR, End	- S _{RG} ← <R>
movi <R> xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{RG} , End	- S _{RG} ← <R>
adi xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{OR} Ck 5: E _{AR} , L _{AR} , End	- - S _{ALU} ← ADD
sbi xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{OR} Ck 5: E _{AR} , L _{AR} , End	- - S _{ALU} ← SUB
xri xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{OR} Ck 5: E _{AR} , L _{AR} , End	- - S _{ALU} ← XOR
ani xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{OR} Ck 5: E _{AR} , L _{AR} , End	- - S _{ALU} ← AND
ori xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{OR} Ck 5: E _{AR} , L _{AR} , End	- - S _{ALU} ← OR
cni xx	Ck 3: E _{PC} , L _{MR} , I _{PC} Ck 4: RD, L _{OR} Ck 5: E _{AR} , End	- - S _{ALU} ← CMP

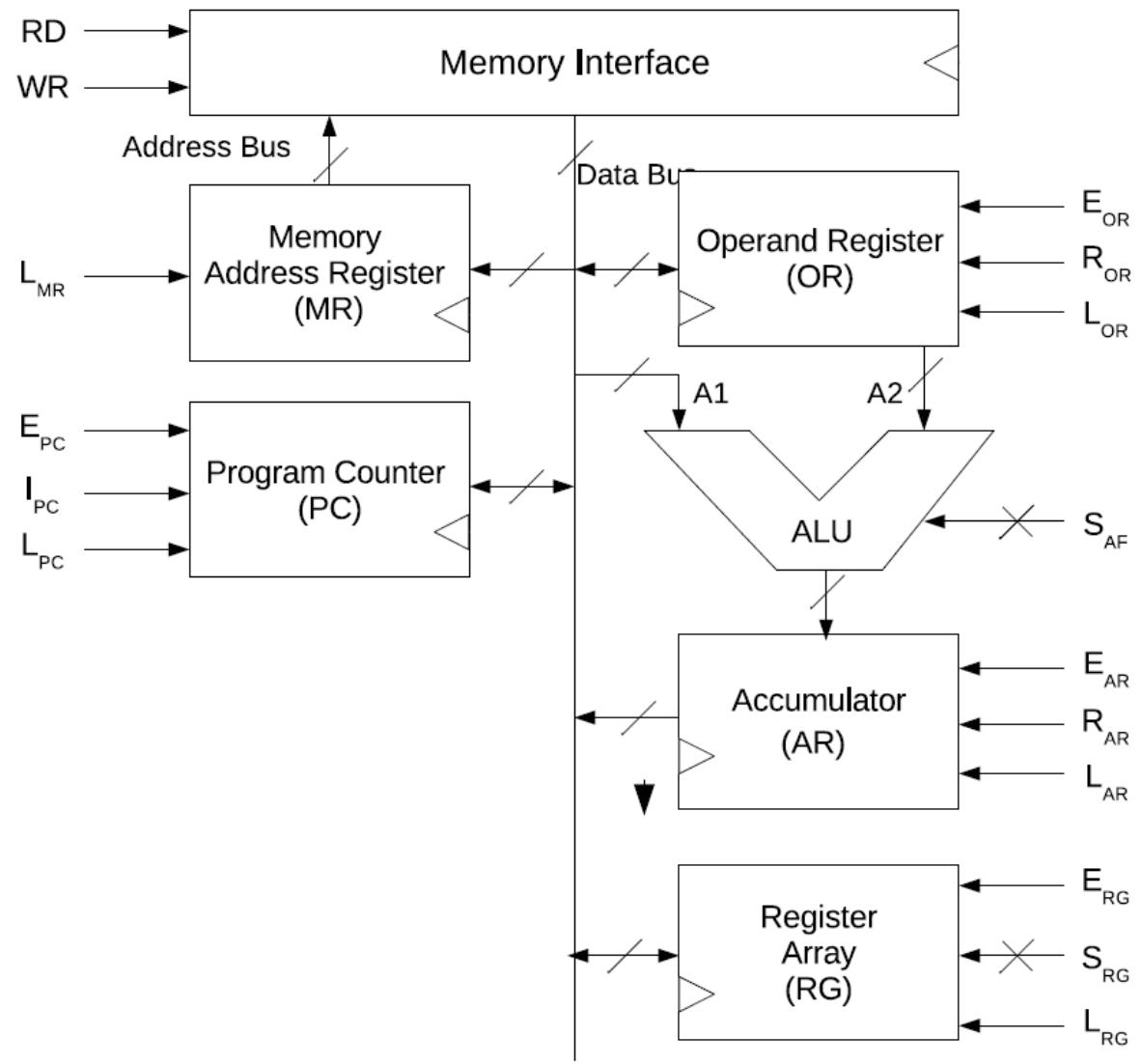

Lecture 30 – Processor design: Far from Home


Dr. Aftab M. Hussain,
Assistant Professor, PATRIoT Lab, CVEST

Jump instructions

- We will now look at the final few instructions to make our processor complete
- We had no branching instructions so far; all programs have to be a strictly linear sequence of instructions
- That is obviously not a very desirable situation
- We need the capability to branch or to break the sequential flow of instructions to implement any sort of loops (for loops, while)
- Additionally, we need the capability to branch based on some condition based on the values of registers (if-else statements etc)
- We use two forms of branching: Conditional and unconditional

Jump instructions

- Branching involves the shifting of the program execution from one point in the program to another
- This is a change in the control flow of the program and may be used to perform different actions on the basis of the results achieved so far
- Jump is a type of branching where the control is transferred absolutely, without any memory of the branching point
- Branching is natural in our every day activities

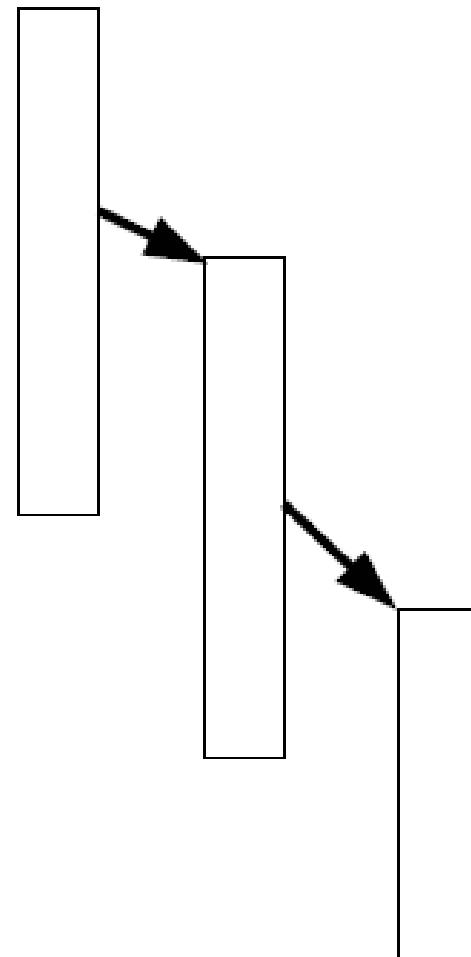

The flag register

- The branching may be conditional, based on a current state of the processor
- For this, we include a flag register in the processor to indicate particular conditions
- The condition of one of the flag register bits can be used for branching
- If the jump is conditioned on a flag bit being set, the branching happens only if that flag has a value of 1 and the program proceeds with the instruction at the branch address
- If the flag is at state 0, execution proceeds normally with the next instruction
- The flag register may include aspects like: Did the last arithmetic operation result in an overflow? Did it result in a carry from the most significant bit? Was the result of the previous operation a zero?
- These, in conjunction with branching, are essential to control the program based on the results of operations

The flag register

- For example, if we want to run a loop ten times, we can repeat the linear code 10 times, which makes the code long
- It also allows no flexibility to run the code 12 times, if we desire it
- An alternative is to use a count (typically stored in a register) that is initialized to 10
- After one set of computations is over, the count is reduced by 1
- The program can branch to the start of the computations if the count is still not zero
- It is clear that the second option results in shorter code
- Even better, if the count is initialized to 12 or 25, the code remains exactly the same

The flag register


- For our simple processor we chose the following 4 flag bits: zero, carry, sign, and parity, with respective flags Z, C, S, and P
- The zero flag is set if the previous ALU operation produced an exact 0 as the result (i.e., if AR is zero)
- Similarly, the carry flag is set if the previous operation resulted in a carry-out or borrow-in from the most significant bit
- The S bit copies the sign bit of the last arithmetic operation and becomes 1 if the result was negative
- The parity bit counts the number of 1 bits in the result of the last operation (AR)

The flag register

- Instructions that do not use the ALU – such as the data movement instructions, branching instructions, and the like – do not change the flag values
- Some processors group all flags into a special register word known as the Program Status Word (PSW)
- Special instructions may move the PSW to or from internal registers or memory
- This allows their manipulation as data

Jump instruction

- For the simple flag register defined, the $\langle FL \rangle$ flag for conditional instructions can take one of the following values: u, z, nz, c, nc, p, m, op
- These respectively stand for unconditional, zero, non-zero, carry, no-carry, positive, minus, and odd-parity
- Unconditional case is always true, irrespective of the state of the flag bits
- Zero condition is true when the Z bit is set and the non-zero condition is true otherwise
- Similarly, the carry and no-carry conditions are true when the C bit of the flags is 1 and 0 respectively
- The plus condition is true when the sign bit S is 0 and the minus condition is true otherwise
- The odd-parity condition is true if the flag bit P is 1

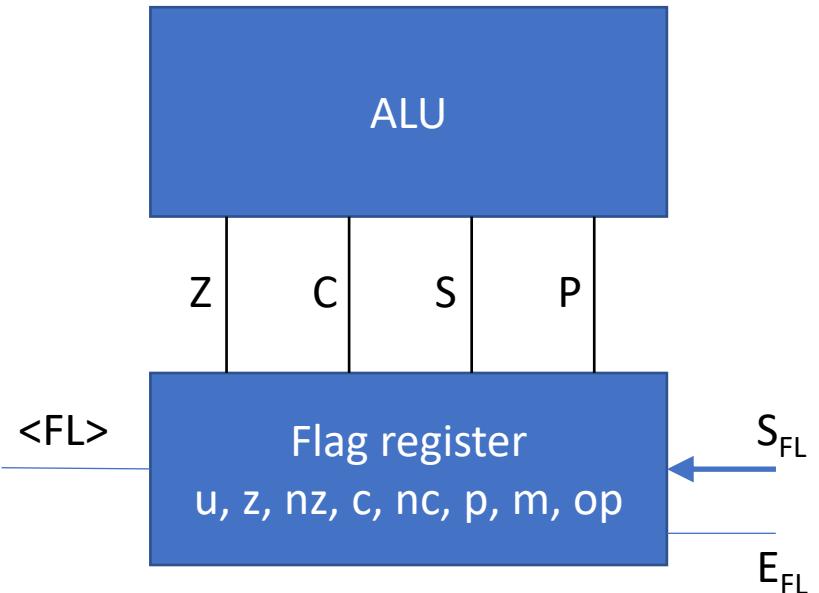

Implementing the jump instruction


- Lets define two jump instructions:

jmpd<FL> xx

- This instruction makes the program jump to address XX if <FL> is true
- 8 different cases are there


jmpr<FL>

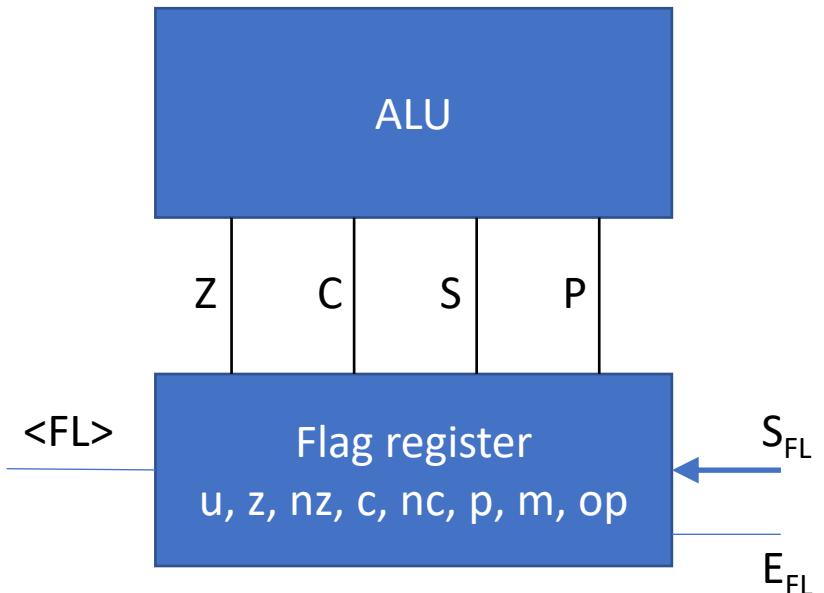- This instruction makes the program jump to address [AR] if <FL> is true
- 8 different cases are there



Implementing the jump instruction


- To implement the jump function, we need to change the PC to the contents of the AR if the flag condition is satisfied
- If not, it should have no effect
- The conditional jump instructions use a modified control signal, labelled “*End if <FL>*”
- This means that the End control signal is activated only if the selected flag is at a 0 level
- This is the case where the condition is not satisfied and hence the instruction has no impact

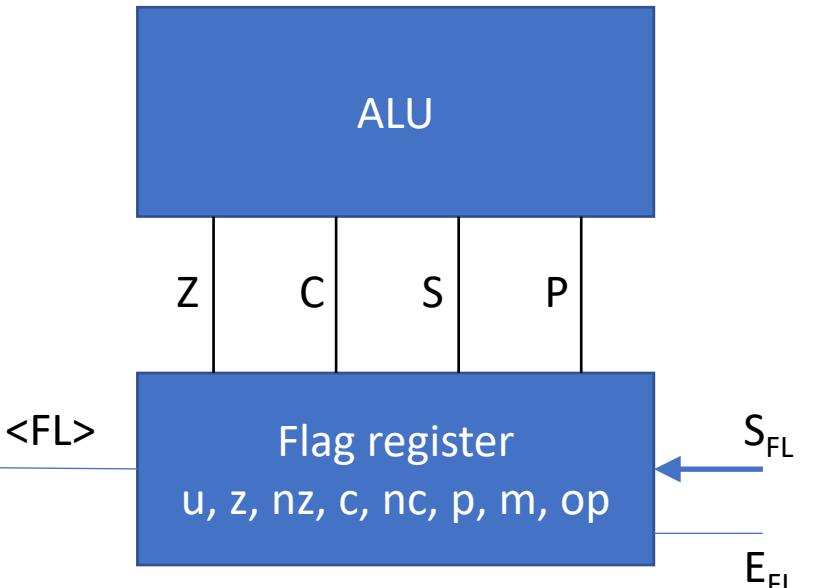

Assembly Instruction	Machine Code	Action
<code>jmpd<FL> xx</code>	E0-E7	$[PC] \leftarrow xx$ if $<FL> = 1$
<code>jmpr<FL></code>	E8-EF	$[PC] \leftarrow [AR]$ if $<FL> = 1$

Implementing the jump instruction

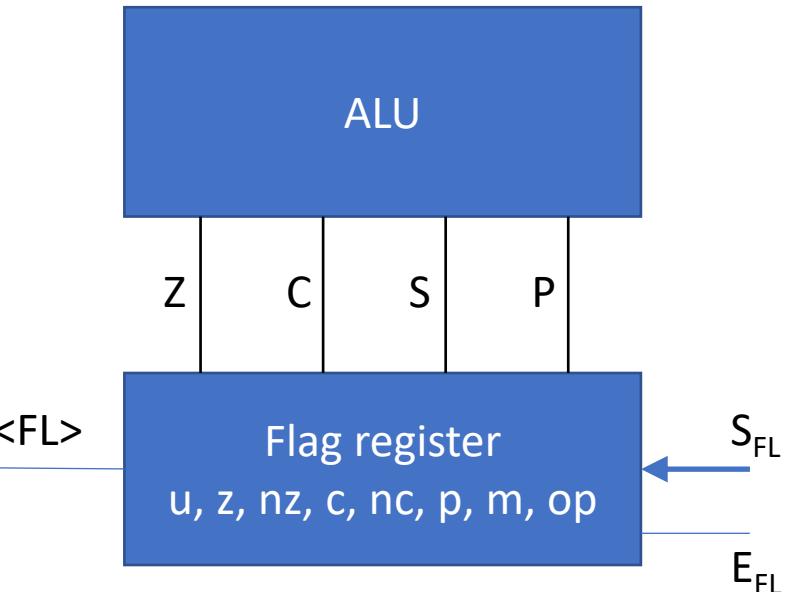- However, for instructions with immediate operands (such as `jmpd`), the next word has to be jumped over so that the PC points to the next real instruction
- At the same time, the value of PC should be incremented whether the value of flag is true or not
- Hence, the PC value is saved in MR and PC is incremented
- Then if the flag condition is satisfied, the value at the address is loaded into PC



Assembly Instruction	Machine Code	Action
<code>jmpd<FL> xx</code>	E0-E7	$[PC] \leftarrow xx$ if $<FL> = 1$
<code>jmpr<FL></code>	E8-EF	$[PC] \leftarrow [AR]$ if $<FL> = 1$

Instruction	Control Signals	Select Signals
<code>jmpd<FL> xx</code>	Ck 3: E_{PC} , L_{MR} , I_{PC} , E_{FL} , End if $<FL>$ Ck 4: RD, L_{PC} , End	$S_{FL} \leftarrow <FL>$ -
<code>jmpr<FL></code>	Ck 3: E_{FL} , End if $<FL>$ Ck 4: E_{AR} , L_{PC} , End	$S_{FL} \leftarrow <FL>$ -

Lecture 30 – Processor design: The End Game

Dr. Aftab M. Hussain,

Assistant Professor, PATRIoT Lab, CVEST


Instruction fetch

- Now let us look at instruction fetch
- We know it involves reading a word from the memory, using the PC value as the address
- This can be achieved using the following two microinstructions:

Ck 1: E_{PC} , L_{MR} , I_{PC}

Ck 2: RD, L_{IR}

- Instruction fetch requires 2 microcycles; in the first cycle, PC value is loaded to MAR
- The PC is simultaneously incremented, so that the next fetch will be from the next word in memory
- In the second cycle, the memory word at the address given by MAR is read and the value obtained is loaded into a special *instruction register* or IR
- The instruction register holds the entire opcode, which then needs to be decoded or deciphered to activate the control signals

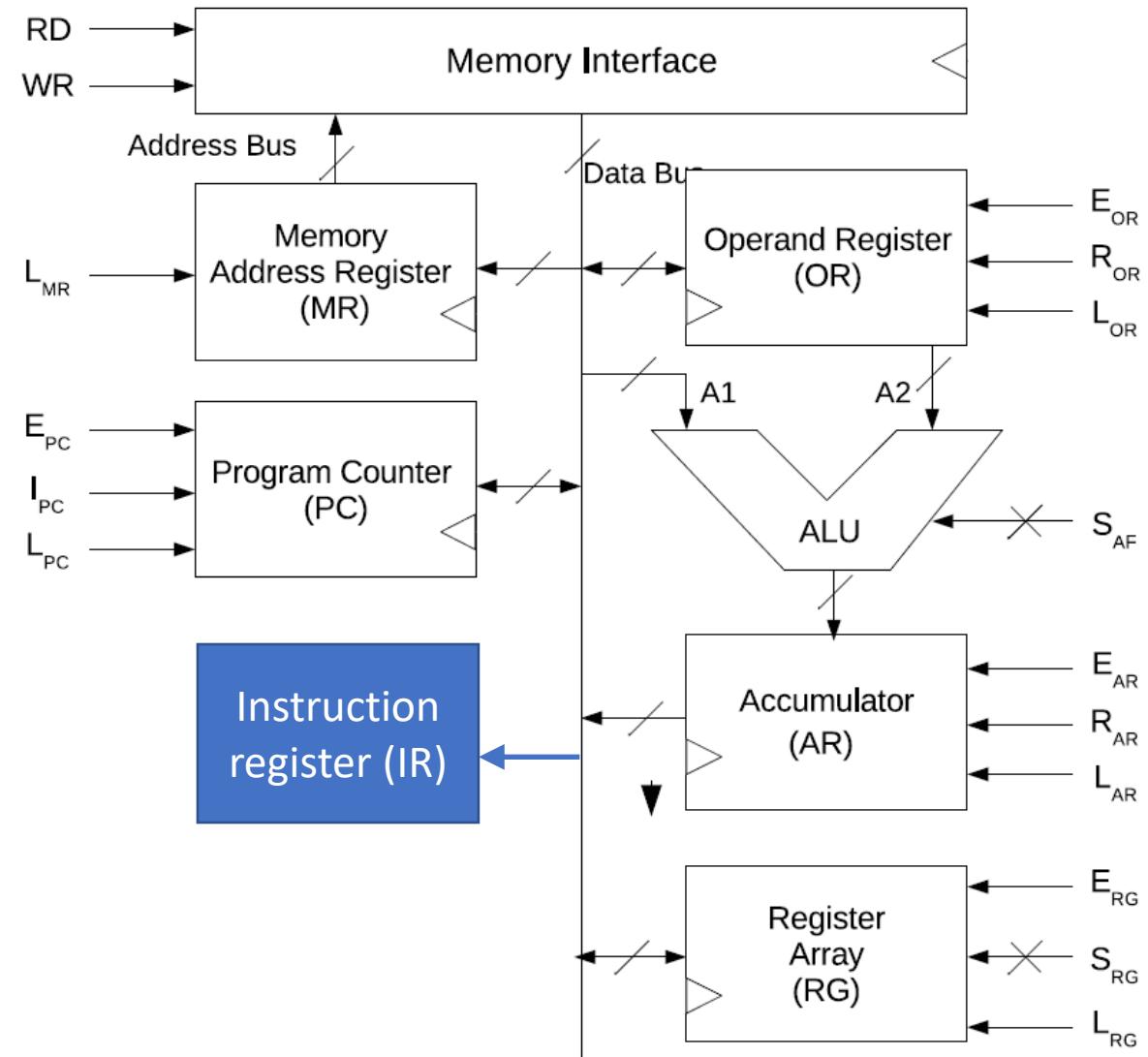


Instruction decoder

- Now, we complete the story of the processor!
- It is clear that the main task is to generate the combination of control signals for each clock cycle for each instruction as per its implementation
- We can think of the control signals being generated using a combinational circuit, whose input is the opcode of the current instruction and the clock cycle number
- The opcode is loaded into the IR register by the fetch process which needs to be decoded into the control signals
- Further, a single opcode can have multiple microcycles associated with it and all of these will have different control signals active
- The process needs to continue until the END signal line is activated

Instruction decoder

- We can use a special ROM, to generate all control signals
- The word-width of the ROM equals the number of control signals used by the processor
- The number of words in the ROM should exceed the number of distinct input combinations to have enough space to encode all the possibilities
- Each bit of the ROM output can directly serve as the control input line
- The set of control signals treated as a word is often referred to as the *microprogram* word or the control word
- Each clock cycle of each instruction maps to a separate microprogram word

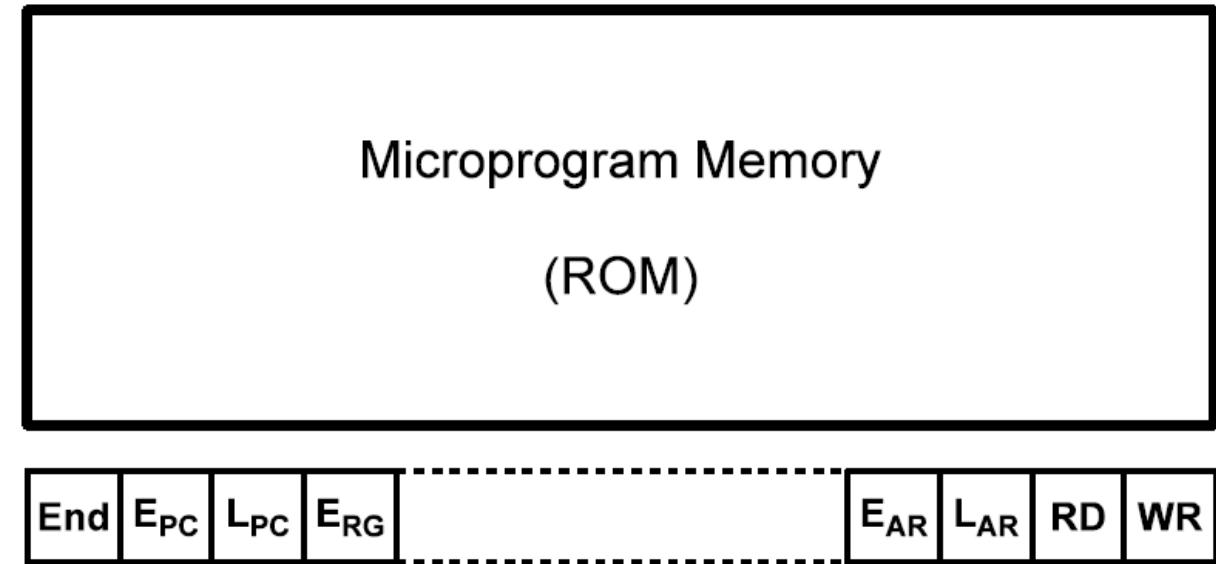


Instruction decoder

- The width of the word is clear from the number of control signals in the processor (close to 30 in this case)
- How to decide the address lines?
- The number of address lines is decided from the number of microprogram words needed to execute all the instructions
- This includes the separate microcycles within a given instruction
- For instance, ADD <R> will have two separate microprogram words associated with it
- In total, we have around 500 words, so we go with 9 address lines

Instruction	Opcode	Clk	Control Signals	Select Signals
Fetch	-	1	E _{PC} , L _{MR} , I _{PC}	-
		2	RD, L _{IR} , L _{MS}	-
nop	00	3	End	-
adi xx	01	3	E _{PC} , L _{MR} , I _{PC}	-
		4	RD, L _{OR}	-
		5	E _{AR} , L _{AR} , End	S _{ALU} ← ADD
		3	E _{PC} , L _{MR} , I _{PC}	-
sbi xx	02	4	RD, L _{OR}	-
		5	E _{AR} , L _{AR} , End	S _{ALU} ← SUB
		3	E _{PC} , L _{MR} , I _{PC}	-
xri xx	03	4	RD, L _{OR}	-
		5	E _{AR} , L _{AR} , End	S _{ALU} ← XOR
		3	E _{PC} , L _{MR} , I _{PC}	-
ani xx	04	4	RD, L _{OR}	-
		5	E _{AR} , L _{AR} , End	S _{ALU} ← AND
		3	E _{PC} , L _{MR} , I _{PC}	-
ori xx	05	4	RD, L _{OR}	-
		5	E _{AR} , L _{AR} , End	S _{ALU} ← OR
		3	E _{PC} , L _{MR} , I _{PC}	-
cmi xx	06	4	RD, L _{OR}	-
		5	E _{AR} , End	S _{ALU} ← CMP


Instruction decoder

- Now, all we need to do is to map the 8-bit opcode to the 9-bit address in the ROM
- This can be done using a simple combinational circuit
- Thus, the opcode from the instruction register (IR) is decoded and stored in a register called microprogram sequencer which has an option to load it from the decoder output (L_{MS})
- Further, we store the microprogram words for a given instruction consecutively in the ROM
- The MS is incremented in every clock cycle to get the next microprogram word, until it is loaded again

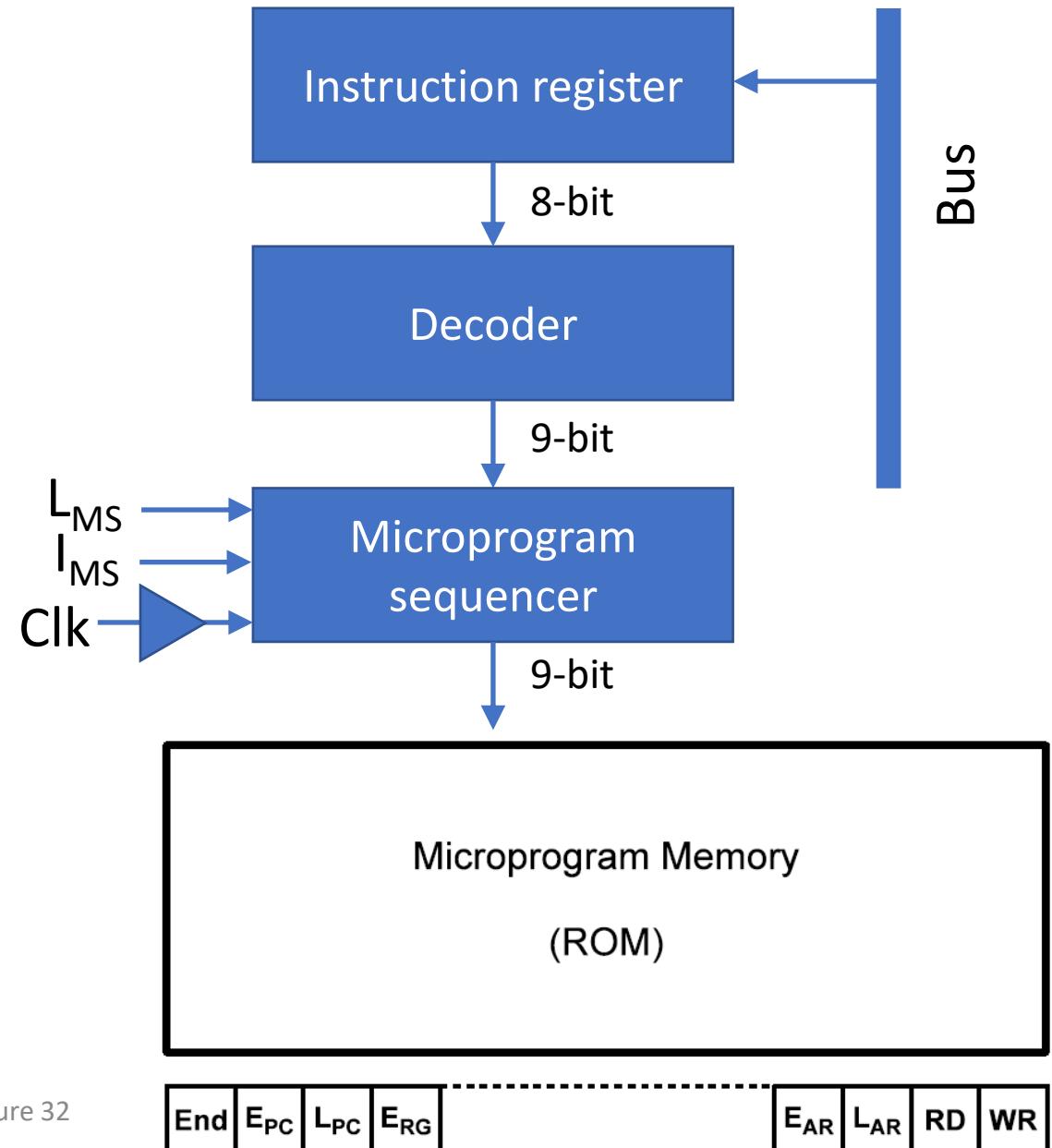


Instruction decoder

- The starting microprogram address is loaded onto the microprogram sequencer using L_{MS} (this is done using the microprogram word after the fetch cycle)
- This will result in the first microinstruction corresponding to the current opcode to be taken up in the following clock cycle
- Since we have stored the microinstructions for each instruction in consecutive locations of the microprogram memory, the microprogram sequencer is a register which gets incremented by 1 every clock cycle at the falling edge
- This continues till the last microinstruction of each opcode and the *End* line is activated

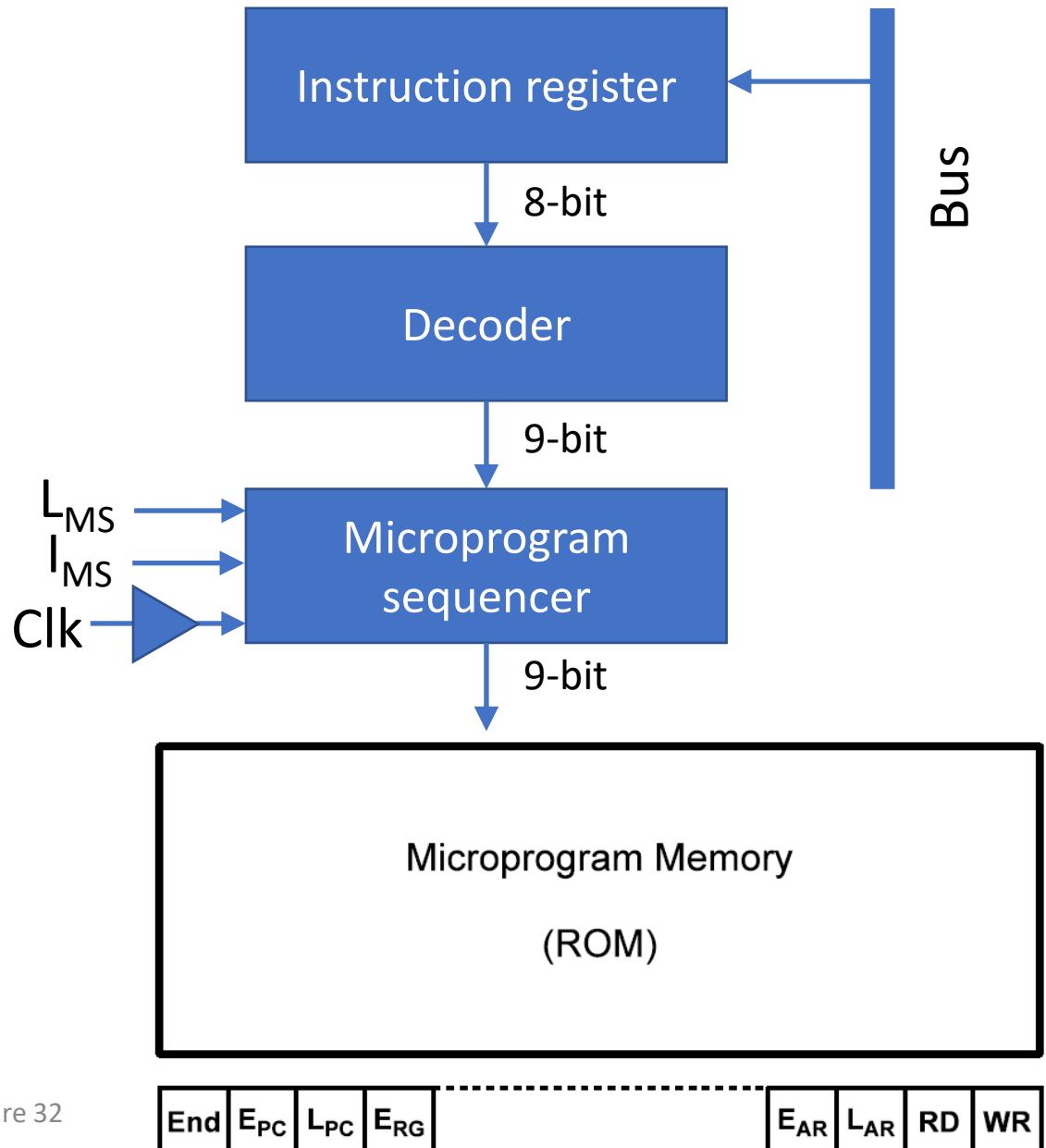


The End Game

- We issue a signal *End* to denote that the execution of the instruction is completed
- The processor is to proceed to fetching the next instruction
- How can we ensure this?
- We do this by putting the microprogram word corresponding to the first cycle of *Fetch* instruction at address 0 of the ROM
- Thus, going to the fetch phase of the next instruction can be achieved by loading 0 to the MS
- We can do that if we use the signal *End* as the reset for the MS, making it a register with load (using L_{MS}), reset (using R_{MS}), and increment facilities
- Have a power-on-reset on *End*, like we have for PC to reset the process to “Fetch” when the power is switched on

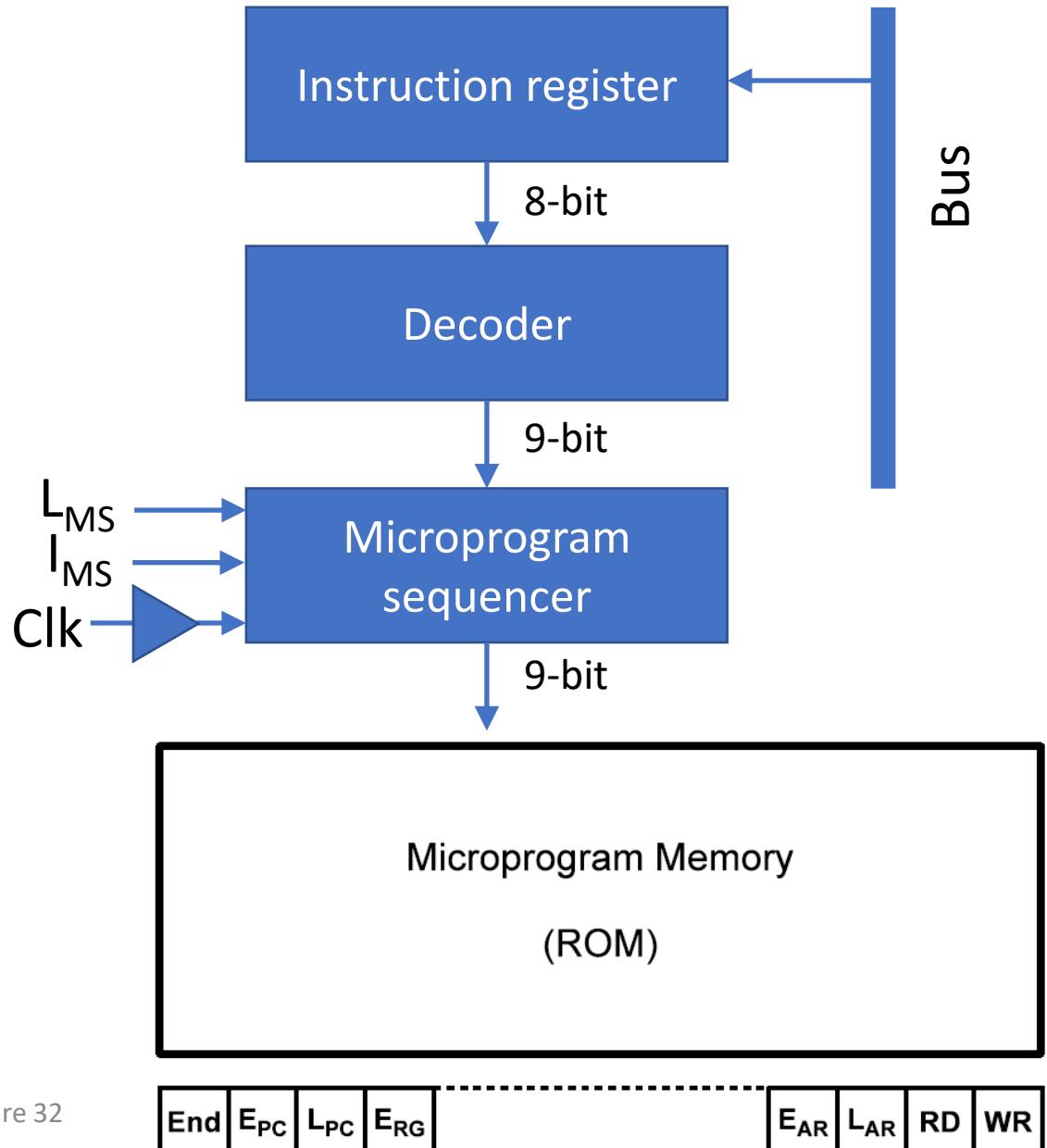

The final processor design

- So finally we are able to reveal the complete processor design
- This 8-bit, single bus processor can take instructions and data stored in the memory and perform tasks
- Each instruction is first fetched from memory into the IR, decoded and stored in the MS
- This is done using the address being pointed at by the PC (through the MR)
- Once, the microprogram word is obtained, the subsequent processing is done by the hardware
- Because the MS updated at the (delayed) negative edge of the clock, the control signals are available just after the negative edge , i.e., just before the positive edge

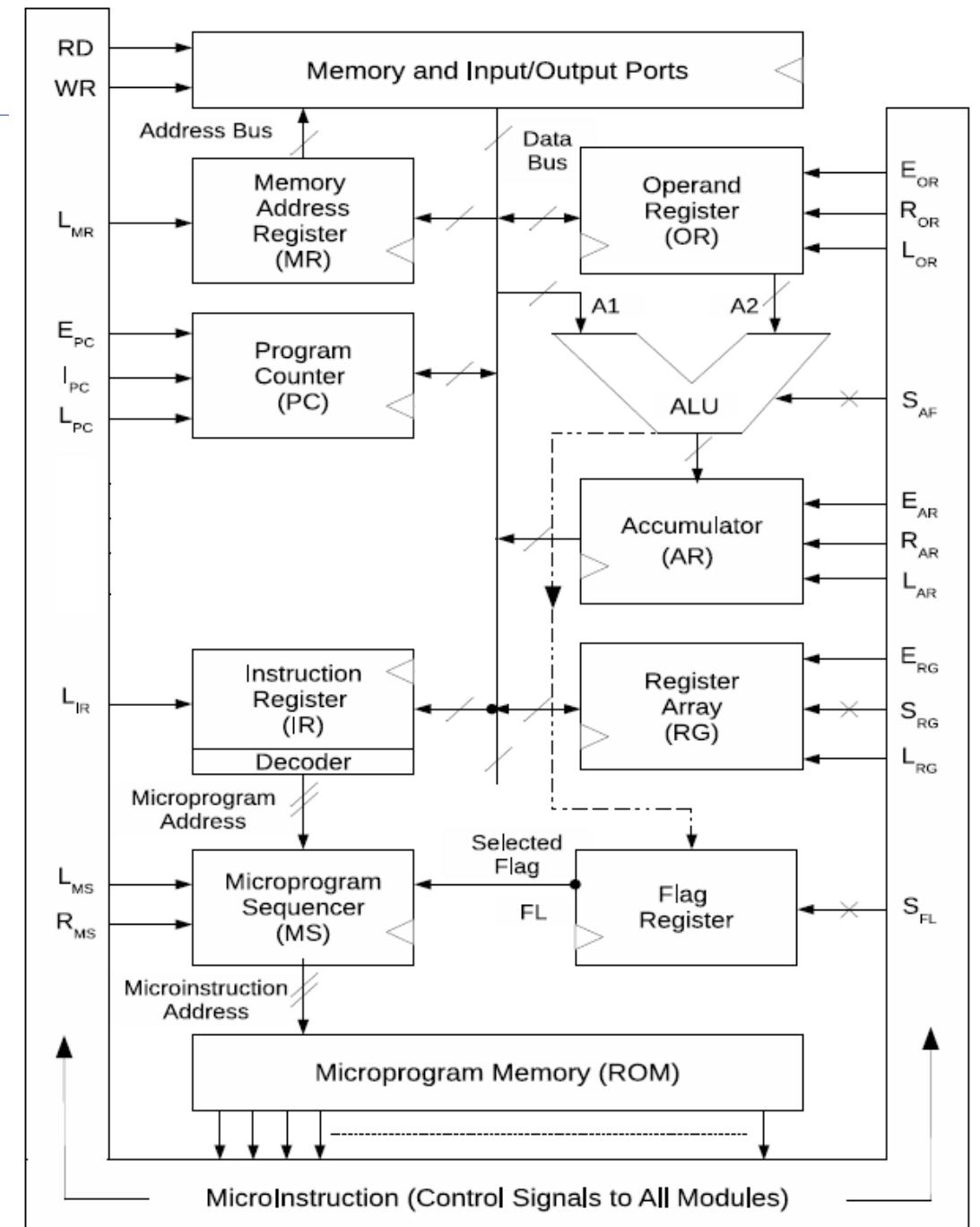

A familiar architecture

- This is the internal architecture of ATMEGA328, which is the brain of the Arduino board
- Very similar to the processor we designed, but many key functions are added such as interrupts, timers, ADC to enable overall functionality – TBD in CCIoT (UG2 ECE elective)

