

# DSM Tutorial Quiz Questions (Pre-Midsem)

Consider the equation  $L + M = N$  where  $L = (312)_8$  and  $N = (451)_8$ . Find the value of  $M$  represent the answer in hexadecimal.

Convert  $3210_5$  to base 3

First find,  $3210_5 = 430_{10}$

Then find,  $430_{10} = 120221_3$

Convert  $212_3$  to base 5

First,  $212_3 = 23_{10}$

Then find,  $23_{10} = 43_5$

## 1. Write the divisibility rule of 3 for binary numbers

A. A binary number  $N$  can be expressed as:

$$N = (b[n-1]) \cdot 2^{(n-1)} + (b[n-2]) \cdot 2^{(n-2)} + \dots + b[0] \cdot 2^0$$

where  $b[i]$  can either be 0 or 1.

We can say that  $2^k$  and  $2^{(k+2)}$  have the same remainder when divided by 3 because their difference is divisible by 3.

$$2^{(k+2)} - 2^k = 2^k (4 - 1) = 2^k (3) \rightarrow \text{divisible by 3}$$

So,  $2^0, 2^2, 2^4, \dots$  will have the same remainder when divided by 3, i.e., 1

Similarly,  $2^1, 2^3, 2^5, \dots$  will have the same remainder when divided by 3, i.e., 2

Hence, the remainder of  $b[i] \cdot 2^i$  will be  $b[i] \% 3$  if  $i$  is even. It will be  $(2 \cdot b[i]) \% 3$  if  $i$  is odd.

For the number  $N$  to be divisible by 3, the sum of these remainders should be divisible by 3, i.e.,  $R = b[0] + 2 \cdot b[1] + b[2] + 2 \cdot b[3] + b[4] + 2 \cdot b[5] + \dots$  should be divisible by 3.

For example, let us consider the binary number 11011. Here,  $b[0] = 1, b[1] = 1, b[2] = 0, b[3] = 1, b[4] = 1$ .  $R = 1 \cdot 1 + 2 \cdot 1 + 1 \cdot 0 + 2 \cdot 1 + 1 \cdot 1 = 6$  which is divisible by 3. Hence, the given binary number is also divisible by 3.

**Question:** “Product of two  $n$ -bit two’s-complement numbers requires fewer than  $2n$  bits to represent it.”

Find a case in which this statement is not correct.

**Answer:** multiplying  $(-2^{n-1})$  with itself will need  $2n$  bits to represent  $2^{(2n-2)}$

**Solution:**

Consider the number  $(-2^{n-1})$ , it belongs to  $n$ -bit two’s-complement system and can be represented as  $100\dots00$ .

On multiplying  $-2^{n-1}$  with itself:

$$-2^{n-1} \times -2^{n-1} = 2^{(2n-2)}$$

In a 2’s complement system,  $2^{(2n-2)}$  requires  $2n$  bits to represent it. (1 sign bit +  $2n - 1$  magnitude bits)

**Question:** How many unique Boolean functions can exist for  $n$  number of inputs?

**Answer:**  $2^{2^n}$

**Solution:**

For  $n$  inputs, the possible number of min-terms are  $2^n$  let this be called  $k$

1

Any boolean function is a combination of minterms (ordering does not matter).

No of boolean function considering exactly 0 minterm  $= {}^kC_0$

No of boolean function considering exactly 1 minterm  $= {}^kC_1$

No of boolean function considering exactly 2 minterm  $= {}^kC_2$

...

No of boolean function considering exactly  $k$  minterm  $= {}^kC_k$

Therefore, total no of boolean functions possible is:

$${}^kC_0 + {}^kC_1 + {}^kC_2 + \dots + {}^kC_k = (1 + 1)^k = 2^k$$

substituting  $k = 2^n$ , the total number of possible boolean functions is  $2^{2^n}$

1. What is the condition for an equation of a sum of minterms in a 4-variable Karnaugh map (K-map) to be **non-simplifiable** based on the positioning of 1s and 0s? Explain why this happens.
- A. Assume that two 1s are adjacent (includes cyclic adjacency). If two 1s are adjacent, they will be in either the same row or the same column:

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

**Adjacent 1s in the Same Row:**

- The 1s can occupy any of the column pairs: (1,2), (2,3), (3,4), or (4,1).
- For pairs (1,2) and (3,4), the adjacent columns share a common variable, either C or C'.
- For pairs (2,3) and (4,1), the adjacent columns share D or D'.
- Each of these pairs has three variables in common, and the terms formed will be of the type  $xyzw' + xyzw$  allowing for simplification by removing w.


**Adjacent 1s in the Same Column:**

- The same logic applies if the 1s are adjacent in a column, where adjacent rows share either A and A' or B and B'.
- The terms will simplify similarly, leading to a reduction.

Therefore, to prevent any simplification, **no two 1s should be adjacent** either directly or cyclically. If this condition is met, no grouping or reduction can occur, and the equation remains non-simplifiable.
 
## Q2

N number of XNOR gates are connected as shown below. How does this circuit work? Explain?



## Ans

two different ways based on N-value. (a) N is odd (b) N is even

(a) If N is odd, there will be even number of XNOR gates in the circuit. Take an example of  $N=3$ , So there are 2 XNOR Gates. The two bubbles will get cancelled and this works as XOR. Same works for any odd N. So if N is odd it works as XOR Gate.

(b) If N is even, the circuit works as XNOR Gate. ( Apply the same logic). One extra bubble will be there to make XOR to XNOR. You may verify the same for  $N=4$ .

2. You are playing a best-of-3 tennis match. Develop a Boolean expression that represents the condition in which you'll win the match. Additionally, provide a logic gate implementation of this expression using only a single type of logic gate.

A. Let  $S_i$  represent the result of the  $i$ -th set, where  $S_i=1$  if you win the set and  $S_i=0$  if you lose. The Boolean expression for winning the match is:

$$F = S_1S_2 + S_1'S_2S_3 + S_1S_2'S_3$$

This expression means you win if:

- You win the first two sets, or
- You lose one of the first two sets but win the third set.

Simplifying further:

$$F = S_1S_3 + S_2S_3 + S_1S_2$$

This represents the possible ways to win the match.

### Implementation using NAND Gates:


Since the goal is to implement this expression using only NAND gates, we apply **De Morgan's law**. The NAND operation is defined as:

$$(ABC)' = A' + B' + C'$$

Using this, we can rewrite the Boolean expression as:

$$F = ((S_1S_3)'(S_2S_3)'(S_1S_2'))'$$

 This representation uses only NAND gates to express the condition for winning the match.



## Question 2

Given the following truth table, represent it as a logic gate circuit with only 3 AND/OR gates. Assume that you have

$$A, \bar{A}, B, \bar{B}, C, \bar{C}$$

as inputs.

Truth Table				
	A	B	C	Y
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

## Answer

$$\bar{A}BC + \bar{A}\bar{B}C + A\bar{B}C$$

Apply the Distributive Law ( $AB + AC = A(B + C)$ )


$$\bar{B}C(\bar{A} + A) + \bar{A}\bar{B}C$$

Apply the Complement Law ( $A + \bar{A} = 1$ )

$$\bar{B}C \cdot 1 + \bar{A}\bar{B}C$$

Apply the Identity Law ( $A1 = A$ )

$$\bar{B}C + \bar{A}\bar{B}C$$

 



## Q1

The grouping of  $k$  adjacent cells, in a  $N$  variable K-Map will lead to a term of \_\_\_\_ literals?

Ans

$N - \log_2(k)$

Soln

In a  $N$  variable k-map,

Having a group of size 1, i.e single cell means that the cell requires the description of all variables to describe the group output.

Having a group of size 2, means that 1 variable is same across the 2 cells, and it only requires us  $N-1$  variables to describe the group output.

Having a group of size 4, means that 2 variables are same across the 4 cells, and it only requires us  $N-2$  variables to describe the group output.

Having a group of size 8, means that 3 variables are same across the 8 cells, and it only requires us  $N-3$  variables to describe the group output.

.... (observing the pattern) ....

Having a group of size  $k$ , means that  $\log_2(k)$  variables are same across the  $k$  cells, and it only requires us  $N - \log_2(k)$  variables to describe the group output.

## Q1


Design a circuit for 3-input majority function using a 4:1 Mux

Ans

The majority function gives 1 if the input has more number of 1s than zeros.

 1. If  $A=B=0$ , the output will be zero irrespective of  $C$
2. If  $A=B=1$ , the output is 1 irrespective of  $C$ .
3. But if  $A=1, B=0$  or  $A=0, B=1$ , we can not decide the majority without knowing  $C$ . if  $C$  is 1, majority is 1, otherwise majority is 0.

So  $I_0 = 0, I_1 = I_2 = C$  and  $I_3 = 1$



## Q2

Using a 4-bit binary adder, design a circuit which multiplies the input by 3?  
Note: you need not handle overflow bit (i.e 5th bit).

## Ans


Lets say input is X (4 bits).

We need to find  $3X$

Can be written as  $3X = 2X + X$

$2X$  is simply a left shift of bits.

 Adding  $2X$  with  $X$  using 4-bit binary adder looks like this:



Note to TAs: You can ignore the left most output channel since it is a overflow bit.

### 1. Design an OR gate using half adders

A. A half adder takes two inputs and provides two outputs:

i. Sum (S) = A XOR B

ii. Carry (C) = A AND B

Required: A OR B

We know that:  $A \text{ OR } B = A \text{ XOR } B \text{ XOR } (A \text{ AND } B)$

To implement the OR gate, we need 2 half adders:

-> Let inputs be A and B

-> First Half Adder: Connect A and B to the inputs of the half adder. The half adder will produce S and C.

-> Second Half Adder: Connect S and C to the inputs of the half adder. The half adder will produce S XOR C (Sum) and S AND B (Carry).

$S \text{ XOR } C = A \text{ XOR } B \text{ XOR } (A \text{ AND } B) = A \text{ OR } B$

Therefore, the sum bit of the second half adder is the output of the newly designed OR gate.