

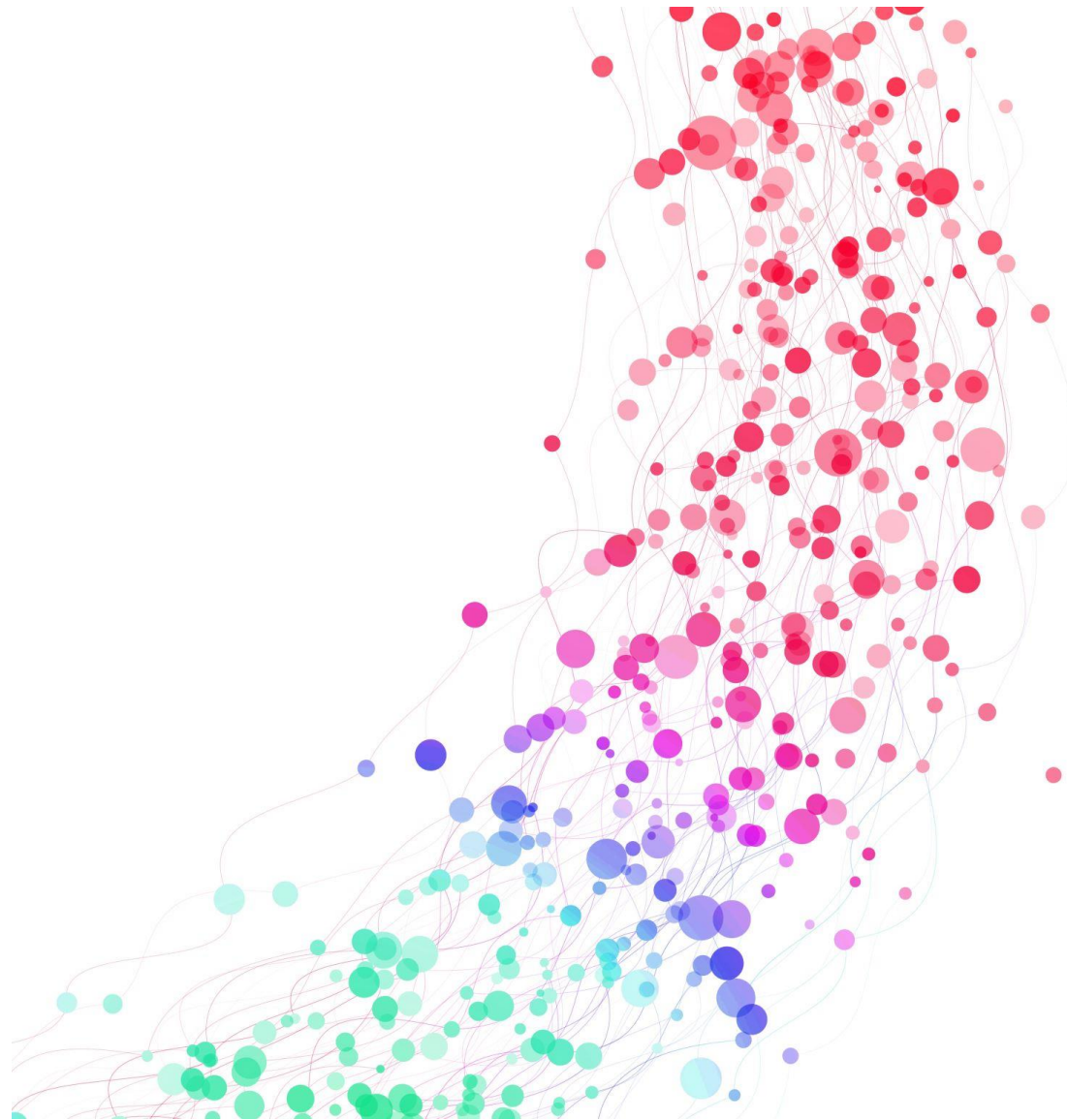
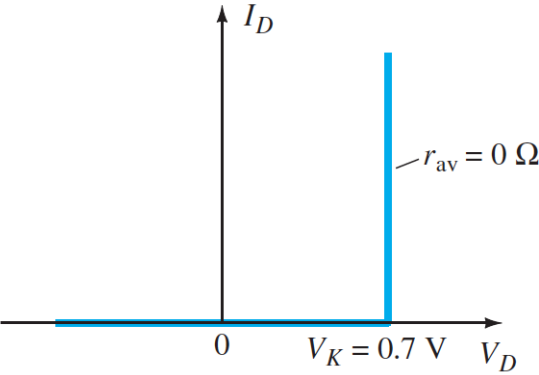
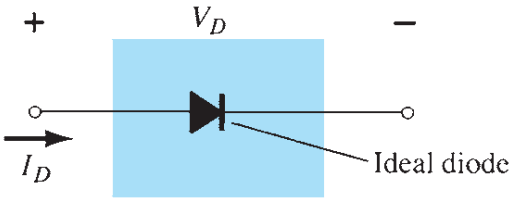


Fundamentals of Electronics







ECE 101

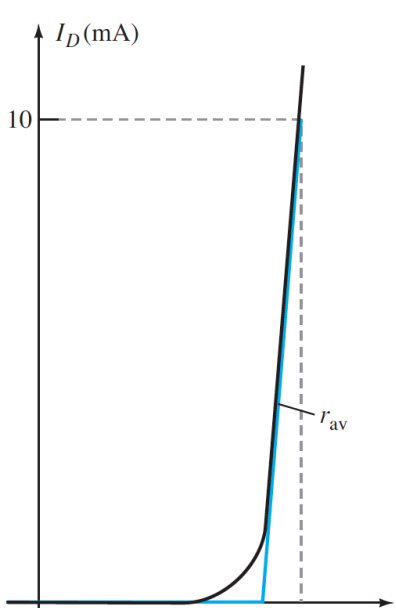

Summary












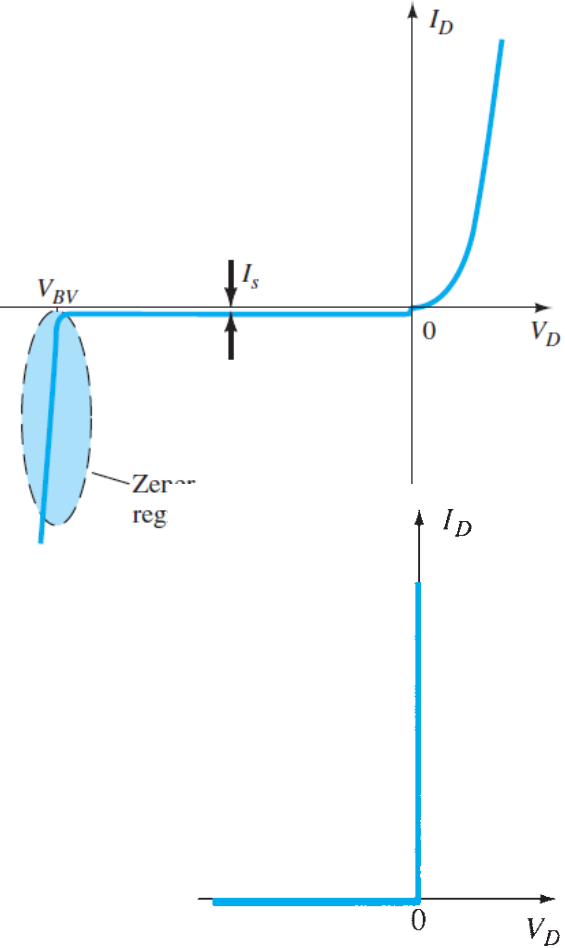


Si

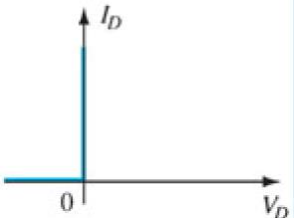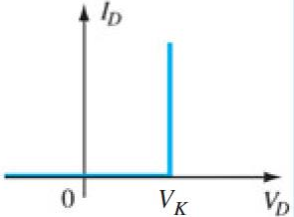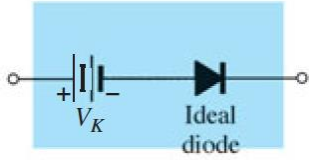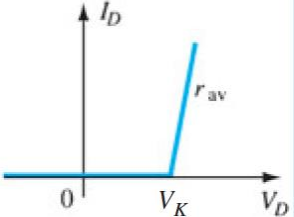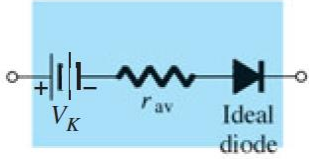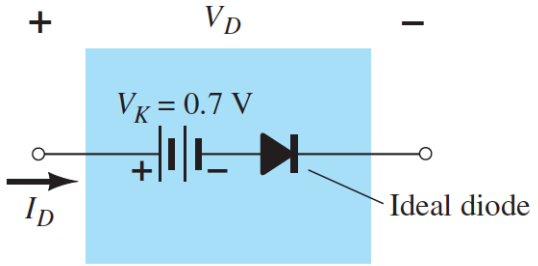





Difference b/w Semiconductors and Metals

Full wave rectification

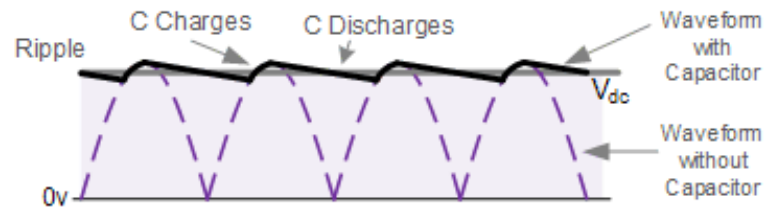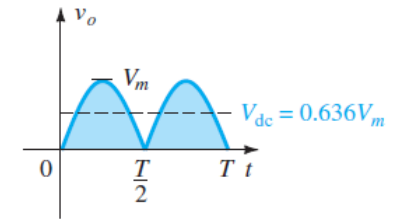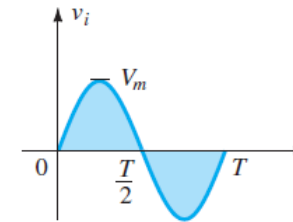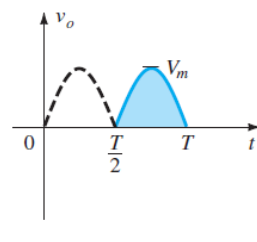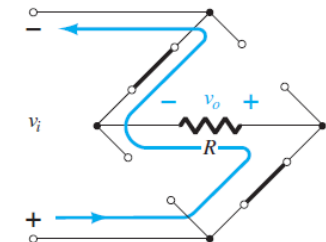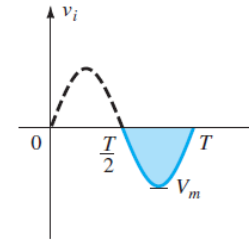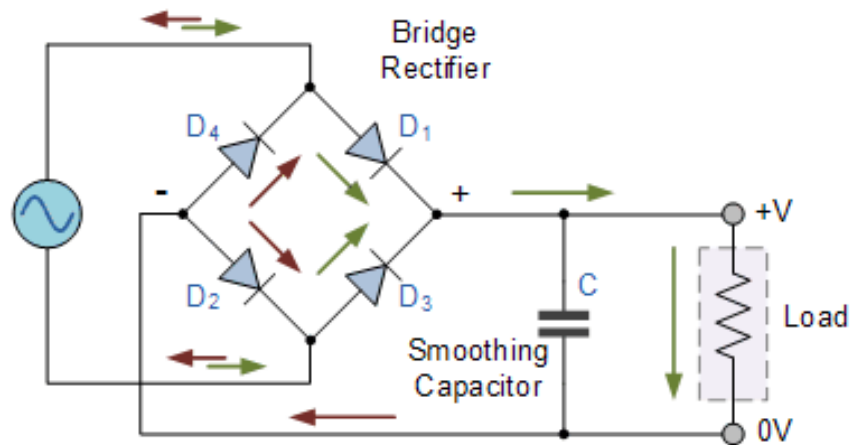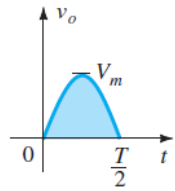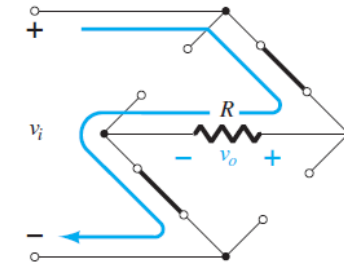
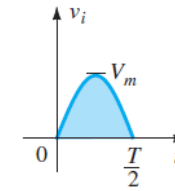
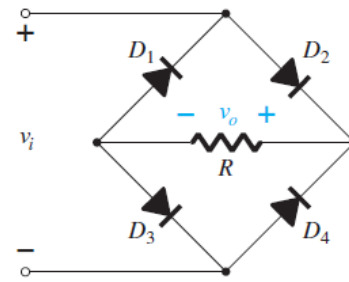
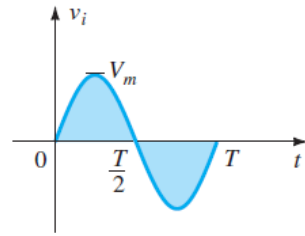


Diode as clipper

In series


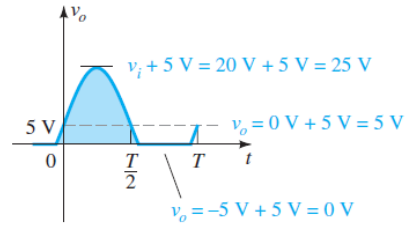
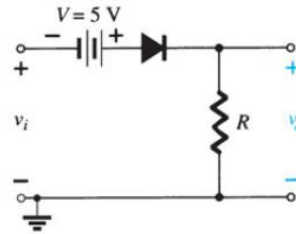
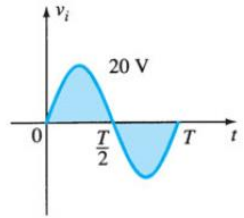
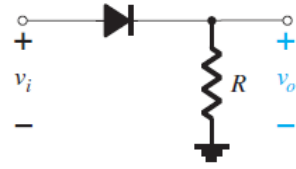


In parallel

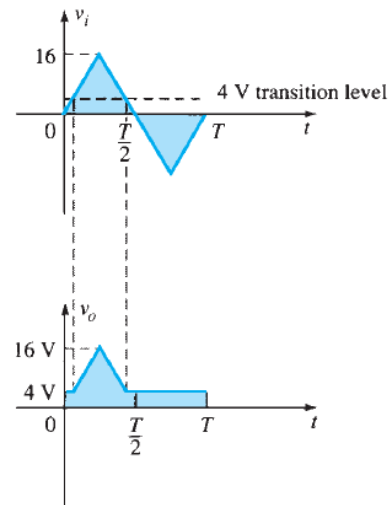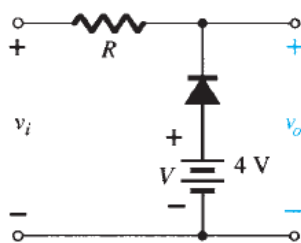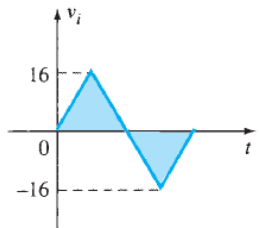
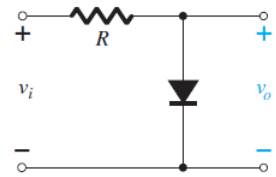


Diode as clamper

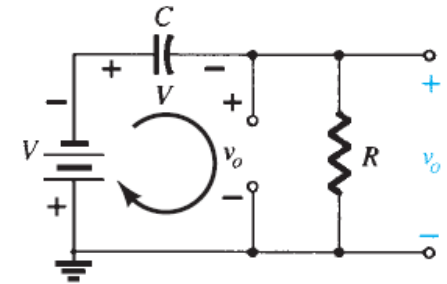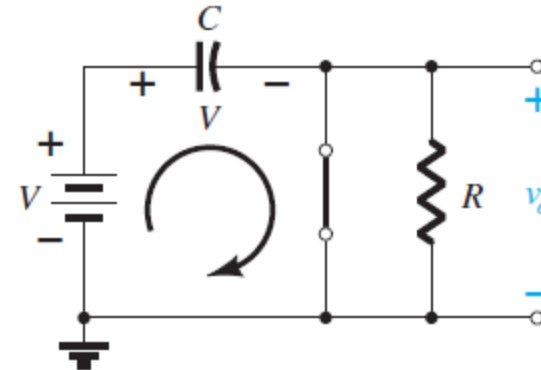
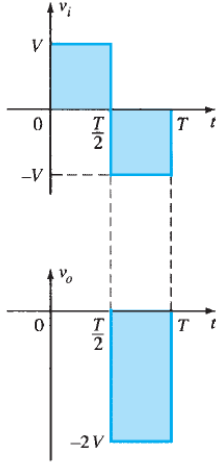
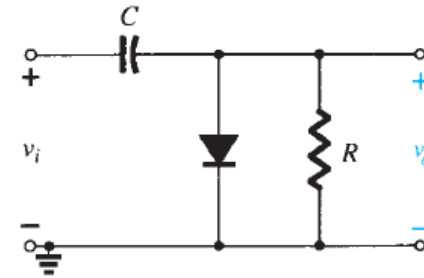
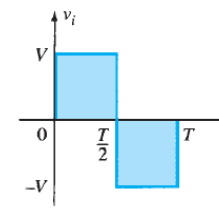
Clamper is a circuit that changes the dc level of a waveform without changing its appearance.



Determine the output voltage


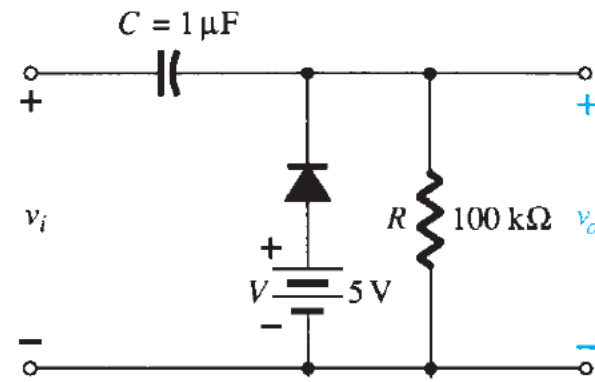
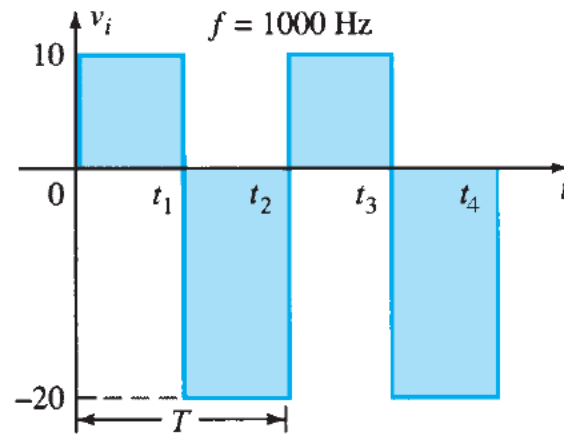


Zener Voltage Regulation

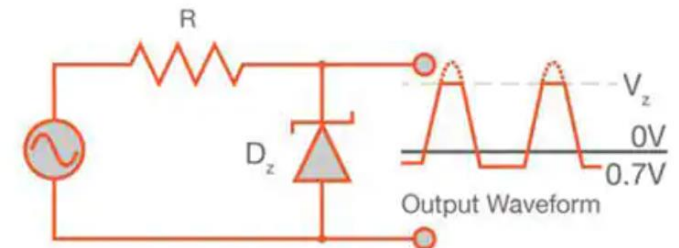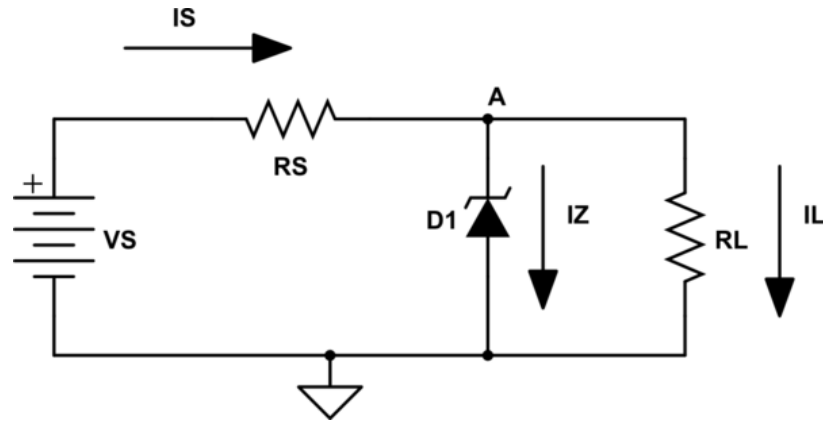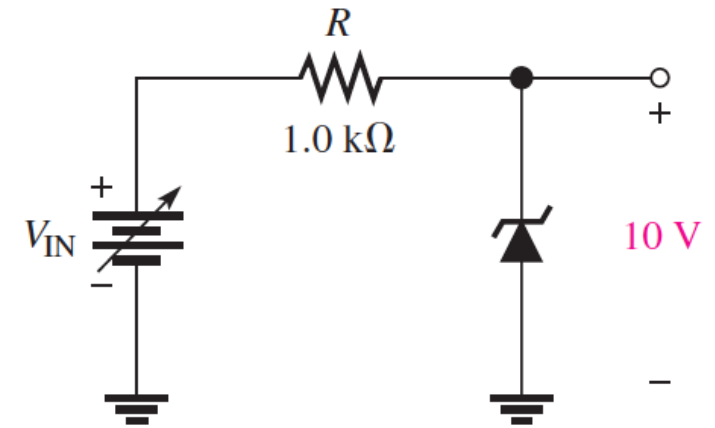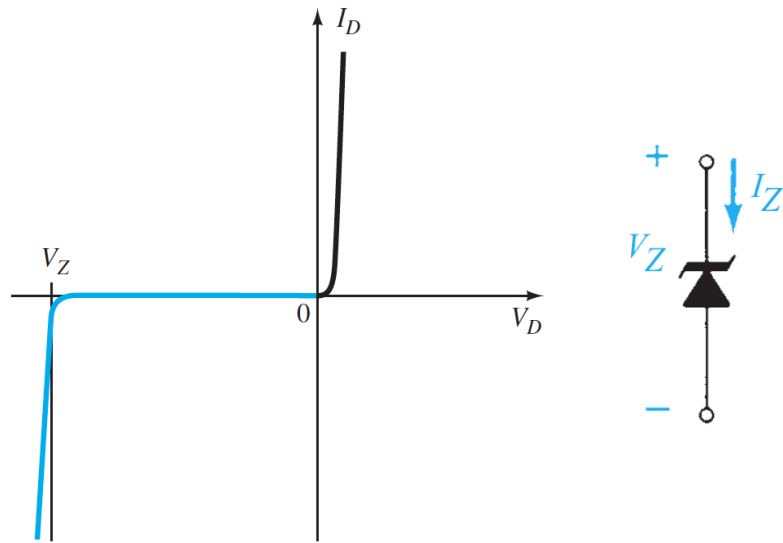


Zener regulation

Voltage regulator

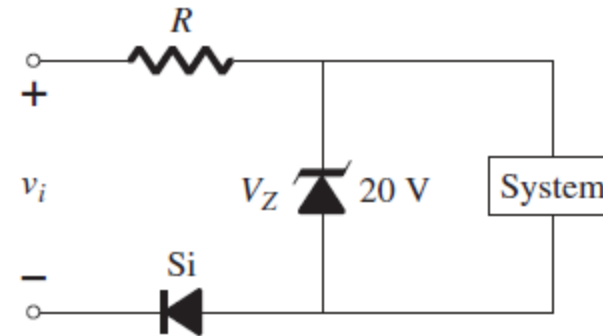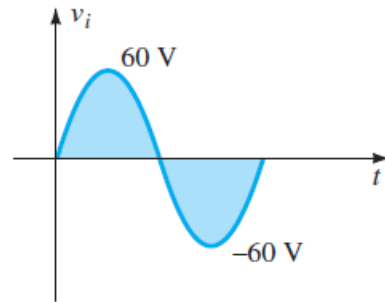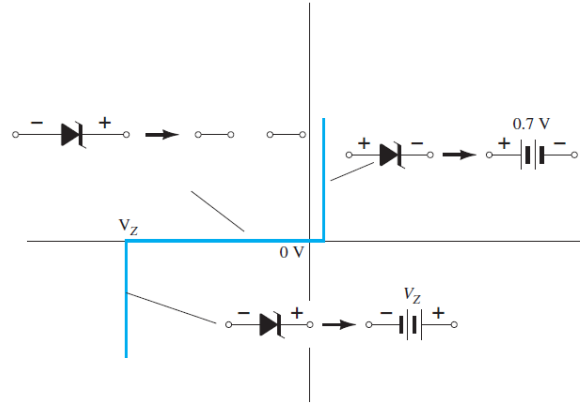

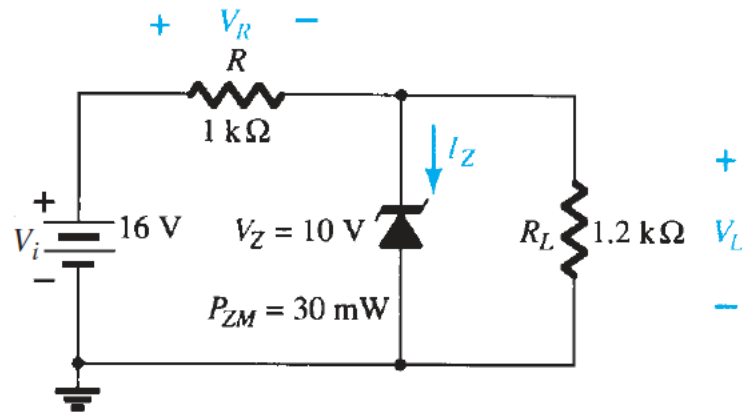- a. For the Zener diode network of Fig. 2.115, determine V_L , V_R , I_Z , and P_Z .
- b. Repeat part (a) with $R_L = 3 \text{ k}\Omega$.




The Transistor

Amplification and switching

Transistor

- Key characteristic:
 - The transistor is a three-terminal device with the feature that the current through two terminals can be controlled by small changes we make in the current or voltage at the third terminal.
 - This control feature allows us to amplify small ac signals or to switch the device from an *on* state to an *off* state and back.
 - These two operations, *amplification* and *switching*, are the basis of a host of electronic functions.
 - This forms the basis for both bipolar junction transistors (BJT) and field effect transistors (FET).


The transistor action - 1

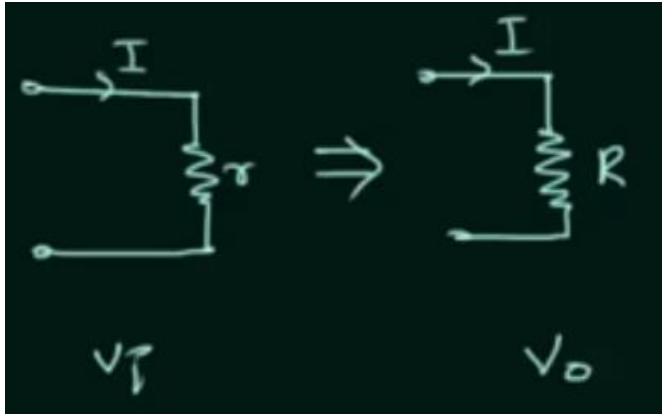

$$V_i = I \times \underline{r} \qquad V_o = I \times \underline{R}$$
$$V_i < \underline{V_o} \quad (\text{amplification})$$

Active mode
 $J_1 \rightarrow f-b. \quad R_{es} = 0$
 $J_2 \rightarrow r-b. \quad R_{es} = \infty$

Bipolar Junction Transistor (BJT)

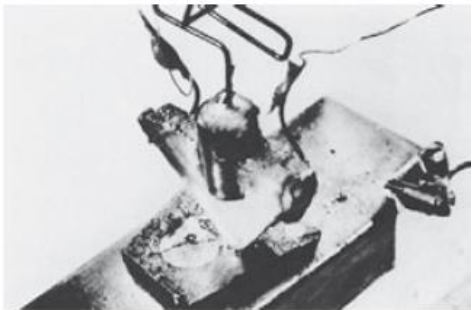




The first transistor



Active mode
 $J_1 \rightarrow f \cdot b \cdot R_{es} = 0$
 $J_2 \rightarrow r \cdot b \cdot R_{es} = \infty$

Basic mechanism

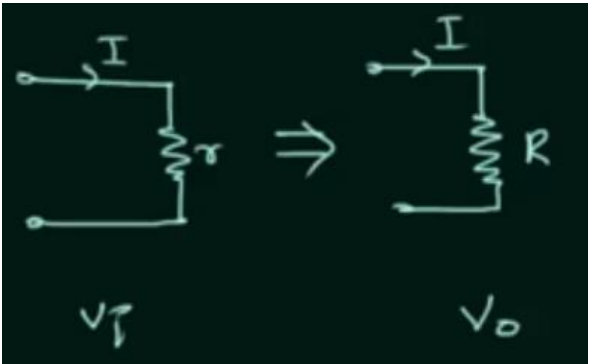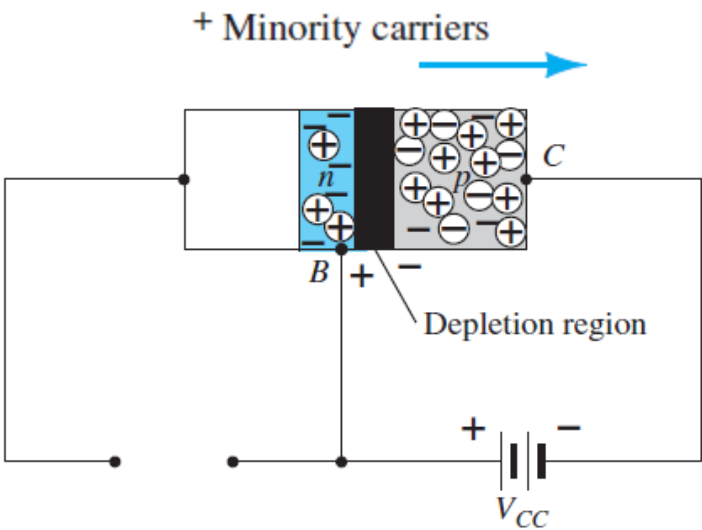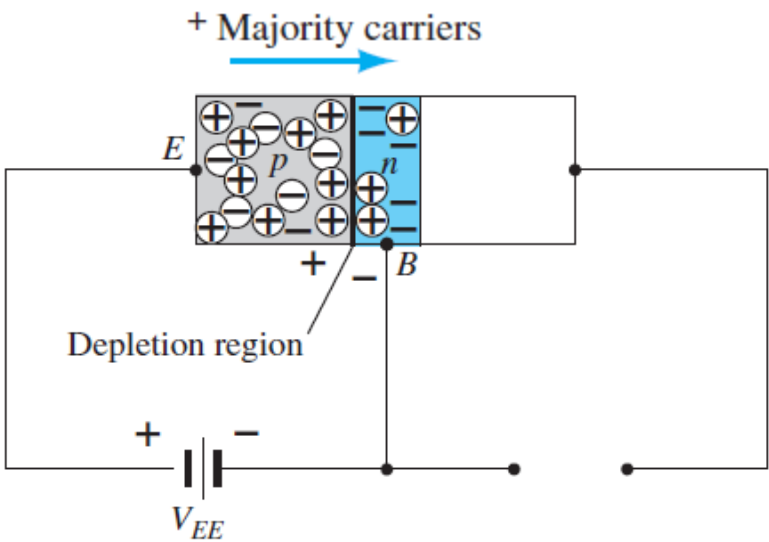One p-n junction is forward biased, the other one is reverse biased.



$$V_i = I \times r \quad V_o = I \times R$$

$V_i < V_o$ (amplification)

Thank you