

Gain expression:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$\underline{v_{gs}}$ = small increment

$$I_D + i_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} + v_{gs} - V_{TH})^2$$

$$\Rightarrow \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH})^2 + v_{gs}^2 + 2v_{gs}(V_{GS} - V_{TH}) \right]$$

$$I_D + i_d = \frac{1}{2} k \left[\cancel{(V_{GS} - V_{TH})^2} + \frac{1}{2} k v_{gs}^2 + k v_{gs} (V_{GS} - V_{TH}) \right]$$

$$\Rightarrow k v_{gs} \left(\frac{v_{gs}}{2} + (V_{GS} - V_{TH}) \right)$$

$$k v_{gs} (V_{GS} - V_{TH})$$

overdrive voltage

$$\underline{V_{GS} - V_{TH}} \gg \frac{v_{gs}}{2}$$

$$v_{gs} \ll 2(V_{OV})$$

$$\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) v_{gs} = i_d$$

Small signal analysis:

$$i_d = \underbrace{C_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}_{\text{DC parameter}} v_{gs}$$


o Drain

o Source



Gate (v_g)

Drain (v_d)

Source (v_s)

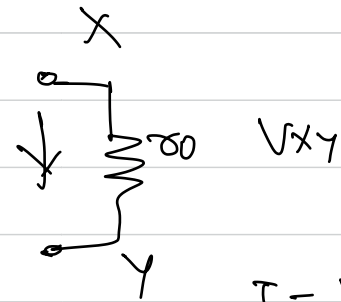

$$I = \frac{V_{xy}}{R_o}$$

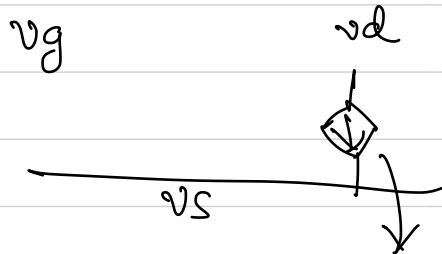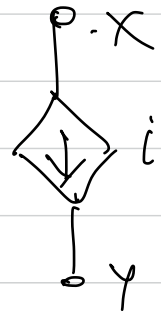

$$I_D = \frac{1}{2} K (V_{GS} - V_{TH})^2$$

$$\frac{dI}{dV_{GS}} = K(V_{GS} - V_{TH})$$


$$dI = K(V_{GS} - V_{TH}) dV_{GS}$$






$$\underbrace{C_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}_{g_m} v_{gs}$$




saturation: (No CLM)

$$g_m = \frac{2I_D}{(V_{GS} - V_{th})} \left| \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}} \right| \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$

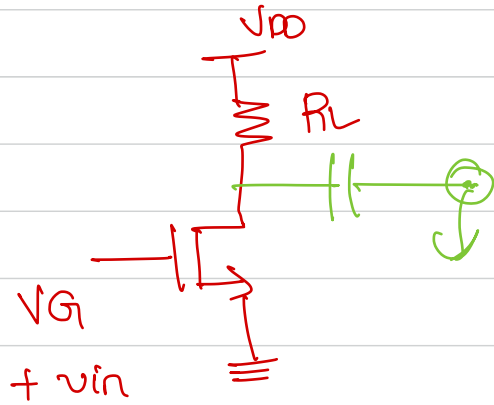
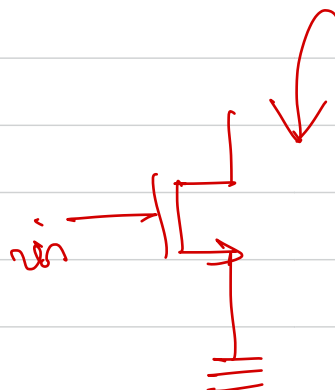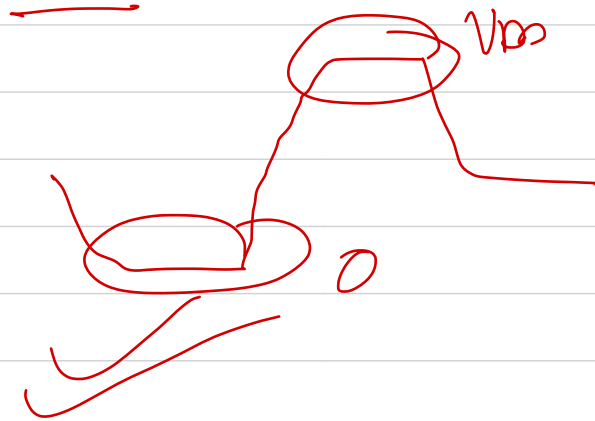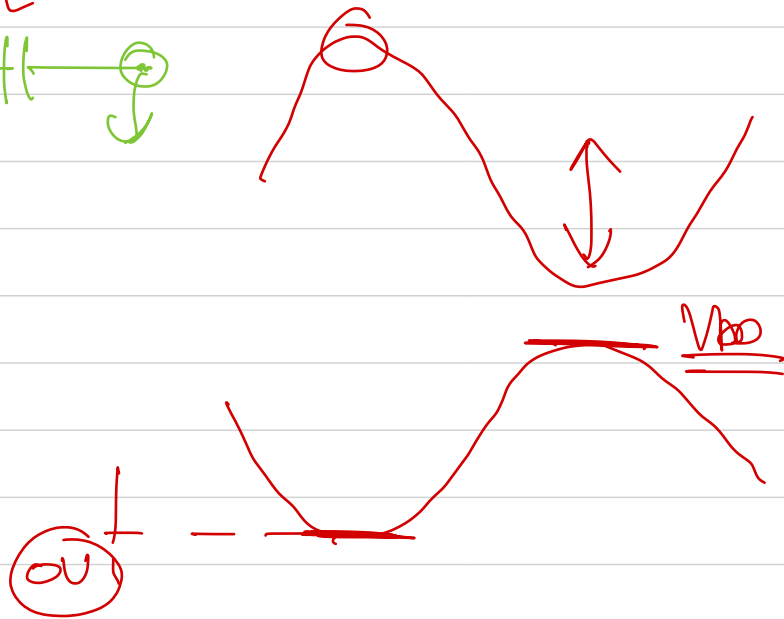
$$\underline{\underline{v_{gs} = v_{in}}}$$



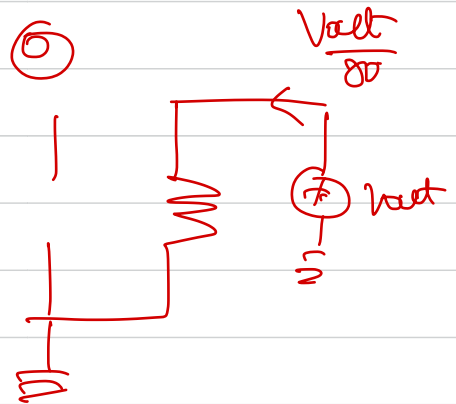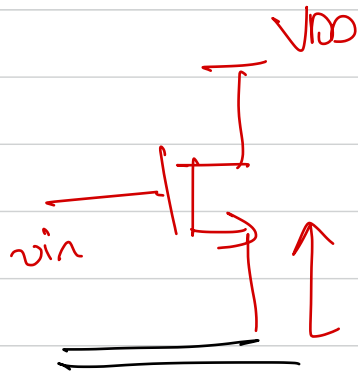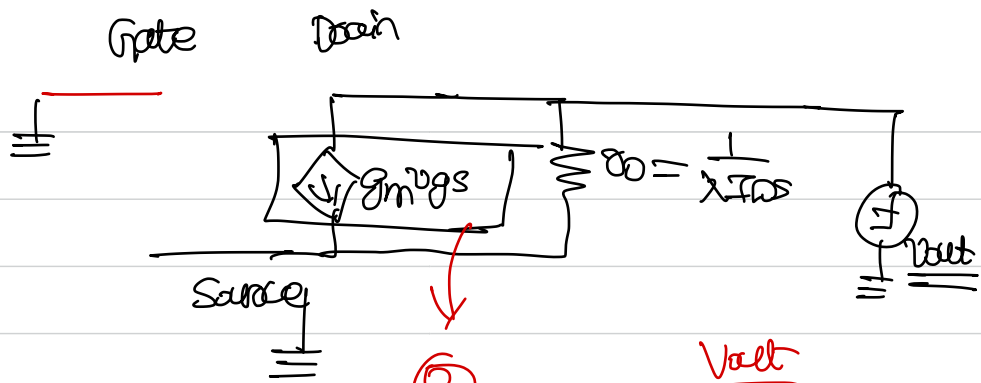


$$\frac{1}{g_m} \parallel r_o$$

$$= \frac{r_o}{1 + g_m r_o}$$

$$Z_{out} = r_o$$

$$= \frac{1}{\lambda I_D}$$


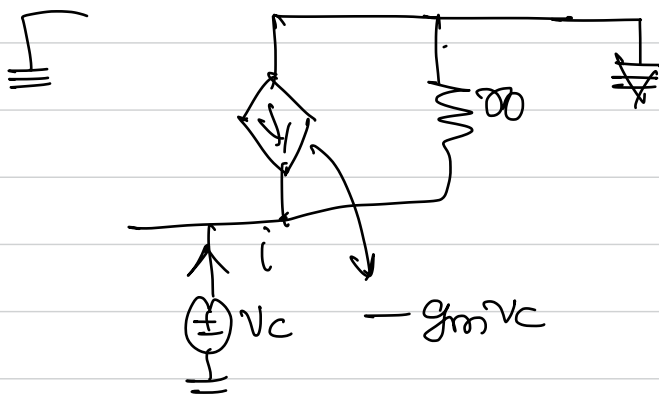


$$g_m v_c + \frac{v_c}{r_o} = i$$

$$\frac{v_c}{i} = \frac{r_o}{1 + g_m r_o}$$

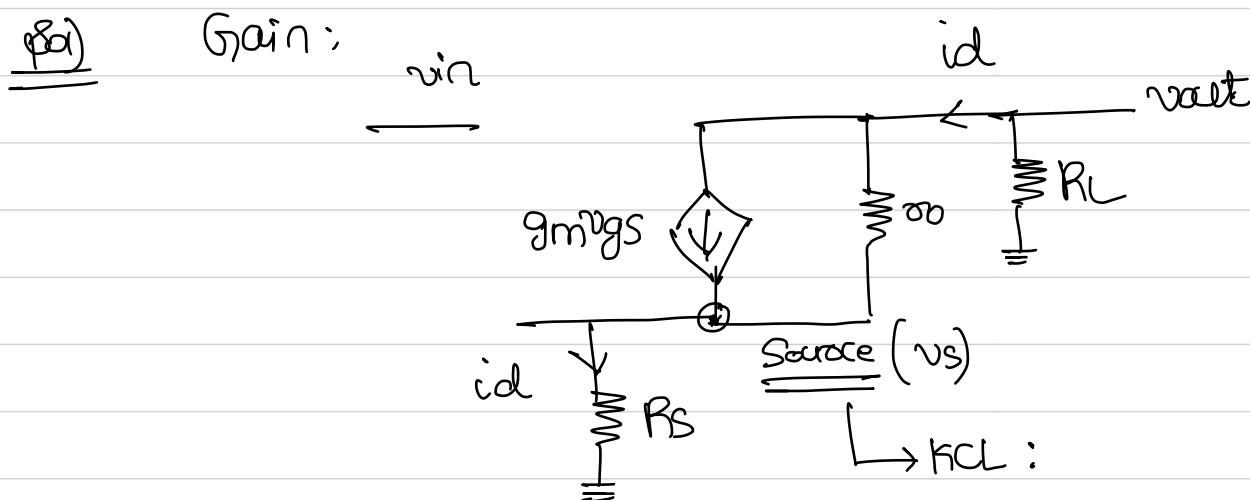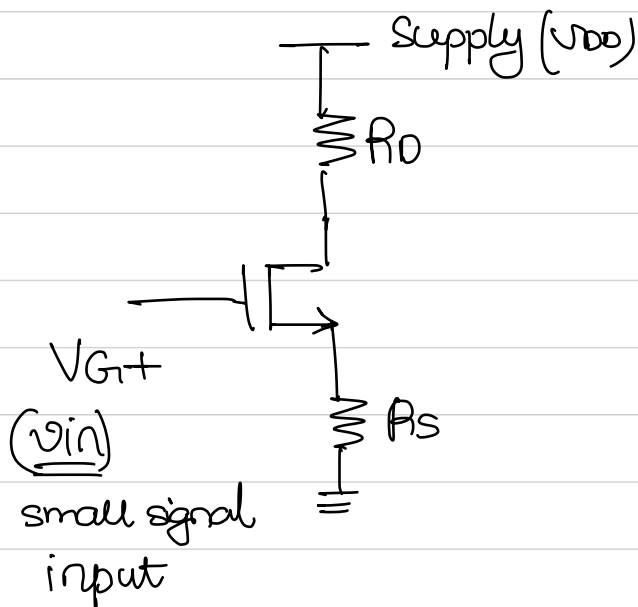Task:

Find gain, impedance from source and drain terminal
(include channel length modulation)



$$\boxed{-\frac{v_{out}}{R_L} = g_m(v_{in} - v_s) + \frac{v_{out} - v_s}{r_o} = \frac{v_s}{R_S}}$$

$$g_m(v_{in} - v_s) + \frac{v_{out} - v_s}{r_o} = \frac{v_s}{R_S}$$

$$\Rightarrow g_m v_{in} + \frac{v_{out}}{r_o} = v_s \left[\frac{1}{r_o} + \frac{1}{R_S} + g_m \right]$$

$$\Rightarrow g_m r_o v_{in} + v_{out} = \frac{v_s (R_S + r_o + g_m r_o R_S)}{R_S}$$

