
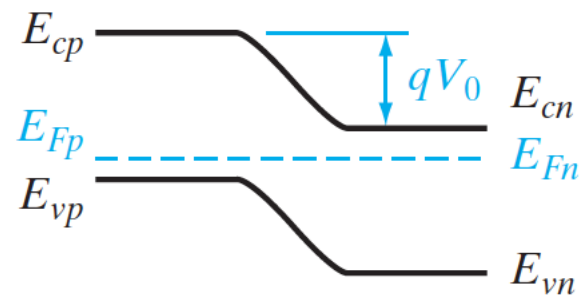


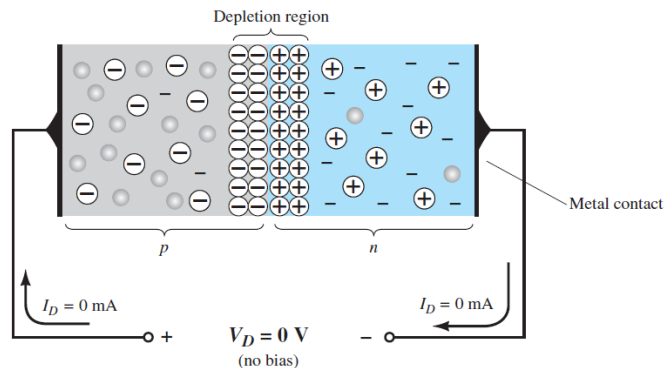

# ECE 101

## Fundamentals of Electronics

# Summary






Equilibrium  
( $V = 0$ )

Forward bias  
( $V = V_f$ )

Reverse bias  
( $V = -V_r$ )

$$I_D = I_s(e^{V_D/nV_T} - 1)$$

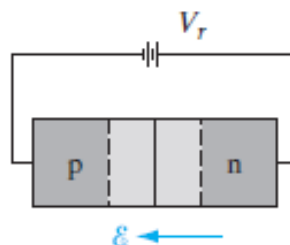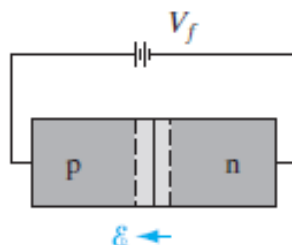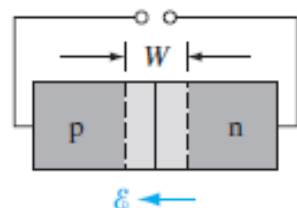




	Particle flow	Current
(1)	→	→
(2)	←	←
(3)	→	→
(4)	←	←

(1) Hole diffusion  
(2) Hole drift





	Particle flow	Current
(1)	→	→
(2)	←	←
(3)	→	→
(4)	←	←

(3) Electron diffusion  
(4) Electron drift









	Particle flow	Current
(1)	→	→
(2)	←	←
(3)	→	→
(4)	←	←

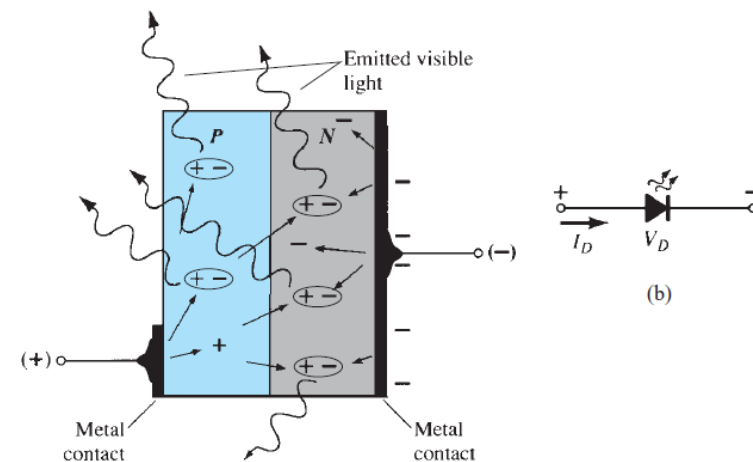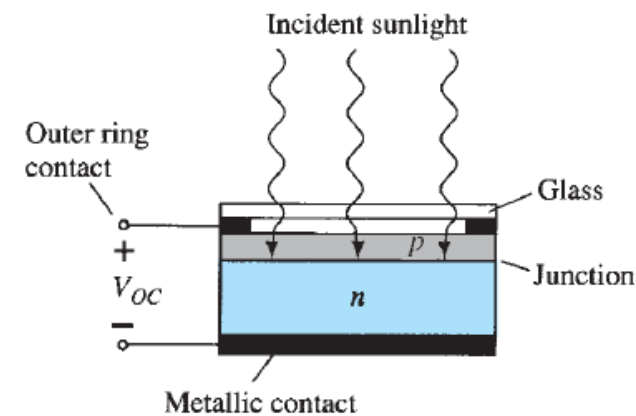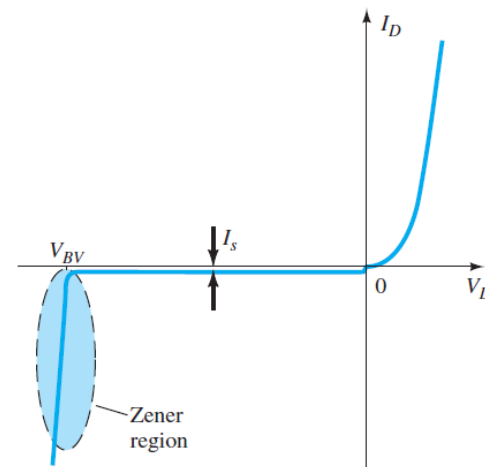

# Diode Circuits

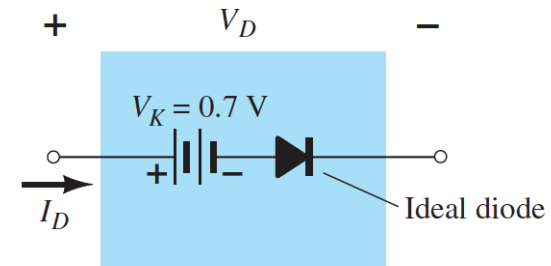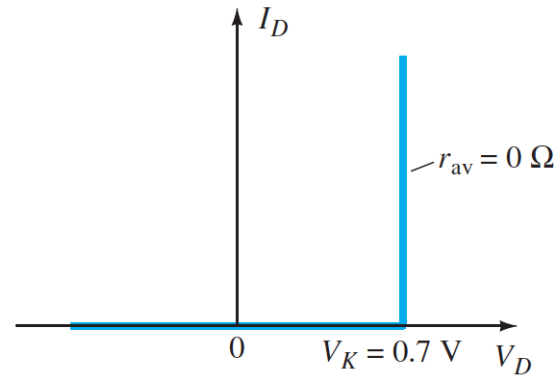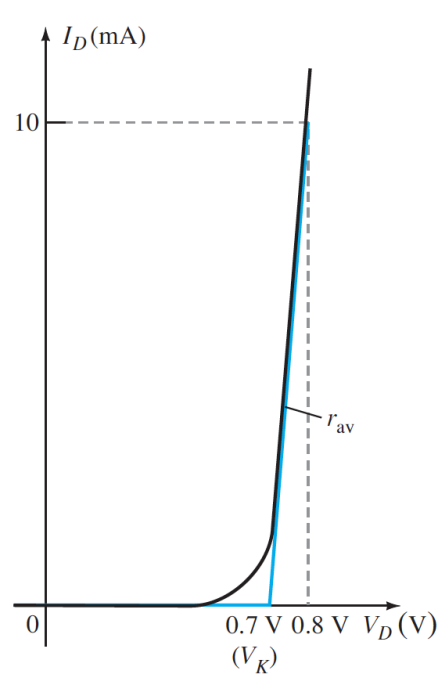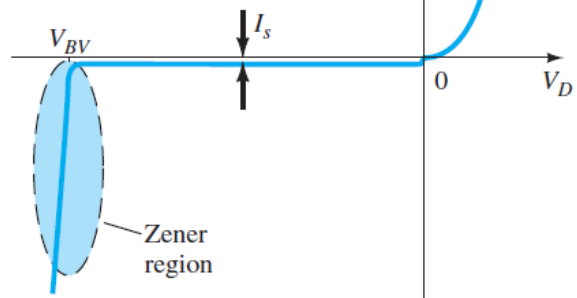





Si

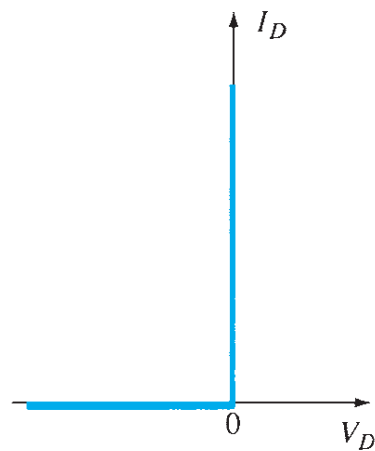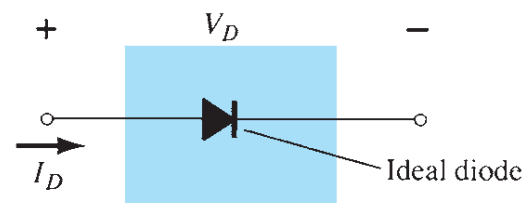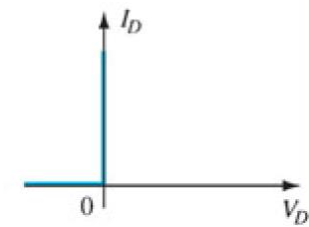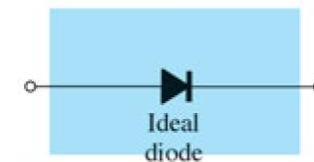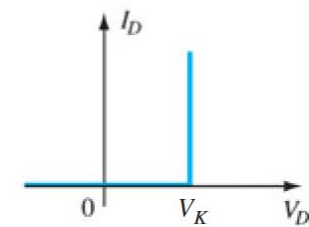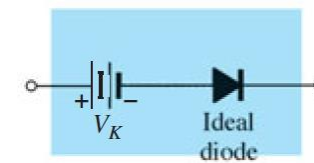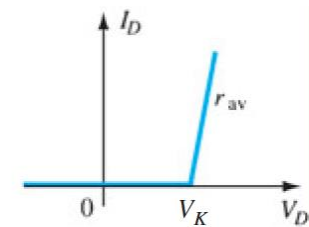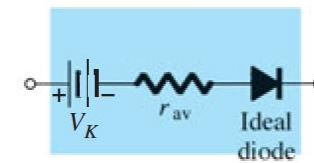

# Electronic circuits




## AC – DC

### Diode circuits

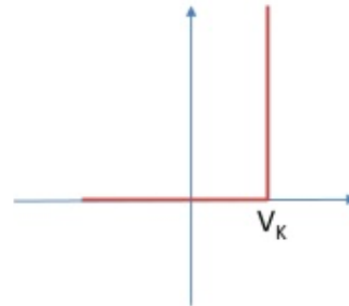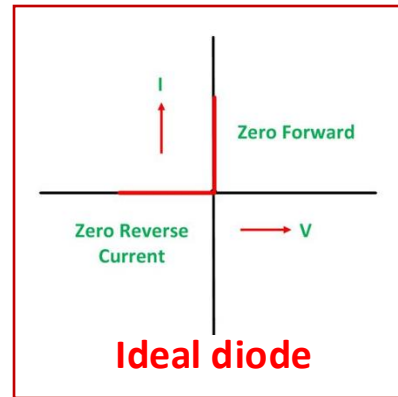
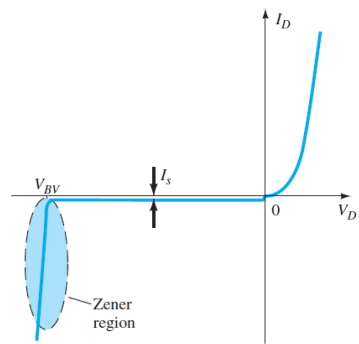
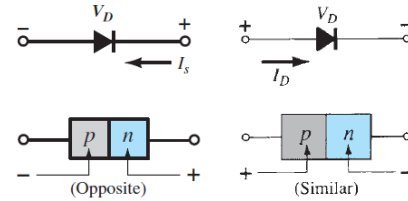


- AC signals can not be stored and DC power or signals can be stored.
- Also, Digital devices require constant voltages
- AC can be transported over long distances because of it's frequency and dc can not be transported as dc has zero frequency.














### Half wave rectification

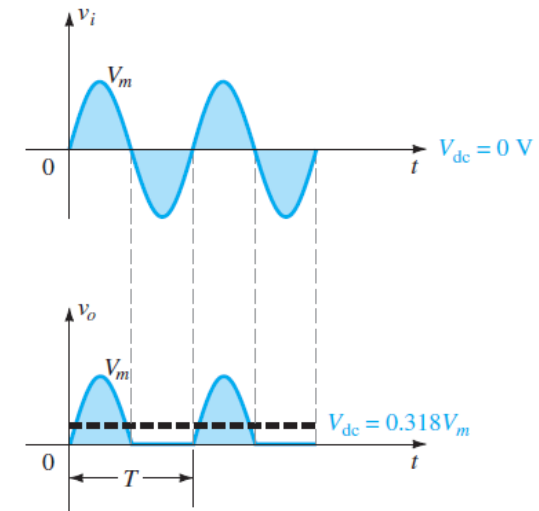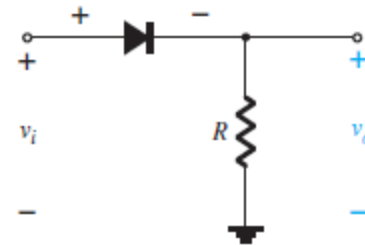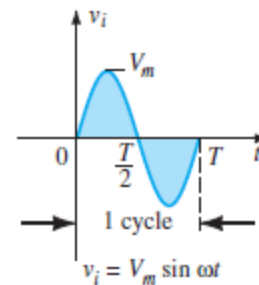

### More realistically


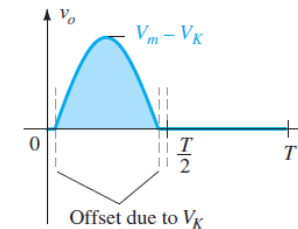
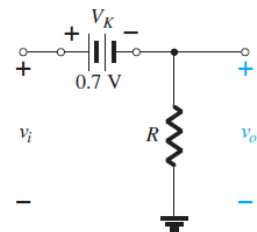
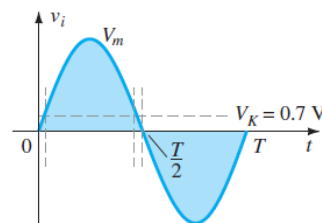


# Full wave rectification

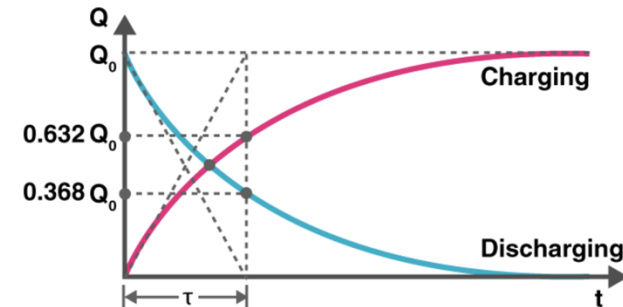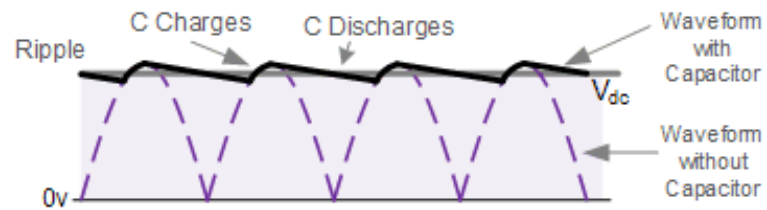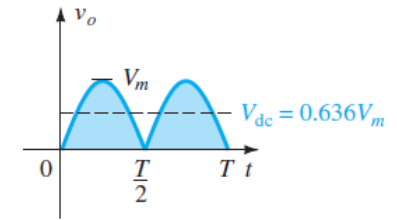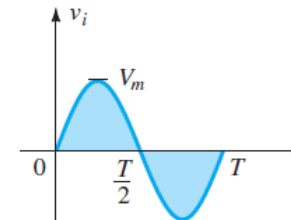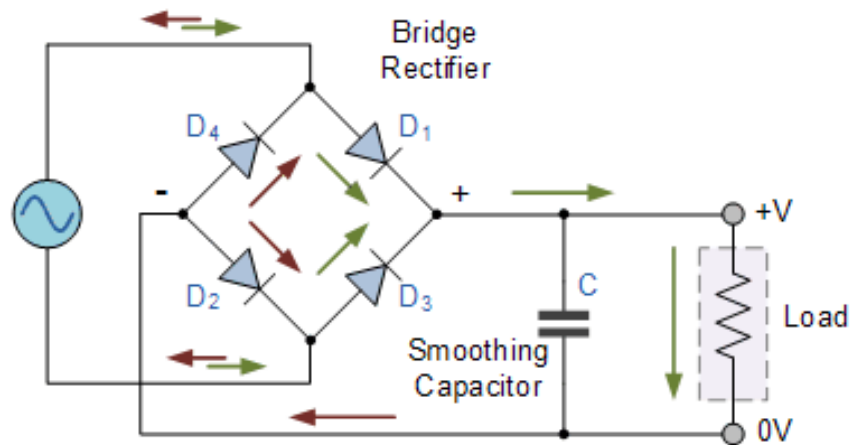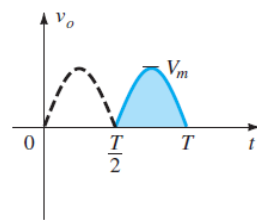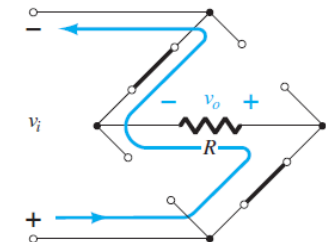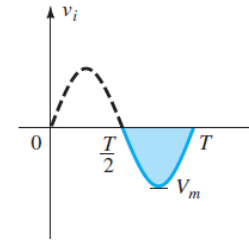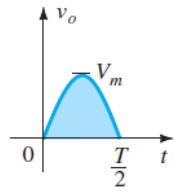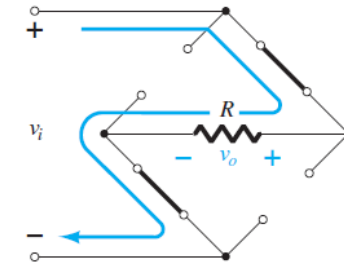
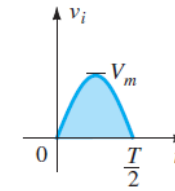
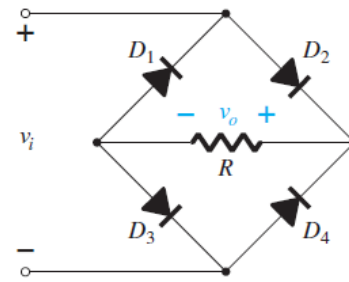
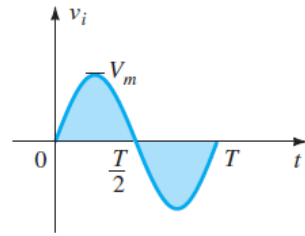


# Diode as clipper

## In series


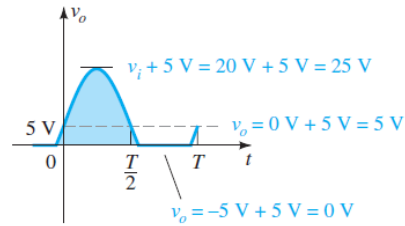
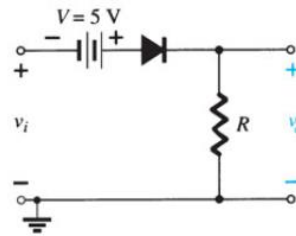
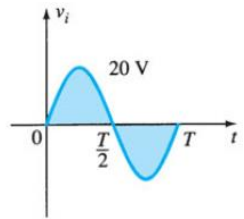
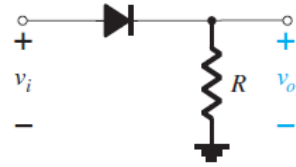


## In parallel

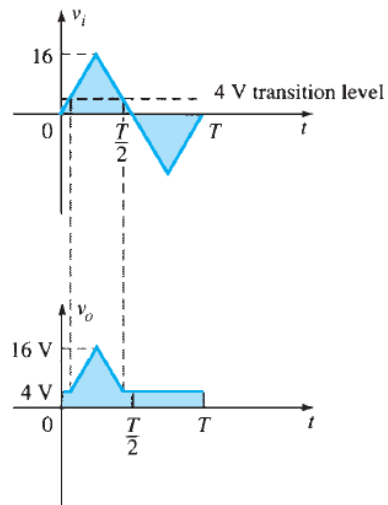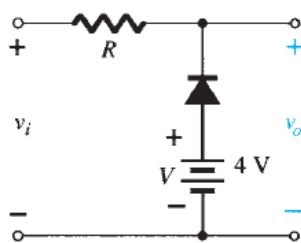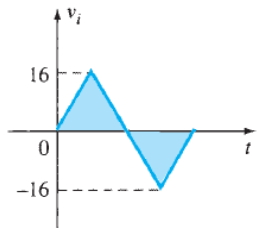
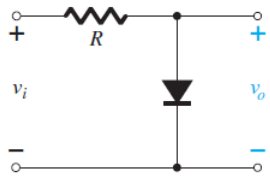

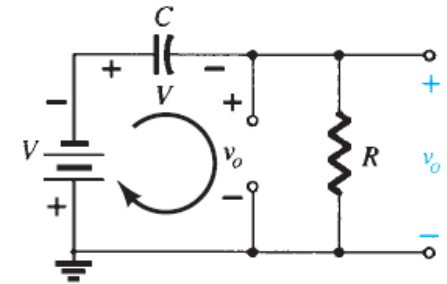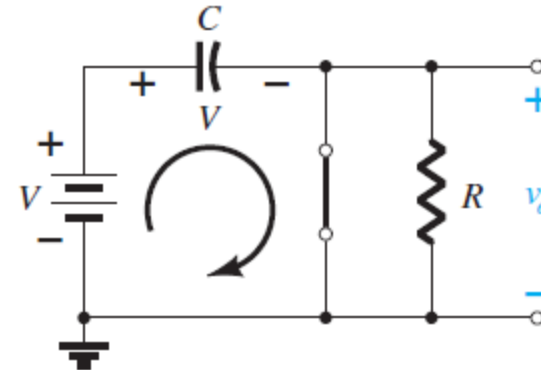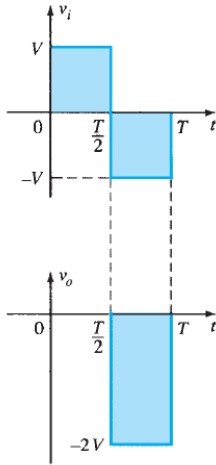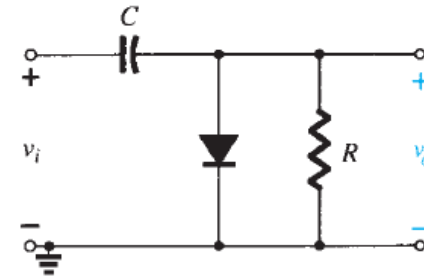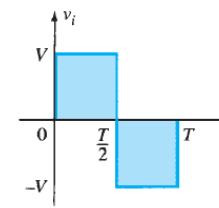
# Diode as clamper

Clamper is a circuit that changes the dc level of a waveform without changing its appearance.



Determine the output voltage

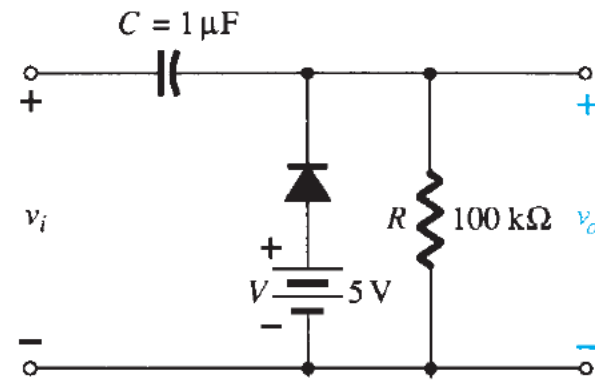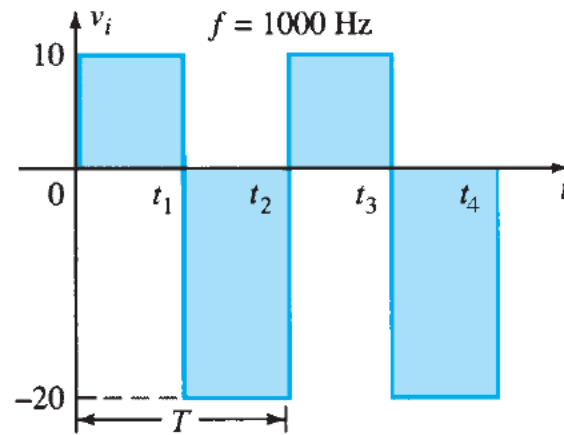

Repeat this using a silicon diode with  $V_K = 0.7 \text{ V}$

**Thank you**