

# **LAB-4 REPORT**

**TABLE NO:-42**

**ROOM NO:-117**

**NAME:-SANTHOSH**

**ROLL NO:-2024102054**

**NAME:-AKSHAY**

**ROLL NO:-2024102014**

## **OBJECTIVE:-**


To show that At breakdown, the diode presents very little incremental resistance to current flow, and so it can act like a good voltage reference.

## **EQUIPMENT REQUIRED:-**

Zener diode, wires, Load resistance, zener resistance
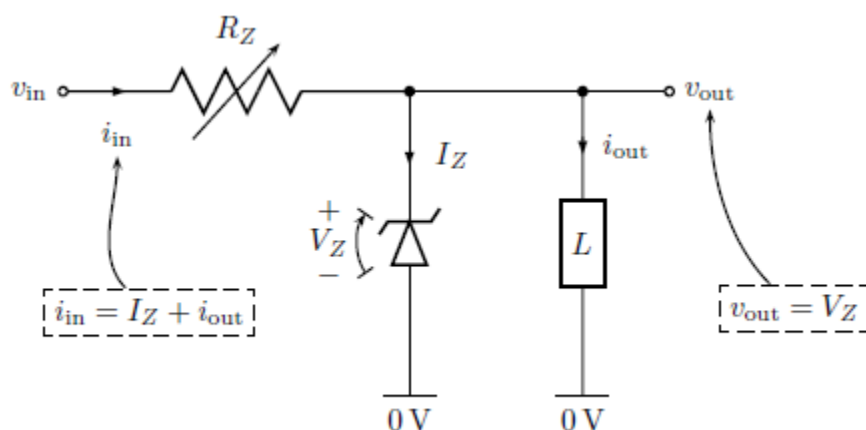
## **PROCEDURE:-**

Construct a circuit with  $v_{in}$  input given to the Zener resistance and the zener diode is connected in series across the zener resistance and connect a resistance parallel to the zener diode which is known as load resistance which is variable give the other end of diode to ground and then calculate the  $v_{out}$  which is the potential difference across zener diode



## **OBSERVATIONS AND RESULTS:-**

We can observe that the diode regulates at different voltages

And we can also observe that after a certain voltage by increasing the load resistance we cannot see much difference in  $V_{out}$  and that voltage is known as breakdown voltage

## **IMAGES AND CALCULATIONS:-**

We can observe from below observations that the break down voltage of the zener diode we have taken is approximately 5.24 volts

④ 05-10-24

780X → regulate +XX voltage  
79XX → regulates -XX voltage

$$R_1 = 11.81 \text{ k}\Omega$$

$$R_2 = 9.8 \text{ k}\Omega$$

$$R_3 = 0.97 \text{ k}\Omega = R_2$$

$$R_4 = 22 \text{ k}\Omega$$

$$R_5 = 1.9 \times 10^6 \Omega$$

$$R_6 = 390 \Omega$$

$$R_7 = 100 \Omega$$

| L (load) $\Omega$                | V <sub>out</sub> (V) | i <sub>n</sub> (mA) |
|----------------------------------|----------------------|---------------------|
| ① 22 k $\Omega$                  | 5.24V                | 9.76 mA             |
| ② 1.9 x 10 <sup>6</sup> $\Omega$ | 5.25V                | 9.77 mA             |
| ③ 11.81 k $\Omega$               | 5.23V                | 9.76 mA             |
| ④ 380 $\Omega$                   | 4.14V                | 10.90 mA            |
| ⑤ 100 $\Omega$                   | 1.38V                | 14.4 mA             |
| ⑥ 9.8 k $\Omega$                 | 5.27V                | 9.9 mA              |

$$I_{in} = \frac{-V_{out} + V_{in}}{R_2}$$

## **CONCLUSION:-**

We can conclude that the zener diode break down at certain voltage after which by even increasing the current there will be no change in the potential difference

## **(PART-2)**

### **OBJECTIVE:-**

The objective of this experiment is to design a zener voltage regulator

### **EQUIPMENT REQUIRED:-**




Potentiometer  
wire, LM317, load resistance

### **PROCEDURE:-**

First we have to take the LM317 which contains 3 pins(input,output,adjust)give the v input to the input pin then ground the resistance of the potentiometer wire then adjust the wire between the resistance then connect a load resistance parallel to the potentiometer wire resistance now calculate the vout which is potential difference across the load resistance

Now by taking vout to be 10 adjust the potentiometer wire

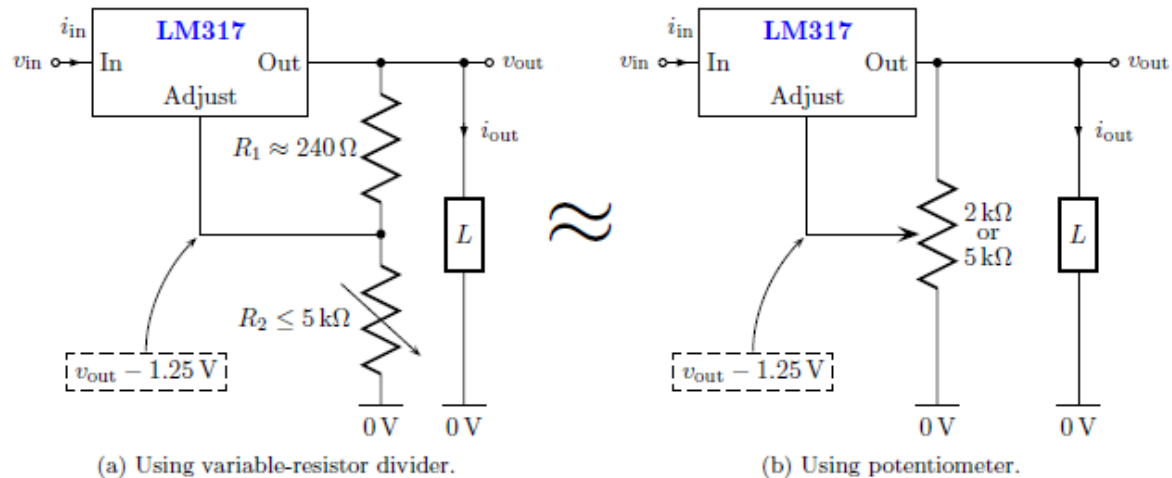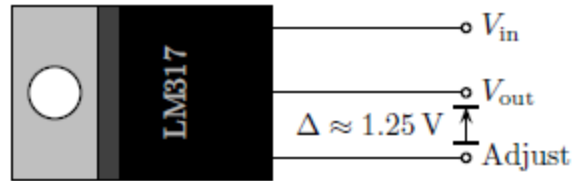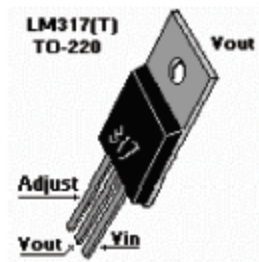We can calculate the ratio of the resistances by the formula  
$$v_{out} = (1.25) * (1 + R2 / R1)$$



## OBSERVATIONS AND RESULTS:-

We can observe that the resistances ratio is independent on the input current and dependent only on Output voltage

## IMAGES AND CALCULATIONS:-



$$(I_{in}) = \frac{-5.24 + 14.98}{970} \approx 10 \text{ mA}$$

②

Load

①  $390 \Omega$

$V_{out}$

10 V

$i_{in}$

29 mA

$R_2/R_1$

7

$$V_{out} = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$$

$$= 10 = 1.25 \left( 1 + \frac{R_2}{R_1} \right) \quad \boxed{R_1 + R_2 = 5000 \Omega}$$

$$\Rightarrow 8 = 1 + \frac{R_2}{R_1} \Rightarrow \boxed{\frac{R_2}{R_1} = 7}$$

②

$390 \Omega$

5 V

14.34 mA

3

$$V_{out} = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$$

$$5 = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$$

$$4 = 1 + \frac{R_2}{R_1}$$

$$\boxed{\frac{R_2}{R_1} = 3}$$

$$\boxed{R_1 + R_2 = 5000 \Omega}$$

③

$100 \Omega$

5 V

52.8 mA

3

$$5 = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$$



## **CONCLUSION:-**

The value of resistances in the potentiometer is dependent only on output voltage and independent on input current but the input current is dependent on the load resistance

## **(PART-3)**

### **OBJECTIVE:-**

To design a regulator


### **EQUIPMENT REQUIRED:-**

LM7805, potentiometer  
wire, load resistance
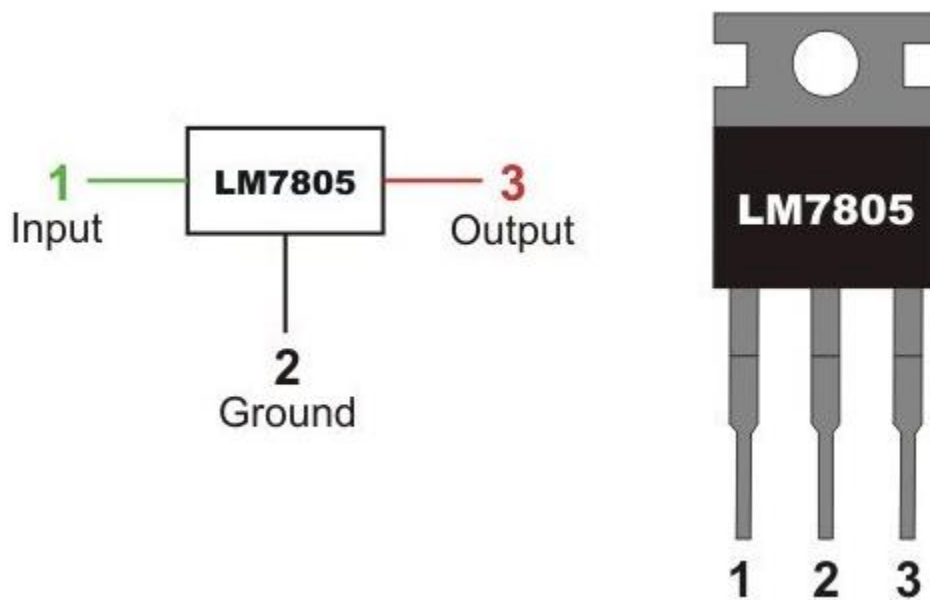
### **PROCEDURE:-**

LM7805 pin also  
contains three pins (input,ground,output)  
Repeat the same experiment as done in  
the previous ont but the difference  
between these two is the output voltage  
is always 5

Now calculate the  $i$  in  
for different values of load resistances



## OBSERVATIONS AND RESULTS:-

We can observe the ratio of  $R_2$  and  $R_1$  is always fixed as 3  
As the output voltage is always fixed

## IMAGES AND CALCULATIONS:-

③

$$V_{out} = 5V$$

As  $V_{out}$  is fixed

$$5 = (1.25) \left(1 + \frac{R_2}{R_1}\right)$$

$$\Rightarrow \frac{R_2}{R_1} = 3 \quad \text{always constant}$$

Load

$I_{in}$

100  $\Omega$

59.8 mA

390  $\Omega$

16.6 mA

Tammy B

## **CONCLUSION:-**

We can conclude that the ratio of resistances are always constant and the value of the input current depends on the load resistance

**NOTE:-i am very sorry for not uploading the photos taken in lab we actually forgot to take the photos and our TA told that the sign is enough**

**I will not repeat this again**